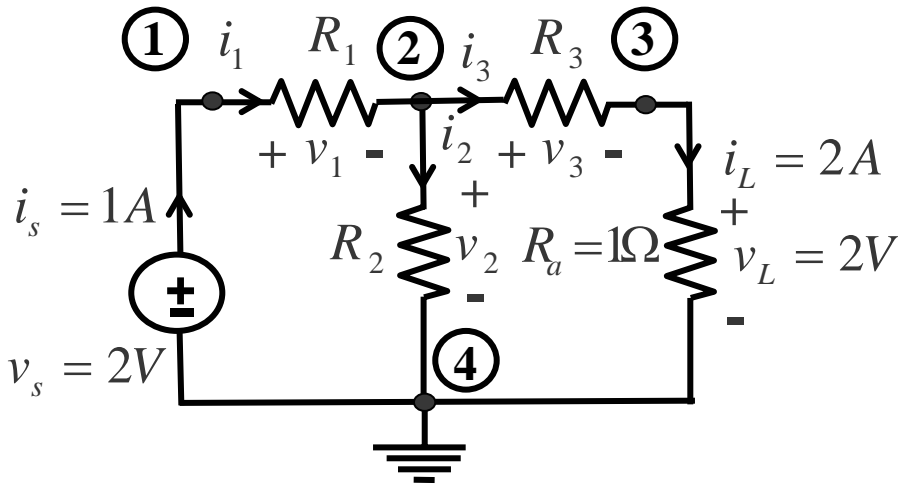


An Example Illustrating A Non-trivial Application of Tellegen's Theorem


Consider the following 2 circuits N and \hat{N} . Let v_j and i_j denote the voltage and current of branch j of N . Let \hat{v}_j and \hat{i}_j denote the voltage and current of \hat{N} . The values of R_1 , R_2 and R_3 are not known in both circuits. But instead, $i_s = 1A$ and $v_L = 2V$ are given for N and $\hat{v}_s = 3V$ is given for \hat{N} . The problem is to find the voltage \hat{v}_L of \hat{N} .

Note : Although the 2 circuits are different (N is driven by a voltage source, but \hat{N} is driven by a current source; the values of R_a and R_b are also different), they have the same digraph.


Circuit N




Graph G

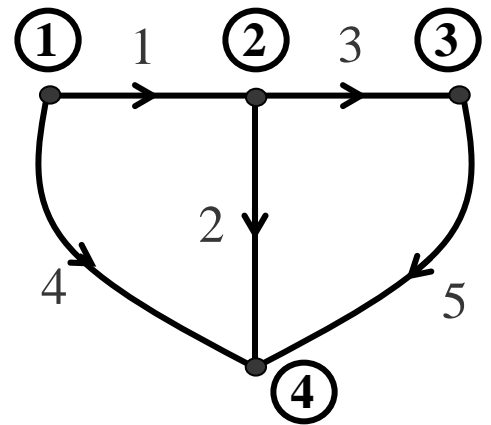

Circuit \hat{N}

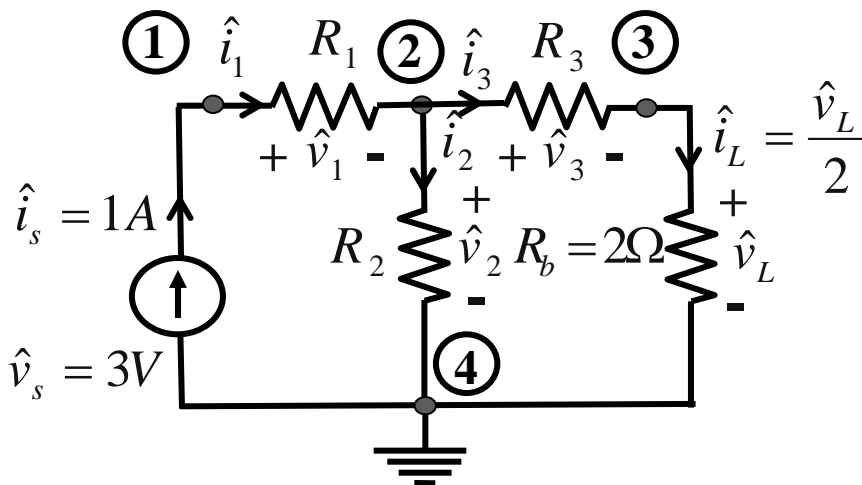

Graph \hat{G}

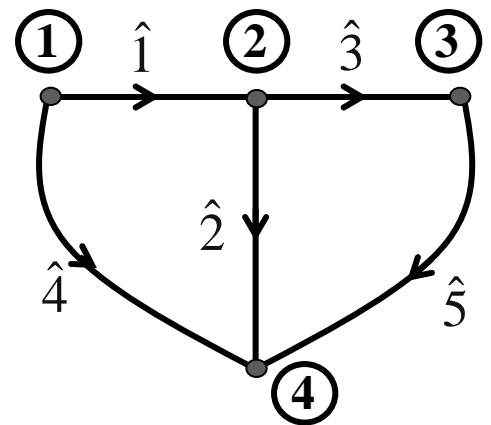

Since the 2 digraph G and \hat{G} are identical, we can apply Tellegen's theorem to either digraph using **any set** of voltages which satisfy KVL for N , and **any set** of currents which satisfy KCL for \hat{N} , and vice versa, paying attention that we must use Associated Reference Convention :

$$\text{For } N : v_4 = 2V, \quad i_4 = -1A$$

$$\text{For } \hat{N} : \hat{v}_4 = 3V, \quad \hat{i}_4 = -1A$$

(a) Applying Tellegen's Theorem using the voltage solutions v_j for N (which must satisfy KVL) and the current solutions \hat{i}_j (which must satisfy KCL) for \hat{N} :

$$\underbrace{(v_1)(\hat{i}_1) + (v_2)(\hat{i}_2) + (v_3)(\hat{i}_3) + (v_4)(\hat{i}_4) + (v_5)(\hat{i}_5)} = 0$$

$$\Rightarrow I = \sum_{j=1}^3 (v_j)(\hat{i}_j) + (2)(-1) + (2)\left(\frac{\hat{v}_L}{2}\right) = 0 \quad (1)$$

(b) Applying Tellegen's Theorem using the voltage solutions \hat{v}_j for \hat{N} (which must satisfy KVL) and the current solutions i_j (which must satisfy KCL) for N :

$$\underbrace{(\hat{v}_1)(i_1) + (\hat{v}_2)(i_2) + (\hat{v}_3)(i_3) + (\hat{v}_4)(i_4) + (\hat{v}_5)(i_5)} = 0$$

$$\Rightarrow \hat{I} = \sum_{j=1}^3 (\hat{v}_j)(i_j) + (3)(-1) + (\hat{v}_L)(2) = 0 \quad (2)$$

Observe

$$I = \sum_{j=1}^3 (v_j)(\hat{i}_j) = (R_1 i_1)(\hat{i}_1) + (R_2 i_2)(\hat{i}_2) + (R_3 i_3)(\hat{i}_3) \quad (3)$$

$$\hat{I} = \sum_{j=1}^3 (\hat{v}_j)(i_j) = (R_1 \hat{i}_1)(i_1) + (R_2 \hat{i}_2)(i_2) + (R_3 \hat{i}_3)(i_3) \quad (4)$$

$$\Rightarrow I = \hat{I}$$

Subtracting (1) - (2) :

$$\left[(2)(-1) + (2)\left(\frac{\hat{v}_L}{2}\right) \right] - \left[(3)(-1) + (\hat{v}_L)(2) \right] = 0$$

$$-2 + \hat{v}_L + 3 - 2\hat{v}_L = 0$$

$$\Rightarrow \boxed{\hat{v}_L = 1V}$$