
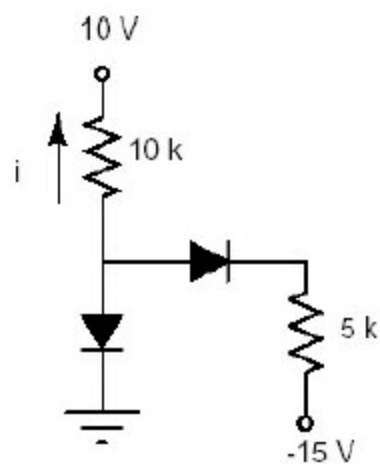



1. In the circuit¹ below, find i .

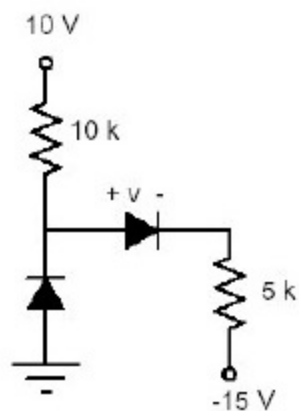

2. In the circuit below, find v .




3. In the circuit below, find i .

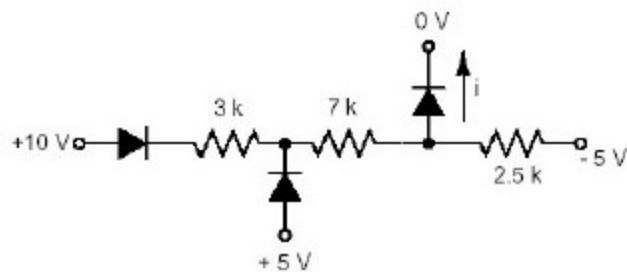


¹ Unless otherwise stated, assume all diodes in this homework are ideal.

4. In the circuit below, find v .

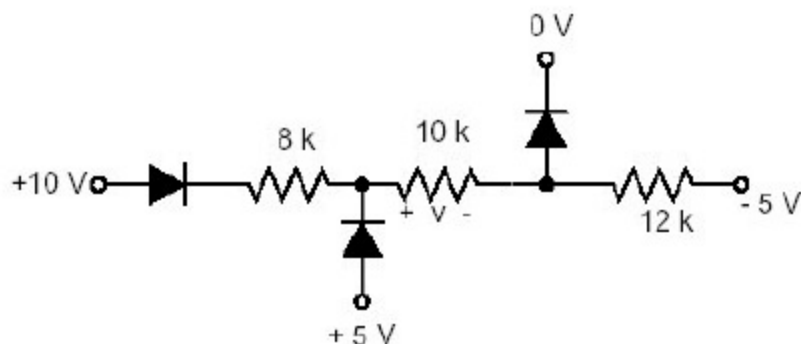

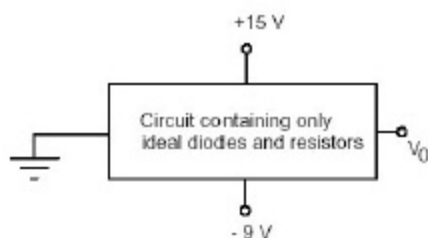5. The circuit in the box below contains ONLY ideal diodes and resistors.



(a) Is the maximum value of V_0 0 V, -6 V, +6 V or 15 V? EXPLAIN your answer, for instance give a circuit justifying your result.

(b) Is the minimum value of V_0 0 V, -9 V, +6 V or 15 V? EXPLAIN your answer, for instance, give a circuit justifying your result.

6. (a) In the circuit below, plot V_0 as a function of V_s . Assume $V_1 = V_2 = 3V$.

(b) If $V_s = 5 \sin(2 \pi 1000t)$ volts, sketch V_0 on the same set of axes. Assume $V_1 = V_2 = 3V$ (as in part (a)). Show 2-3 cycles of the output. Briefly explain why this circuit is called as a **diode clipper**.

