

Problem 1 of 3 Answer each question briefly and clearly. (30 points)Explain briefly why BJT performance depends so much on the diffusivity of minority carriers (5pts)

It is the diffusion of minority carriers that brings them to the reverse-biased collector junction that makes the transistor work

How does the small signal output resistance of a BJT depend on its size (emitter-to-base junction area), when V_{BE} is held constant? (5pts)

$$I_C = I_S \cdot e^{V_{BE}/V_{th}} \quad r_o = \frac{V_A}{I_C}$$

I_C is proportional to I_S , and I_S is proportional to AE .

So: $AE \uparrow \Rightarrow I_S \uparrow \Rightarrow I_C \uparrow \Rightarrow r_o \downarrow$

Why is it desirable for $V_{BS} = 0V$ in MOS Common Gate applications? (5pts)

The current buffer dc gain is -1 in general

but $R_{in} = \frac{1}{g_m + g_{mb}}$. The lower R_{in} (due to g_{mb}) is desirable,

but the added capacitance is not!


What happens to the overall (loaded) $|A_v|$ when I_c increases in a CE amplifier? (Assume that R_L is initially equal to r_o , $R_s \ll r_\pi$ and $r_{oc} = \infty$) (5 pts)

$$g_m = \frac{I_c}{V_{th}} \quad z_o = \frac{V_A}{I_c}$$

$$|A_v| = g_m (z_o \parallel R_L) = \frac{I_c}{V_{th}} \frac{z_o R_L}{z_o + R_L} = \frac{I_c}{V_{th}} \frac{\frac{V_A}{I_c} R_L}{\frac{V_A}{I_c} + R_L} =$$

$$\Rightarrow |A_v| = \frac{V_A}{V_{th}} \frac{R_L}{\frac{V_A}{I_c} + R_L} \quad \text{so, if } I_c \uparrow \text{ then } |A_v| \uparrow$$

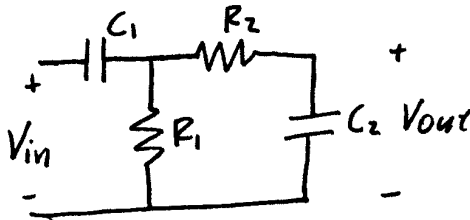How many poles and how many zeros does this circuit have? What is its function, assuming that $R_1 C_1 \ll R_2 C_2$? (5pts)



this is a band pass filter, with one $j\omega R_1 C_1$ multi.
 a pole at $\frac{1}{R_2 C_2}$ and one pole at $\frac{1}{R_1 C_1}$
 (notice that you have two cascaded voltage dividers).

Assuming "no loading"


$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 + \frac{1}{j\omega C_1}} \cdot \frac{\frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} =$$

$$\frac{V_{R_1}}{V_{in}} \cdot \frac{V_{out}}{V_{R_1}}$$

$$\frac{j\omega R_1 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

dominant

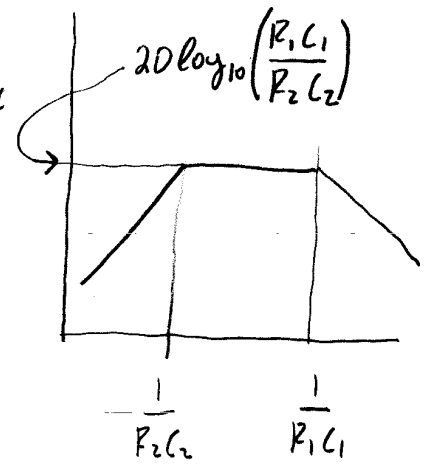
$$\omega_{p_1} = \frac{1}{R_1 C_1} \quad \omega_{p_2} = \frac{1}{R_2 C_2}$$



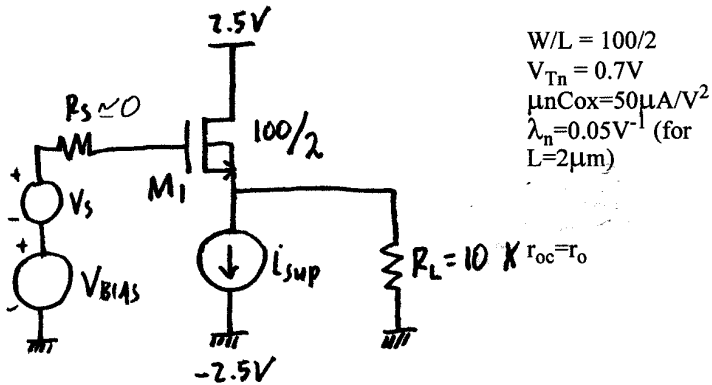Problem 2 of 3 (35 points)

For each of the following questions, make sure that you show the expressions before you plug in the specific values. A correct expression is worth 70% of the credit, even if the numerical calculation is incorrect!

You are given the following nmos common drain amplifier.



a) Assume $V_{bs}=0V$, and find V_{bias} so that $I_{sup} = 500\mu A$. (10pts) And $V_{out} = 0V$

$$V_{GS} = \sqrt{\frac{2I_{D_S}}{\frac{W}{L}\mu_n C_{ox}}} + V_{Tn} = 1.332V. \text{ Since } V_s = 0V, \text{ the } V_{GS} = V_{BIAS} = 1.332V$$

b) Calculate the overall (loaded) voltage gain, with $V_{bs}=0V$. (10pts)

The unloaded voltage gain is

$$A_v = \frac{g_m}{\frac{1}{r_o \parallel r_{oc}} + g_m} = 0.969$$


$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D} = 1.58 mS$$

$$r_o = (\lambda_n \cdot I_{D_S})^{-1} = 40K = r_{oc}, \Rightarrow r_o \parallel r_{oc} = 20K$$

$$R_{out} = \frac{1}{\frac{1}{r_o \parallel r_{oc}} + g_m} = 613\Omega$$

overall gain is $A_v \cdot \frac{R_L}{R_{out} + R_L} = \frac{10,000}{10,613} A_v = \underline{\underline{0.913}}$

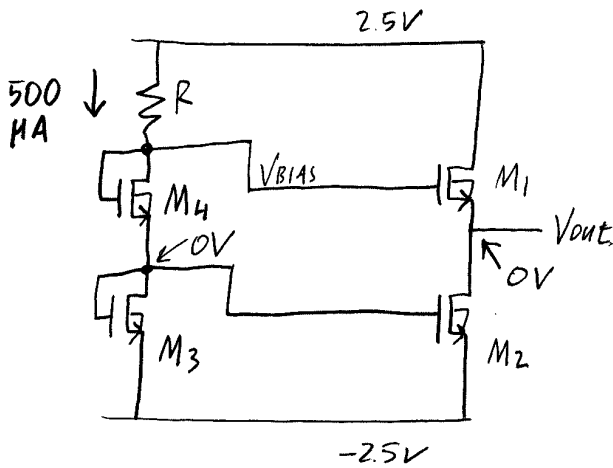c) Size the biasing transistors and resistor in order to get the proper V_{bias} and proper supply current (10pts)



$$V_{\text{BIAS}} = 1.332\text{V} \Rightarrow R = \frac{2.5\text{V} - 1.332\text{V}}{500\mu\text{A}} = 2336\Omega$$

M_4 must have 1.332 of $V_{\text{GS}} \Rightarrow$

$$\sqrt{\frac{2I_{\text{DS}}}{\left(\frac{W}{L}\right)_4 \mu_n C_{\text{ox}}}} + V_{\text{TN}} = 1.332 \Rightarrow \left(\frac{W}{L}\right)_4 = \frac{2I_{\text{DS}}/\mu_n C_{\text{ox}}}{(1.332 - V_{\text{TN}})^2} = 50 = \frac{100}{2}$$

$$V_{\text{GS}_3} = 2.5\text{V} \Rightarrow$$


$$\sqrt{\frac{2I_{\text{DS}}}{\left(\frac{W}{L}\right)_3 \mu_n C_{\text{ox}}}} + V_{\text{TN}} = 2.5 \Rightarrow \left(\frac{W}{L}\right)_3 = \frac{2I_{\text{DS}}/\mu_n C_{\text{ox}}}{(2.5 - V_{\text{TN}})^2} = 6.17$$

$$\text{also, } \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = 6.17 = \frac{12.30}{2}$$

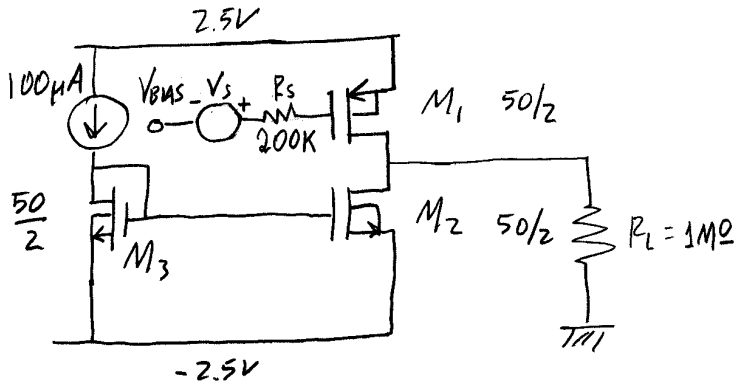
Problem 3 of 3 (35 points)

For each of the following questions, make sure that you show the expressions before you plug in the specific values. A correct expression is worth 70% of the credit, even if the numerical calculation is incorrect!

You are given the following p-channel common-source amplifier.



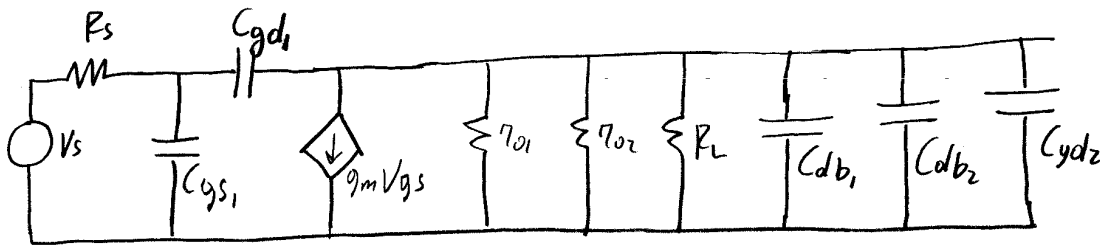- a) Draw the small signal model of the amplifier. Make sure that you include the entire small signal model of transistor M_1 , along with all the relevant capacitances, including r_{o2} , C_{db2} and C_{gd2} from the current sink transistor M_2 . (10 points)



Notice that all the following small signal voltages are grounds: (0V)

$$V_{s2} \quad V_{g2} \quad V_{b1} \quad V_{b2} \dots$$

This is why all these caps are here

Also: $V_{gs2} = 0V$ $V_{bs2} = 0V$, that is why there are no dependent sources from M_2 in this model...

- b) Apply the Miller approximation (ignore all capacitances when calculating the Miller gain), and derive a symbolic expression for the complete transfer function (hint: this function has two poles and no zeros) (7 points).

$$C_M = (1 + |A_v|) C_{GD1} \quad A_v = -g_m (r_{o1} \parallel r_{o2} \parallel R_L)$$

$$V_{out} = -V_s \cdot \frac{1}{R_s + \frac{1}{j\omega(C_{gs1} + C_M)}} \cdot g_m (r_{o1} \parallel r_{o2} \parallel R_L) \frac{1}{j\omega(C_{db1} + C_{db2} + C_{gd2})} \Rightarrow$$

$$\frac{V_{out}}{V_s} = - \frac{g_m}{\underbrace{\left[1 + j\omega R_s (C_{gs1} + C_M)\right]}_{\text{pole}}} \cdot \frac{r_{o1} \parallel r_{o2} \parallel R_L}{\underbrace{\left[1 + R_L \parallel r_{o1} \parallel r_{o2} \cdot j\omega (C_{db1} + C_{db2} + C_{gd2})\right]}_{\text{pole}}}$$

$$\omega = \frac{1}{R_s (C_{gs1} + C_M)}$$

$$\omega = \frac{1}{(R_L \parallel r_{o1} \parallel r_{o2}) \cdot (C_{db1} + C_{db2} + C_{gd2})}$$

- c) Calculate dc gain and the values of the two poles, given that $C_{gs1}=78\text{fF}$, $C_{gd1}=25\text{fF}$, $C_{gd2}=25\text{fF}$, $C_{db1}=90\text{fF}$, $C_{db2}=30\text{fF}$ (8 points)

$$\text{dc gain} = -g_m \overbrace{(r_{o1} \parallel r_{o2} \parallel R_L)}^{91\text{K}\Omega} = -32.214$$

$$g_m = \sqrt{2 \frac{W}{L} \mu_n \text{ox} I_D} = 0.354\text{mS}$$

$$r_{o1} = (I_n \cdot I_D)^{-1} = 200\text{K} = r_{o2}$$

$$\text{pole 1 (dominant)} = \frac{1}{R_s (C_{gs1} + C_{M1})} \approx 5.5\text{Mrad/sec}$$

$$\uparrow 25\text{fF} \times (1 + 32.214) = 805\text{fF}$$

$$\text{pole 2} = \frac{1}{(r_{o1} \parallel r_{o2} \parallel R_L) \cdot (C_{db1} + C_{db2} + C_{gd2})} = 75.7\text{Mrad/sec}$$

d) Draw the Bode plot for amplitude and phase of the gain of this amplifier (10 points).

$$|A_v| = 32.214 = 30 \text{ dB} \quad (20 \log_{10}(32.214))$$

