

Lecture 21: Voltage/Current Buffer Freq Response

Prof. Niknejad




Lecture Outline

- Last Time: Frequency Response of Voltage Buffer
- Frequency Response of Current Buffer
- Current Mirrors
- Biasing Schemes
- Detailed Example


Common-Collector Amplifier

Procedure:

 1. Small-signal two-port model
2. Add device (and other) capacitors



Two-Port CC Model with Capacitors

 

Find Miller capacitor for C_π -- note that the base-emitter capacitor is between the input and output

Voltage Gain A_{vC_π} Across C_π

$$A_{vC_\pi} \approx R_{out} / (R_{out} + R_L) \sim 1 \quad R_{out} = \frac{1}{g_m}$$

$$g_m R_L \gg 1$$

Note: this voltage gain is neither the two-port gain nor the “loaded” voltage gain

$$C_{in} = C_\mu + C_M = C_\mu + (1 - A_{vC_\pi})C_\pi$$

$$C_{in} = C_\mu + \frac{1}{1 + g_m R_L} C_\pi$$

$$C_{in} \approx C_\mu$$

Bandwidth of CC Amplifier

Input low-pass filter's -3 dB frequency:

$$\omega_p^{-1} = (R_S \parallel R_{in}) \left(C_\mu + \frac{C_\pi}{1 + g_m R_L} \right)$$

Substitute favorable values of R_S, R_L :


$$R_S \approx 1/g_m \quad R_L \gg 1/g_m$$

$$\omega_p^{-1} \approx (1/g_m) \left(C_\mu + \frac{C_\pi}{1 + \mathbf{BIG}} \right) \approx C_\mu / g_m$$

Model not valid at these high frequencies


$$\omega_p \approx g_m / C_\mu > \omega_T$$

CB Current Buffer Bandwidth

 

Same procedure: start with two-port model and capacitors

Two-Port CB Model with Capacitors

 


No Miller-transformed capacitor!

Unity-gain frequency is on the order of ω_T for small R_L

Summ of Single-Stage Amp Freq Resp

- CE, CS: suffer from Miller-magnified capacitor for high-gain case
- CC, CD: Miller transformation \rightarrow nulled capacitor \rightarrow “wideband stage”
- CB, CG: no Millerized capacitor \rightarrow wideband stage (for low load resistance)


CMOS Diode Connected Transistor

 

- Short gate/drain of a transistor and pass current through it
- Since $V_{GS} = V_{DS}$, the device is in saturation since $V_{DS} > V_{GS} - V_T$
- Since FET is a square-law (or weaker) device, the I-V curve is very soft compared to PN junction diode
- What's the input impedance of circuit?


Diode Equivalent Circuit

$$R_D = \left(\frac{di_{OUT}}{dv_{OUT}} \Big|_{I_{OUT}=0} \right)^{-1} = \frac{v_t}{i_t}$$

 


$$R_D \approx \frac{1}{g_m}$$

Equivalent Circuit:

 


The Integrated “Current Mirror”

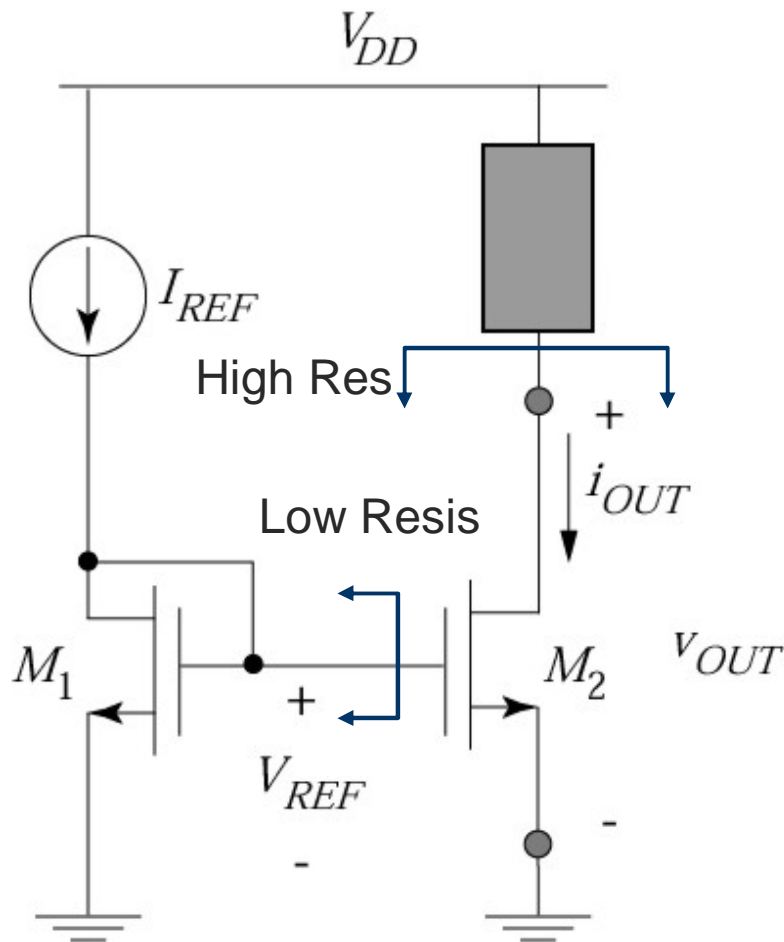


- M_1 and M_2 have the same V_{GS}
- If we neglect CLM ($\lambda=0$), then the drain currents are equal
- Since λ is small, the currents will nearly mirror one another even if V_{out} is not equal to V_{GS1}
- We say that the current I_{REF} is mirrored into i_{OUT}
- Notice that the mirror works for small and large signals!

Current Mirror as Current Source

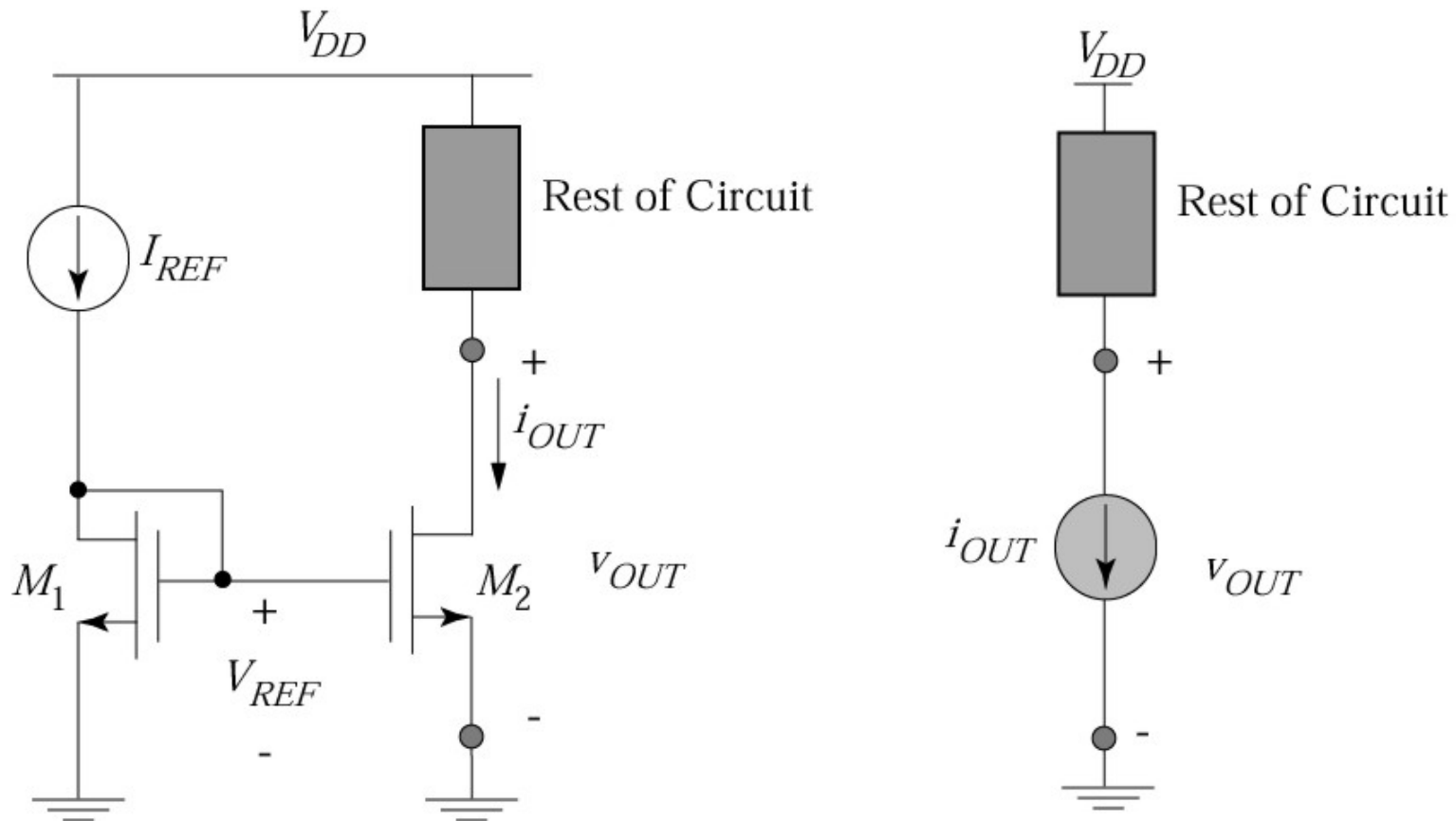

- The output current of M_2 is only weakly dependent on V_{OUT} due to high output resistance of FET
- M_2 acts like a current source to the rest of the circuit


Small-Signal Resistance of I -Source

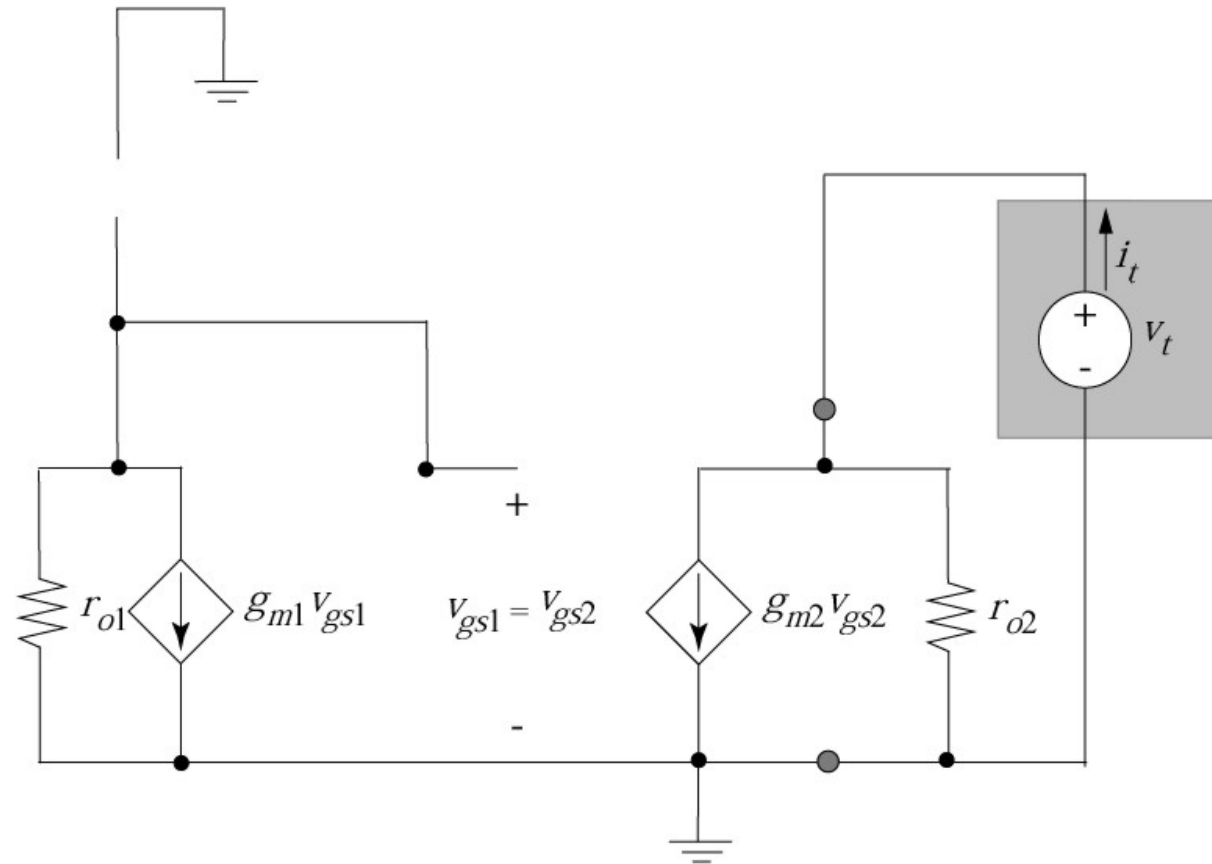


Improved Current Sources

Goal: increase r_{oc}

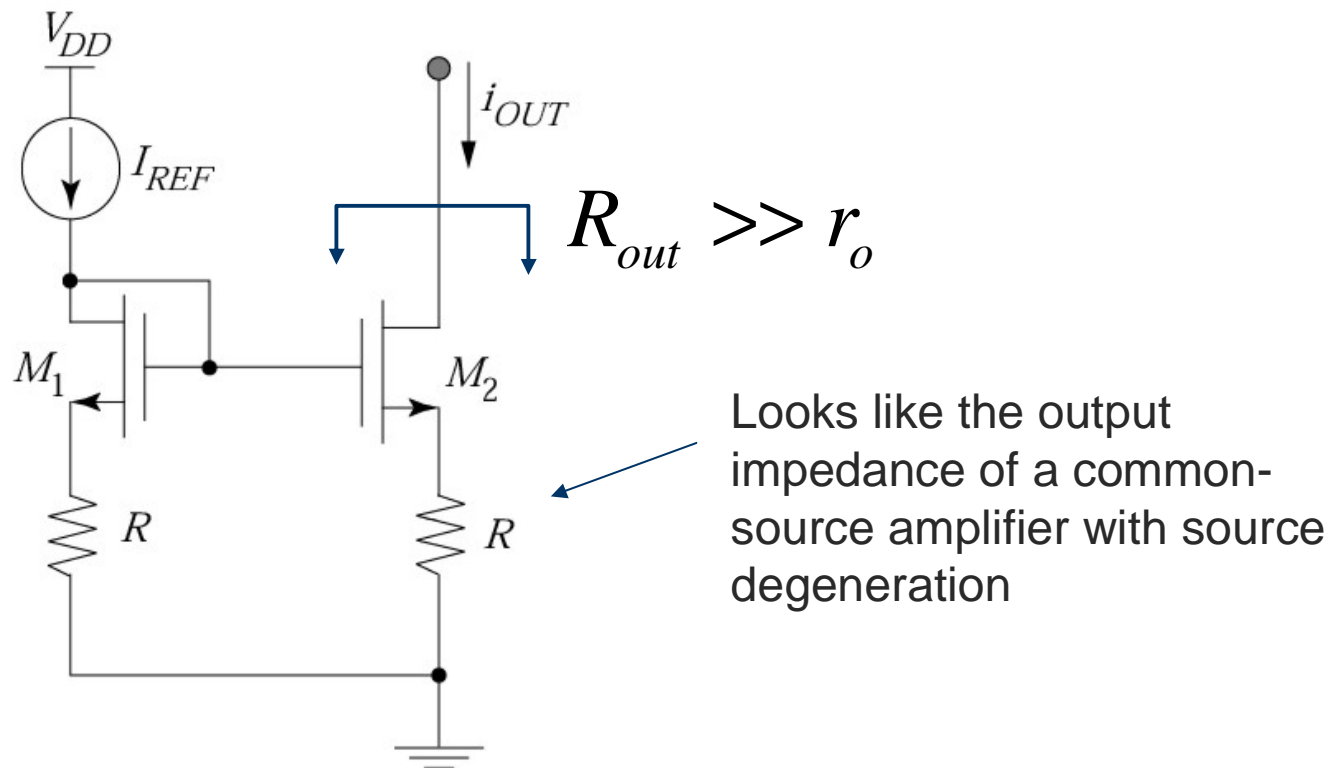Approach: look at *amplifier* output resistance results ... to see topologies that boost resistance



Effect of Source Degeneration

 

$$R_{eq} \approx \frac{1}{g_m}$$

$$v_t = (i_t - g_m v_{gs}) r_o + v_{R_S}$$

$$v_{gs} \approx -v_{R_S}$$


$$v_{R_S} = i_t R_S$$

$$v_t = (i_t + g_m R_S i_t) r_o + i_t R_S$$

$$R_o = \frac{v_t}{i_t} \approx (1 + g_m R_S) r_o$$

- Equivalent resistance loading gate is dominated by the diode resistance ... assume this is a small impedance
- Output impedance is boosted by factor $(1 + g_m R_S)$

Cascode (or Stacked) Current Source

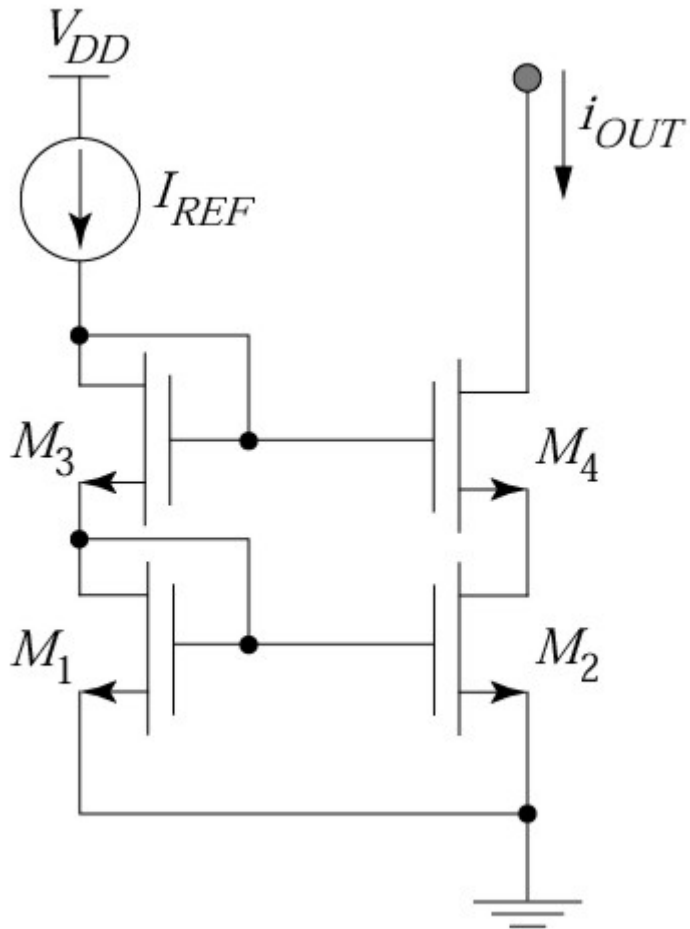

Insight: $V_{GS2} = \text{constant}$ AND
 $V_{DS2} = \text{constant}$

Small-Signal Resistance r_{oc} :

$$R_o \approx (1 + g_m R_S) r_o$$

$$R_o \approx (1 + g_m r_o) r_o$$

$$R_o \approx g_m r_o^2 \gg r_o$$



Drawback of Cascode I-Source

Minimum output voltage to keep both transistors in saturation:

$$V_{OUT,MIN} = V_{DS4,MIN} + V_{DS2,MIN}$$


$$V_{DS2,MIN} > V_{GS2} - V_{T0} = V_{DSAT2}$$
  
$$V_{D4} > V_{DSAT2} + V_{GS4} = V_{GS2} + V_{GS4} - V_{T0}$$




Current Sinks and Sources

Sink: output current goes to ground

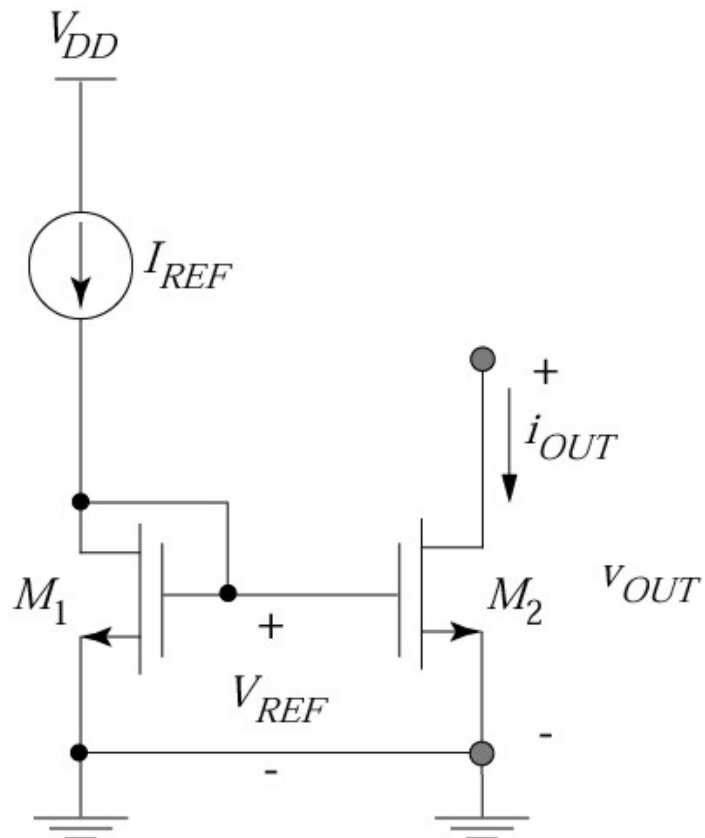

 Source: output current comes from voltage supply



Current Mirrors

Idea: we only need one reference current to set up all the current sources and sinks needed for a multistage amplifier.

