

EE 105 Discussion Session #1 Week Sept 0.8

1. Probability derivation for HW #2 Problem 2

$$A_0 = 1 + \frac{R_2}{R_1} = 1 + \frac{R_{20}}{R_0} \frac{y}{x}, \quad x, y \in [0.9, 1.1]$$

$$x, y \text{ independent and } f_x(x) = \begin{cases} 5, & x \in [0.9, 1.1] \\ 0, & \text{otherwise} \end{cases}$$

$$f_{x,y} = \begin{cases} 5, & y \in [0.9, 1.1] \\ 0, & \text{otherwise} \end{cases}$$

$$F_{Y|X}(z) = P(Y|X \leq z) = \iint_{y/x \leq 0, x < 0} f_{x,y} dy dx + \iint_{y/x \leq 0, x > 0} f_{x,y} dy dx$$

$$= \int_{-\infty}^0 \int_{x/2}^{\infty} f_{x,y} dy dx + \int_0^{\infty} \int_{-\infty}^{x/2} f_{x,y} dy dx$$

$$\frac{y}{x} \leq z \begin{cases} x \leq x/2, x > 0 \\ y > x/2, x < 0 \end{cases}$$

$$\text{Let } y = xu \rightarrow = \int_{-\infty}^0 \int_{x/2}^{\infty} x f_{x,xu} du dx + \int_0^{\infty} \int_{-\infty}^{x/2} x f_{x,xu} du dx$$

$$= \int_{-\infty}^0 \int_{x/2}^{\infty} x f_{x,xu} du dx + \int_0^{\infty} \int_{-\infty}^{x/2} x f_{x,xu} du dx$$


$$= \int_{-\infty}^0 \int_{-\infty}^{\infty} (-u) f_{x,xu} du dx + \int_0^{\infty} \int_{-\infty}^{\infty} u f_{x,xu} du dx$$

$$= \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} |u| f_{x,xu} du dx$$

$$= \int_{-\infty}^{\infty} du \int_{-\infty}^{\infty} |u| f_{x,xu} du dx$$

$$f_{z|0} = \frac{dF_{z|0}}{dz} = \int_{-\infty}^{\infty} |u| f_{x,xu} du dx$$

2. Calculate A , R_{in} , R_{out}

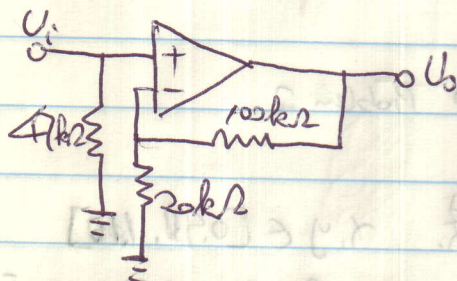


$$A = \frac{R_f + R_2}{R_1} = \frac{100 + 20}{20} = 6$$

$$R_{in} = 47k\Omega$$

$$R_{out} = 0\Omega$$

3. Calculate A , R_{in} , R_{out}

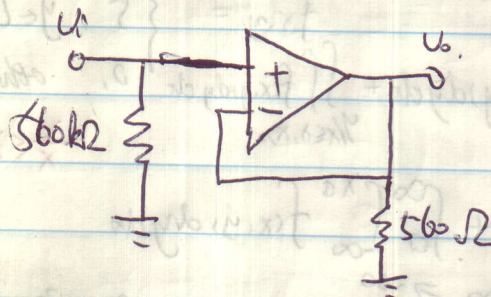


$$R_{in} = 560k\Omega$$

$$A = 1$$

$$R_{out} = 0\Omega$$


4. Summation Amplifier

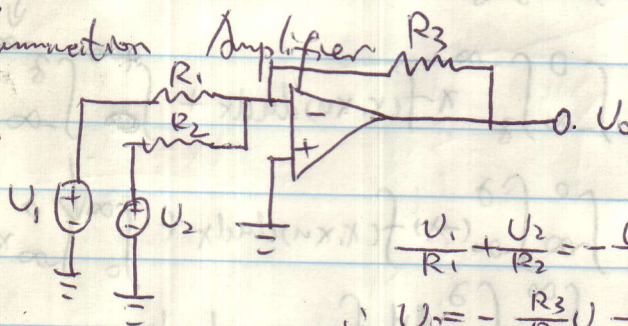


$$\frac{U_1}{R_1} + \frac{U_2}{R_2} = -\frac{U_o}{R_3}$$

$$\therefore U_o = -\frac{R_3}{R_1}U_1 - \frac{R_3}{R_2}U_2$$

5.

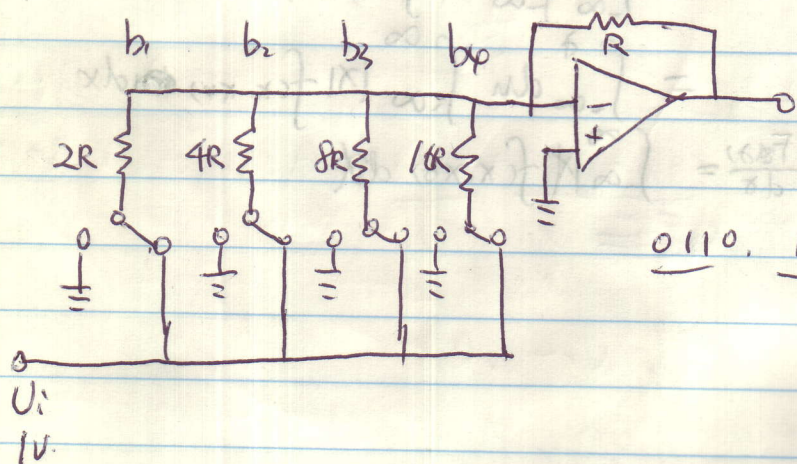

$$0110, 1011, 1101$$

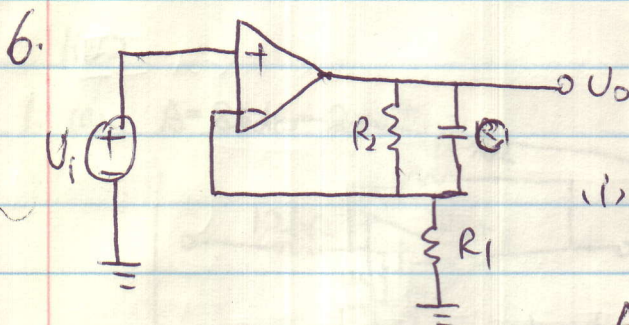

(i). no capacitor

$$A = \frac{R_2}{R_1} + 1$$

(ii) $A_{oc} = 1 + \frac{Z_2}{Z_1}$, $\begin{cases} Z_2 = R_2 \parallel \frac{1}{sC} = \frac{R_2/sC}{R_2 + 1/sC} = \frac{R_2}{1 + R_2 sC} \\ Z_1 = R_1 \end{cases}$

$\therefore A(s) = 1 + \frac{R_2}{R_1(1 + R_2 sC)}$ Low Pass Filter

