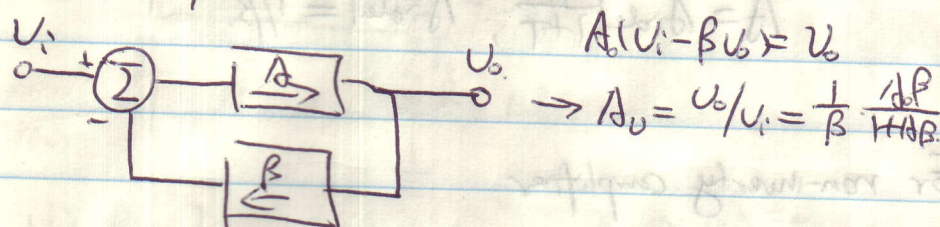


EE105 Discussion Session #2 Week Sept. 15

1. Feedback System



Define: $T = AB$, loop gain

A_o , open-loop gain

A_u , closed-loop gain


$A_{ideal} = 1/\beta$, ideal gain

β , feedback coefficient

$$GE = A_{ideal} - A_u = \frac{1}{\beta} \frac{1}{1+T}$$

$$FGE = GE / A_{ideal} = \frac{1}{1+T}$$

Q1.

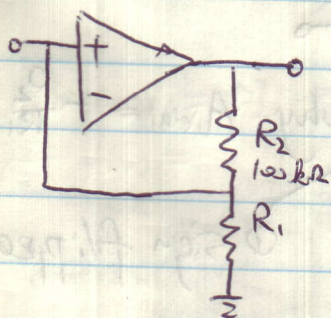

$$A_o = 86 \text{ dB}$$

? A_u , FGE

$$(i). R_1 = 10 \text{ k}\Omega \quad (ii). R_1 = 1 \text{ k}\Omega$$

$$(i) \beta = \frac{R_1}{R_1 + R_2} = \frac{10}{110} = \frac{1}{11}, \quad A_o = 86 \text{ dB} = 2 \times 10^4$$

$$T = A_o \beta = \frac{2 \times 10^4}{11} \approx 2000 \quad \left\{ \begin{array}{l} A_u = \frac{1}{\beta} \frac{T}{1+T} \approx \frac{1}{\beta} = 11 \\ FGE = \frac{1}{1+T} \approx \frac{1}{2000} = 0.05\% \end{array} \right.$$

$$(ii) \beta = \frac{1}{1+100} = \frac{1}{101}, \quad T = A_o \beta \approx 200$$


$$A_u = \frac{1}{\beta} \frac{T}{1+T} \approx 101, \quad FGE = \frac{1}{1+T} = \frac{1}{1200} \approx 0.5\%$$

Non-ideal gain

For the feedback system in the diagrams.

$$A = A_{ideal} \frac{T}{1+T}, \quad A_{ideal} = 1/\beta$$


① For non-inverting amplifier

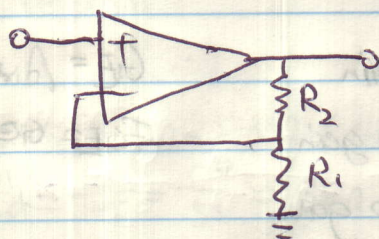


$$\beta = \frac{R_1}{R_1 + R_2}$$

$$A_{ideal} = 1/\beta = \frac{R_1 + R_2}{R_1}$$

② For inverting

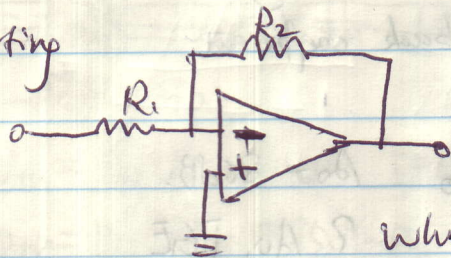


why $A_{ideal} = -\frac{R_2}{R_1}$?

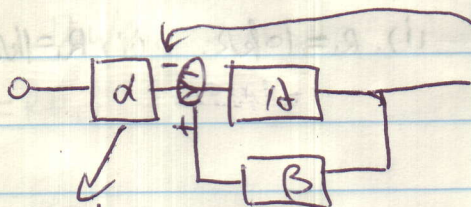

① Sign flipped

$$\alpha = \frac{R_2}{R_1 + R_2}$$
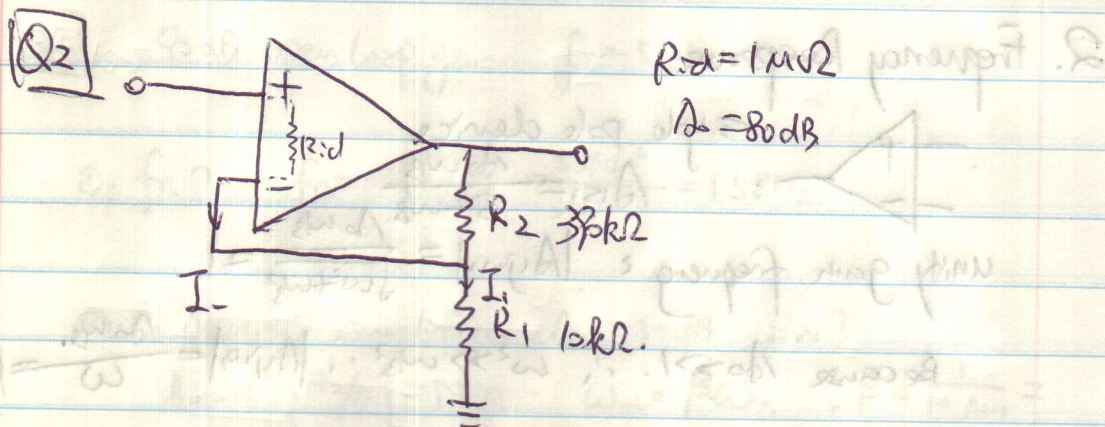
$$A_{ideal} = -\frac{1}{\beta} \cdot \alpha = -\frac{R_1 + R_2}{R_1} \cdot \frac{R_2}{R_1 + R_2} = -\frac{R_2}{R_1}$$



(i). $R_{in} ?$

$A = 80 \text{ dB} = 10^4$

$R_{in} = R_{id}(1+T), T = A\beta = 10^4 \cdot \frac{10}{10+30} = 250$

$R_{in} = 251 \text{ M}\Omega$

(ii) $I_- ? I_1 ?$

Or: $V_o = A V_i = \frac{1}{\beta} V_i = 40 \text{ V}$


$I_- = V_i / R_{in} = 4 \text{ nA}$

$V_{id} = V_o / A = 4 \text{ mV}$

$I_- = V_{id} / R_{id} = 4 \text{ nA}$

$I_1 \approx V_o / (R_1 + R_2) = 100 \text{ nA}$

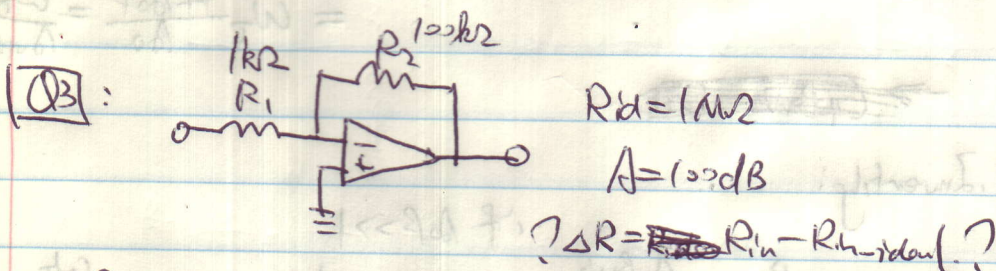Because $I_- \gg I_1 \rightarrow I_1 / I_- = 25000$ here.




$\Delta R = R_{in} - R_{in-id} ?$

$R_{in-id} = R_1 = 1 \text{ k}\Omega$

$R_{in} = R_1 + R_{id} \parallel \frac{R_2}{1+A} \approx R_1 + \frac{R_2}{1+A}$

$\Delta R \approx \frac{R_2}{1+A} = \frac{R_2}{A} = \frac{100 \text{ k}\Omega}{10^5} = 1 \text{ }\Omega$

2. Frequency Response

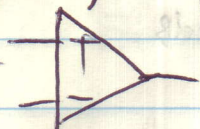

single pole device

$$A(s) = \frac{A_0 \omega_B}{s + \omega_B}$$

unity gain frequency: $|A(j\omega)| = \frac{A_0 \omega_B}{\sqrt{\omega^2 + \omega_B^2}} = 1$

Because $A_0 \gg 1$, $\therefore \omega^2 \gg \omega_B^2$, $\therefore |A(j\omega)| = \frac{A_0 \omega_B}{\omega} = 1$

$\therefore \omega_T = A_0 \omega_B$ $GBW \approx \omega_T$

①. non-inverting

$$A_{v(s)} = \frac{1}{\beta} \cdot \frac{A_0 \beta}{1 + A_0 \beta} = \frac{\frac{A_0 \omega_B}{s + \omega_B}}{1 + \frac{A_0 \omega_B \beta}{s + \omega_B}} = \frac{A_0 \omega_B}{s + \omega_B (1 + A_0 \beta)}$$

$$= \frac{A_0 (1 + A_0 \beta)}{\frac{s}{\omega_B (1 + A_0 \beta)} + 1}$$

$$\left\{ \begin{aligned} A_{v(s)} &\approx \frac{A_0}{1 + A_0 \beta} \\ \omega_H &= \omega_B (1 + A_0 \beta) \\ &= \omega_T \frac{1 + A_0 \beta}{A_0} = \frac{\omega_T}{A_{v(s)}} \end{aligned} \right.$$

~~$GBW = \omega_H$~~

②. Inverting:

if $A_0 \beta \gg 1$

$$A_{v(s)} = -\frac{R_2}{R_1} \cdot \frac{A_0 \beta \omega_B}{s + \omega_B (1 + A_0 \beta)} \approx -\frac{R_2}{R_1} \frac{1}{\frac{s}{\omega_H} + 1} \quad \omega_H = \frac{\omega_T}{A_0 / (1 + A_0 \beta)} \approx \beta \omega_T$$

(Q4) 90 dB open loop gain. $f_T = 5 \text{ MHz}$.

①. $f_B?$ $f_B = f_T / A_o = \frac{5 \times 10^6}{31623} = 158 \text{ Hz}$.

③. in inverting amplifier. $A_v = 50 \text{ dB}$. BW?

$$A_{vol} = |R_2/R_1| = 50 \text{ dB}. \quad \omega_{-3\text{dB}} = \beta \omega_T, \quad \beta = \frac{1}{1 + A_{vol}} =$$
$$f_H = 15.8 \text{ kHz}$$

~~Q5~~