

EE 105 Discussion

Welcome!

K. Peleaux & Qianyi Xie

Today


- Lab
- Non-ideal OpAmp
 - Gain-BW
 - Gain Error in Feedback
 - Two-pole System
 - Input Offset
 - Slew Rate

Lab


- Pre-Lab
 - Turn in Pre-Lab before the start of your lab session
 - **Berkeley Time**
- Lab report
 - Turn in lab report before the start of your next lab session
 - **Berkeley Time**

Non-Ideal OpAmp

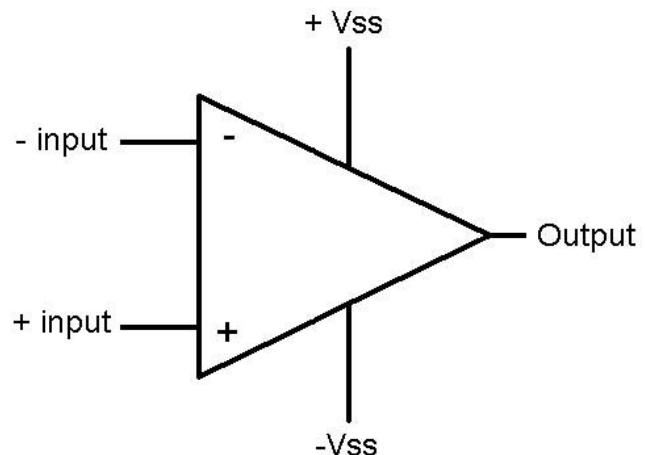- Finite Gain
- Finite Input Impedance
- Finite Output Impedance
- Input Offset Current
- Input Offset Voltage





Non-Ideal OpAmp

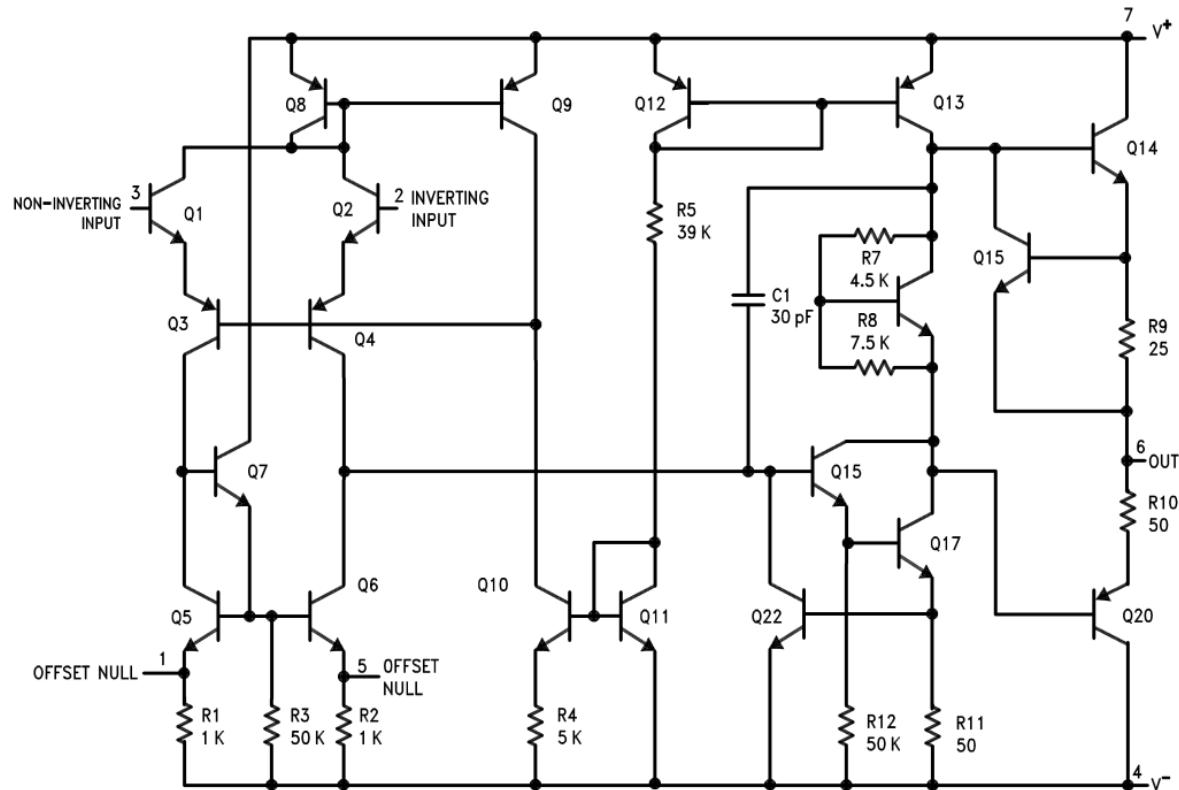


Gain-BW

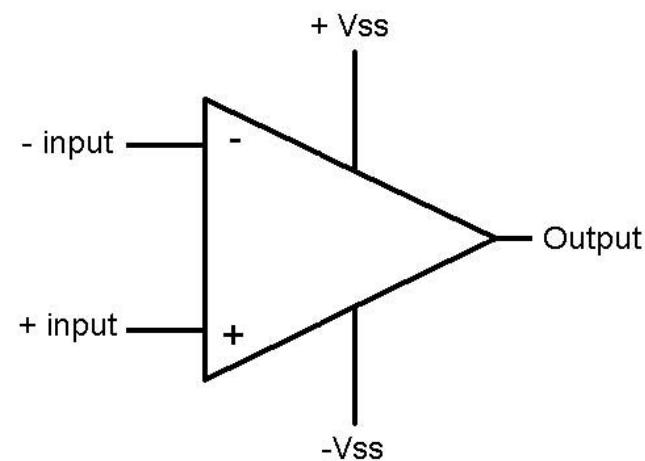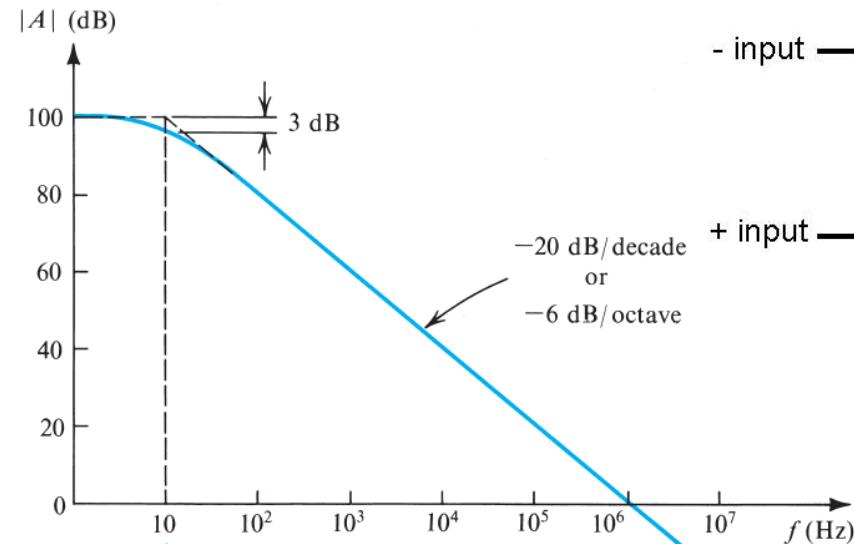
- DC Gain
- 3dB Frequency
- Unity-Gain Frequency




Gain Error in Feedback

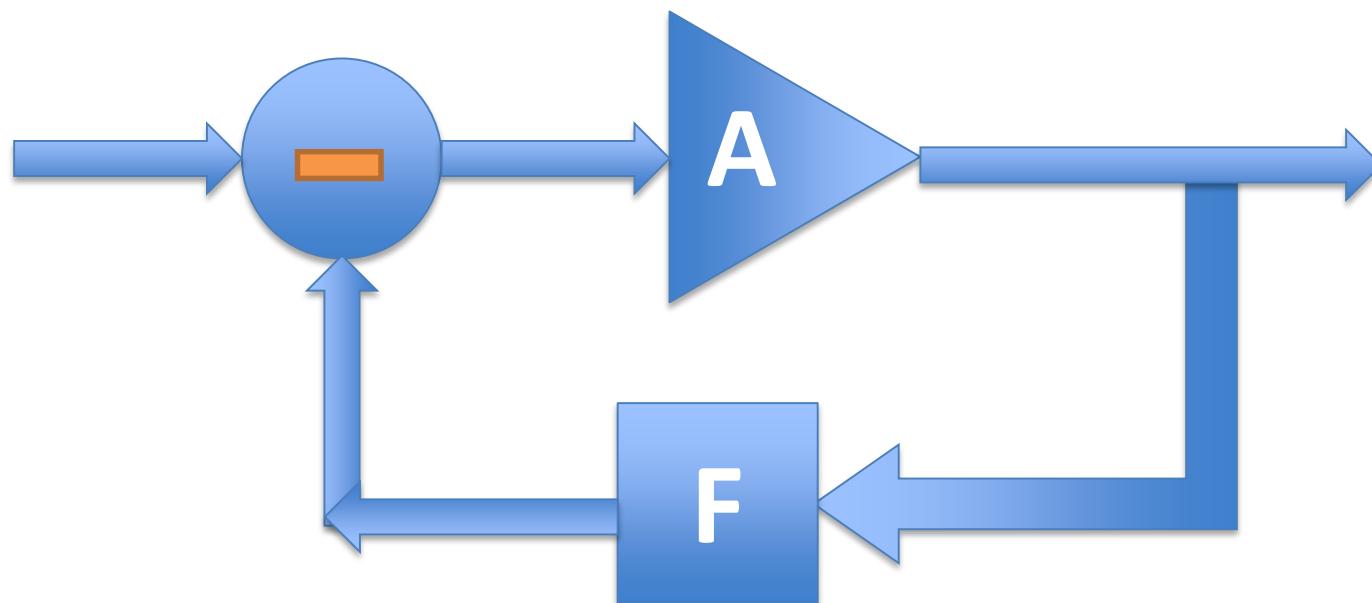


Two-pole System

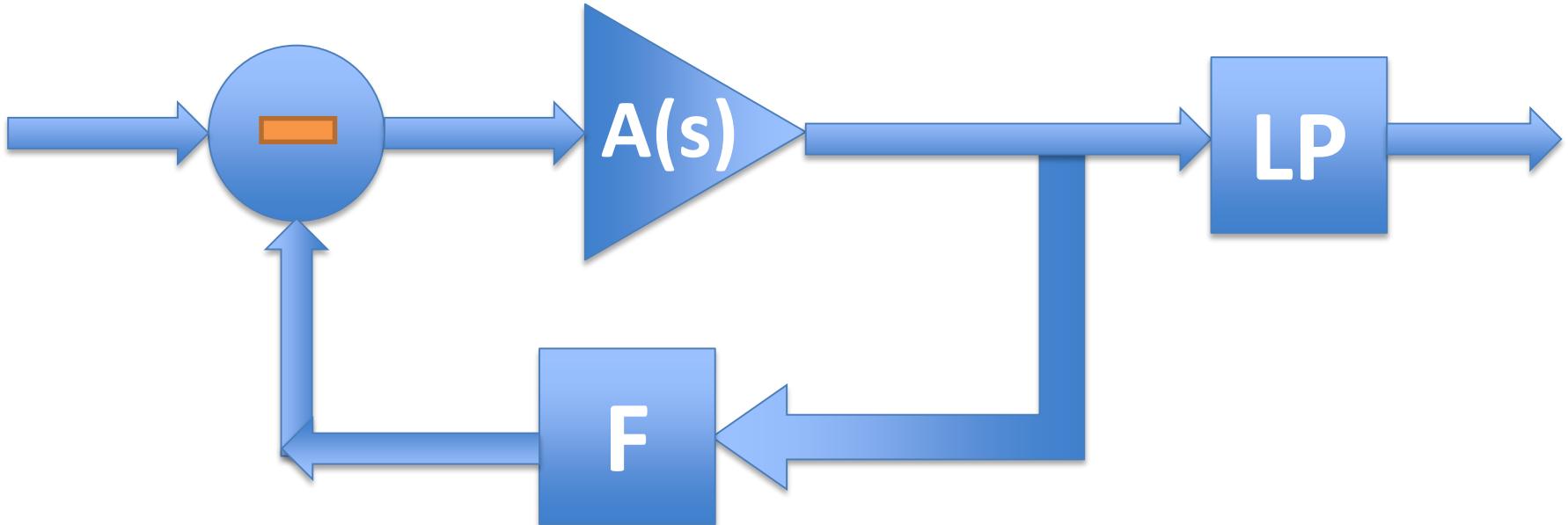


Two-pole System

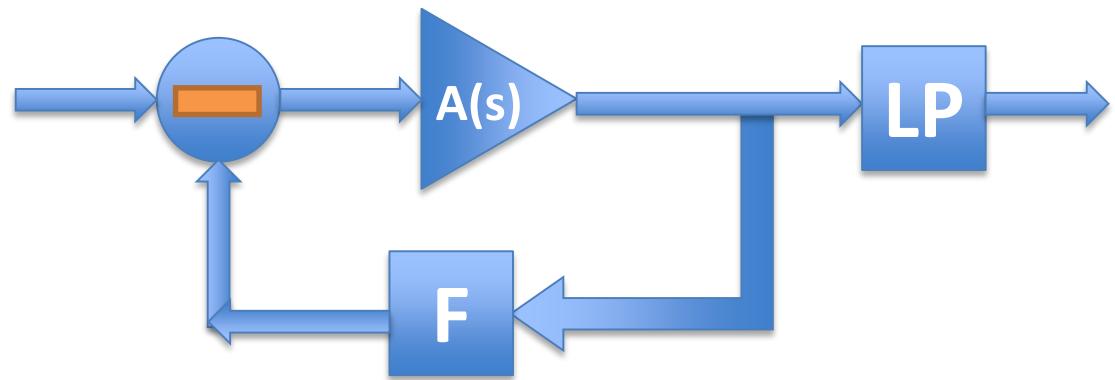

Two-pole System

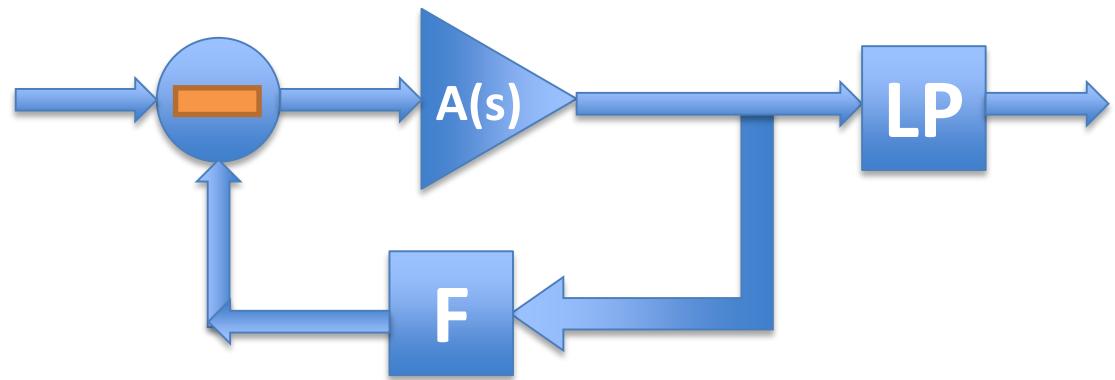


Input Offset

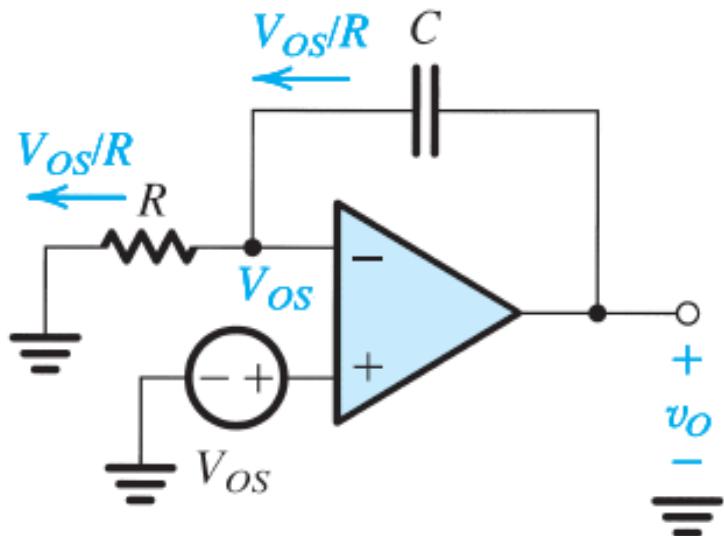

Determine the effect of V_{os} on v_o

Slew Rate

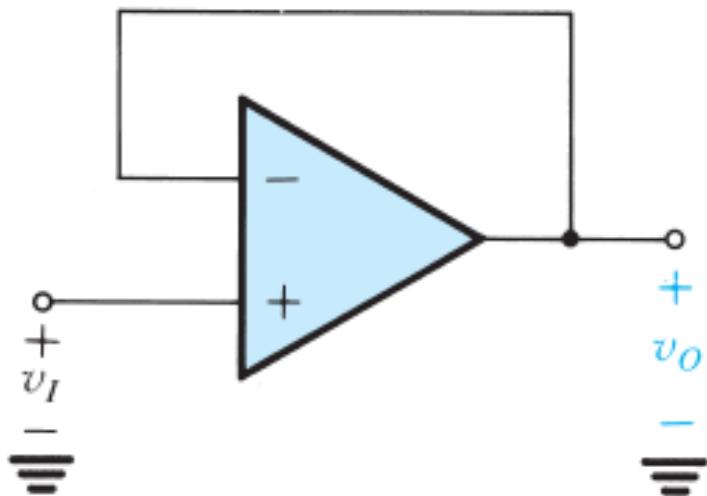

$$v_I = V \sin \omega t$$

$$\frac{dv_o}{dt} = ?$$

