


University of California  
College of Engineering  
Department of Electrical Engineering and Computer Sciences

Problem Set #12  
Review Problems - Not Due

EECS105

FALL, 1998

1. P8.8
2. This circuit buffers the small-signal current from a photodiode. The small-signal model for the photodiode is shown.  $I_{sup} = 125 \mu\text{A}$ ,  $r_{oc} = 250 \text{ k}\Omega$ , and  $L = 2 \mu\text{m}$ . Use the MOSFET parameters from p. 319. (Note the typo in the channel length modulation parameters.  $\lambda n = 0.067 \text{ V}^{-1}$ .)
  - (a) Given that  $I_{out} = 0 \text{ A}$  and  $I_{BIAS} = -125 \mu\text{A}$ . Select the width  $W$  of the NMOS such that the DC bias on the photodiode is  $V_D = -1.25 \text{ V}$ .
  - (b) Draw the two-port small-signal model for this amplifier (with source and load).
  - (c) Find the numerical value of the input resistance  $R_{in}$  of this amplifier.
  - (d) Find the numerical value of the output resistance  $R_{out}$  of this amplifier.
  - (e) Find the overall current gain  $i_{out}/i_s$  for this amplifier for the case where  $R_S = 50 \text{ k}\Omega$  and  $R_L = 100 \text{ k}\Omega$ .

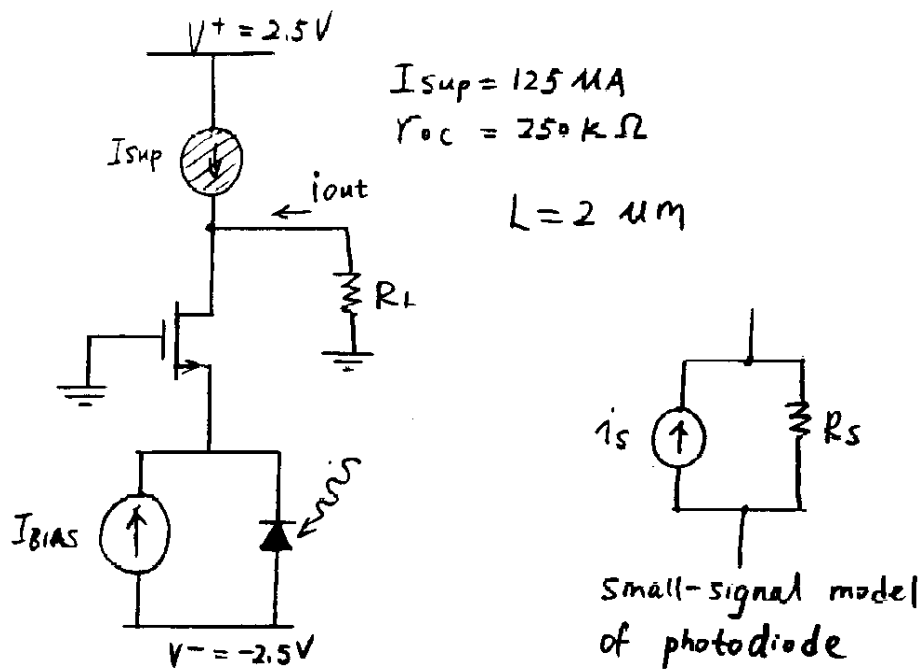


Question 2

3. P9.17



- (b) Two identical inverters are located  $1000 \mu\text{m}$  from the driving inverter. The connecting wire is  $2 \mu\text{m}$  wide aluminum and lies on a deposited glass and field oxide layer. The total thickness of the dielectric layer is  $1.0 \mu\text{m}$  and you can assume it behaves like a parallel capacitor. The permittivity of the dielectric is  $3.9\epsilon_0$ . Calculate the propagation delay  $t_p$ .
- (c) What is the static power consumed by this circuit?
- (d) Calculate the device widths such that  $C_{DB} = 100 \text{ fF}$  while maintaining the same  $V_M$ .
- (e) What is  $t_p$  for the device sizes calculated in (d)?

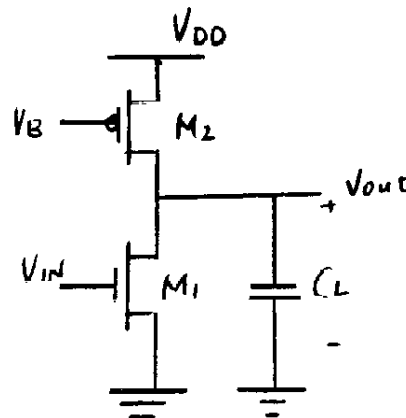

Question 6.