Slides Week 1, ECS 105, Spring 2001, A. R. Neureuther



Analog Integrated Circuits

How Does a Digital Camera Work?

 Physics (semiconductor junction) » Photons => charge => voltage Analog Circuits » Amplify, gray level conversion Digital Circuits » Encode, store, move, play Analog Circuits » Display drivers

Model for Photo Detector

 Film sensitivity ~ 3x10⁴ photons $\Delta Q_{\rm S} = 3 \times 10^4$ electrons Junction capacitance C₁ ~ 30 fF • $\Delta V_{S} = \Delta Q/C_{1} = 3 \times 10^{4} \times 1.6 \times 10^{-19}/3 \times 10^{-14}$ R_S $\Delta V_s = 160 \text{ mV}$ ╈ Series resistance R_s = 200 Ohms C_J DQ V_{IN} $V_{\text{SOURCE}} = V_{\text{BIAS}} + \Delta V_{\text{S}}$ $= V_{BIAS} + \Delta Q/C_{I}$

Analog Integrated Circuits

Current to Voltage Conversion



Analog Integrated Circuits

Op-Amps are Ideal but EE 105 is Not

- Ideal Op-Amp properties
 - » No input current (Infinite R_{IN}!) get these?
 - » V_{_} = V₊ (Infinite voltage gain! With feedback) ← Topic for EE 140
- Circuit configurations give the leverage to build nearly ideal circuits from devices with les than idea properties.

Don't forget about Op-Amps from EE 40 as in EE 105 we will use Op-Amps to study circuit concepts like frequency-response.

Back to the Future

- 3 MegaPixels with 3 colors requires nearly 10M Op-Amps.
- If each draws 100 μ A, the battery must supply 1000A. A car battery would last only 3 minutes!
- Solution: Analog switch array of 10 levels and 2¹⁰ 1024 factor of sharing. Resistance and Capacitance of

10 analog switches in series

1024 Photodiodes

R_{SA} = 10*10 kOhms = 100 kOhms

Model For Switching and Amplifier



 $\mathbf{V}_{\text{OUT}} = \mathbf{V}_{\text{R}} - \mathbf{R}_{\text{F}} \{ (\mathbf{V}_{\text{BIAS}} + \Delta \mathbf{V}_{\text{S}} - \mathbf{V}_{\text{R}}) / (\mathbf{R}_{\text{S}+} \mathbf{R}_{\text{S}A}) \}$

 $\Delta V_{\rm S}$ is 10 times smaller due to $C_{\rm SA}$

From 200 Ohms to 100,200 Ohms => 500X smaller signal!

Analog Integrated Circuits

Simple EE 105 Amplifier



Circuit to Hold the Charge Longer

• Problem C_J Discharges Quickly T = C_J*R_{SA} = 30fF * 100k Ω = 3*10⁻¹⁰ Sec

 Solution: Add Value Through Circuit Design of High Input Resistance Amplifier

Analog Integrated Circuits

High Input Impedance Circuit

 $R_{E} = 30 \text{ k}\Omega \quad R_{IN EQ} = R_{IN} + (\beta + 1)R_{E} = 3.06 \text{ M}\Omega$ 32 times less current $R_{S} \quad R_{SA} \quad i_{IN} \quad f_{IN} \quad$

 $V_{OUT} = [\Delta V_S / (R_S + R_{SA} + R_{IN EQ})](-\beta)R_{LOAD} = 33 \text{ mV}$ 37 times smaller gain

Analog Integrated Circuits

Adding a Second Stage



Analog Integrated Circuits

Visualizing as a Multistage Amplifier



Analog Integrated Circuits

Visualizing as an Equivalent Two-Port



$$\begin{split} R_{\rm IN} &= R_{\rm SA} + R_{\rm IN \ EQ1} \\ G_{\rm M} &= [1/(R_{\rm S} + R_{\rm SA} + R_{\rm IN \ EQ1})](-\beta_1)R_{\rm in2} \ (1/R_{\rm in2})(-\beta_2) \\ R_{\rm OUT} &= {\rm Infinite} \end{split}$$

Analog Integrated Circuits

Multistage Amplifiers



This example from the reading in Chapter 8 this week.

Classification of Two-Port Amplifiers



Analog Integrated Circuits

What Goes in the Amplifier Box



Material from Chapter 8 from week 11.

Analog Integrated Circuits

Small Signal Models for Transistors





MOS Week 5

BJT Week 8

Analog Integrated Circuits

Layout of Transistors





Week 2

Week 8