

Homework Assignment #3

Due in the 105 box on the 2nd floor of Cory, 5pm Friday 2/4/2010

1. [30] "**No calculator**" questions. You should be able to answer these quickly without using a calculator.
 - a) A junction is doped with $N_A=1e15$ boron atoms per cc, and $N_D = 1e14$ arsenic atoms per cc. Calculate the built-in potential at room temperature.
 - b) In the previous junction, if the doping on one side of the junction is increased by 10x, how does the built-in potential change at room temp?
 - c) In the previous junction running at a particular bias voltage, if the hole current across the junction is 1mA, what is a rough estimate for the electron current?
 - d) if the temperature changes by +/- 30C around room temperature, what is the percentage change in the built-in potential for any semiconductor diode?
 - e) You have a diode with $I_S = 1e-16$. What is the current with an applied voltage of 300mV? What is the voltage with an applied current of 1uA?
 - f) If you have ten identical diodes, and each one passes 1mA when biased at 0.7V,
 - i) what current will be conducted at 0.7V with all diodes in parallel?
 - ii) what current will be conducted at 0.7V with all diodes in series?
 - iii) what voltage will be necessary to achieve 1mA with all diodes in parallel?
 - iv) what voltage will be necessary to achieve 1mA with all diodes in series?
2. [20] You bias a diode at 600mV with a current of 26uA at room temperature, and then apply a 10mV sinusoidal signal.
 - a. Write an exact expression for the output current. Calculate the maximum and minimum currents through the diode with this bias. (You may use some silicon devices to do this calculation)
 - b. Estimate the small signal resistance, r_d , of the diode at this bias point ($I_d=26uA$). You should be able to do this without a calculator.
 - c. Calculate the small signal current through the diode
 - d. Compare the large-signal calculation from part a to the linearized estimate of total current (bias current plus small-signal current from part c). What is the % error?
 - e. Would your error be this small if you had used a 100mV sinusoidal signal? What about a 1V sinusoidal signal?
3. [50] The voltage doubler circuit in Figures 3.57 and 3.58 can also be used as a low cost power supply for small loads. Assuming a 110VAC 60Hz input, $C1=100nF$, a 3V Zener diode on the output, and steady-state operation:
 - a. Sketch a cycle or two of the waveforms at the input, X, and the output. Clearly label your axes!
 - b. Estimate the charge on the right plate of C1 when V_{in} is at its minimum, 3V, and at its maximum.
 - c. Describe where that charge comes from, and where it goes.
 - d. Calculate the current through the Zener diode.
 - e. Use spice to verify parts a and d, and turn in your plots.