

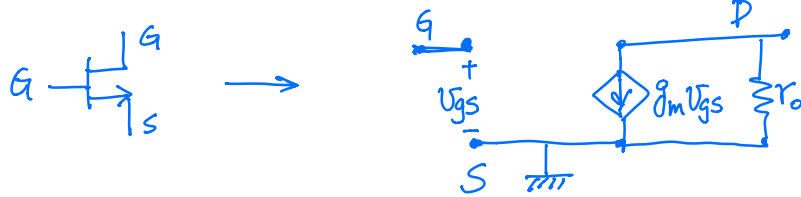


Small-Signal Model : Hybrid π

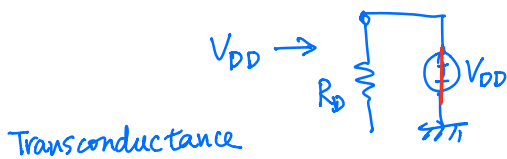

Example

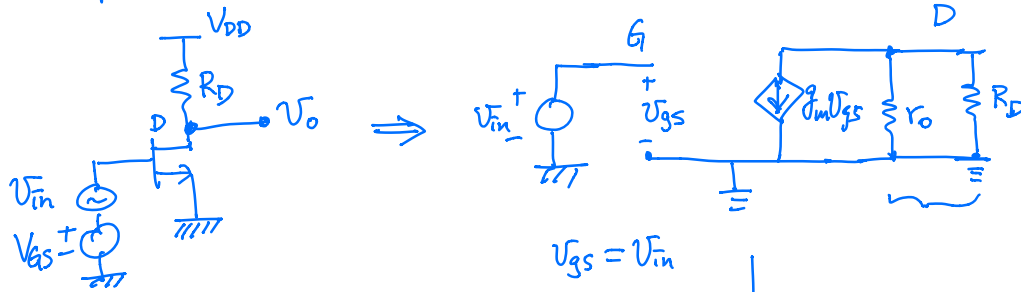

$$g_m = \frac{\partial i_D}{\partial v_{gs}} = k_n \cdot v_{ov}$$


$$[S] = \left[\frac{mA}{V} \right] \quad \left[\frac{mA}{V^2} \right] [V]$$

$$r_o = \frac{1}{\frac{\partial i_D}{\partial v_{ds}}} \Rightarrow \left[\frac{V}{A} \right] = [S\Omega] \quad A_v = \frac{v_o}{v_{in}} = -g_m (r_o \parallel R_D)$$

want this as large as possible

Think $r_o \sim 100k\Omega$

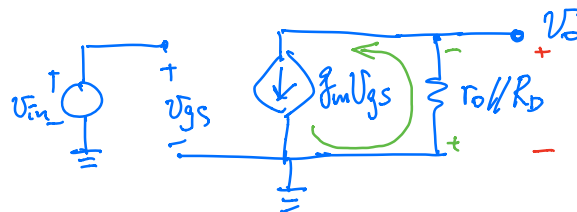If $R_D = 5k\Omega$ $r_o \parallel R_D \approx R_D$




$$v_o = -(g_m v_{gs}) \cdot (r_o \parallel R_D)$$

$$v_{in} = v_{gs}$$

$$[S] \times [S\Omega] = [1]$$

Design Example

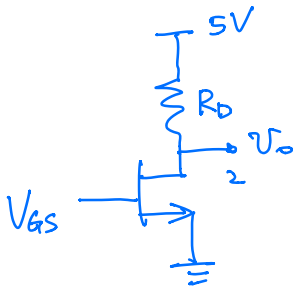

Assume $k_n = 1 \text{ mA/V}^2$, $V_{t,n} = 1 \text{ V}$

Goal: obtain $|A_v| = 10$

$$|A_v| = g_m \cdot (r_o // R_D) \approx g_m R_D = 10$$

$r_o \gg R_D$ ↑

Choose $I_D = 2 \text{ mA} \Rightarrow g_m = k_n V_{ov} = 2 \text{ mS}$

$$I_D = \frac{1}{2} k_n V_{ov}^2 \Rightarrow V_{ov} = 2 \text{ V}$$

$$V_{DS, \text{min}} = V_{GS} - V_t = V_{ov} = 2 \text{ V}$$



Choose $V_D = 3.5 \text{ V}$

$$R_D = \frac{5 - 3.5}{2 \text{ mA}} = \frac{1.5 \text{ V}}{2 \text{ mA}} = 0.75 \text{ k}\Omega$$

$$A_v = 2 \text{ mS} \times 0.75 \text{ k}\Omega = 1.5$$

Alternative Design

Superior Bias Scheme

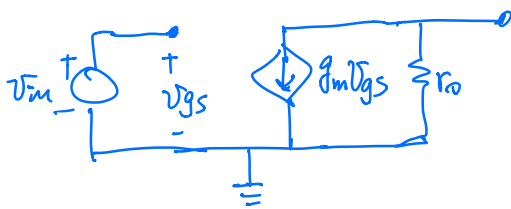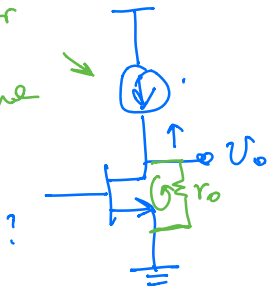

$k_n = 1 \text{ mA/V}^2$, $V_{t,n} = 1 \text{ V}$ $\lambda \rightarrow r_o = 100 \text{ k}\Omega$

$g_m = k_n V_{ov} \rightarrow$ Express g_m in terms of I_D

$$I_D = \frac{1}{2} k_n V_{ov}^2 \Rightarrow \sqrt{2 I_D k_n} = \sqrt{k_n^2 V_{ov}^2} = k_n V_{ov}$$

$$g_m = \sqrt{2 I_D k_n}$$

$$v_o = -(g_m v_{gs}) r_o \Rightarrow A_v = -g_m r_o$$

↑

Intrinsic voltage gain of a transistor

$$|A_v| = g_m \cdot 100 \text{ k}\Omega = 10$$


$$g_m = \frac{10}{10^5} = 10^{-4} \text{ S}$$

$$10^{-4} = \sqrt{2 I_D k_n} \Rightarrow 10^{-8} = 2 I_D k_n$$

10^{-3}
↓
 k_n

$$I_D = \frac{1}{2} \times 10^{-8} = 5 \text{ }\mu\text{A}$$

$\Rightarrow V_{ov}, \Rightarrow V_{GS}$

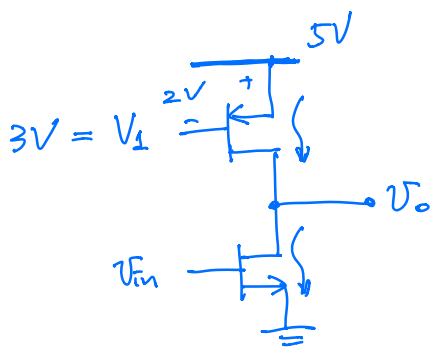

$$I_D = I_{D,p} = I_{D,n}$$

$$= \frac{1}{2} \mu_p C_{ox} |V_{ov,p}|^2$$

$$\mu_n = \mu_p = 1 \text{ mA/V}^2$$


$$V_{t,p} = -1 \text{ V}$$

Want $I_D = 0.5 \text{ mA}$

$$|V_{ov,p}| = \frac{2I_D}{\mu_p} = 1 \text{ V} = |V_{gs,p}| - |V_{t,p}|$$


$$g_m = \sqrt{2I_D \mu_n} = \sqrt{2 \times 0.5 \text{ mA} \cdot 1 \text{ mA/V}^2}$$

$$= 1 \text{ mA/V} = 1 \text{ mS}$$

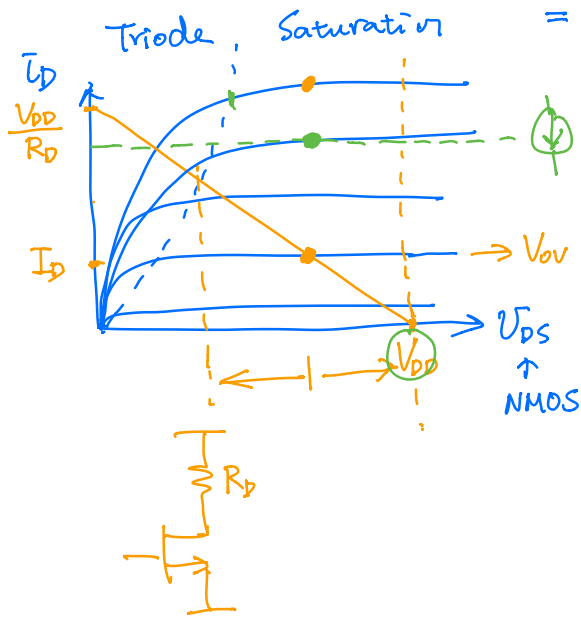


Recap small-signal analysis

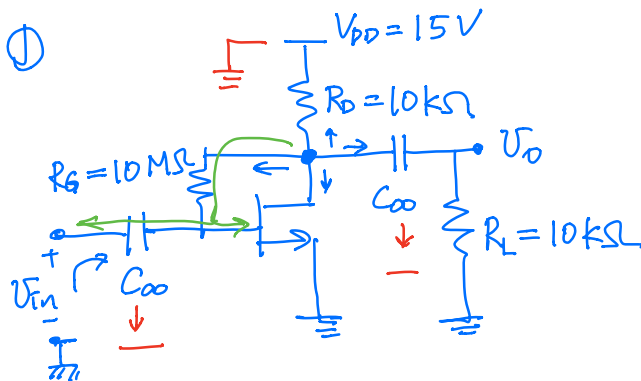
- ① Solve DC bias problem
- ② Calculate g_m , r_o
- ③ Draw AC equivalent circuit
 - Replace independent voltage source → short ckt
 - Replace independent current source → open
 - MOS → Hybrid π
- ④ Do KCV, KVL, solve V_o


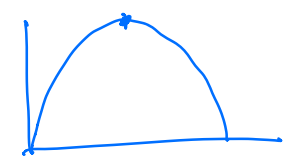
$$\begin{cases} k_n = 0.25 \text{ mA/V}^2 \\ V_{tn} = 1.5 \text{ V} \\ \lambda = \frac{1}{50 \text{ V}} \end{cases}$$



DC \rightarrow $C_{oo} \equiv$ Open ckt

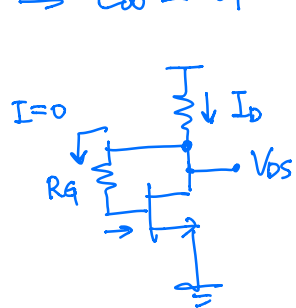

$V_{gs} = V_{ds}$

(i) $I_D = \frac{1}{2} k_n V_{ov}^2 = \frac{1}{2} k_n (V_{gs} - V_{tn})^2 = \frac{1}{2} k_n (V_{ds} - V_{tn})^2$

KVL:

(ii) $V_{DD} = I_D R_D + V_{ds}$

\Rightarrow Quadratic equation for V_{ds}


$V_{ds} = 4.4 \text{ V}$ \hookrightarrow 2 solutions
 Only one is physical

$\Rightarrow I_D = 1.06 \text{ mA}$


Check KVL indeed satisfied

② $I_m = k_n V_{ov} = (0.25 \text{ mA/V}^2)(4.4 - 1.5) \text{ V} = 0.725 \text{ mA/V} = 0.725 \text{ mS}$

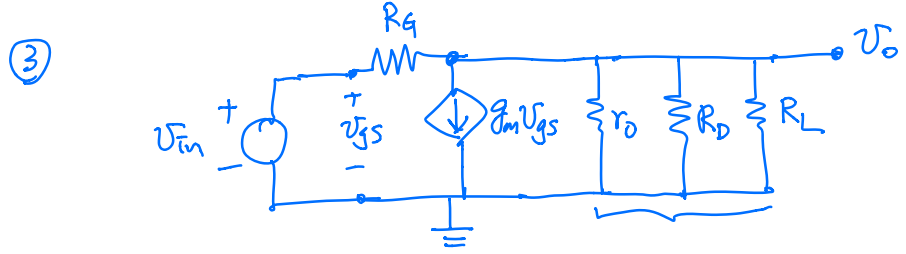$r_o = \frac{1}{\lambda I_D} = 47 \text{ k}\Omega$



$U_{gs} = V_{in}$

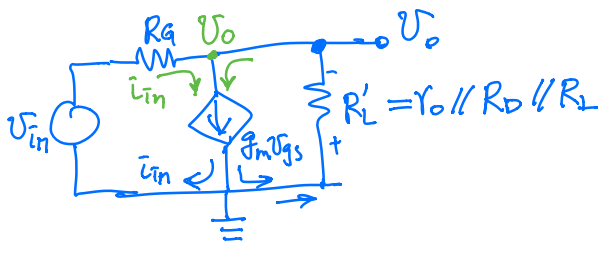

$$\bar{I}_{in} = \frac{V_{in} - V_o}{R_G}$$

$$V_o = -(\underbrace{g_m V_{gs}}_{V_{in}} - \bar{I}_{in}) \cdot R_L'$$



$$A_v = \frac{V_o}{V_{in}} = -g_m R_L' \frac{1 - \cancel{\frac{g_m R_G}{1 + \frac{R_L'}{R_G}}}}$$

$$R_L' = r_o \parallel R_D \parallel R_L \approx 4.5 \text{ k}\Omega$$

$\downarrow \quad \downarrow \quad \downarrow$
 $47 \text{ k}\Omega \quad 10 \text{ k}\Omega \quad 10 \text{ k}\Omega$
 \downarrow
 $5 \text{ k}\Omega$

$$g_m = 0.725 \text{ mS}, \quad R_G = 10 \text{ M}\Omega$$
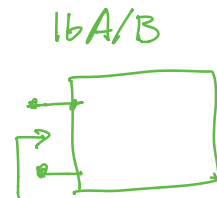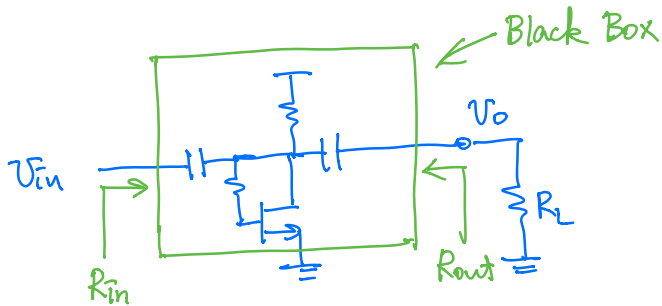
$$A_v \approx -g_m R_L' = -3.3 \text{ V/V}$$



Thevenin equivalent
ckt.

Input Resistance R_{in} of the "Whole" amplifier:

Replace DC source with short
 current " open
 $C_{\infty} \rightarrow$ short

* Include load, R_L