

- * Website, courses up
- * Sign up Piazza
- * Lab, Discussion start next week
 - ↳ SPICE

EE105

Microelectronic Devices and Circuits


Prof. Ming C. Wu

wu@eecs.berkeley.edu


511 Sutardja Dai Hall (SDH)

Linear Time-Invariant (LTI) System


- Response of a system

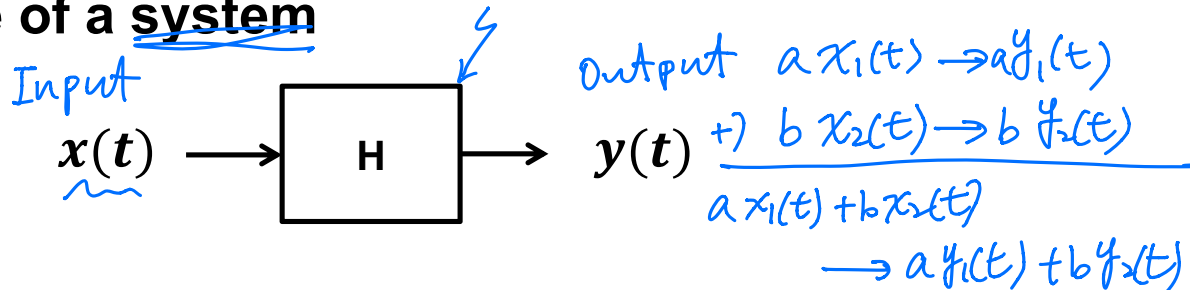

- The system is linear if

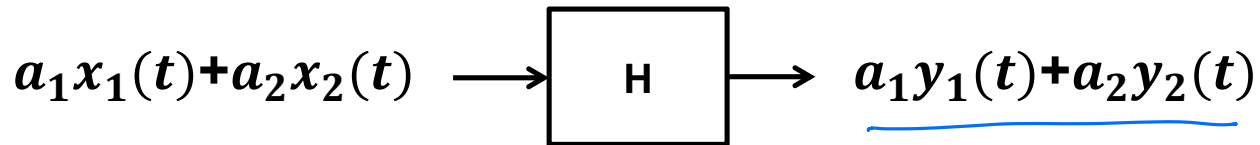


- The system is time-invariant if

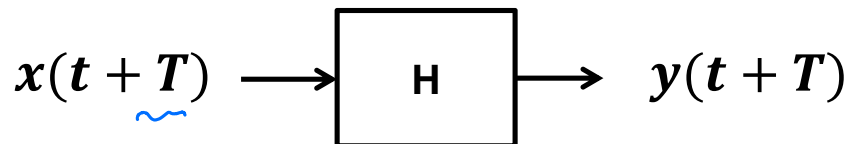

What's Nice about LTI System?

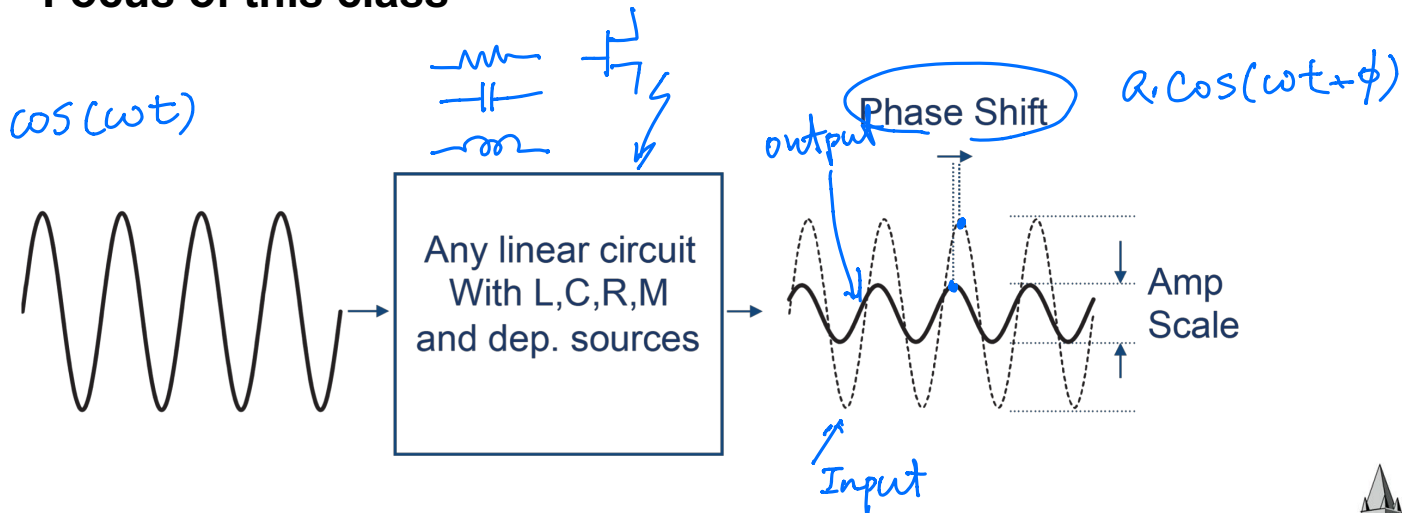
- Can use superposition
- Easy conversion between time and frequency response
- Most systems in real life are LTI systems
 - Focus of this class



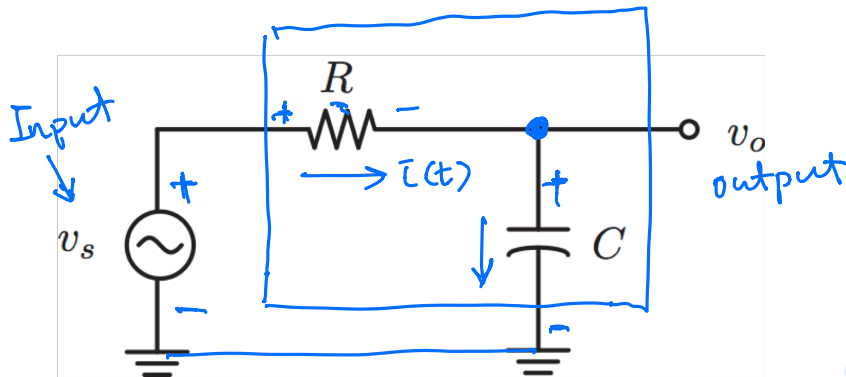Example: Low Pass Filter (LPF)

$$\left[\frac{\text{rad}}{\text{s}} \right] \xrightarrow{\omega = 2\pi \cdot f} \left[\text{Hz} \right] = \left[\frac{1}{\text{s}} \right]$$

- **Input signal:** $v_s(t) = V_s \cos(\omega t)$
- **We know that:** $v_o(t) = \underbrace{K \cdot V_s}_{V_0} \cos(\omega t + \phi)$
 - Phase shift ϕ
 - Amp scale V_0



$$v_o(t) = v_s(t) - i(t)R$$

$$i(t) = C \frac{dv_o}{dt}$$

$$v_o(t) = v_s(t) - RC \frac{dv_o}{dt}$$

$$v_s(t) = v_o(t) + \tau \frac{dv_o}{dt} \quad \tau = RC$$

$$Q = C \cdot V \quad \tau_c = \frac{dQ}{dt} = C \cdot \frac{dV}{dt} \quad [F] = \left[\frac{\text{Coul}}{\text{V}} \right]$$


Exponential Representation

- Euler's Theorem

$j = \text{imaginary unit}$

Phase
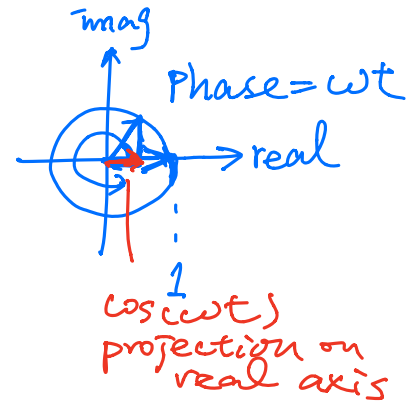
$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$



- $\sin(\omega t)$ and $\cos(\omega t)$ can be represented by linear combination of complex exponential:

$$\cos(\omega t) = \frac{1}{2} (e^{j\omega t} + e^{-j\omega t})$$
$$\sin(\omega t) = \frac{1}{2j} (e^{j\omega t} - e^{-j\omega t})$$

Magic: Turn Diff Eq into Algebraic Eq

- Integration and differentiation are trivial with complex numbers:

$$\frac{d}{dt} e^{j\omega t} = j\omega e^{j\omega t} \qquad \int e^{i\omega\tau} d\tau = \frac{1}{i\omega} e^{i\omega t}$$

- Any ODE is now trivial algebraic manipulations ... in fact, we'll show that you don't even need to directly derive the ODE by using phasors
- The key is to observe that the current/voltage relation for any element can be derived for complex exponential excitation

Solving LPF with Phasors

- Let's excite the system with a complex exp:

$$\begin{aligned}
 & \rightarrow v_s(t) = v_0(t) + \tau \frac{dv_0}{dt} \\
 & v_s(t) = \underline{V_s e^{j\omega t}} \\
 & v_o(t) = |V_0| e^{j(\omega t + \phi)} = \underline{V_0 e^{j\omega t}}
 \end{aligned}$$

use j to avoid confusion

$V_0 = |V_0| e^{j\phi}$

real complex

$$\underline{V_s e^{j\omega t}} = \underline{V_0 e^{j\omega t}} + \tau \cdot \underline{j\omega \cdot V_0 e^{j\omega t}}$$

$$\underline{V_s = V_0(1 + j\omega \cdot \tau)}$$

Transfer fx

$$\frac{V_0}{V_s} = \frac{1}{(1 + j\omega \cdot \tau)}$$

Easy!!!

Magnitude and Phase Response

- The system is characterized by the complex function

$$\underline{H(\omega)} = \frac{V_0}{V_s} = \frac{1}{(1 + j\omega \cdot \tau)}$$

Frequency Domain

$$\tau = RC \\ [s] = [R][C]$$

- The magnitude and phase response match our previous calculation:

magnitude


$$|H(\omega)| = \left| \frac{V_0}{V_s} \right| = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

$$\angle H(\omega) = -\tan^{-1} \omega\tau$$

$$P = a + jb$$

$$|P| = \sqrt{a^2 + b^2}$$
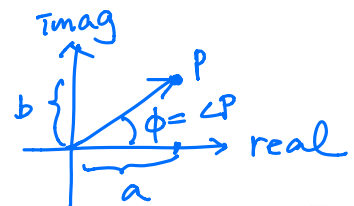
$$\angle P = \tan^{-1}\left(\frac{b}{a}\right)$$




Why did it work?

- Again, the system is linear:

$$y = \mathbf{L}(x_1 + x_2) = \mathbf{L}(x_1) + \mathbf{L}(x_2)$$

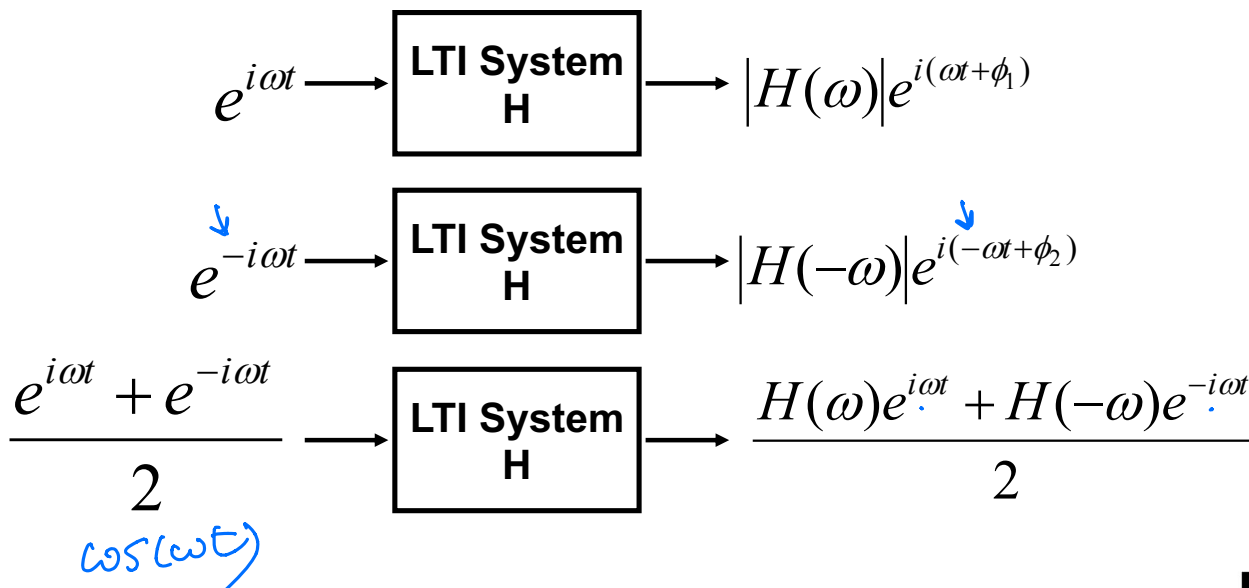- To find the response to a sinusoid, we can find the response to $e^{i\omega t}$ and $e^{-i\omega t}$ and sum the results:



(cont.)

- Since the input is real, the output has to be real:

$$y(t) = \frac{H(\omega)e^{i\omega t} + H(-\omega)e^{-i\omega t}}{2}$$

- That means the second term is the conjugate of the first:

$$H(-\omega) = H(\omega)^*$$

$$\underline{|H(-\omega)| = |H(\omega)|} \quad (\text{even function})$$

$$\angle H(-\omega) = -\angle H(\omega) = -\phi \quad (\text{odd function})$$

- Therefore the output is:

$$y(t) = \frac{|H(\omega)|}{2} \left(e^{i(\omega t + \phi)} + e^{-i(\omega t + \phi)} \right)$$

$$x(t) = \cos(\omega t + \phi)$$

$$= |H(\omega)| \underline{\cos(\omega t + \phi)}$$


Phasors

$$e^{j\omega t + \phi}$$

drop $e^{j\omega t}$, track $e^{j\phi}$

- With our new confidence in complex numbers, we go full steam ahead and work directly with them ... we can even drop the time factor $e^{j\omega t}$ since it will cancel out of the equations.

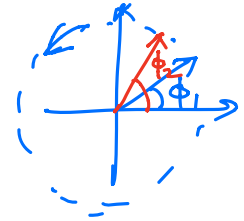- Excite system with a phasor: $\underline{\tilde{V}}_1 = \underline{V}_1 e^{j\phi_1}$
- Response will also be phasor: $\underline{\tilde{V}}_2 = \underline{V}_2 e^{j\phi_2}$



- For those with a Linear System background, we're going to work in the frequency domain


– This is the Laplace domain with

$$s = j\omega$$

Capacitor I-V Phasor Relation

- Find the Phasor relation for current and voltage in a cap:

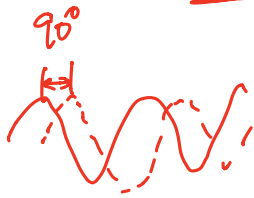
$nF = 10^{-9} F$
 $pF = 10^{-12} F$
 $fF = 10^{-15} F$



$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$i_c(t) = \underline{I_c e^{j\omega t}}$ (complex)
 $v_c(t) = \underline{V_c e^{j\omega t}}$ (complex)

different phase

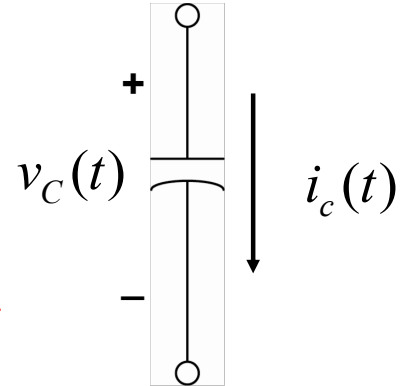

$$I_c e^{j\omega t} = C \frac{d}{dt} [V_c e^{j\omega t}]$$

$$C V_c \frac{d}{dt} e^{j\omega t} = \underline{j\omega C V_c e^{j\omega t}}$$

90° phase shift between current & voltage

$$\cancel{I_c e^{j\omega t}} = j\omega C V_c \cancel{e^{j\omega t}}$$

$$I_c = j\omega C V_c$$

Impedance

$$\frac{V_c}{I_c} = \frac{1}{j\omega C} = \underline{Z}$$

Resistor $V = IR$

$$\frac{V}{I} = R$$

$$\frac{1}{\left[\frac{F}{s}\right]} = \left[\frac{s}{F}\right] = [Z]$$


Inductor I-V Phasor Relation

- Find the Phasor relation for current and voltage in an inductor:

$$\underline{v(t)} = L \frac{di(t)}{dt} \qquad \underline{i(t)} = I e^{j\omega t}$$

Inductance [H]

$$\underline{v(t)} = V e^{j\omega t}$$

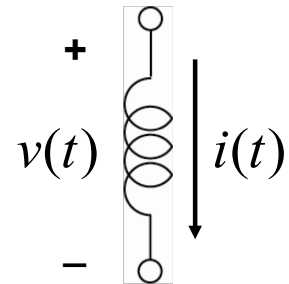

$$V e^{j\omega t} = L \frac{d}{dt} [I e^{j\omega t}]$$

$$L I \frac{d}{dt} e^{j\omega t} = j\omega L I e^{j\omega t}$$

$$\cancel{V e^{j\omega t}} = j\omega L \cancel{I e^{j\omega t}}$$

$$\underline{V} = j\omega L \underline{I}$$


$$\frac{V}{I} = j\omega L = Z_L$$

↑ ↑

$$[\frac{1}{S}] [H] = [\Omega]$$

Impede the Currents !

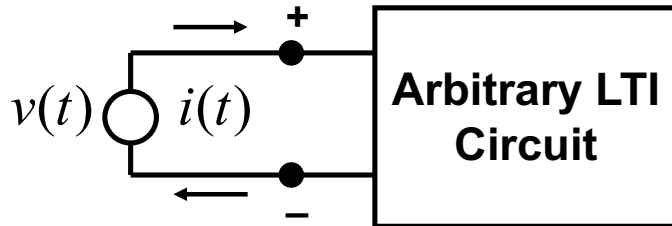- Suppose that the “input” is defined as the voltage of a terminal pair (port) and the “output” is defined as the current into the port:



$$v(t) = Ve^{j\omega t} = |V|e^{j(\omega t + \phi_v)}$$

$$i(t) = Ie^{j\omega t} = |I|e^{j(\omega t + \phi_i)}$$


- The impedance Z is defined as the ratio of the phasor voltage to phasor current (“self” transfer function)

Complex

$$\underline{Z(\omega)} = H(\omega) = \frac{V}{I} = \left| \frac{V}{I} \right| e^{j(\phi_v - \phi_i)}$$

Admit the Currents!

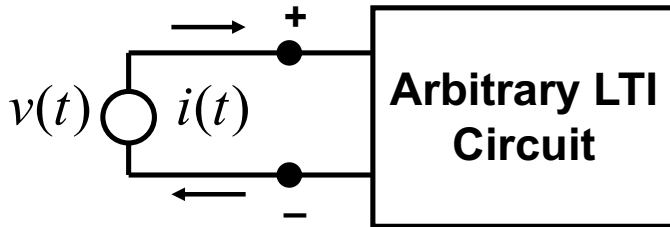- Suppose that the “input” is defined as the current of a terminal pair (port) and the “output” is defined as the voltage into the port:



$$v(t) = Ve^{j\omega t} = |V|e^{j(\omega t + \phi_v)}$$

$$i(t) = Ie^{j\omega t} = |I|e^{j(\omega t + \phi_i)}$$

- The admittance Y is defined as the ratio of the phasor current to phasor voltage (“self” transfer function)


Admittance $Y(\omega) = H(\omega) = \frac{I}{V} = \left| \frac{I}{V} \right| e^{j(\phi_i - \phi_v)}$

$[Y] = [S]$
mho Sines

$[Z] \text{ Ohm}$

Voltage and Current Gain

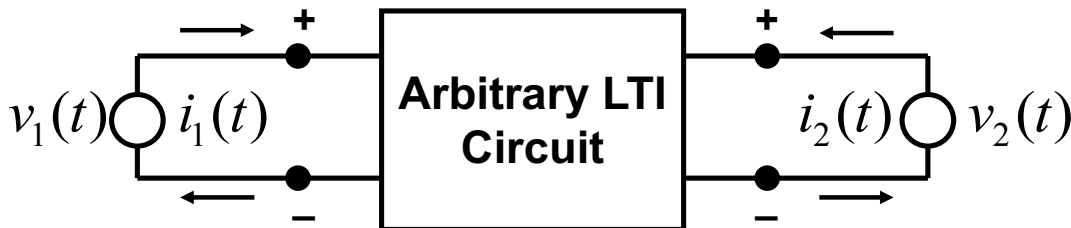- The voltage (current) gain is just the voltage (current) transfer function from one port to another port:




$$G_v(\omega) = \frac{V_2}{V_1} = \left| \frac{V_2}{V_1} \right| e^{j(\phi_2 - \phi_1)} \quad \text{Voltage Gain: complex}$$

$$G_i(\omega) = \frac{I_2}{I_1} = \left| \frac{I_2}{I_1} \right| e^{j(\phi_2 - \phi_1)} \quad \text{Current Gain: complex}$$

- If $|G| > 1$, the circuit has voltage (current) gain
- If $|G| < 1$, the circuit has loss or attenuation

Transimpedance/admittance

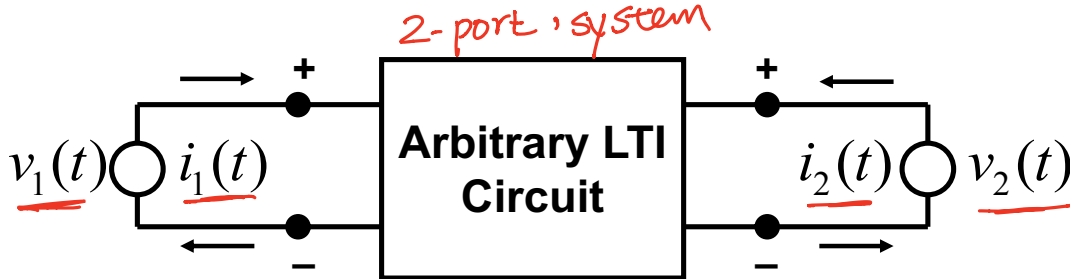- Current/voltage gain are unit-less quantities
- Sometimes we are interested in the transfer of voltage to current or vice versa



$$V = \text{Gain} = \frac{V_2}{V_1}$$

$$I = \text{Gain} = \frac{I_2}{I_1}$$

output = voltage

$$J(\omega) = \frac{V_2}{I_1} = \left| \frac{V_2}{I_1} \right| e^{j(\phi_2 - \phi_1)} \quad [\Omega] \text{ Transimpedance}$$

Input = current (I_1)

→ V_1



$$K(\omega) = \frac{I_2}{V_1} = \left| \frac{I_2}{V_1} \right| e^{j(\phi_2 - \phi_1)} \quad [S] \text{ Transconductance}$$

Direct Calculation of H (no DEs)


- To directly calculate the transfer function (impedance, trans-impedance, etc) we can generalize the circuit analysis concept from the “real” domain to the “phasor” domain
- With the concept of impedance (admittance), we can now directly analyze a circuit without explicitly writing down any differential equations
- Use KVL, KCL, mesh analysis, loop analysis, or node analysis where inductors and capacitors are treated as complex resistors

LPF Example: Again!

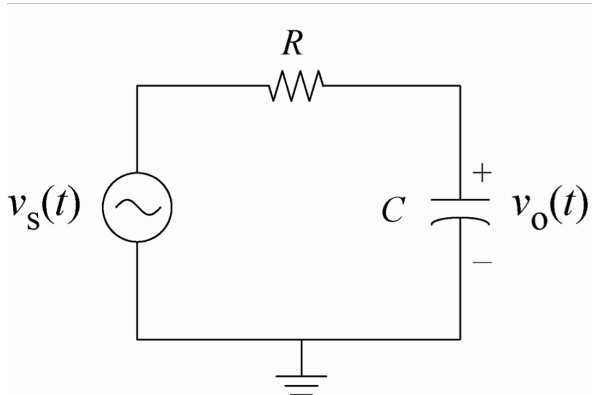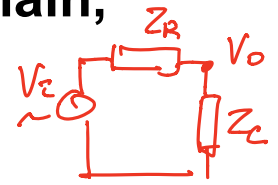- Instead of setting up the DE in the time-domain, let's do it directly in the frequency domain
- Treat the capacitor as an impedance:



time domain "real" circuit

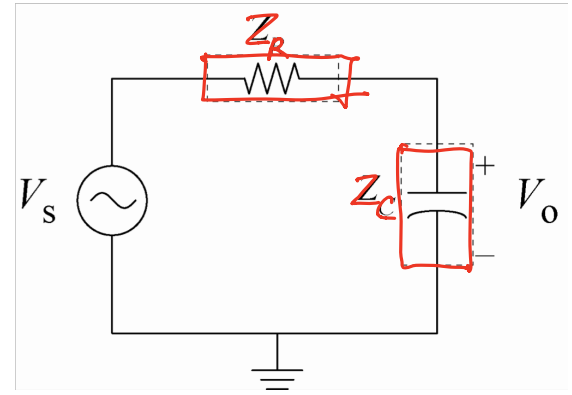

frequency domain "phasor" circuit

- We know the impedances:

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$


$$V_o = V_i \cdot \frac{Z_C}{Z_R + Z_C}$$

$$H = \frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

Bode Plots

- Simply the log-log plot of the magnitude and phase response of a circuit (impedance, transimpedance, gain, ...)
- Gives insight into the behavior of a circuit as a function of frequency
- The “log” expands the scale so that breakpoints in the transfer function are clearly delineated

Frequency Response of Low-Pass Filters

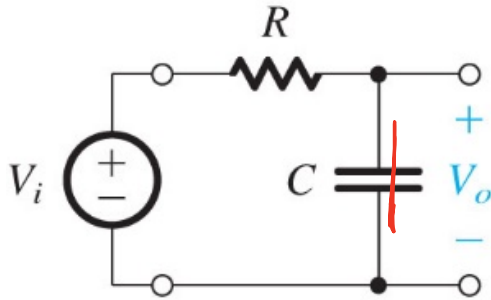

$$H(\omega) = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega / \omega_0}$$

$RC = \tau$

$$\omega_0 = \frac{1}{RC} = \frac{1}{\tau}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega / \omega_0)^2}}$$



$$\angle T(\omega) = -\tan^{-1}(\omega / \omega_0)$$

$$\omega_{3dB} = \omega_0 \quad [\text{rad/sec}]$$


$$f_{3dB} = \frac{\omega_0}{2\pi} \quad [\text{Hz}]$$

$20 \log \left| \frac{T(j\omega)}{K} \right|$ (dB)

Magnitude

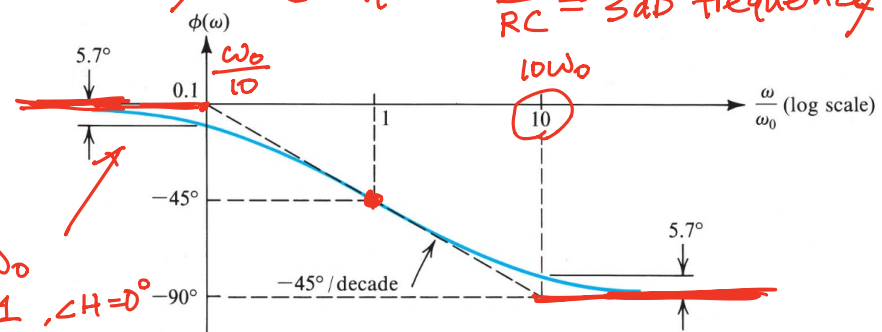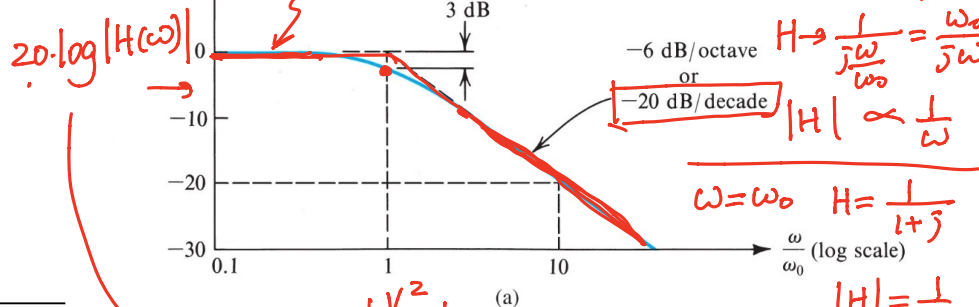

Frequency Response of High-Pass Filters

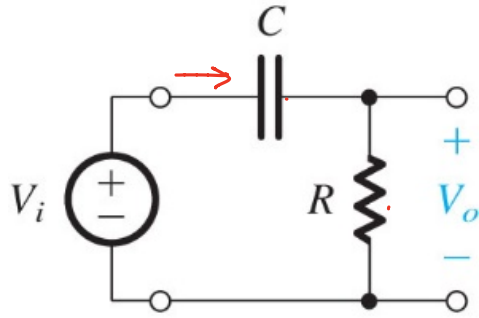

$$T(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega RC}} = \frac{1}{1 - j\omega_0 / \omega}$$



$$\omega_0 = \frac{1}{RC}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega_0 / \omega)^2}}$$

$$\angle T(\omega) = \tan^{-1}(\omega_0 / \omega)$$


$$\omega_{3dB} = \omega_0 \quad [\text{rad/sec}]$$
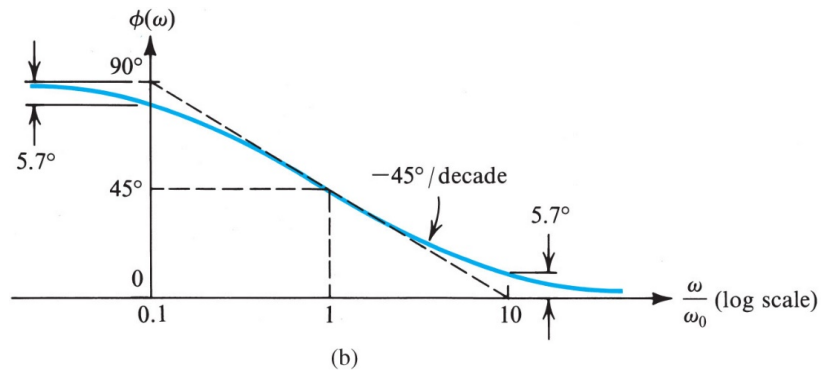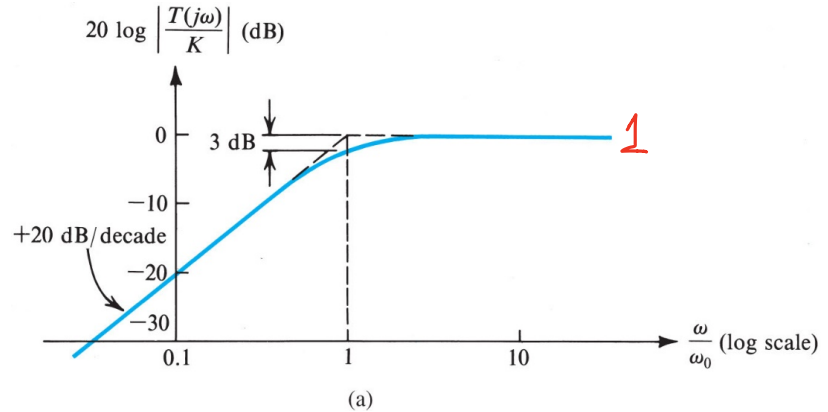
$$f_{3dB} = \frac{\omega_0}{2\pi} \quad [\text{Hz}]$$



Example: High-Pass Filter

- Using the voltage divider rule:

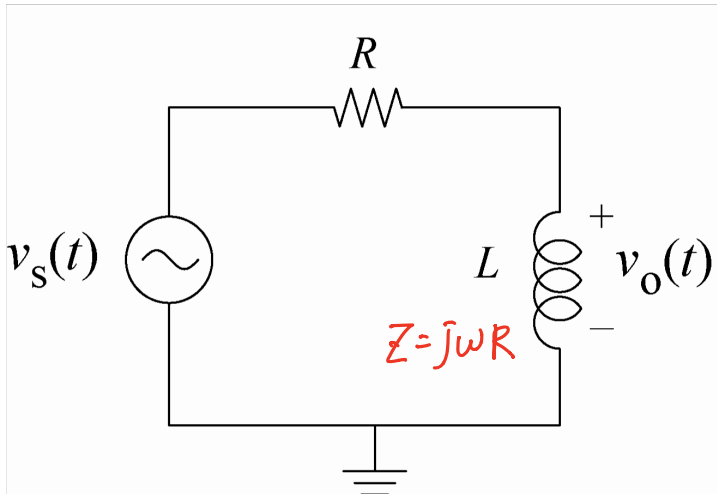

$$H(\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}}$$


$$H(\omega) = \frac{j\omega\tau}{1 + j\omega\tau}$$

$$\omega \rightarrow \infty \quad |H| \rightarrow \left| \frac{j\omega\tau}{j\omega\tau} \right| = 1$$

$$\omega \rightarrow 0 \quad |H| \rightarrow \frac{0}{1+0} = 0$$

$$\omega = \frac{1}{\tau} \quad |H| = \left| \frac{j}{1+j} \right| = \frac{1}{\sqrt{2}}$$

Approximate versus Actual Plot

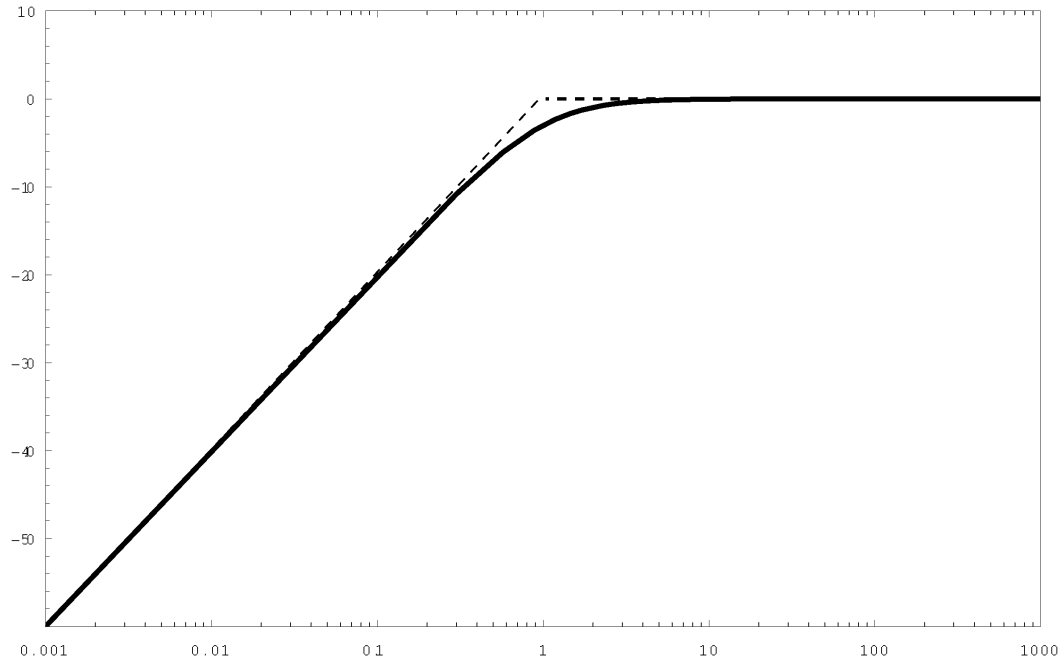


- **Approximate curve accurate away from breakpoint**
- **At breakpoint there is a 3 dB error**

HPF Phase Plot

- Phase can be naturally decomposed as well:

$$\angle H(\omega) = \angle \frac{j\omega\tau}{1+j\omega\tau} = \angle j\omega\tau + \angle \frac{1}{1+j\omega\tau} = \frac{\pi}{2} - \tan^{-1} \omega\tau$$

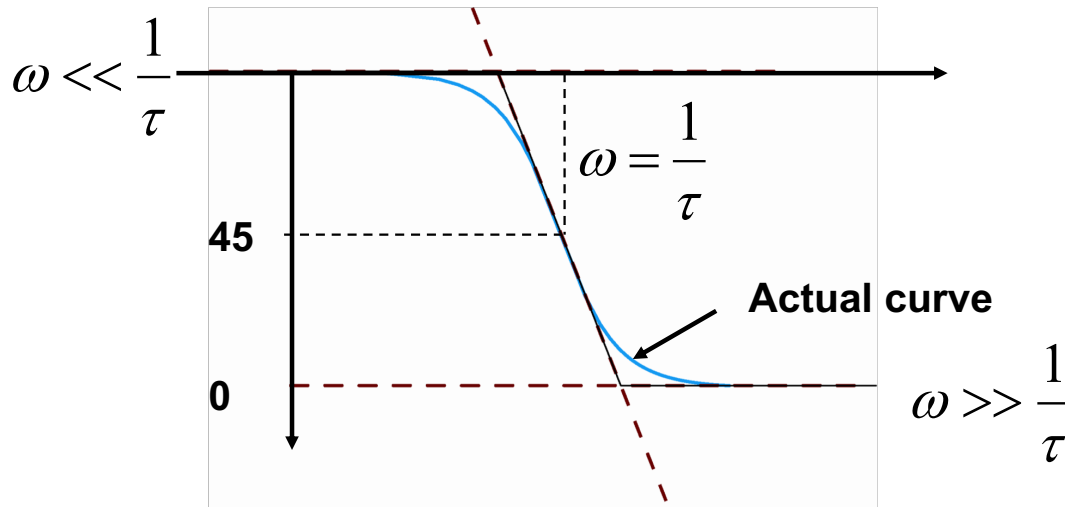- First term is simply a constant phase of 90 degrees
- The second term is the arctan function
- Estimate arctan function:



Power Flow

- The instantaneous power flow into any element is the product of the voltage and current: $P(t) = i(t)v(t)$
- For a periodic excitation, the average power is:

$$P_{av} = \int_T i(\tau)v(\tau)d\tau$$

$$i(t) = |I| \cos(\omega t + \phi_i)$$

$$v(t) = |V| \cos(\omega t + \phi_v)$$

Power = $I \times V$

- In terms of sinusoids we have

$$P_{av} = \int_T |I| \cos(\omega t + \phi_i) |V| \cos(\omega t + \phi_v) d\tau$$

$$= |I| \cdot |V| \int_T (\cos \omega t \cos \phi_i - \sin \omega t \sin \phi_i) \cdot (\cos \omega t \cos \phi_v - \sin \omega t \sin \phi_v) d\tau$$

$$= |I| \cdot |V| \int_T d\tau \cos^2 \omega t \cos \phi_i \cos \phi_v + \sin^2 \omega t \sin \phi_i \sin \phi_v + c \sin \omega t \cos \omega t$$

$$= \frac{|I| \cdot |V|}{2} (\cos \phi_i \cos \phi_v + \sin \phi_i \sin \phi_v) = \frac{|I| |V|}{2} \cos(\phi_i - \phi_v)$$

Power Flow with Phasors

$$P_{av} = \frac{|I| \cdot |V|}{2} \cos(\phi_i - \phi_v)$$

↑
Power Factor

- Note that if $(\phi_i - \phi_v) = \frac{\pi}{2}$, then $P_{av} = \frac{|I| \cdot |V|}{2} \cos\left(\frac{\pi}{2}\right) = 0$
- Important: Power is a non-linear function so we can't simply take the real part of the product of the phasors:

$$P \neq \text{Re}[I \cdot V]$$

- From our previous calculation:

$$P = \frac{|I| \cdot |V|}{2} \cos(\phi_i - \phi_v) = \frac{1}{2} \text{Re}[I \cdot V^*] = \frac{1}{2} \text{Re}[I^* \cdot V]$$

Summary

- **Complex exponentials are eigen-functions of LTI systems**
 - Steady-state response of LCR circuits are LTI systems
 - Phasor analysis allows us to treat all LCR circuits as simple “resistive” circuits by using the concept of impedance (admittance)
- **Frequency response allows us to completely characterize a system**
 - Any input can be decomposed into either a continuum or discrete sum of frequency components
 - The transfer function is usually plotted in the log-log domain (Bode plot) – magnitude and phase
 - Location of poles/zeros is key

$$V = I R$$

$$Z_C = \frac{1}{j\omega C}$$

$$Z_L = j\omega L$$

$$V_C = I_C \cdot Z_C$$

$$V_L = I_L \cdot Z_L$$

