

# **EE105**

## **Microelectronic Devices and Circuits**


**Prof. Ming C. Wu**

**wu@eecs.berkeley.edu**


**511 Sutardja Dai Hall (SDH)**

# Linear Time-Invariant (LTI) System


- Response of a system

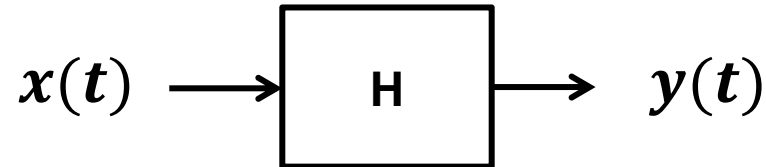

- The system is linear if

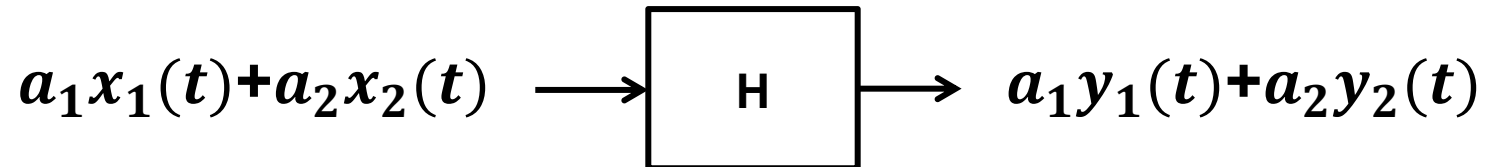


- The system is time-invariant if

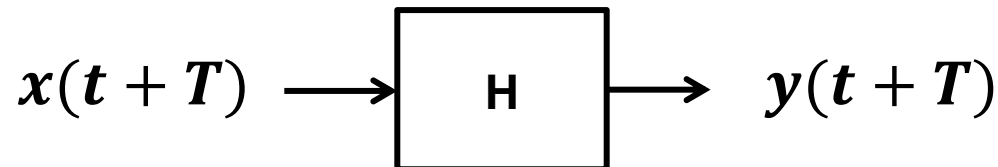

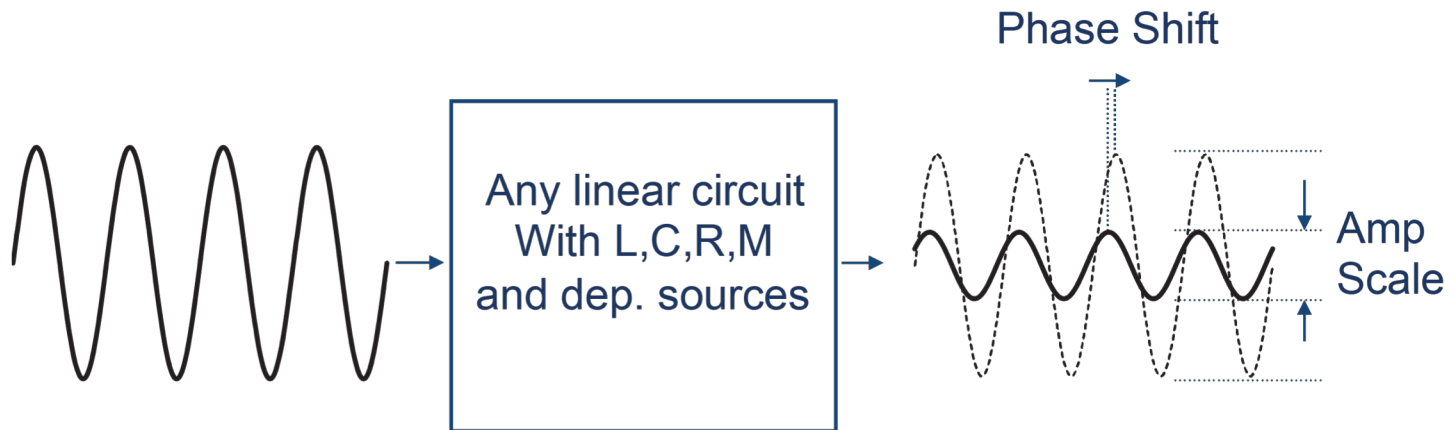
# What's Nice about LTI System?

- Can use superposition
- Easy conversion between time and frequency response
- Most systems in real life are LTI systems
  - Focus of this class


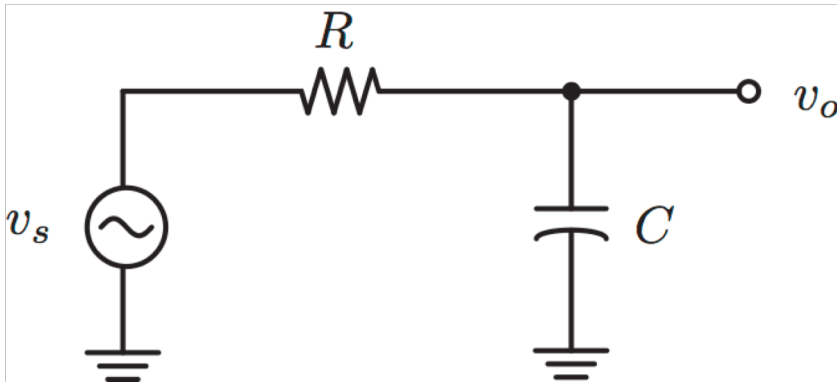
# Example: Low Pass Filter (LPF)

- **Input signal:**  $v_s(t) = V_s \cos(\omega t)$
  - **We know that:**  $v_o(t) = \underbrace{K \cdot V_s}_{V_0} \cos(\omega t + \phi)$
- Phase shift
- Amp scale



$$v_o(t) = v_s(t) - i(t)R$$

$$i(t) = C \frac{dv_o}{dt}$$

$$v_o(t) = v_s(t) - RC \frac{dv_o}{dt}$$

$$v_s(t) = v_o(t) + \tau \frac{dv_o}{dt}$$

# Exponential Representation

- Euler's Theorem

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

- $\sin(\omega t)$  and  $\cos(\omega t)$  can be represented by linear combination of complex exponential:

$$\cos(\omega t) = \frac{1}{2} (e^{j\omega t} + e^{-j\omega t})$$
$$\sin(\omega t) = \frac{1}{2j} (e^{j\omega t} - e^{-j\omega t})$$

# Magic: Turn Diff Eq into Algebraic Eq

- Integration and differentiation are trivial with complex numbers:

$$\frac{d}{dt} e^{i\omega t} = i\omega e^{i\omega t} \qquad \int e^{i\omega\tau} d\tau = \frac{1}{i\omega} e^{i\omega\tau}$$

- Any ODE is now trivial algebraic manipulations ... in fact, we'll show that you don't even need to directly derive the ODE by using phasors
- The key is to observe that the current/voltage relation for any element can be derived for complex exponential excitation

# Solving LPF with Phasors

- Let's excite the system with a complex exp:

$$v_s(t) = v_0(t) + \tau \frac{dv_0}{dt}$$

$$v_s(t) = V_s e^{j\omega t}$$

$$v_0(t) = |V_0| e^{j(\omega t + \phi)} = V_0 e^{j\omega t}$$

use  $j$  to avoid confusion

real

complex

$$V_s e^{j\omega t} = V_0 e^{j\omega t} + \tau \cdot j\omega \cdot V_0 e^{j\omega t}$$

$$V_s = V_0 (1 + j\omega \cdot \tau)$$

$$\frac{V_0}{V_s} = \frac{1}{(1 + j\omega \cdot \tau)}$$

Easy!!!

# Magnitude and Phase Response

- The system is characterized by the complex function

$$H(\omega) = \frac{V_0}{V_s} = \frac{1}{(1 + j\omega \cdot \tau)}$$

- The magnitude and phase response match our previous calculation:

$$|H(\omega)| = \left| \frac{V_0}{V_s} \right| = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

$$\angle H(\omega) = -\tan^{-1} \omega\tau$$




# Why did it work?

- Again, the system is linear:

$$y = \mathbf{L}(x_1 + x_2) = \mathbf{L}(x_1) + \mathbf{L}(x_2)$$

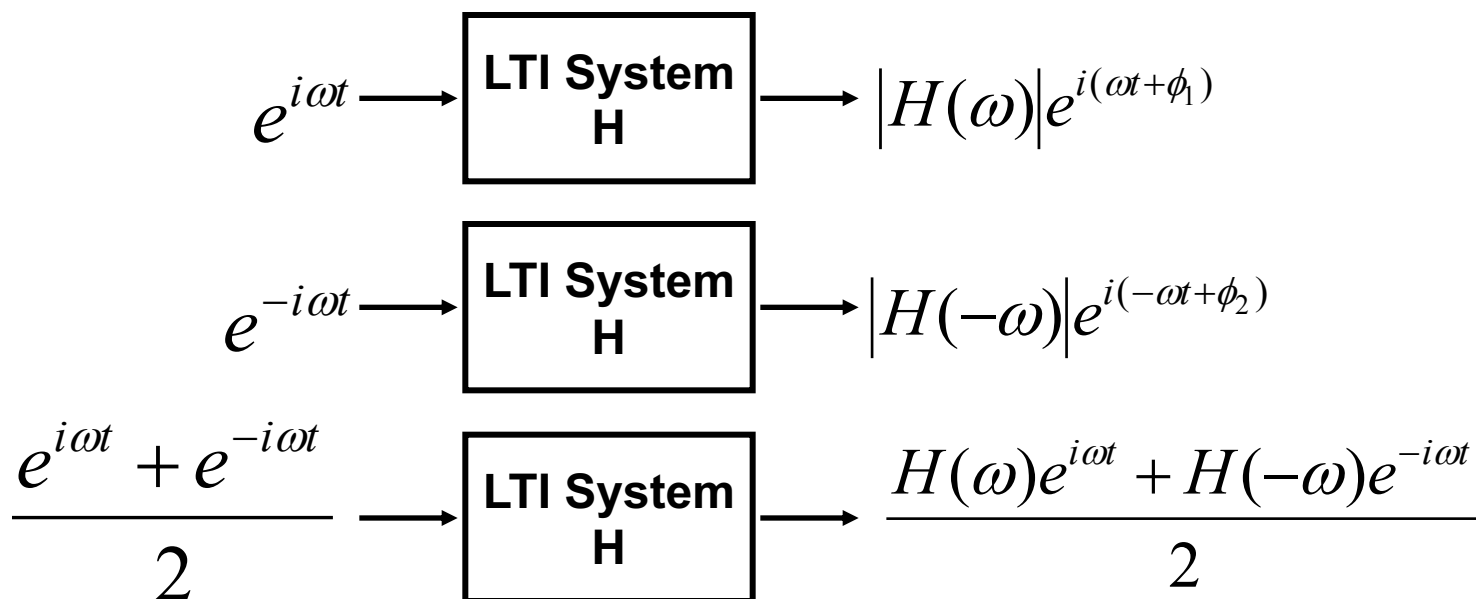- To find the response to a sinusoid, we can find the response to  $e^{i\omega t}$  and  $e^{-i\omega t}$  and sum the results:



## (cont.)

- **Since the input is real, the output has to be real:**

$$y(t) = \frac{H(\omega)e^{i\omega t} + H(-\omega)e^{-i\omega t}}{2}$$

- **That means the second term is the conjugate of the first:**

$$|H(-\omega)| = |H(\omega)| \quad (\text{even function})$$

$$\angle H(-\omega) = -\angle H(\omega) = -\phi \quad (\text{odd function})$$

- **Therefore the output is:**

$$\begin{aligned} y(t) &= \frac{|H(\omega)|}{2} \left( e^{i(\omega t + \phi)} + e^{-i(\omega t + \phi)} \right) \\ &= |H(\omega)| \cos(\omega t + \phi) \end{aligned}$$


# Phasors

- With our new confidence in complex numbers, we go full steam ahead and work directly with them ... we can even drop the time factor  $e^{i\omega t}$  since it will cancel out of the equations.
- Excite system with a phasor:  $\tilde{V}_1 = V_1 e^{j\phi_1}$
- Response will also be phasor:  $\tilde{V}_2 = V_2 e^{j\phi_2}$
- For those with a Linear System background, we're going to work in the frequency domain
  - This is the Laplace domain with  $s = j\omega$
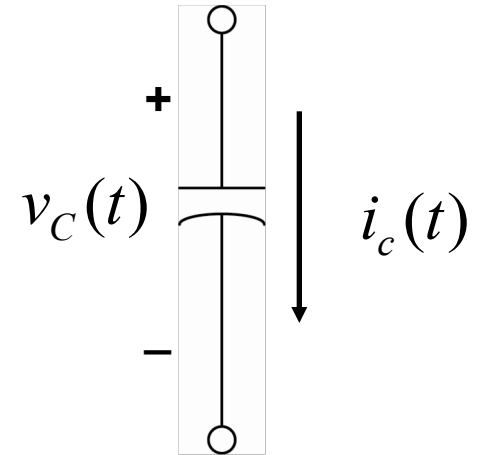
# Capacitor I-V Phasor Relation

- Find the Phasor relation for current and voltage in a cap:

$$i_c(t) = C \frac{dv_c(t)}{dt} \quad \begin{array}{l} i_c(t) = I_c e^{j\omega t} \\ v_c(t) = V_c e^{j\omega t} \end{array}$$



$$I_c e^{j\omega t} = C \frac{d}{dt} [V_c e^{j\omega t}]$$

$$C V_c \frac{d}{dt} e^{j\omega t} = j\omega C V_c e^{j\omega t}$$


$$I_c e^{j\omega t} = j\omega C V_c e^{j\omega t}$$

$$I_c = j\omega C V_c$$
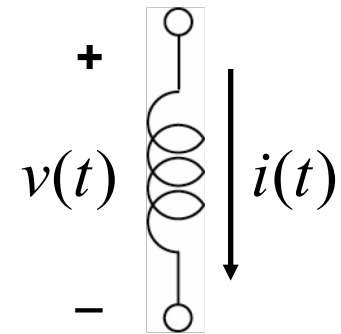
# Inductor I-V Phasor Relation

- Find the Phasor relation for current and voltage in an inductor:

$$v(t) = L \frac{di(t)}{dt} \quad \begin{array}{l} i(t) = Ie^{j\omega t} \\ v(t) = Ve^{j\omega t} \end{array}$$



$$Ve^{j\omega t} = L \frac{d}{dt} [Ie^{j\omega t}]$$


$$LI \frac{d}{dt} e^{j\omega t} = j\omega LIe^{j\omega t}$$

$$Ve^{j\omega t} = j\omega LIe^{j\omega t}$$

$$V = j\omega LI$$
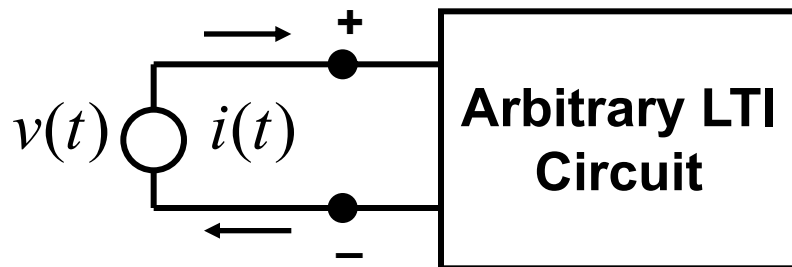
# Impede the Currents !

- Suppose that the “input” is defined as the voltage of a terminal pair (port) and the “output” is defined as the current into the port:



$$v(t) = Ve^{j\omega t} = |V|e^{j(\omega t + \phi_v)}$$


$$i(t) = Ie^{j\omega t} = |I|e^{j(\omega t + \phi_i)}$$

- The impedance  $Z$  is defined as the ratio of the phasor voltage to phasor current (“self” transfer function)

$$Z(\omega) = H(\omega) = \frac{V}{I} = \left| \frac{V}{I} \right| e^{j(\phi_v - \phi_i)}$$
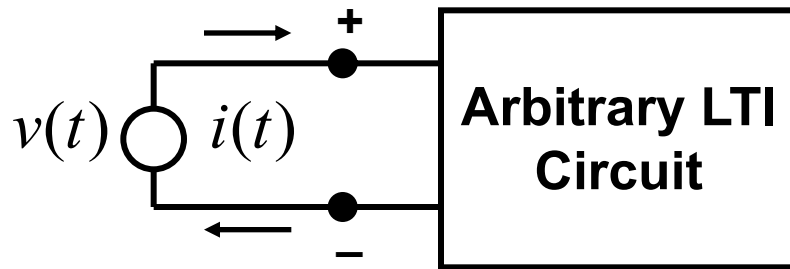
# Admit the Currents!

- Suppose that the “input” is defined as the current of a terminal pair (port) and the “output” is defined as the voltage into the port:



$$v(t) = Ve^{j\omega t} = |V|e^{j(\omega t + \phi_v)}$$


$$i(t) = Ie^{j\omega t} = |I|e^{j(\omega t + \phi_i)}$$

- The admittance  $Y$  is defined as the ratio of the phasor current to phasor voltage (“self” transfer function)

$$Y(\omega) = H(\omega) = \frac{I}{V} = \left| \frac{I}{V} \right| e^{j(\phi_i - \phi_v)}$$
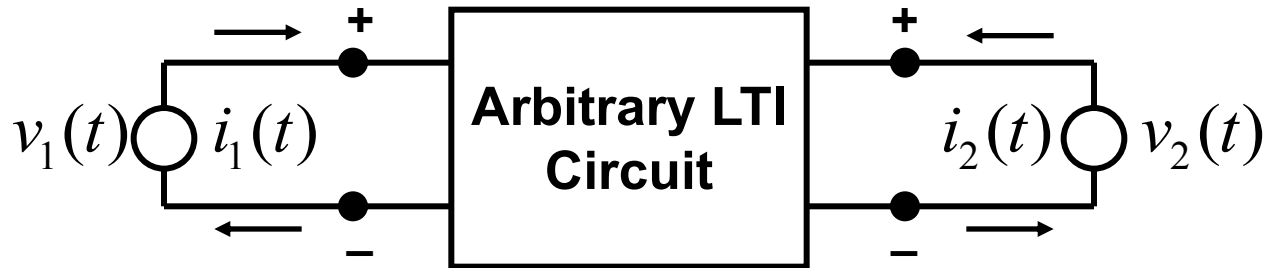
# Voltage and Current Gain

- The voltage (current) gain is just the voltage (current) transfer function from one port to another port:



$$G_v(\omega) = \frac{V_2}{V_1} = \left| \frac{V_2}{V_1} \right| e^{j(\phi_2 - \phi_1)}$$


$$G_i(\omega) = \frac{I_2}{I_1} = \left| \frac{I_2}{I_1} \right| e^{j(\phi_2 - \phi_1)}$$

- If  $|G| > 1$ , the circuit has voltage (current) gain
- If  $|G| < 1$ , the circuit has loss or attenuation


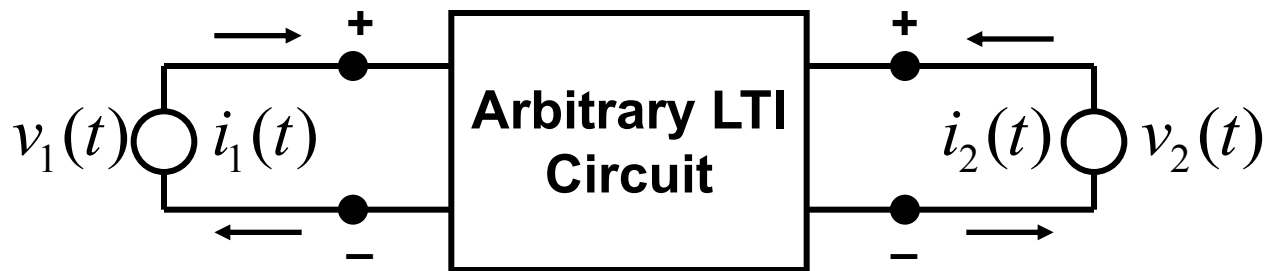
# Transimpedance/admittance

- Current/voltage gain are unit-less quantities
- Sometimes we are interested in the transfer of voltage to current or vice versa



$$J(\omega) = \frac{V_2}{I_1} = \left| \frac{V_2}{I_1} \right| e^{j(\phi_2 - \phi_1)} \quad [\Omega]$$


$$K(\omega) = \frac{I_2}{V_1} = \left| \frac{I_2}{V_1} \right| e^{j(\phi_2 - \phi_1)} \quad [S]$$

# Direct Calculation of $H$ (no DEs)


- To directly calculate the transfer function (impedance, trans-impedance, etc) we can generalize the circuit analysis concept from the “real” domain to the “phasor” domain
- With the concept of impedance (admittance), we can now directly analyze a circuit without explicitly writing down any differential equations
- Use KVL, KCL, mesh analysis, loop analysis, or node analysis where inductors and capacitors are treated as complex resistors
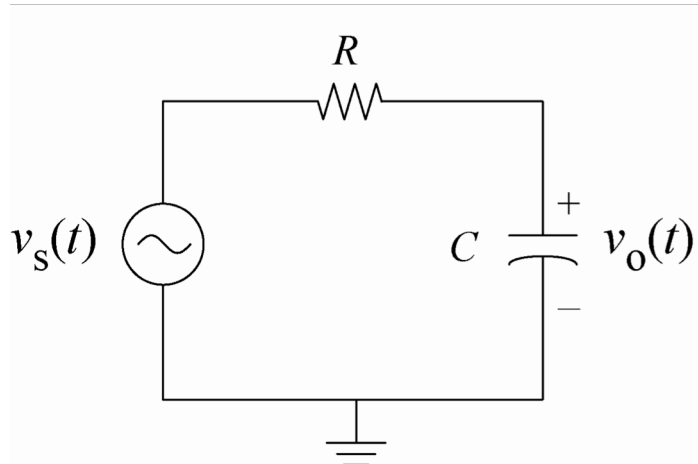
# LPF Example: Again!

- Instead of setting up the DE in the time-domain, let's do it directly in the frequency domain
- Treat the capacitor as an impedance:



time domain “real” circuit

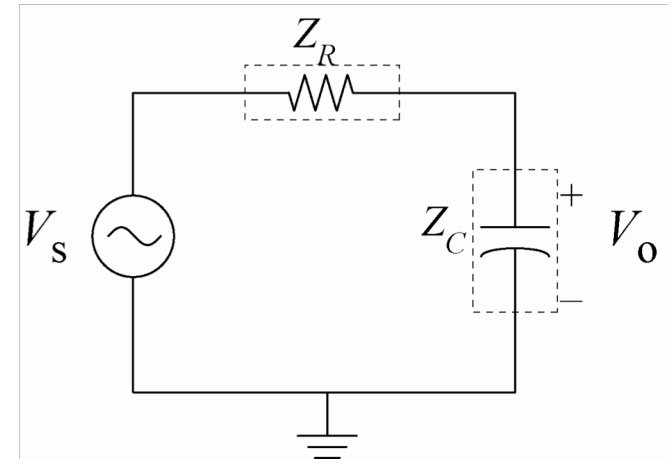

frequency domain “phasor” circuit

- We know the impedances:


$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

# Bode Plots

- **Simply the log-log plot of the magnitude and phase response of a circuit (impedance, transimpedance, gain, ...)**
- **Gives insight into the behavior of a circuit as a function of frequency**
- **The “log” expands the scale so that breakpoints in the transfer function are clearly delineated**

# Frequency Response of Low-Pass Filters

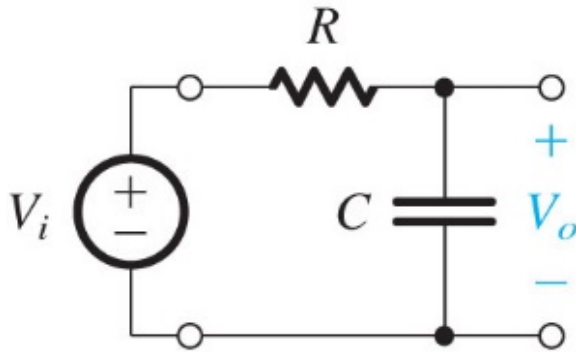

$$T(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega / \omega_0}$$



$$\omega_0 = \frac{1}{RC}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega / \omega_0)^2}}$$


$$\angle T(\omega) = -\tan^{-1}(\omega / \omega_0)$$

$$\omega_{3dB} = \omega_0 \quad [\text{rad/sec}]$$
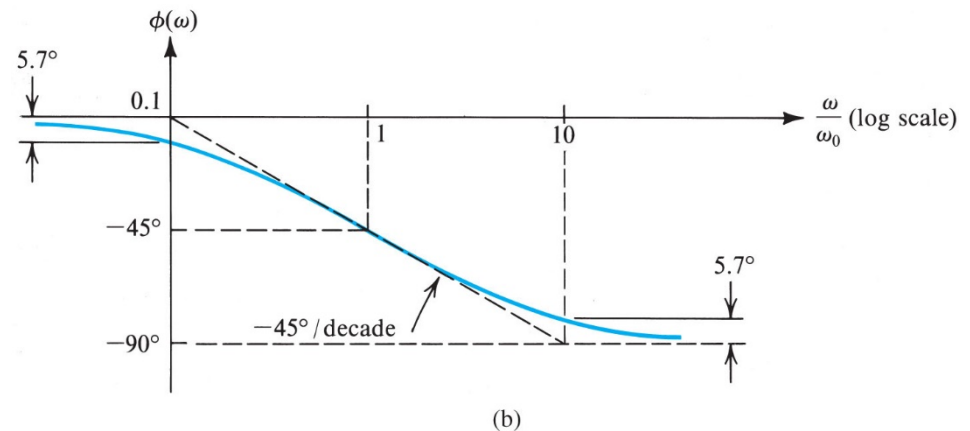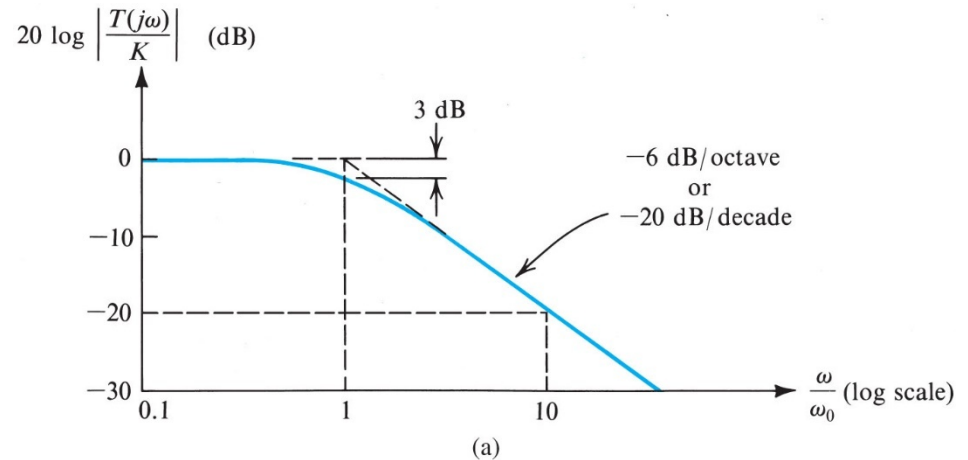
$$f_{3dB} = \frac{\omega_0}{2\pi} \quad [\text{Hz}]$$


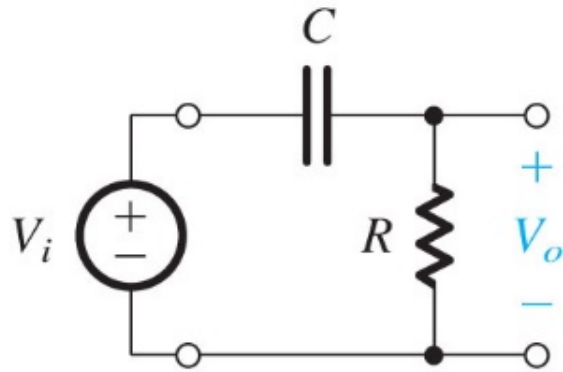
# Frequency Response of High-Pass Filters



$$T(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega RC}} = \frac{1}{1 - j\omega_0 / \omega}$$


$$\omega_0 = \frac{1}{RC}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega_0 / \omega)^2}}$$


$$\angle T(\omega) = \tan^{-1}(\omega_0 / \omega)$$

$$\omega_{3dB} = \omega_0 \quad [\text{rad/sec}]$$
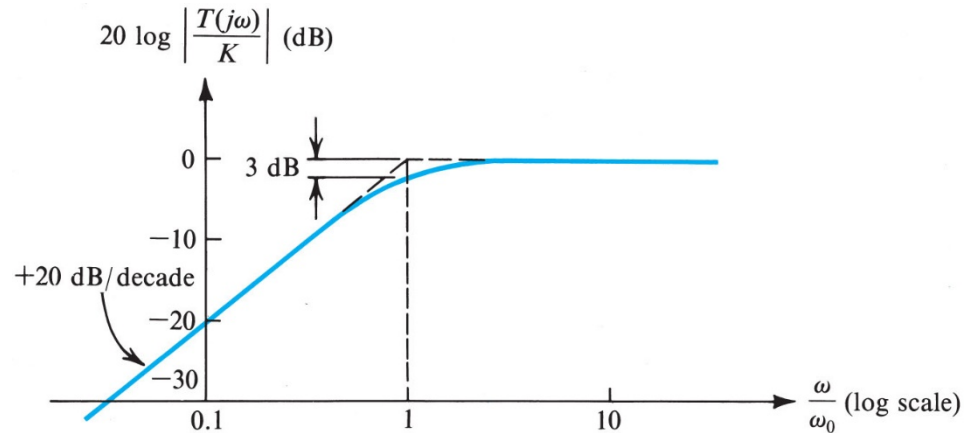
$$f_{3dB} = \frac{\omega_0}{2\pi} \quad [\text{Hz}]$$




(a)

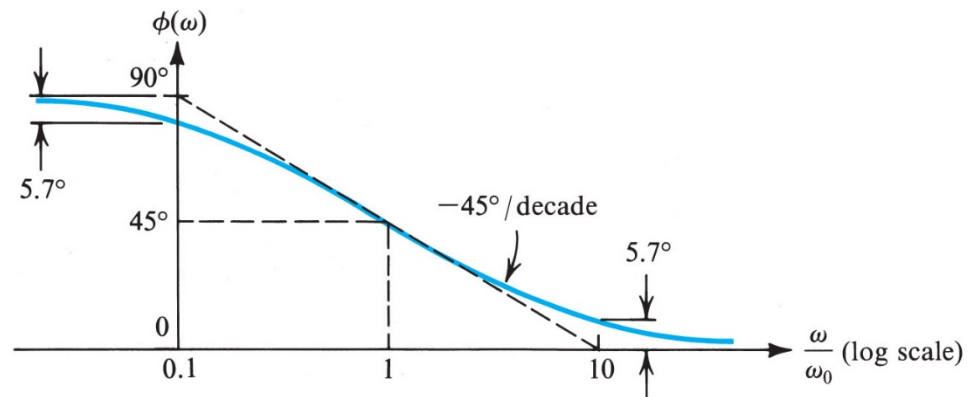

(b)

# Example: High-Pass Filter

- Using the voltage divider rule:

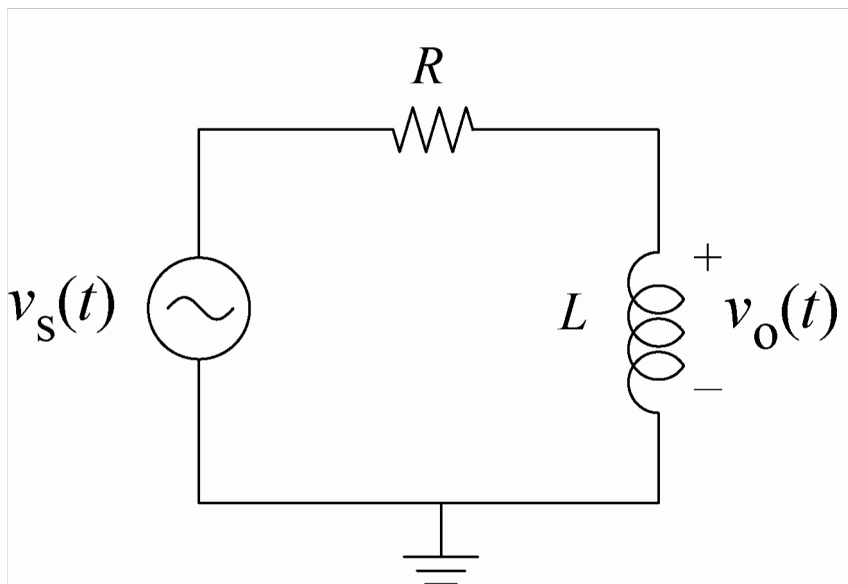

$$H(\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}}$$


$$H(\omega) = \frac{j\omega\tau}{1 + j\omega\tau}$$

$$\omega \rightarrow \infty \quad |H| \rightarrow \left| \frac{j\omega\tau}{j\omega\tau} \right| = 1$$

$$\omega \rightarrow 0 \quad |H| \rightarrow \frac{0}{1+0} = 0$$

$$\omega = \frac{1}{\tau} \quad |H| = \left| \frac{j}{1+j} \right| = \frac{1}{\sqrt{2}}$$

# Approximate versus Actual Plot

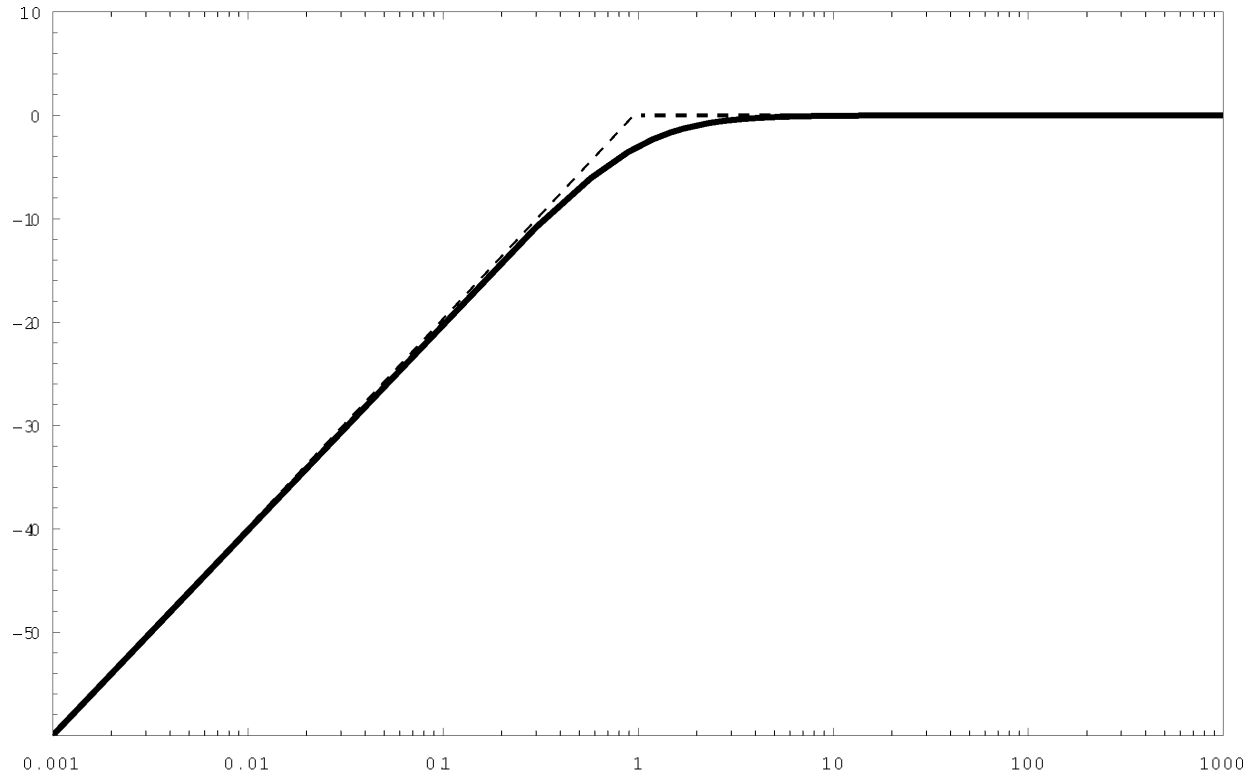

- **Approximate curve accurate away from breakpoint**
- **At breakpoint there is a 3 dB error**




# HPF Phase Plot

- Phase can be naturally decomposed as well:

$$\angle H(\omega) = \angle \frac{j\omega\tau}{1+j\omega\tau} = \angle j\omega\tau + \angle \frac{1}{1+j\omega\tau} = \frac{\pi}{2} - \tan^{-1} \omega\tau$$

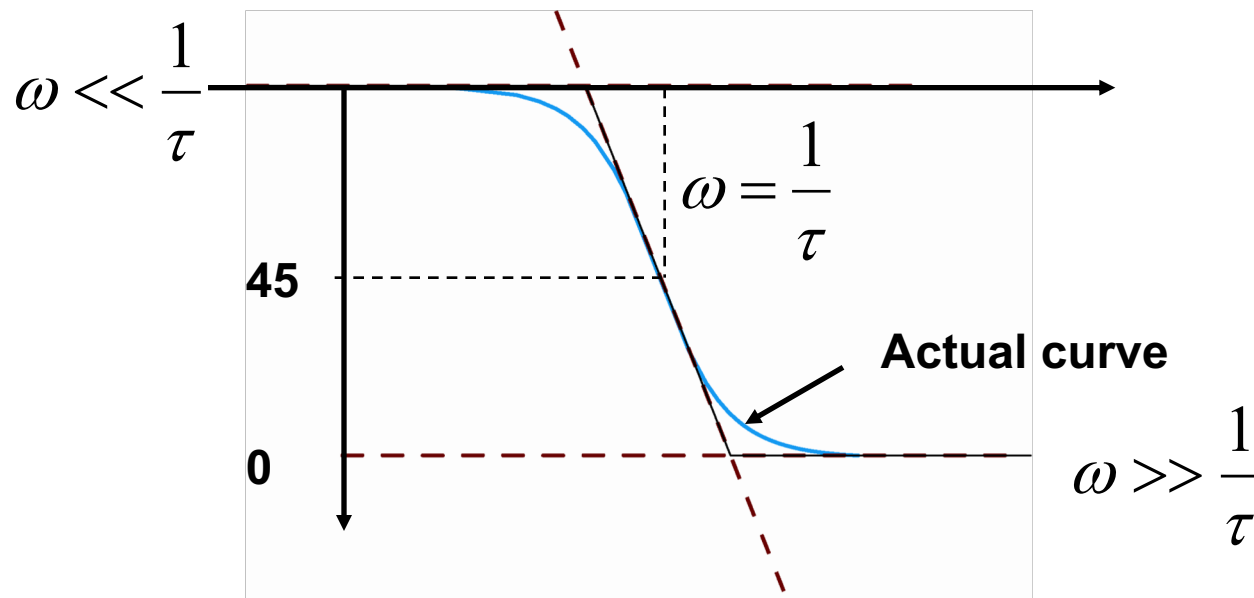- First term is simply a constant phase of 90 degrees
- The second term is the arctan function
- Estimate arctan function:



# Power Flow

- The instantaneous power flow into any element is the product of the voltage and current:  $P(t) = i(t)v(t)$
- For a periodic excitation, the average power is:

$$P_{av} = \int_T i(\tau)v(\tau)d\tau$$

- In terms of sinusoids we have

$$\begin{aligned} P_{av} &= \int_T |I| \cos(\omega t + \varphi_i) |V| \cos(\omega t + \varphi_v) d\tau \\ &= |I| \cdot |V| \int_T (\cos \omega t \cos \varphi_i - \sin \omega t \sin \varphi_i) \cdot (\cos \omega t \cos \varphi_v - \sin \omega t \sin \varphi_v) d\tau \\ &= |I| \cdot |V| \int_T d\tau \cos^2 \omega t \cos \varphi_i \cos \varphi_v + \sin^2 \omega t \sin \varphi_i \sin \varphi_v + \cancel{c \sin \omega t \cos \omega t} \\ &= \frac{|I| \cdot |V|}{2} (\cos \varphi_i \cos \varphi_v + \sin \varphi_i \sin \varphi_v) = \frac{|I| \cdot |V|}{2} \cos(\varphi_i - \varphi_v) \end{aligned}$$

# Power Flow with Phasors

$$P_{av} = \frac{|I| \cdot |V|}{2} \cos(\phi_i - \phi_v)$$

↑  
Power Factor

- **Note that if  $(\phi_i - \phi_v) = \frac{\pi}{2}$ , then  $P_{av} = \frac{|I| \cdot |V|}{2} \cos\left(\frac{\pi}{2}\right) = 0$**
- **Important: Power is a non-linear function so we can't simply take the real part of the product of the phasors:**

$$P \neq \text{Re}[I \cdot V]$$

- **From our previous calculation:**

$$P = \frac{|I| \cdot |V|}{2} \cos(\phi_i - \phi_v) = \frac{1}{2} \text{Re}[I \cdot V^*] = \frac{1}{2} \text{Re}[I^* \cdot V]$$

# Summary

- **Complex exponentials are eigen-functions of LTI systems**
  - Steady-state response of LCR circuits are LTI systems
  - Phasor analysis allows us to treat all LCR circuits as simple “resistive” circuits by using the concept of impedance (admittance)
- **Frequency response allows us to completely characterize a system**
  - Any input can be decomposed into either a continuum or discrete sum of frequency components
  - The transfer function is usually plotted in the log-log domain (Bode plot) – magnitude and phase
  - Location of poles/zeros is key