

EE105


Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)


Ideal Op Amp

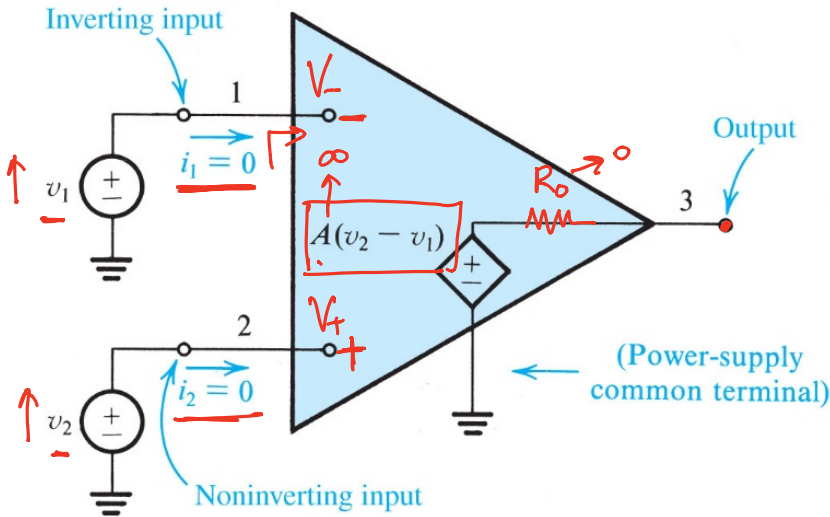


Golden Rules:

- Infinite open-loop gain, $A = \infty$
- Infinite input impedance
 - No current goes in
- Zero output impedance
- $V_- = V_+$ with feedback circuit
- Infinite bandwidth
- Infinite common-mode rejection

Op-Amp with dc bias

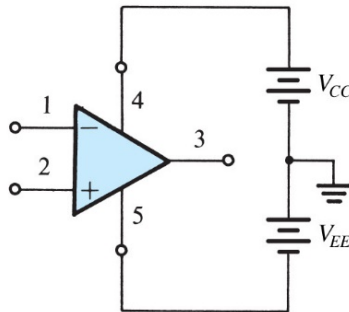

Inverting Amplifier

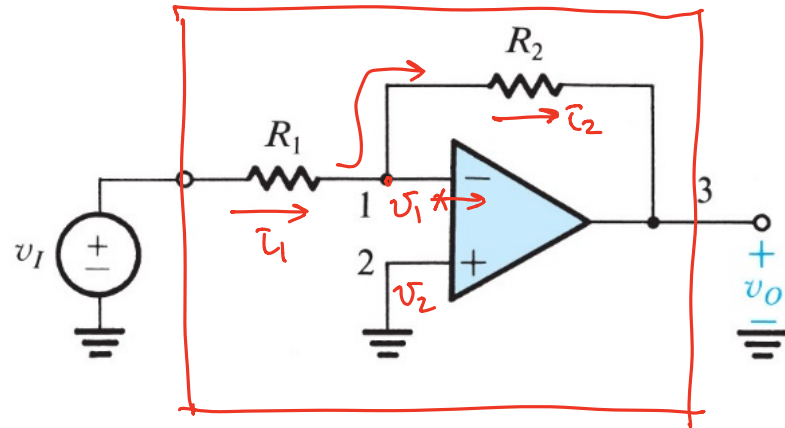

Ideal Op Amp

$$v_1 = v_2 = 0$$

$$\begin{aligned} v_O &= v_1 - i_2 R_2 \\ &= 0 - \frac{v_I - 0}{R_1} \cdot R_2 \\ &= v_I \cdot \left(-\frac{R_2}{R_1}\right) \end{aligned}$$

$$G = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

↑ Gain is determined by external circuit elements



Inverting Amplifier: Input and Output Resistances

R_i

R_o

$R_i = R_1$

R_o

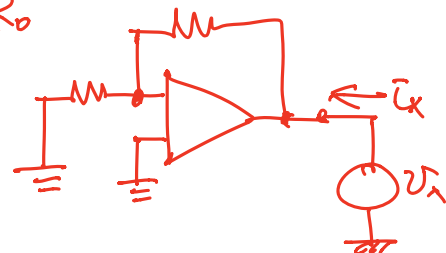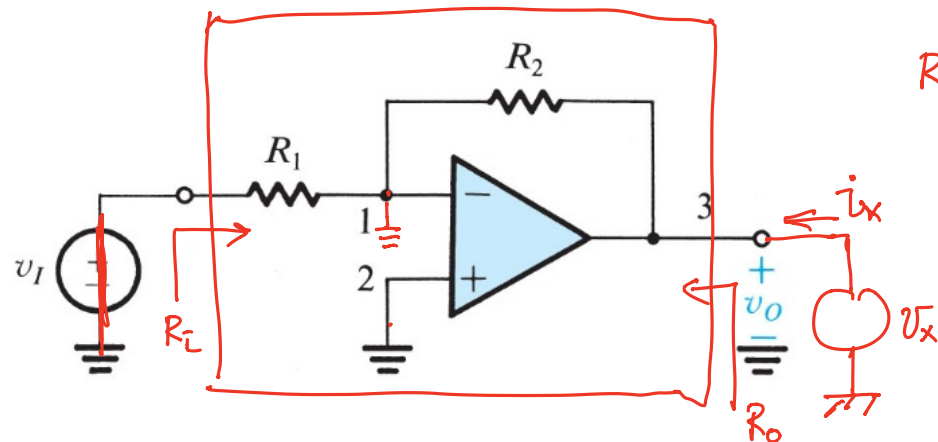

To solve R_o :


- ① Replace v_I by short ckt
- ② Apply test voltage source v_x
- ③ Solve i_x using KCL, KVL

④ $R_o = \frac{v_x}{i_x}$

$v_1 = v_2$ ideal Op Amp
 $v_o = v_x = A(v_1 - v_2) = 0$
 $\downarrow \quad \downarrow$
 $\infty \quad 0$
 \downarrow
 $\sim 10^6$


$R_o = \frac{v_x}{i_x} = 0$

Non-Inverting Amplifier

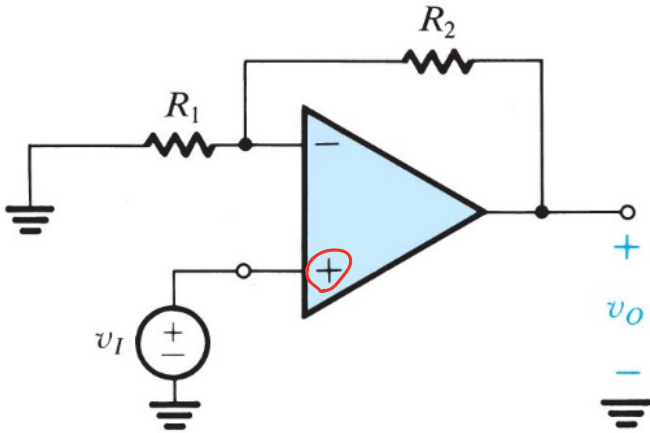


$$G = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right)$$

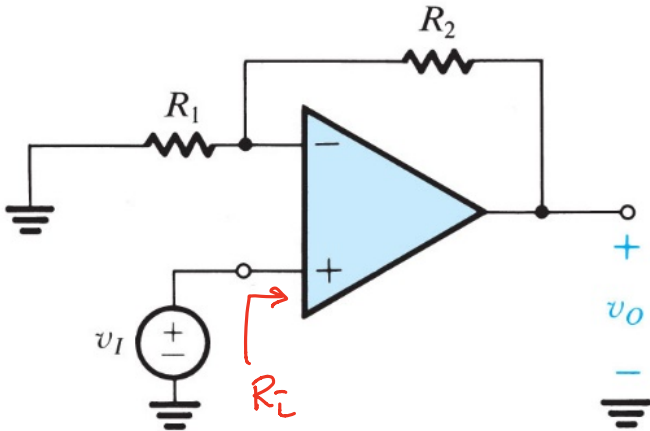Non-Inverting Amplifier: Input and Output Resistances



$$R_i = \infty$$

$$R_o$$

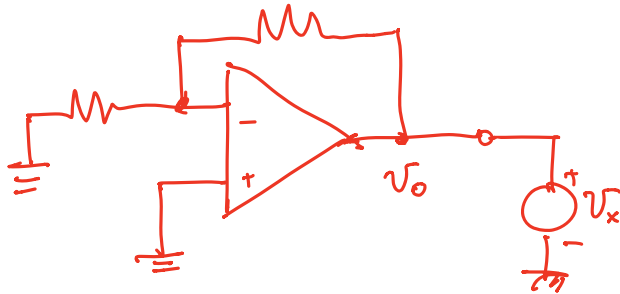

Identical to Inverting Amp

$$R_o = 0$$

$$v_x = v_o = A (v_+ - v_-) = 0$$


$$R_o = \frac{v_x}{i_x} = 0$$

Practical Op-Amps

- **Linear Imperfections:**
 - Finite open-loop gain ($A_0 < \infty$)
 - Finite input resistance ($R_i < \infty$)
 - Non-zero output resistance ($R_o > 0$)
 - Finite bandwidth / Gain-BW Trade-off
- **Other (non-linear) imperfections:**
 - Slew rate limitations
 - Finite swing
 - Offset voltage
 - Input bias and offset currents
 - Noise and distortion


Two-Port

Simple Model of Amplifier

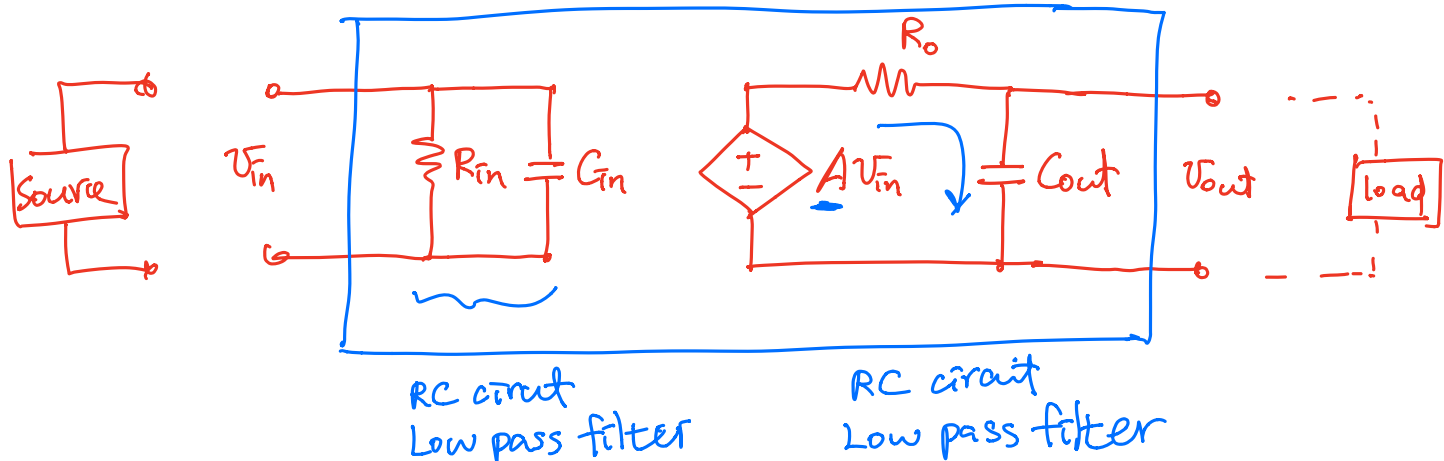


- Input and output capacitances are added
- Any amplifier has input capacitance due to transistors and packaging / board parasitics
- Output capacitance is usually dominated by load
 - Driving cables or a board trace

Transfer Function

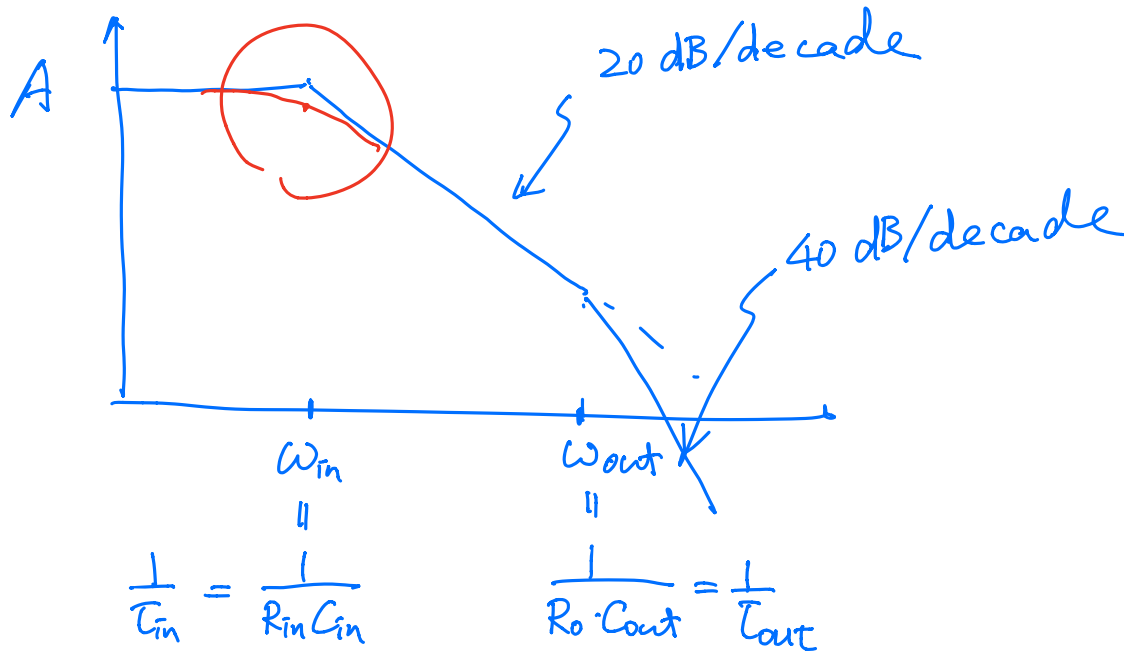


- Using the concept of impedance, it's easy to derive the transfer function

Operational Transconductance Amp

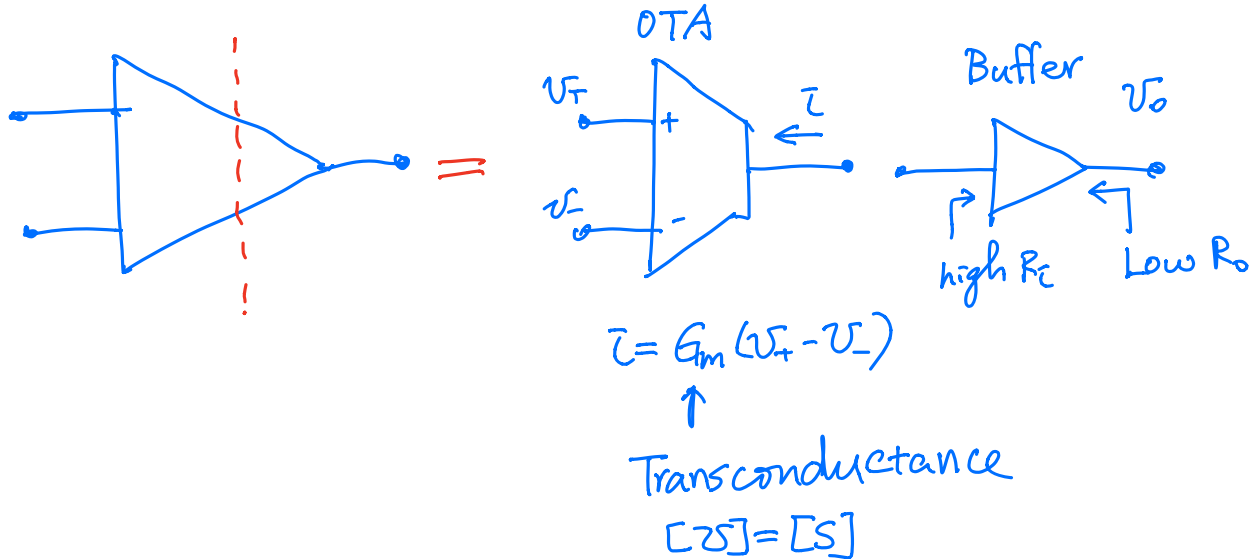

- Also known as an “OTA”
 - If we “chop off” the output stage of an op-amp, we get an OTA
- An OTA is essentially a G_m amplifier. It has a current output, so if we want to drive a load resistor, we need an output stage (buffer)
- Many op-amps are internally constructed from an OTA + buffer

Op-Amp Model

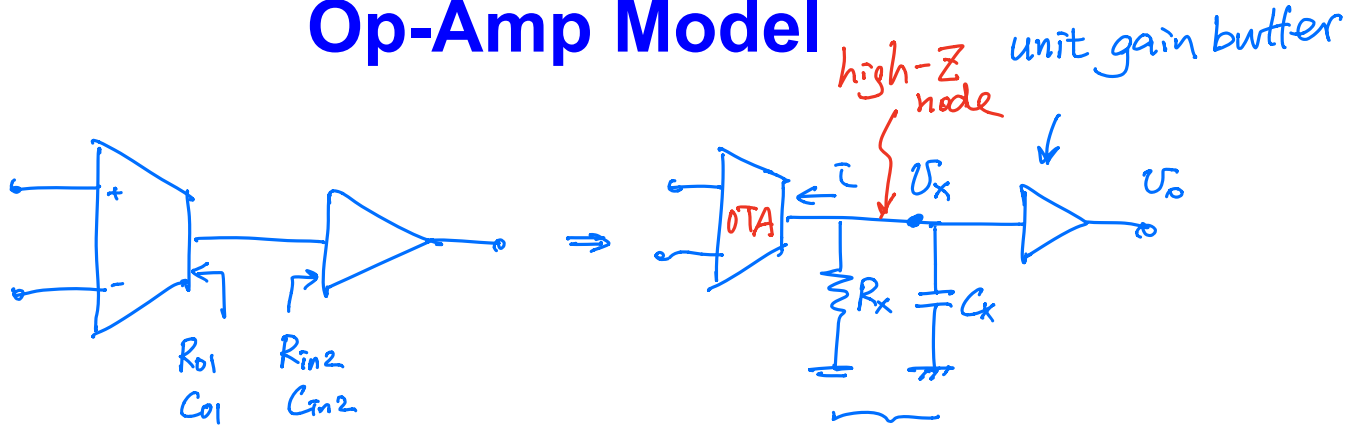

$$i = G_m (V_x - V_-)$$

$$V_x = i R_x = G_m R_x (V_x - V_-)$$

$$V_o = V_x$$

$$RC \text{ time} = R_x C_x$$


$$\omega_{3dB} = \frac{1}{R_x C_x}$$

$$\text{Gain} = G_m R_x \quad R_x \text{ should be large}$$

- The model closely resembles the insides of an op-amp
- The input OTA stage drives a high Z node to generate a very large voltage gain
- The output buffer then can drive a low impedance load and preserve the high voltage gain

Op-Amp Gain / Bandwidth

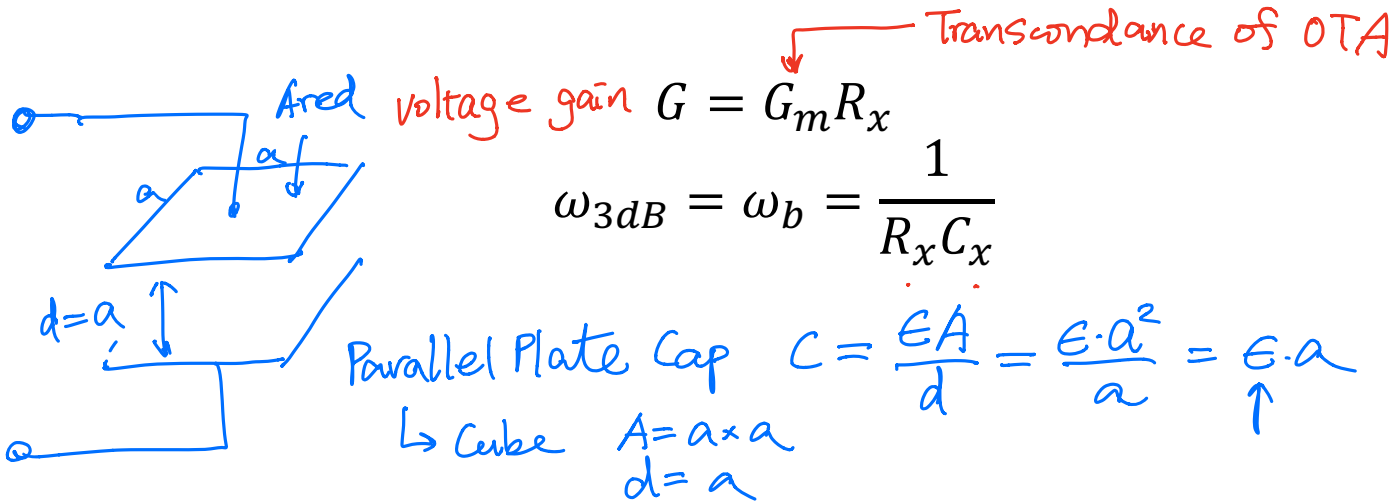- The dominant frequency response of the op-amp is due to the time constant formed at the high-Z node



- An interesting observation is that the gain-bandwidth product depends on G_m and C_x only

$$\underline{G \times \omega_{3dB}} = \left(G_m R_x \right) \left(\frac{1}{R_x C_x} \right) = \frac{G_m}{C_x} \quad \text{Figure of Merit}$$

Gain-Bandwidth Trade-off

Frequency Response of Open-Loop Op Amp

Same Gain x BW

$$A(j\omega) = \frac{A_0}{1 + j\omega / \omega_b}$$

A_0 : dc gain = $G_m R_x$ large $\ll \infty$

ω_b : 3dB frequency

$\omega_t = A_0 \omega_b$: unity-gain bandwidth
(or "gain-bandwidth product")


For high frequency, $\omega \gg \omega_b$

$$A(j\omega) = \frac{\omega_t}{j\omega}$$

$$\omega \gg \omega_b = \omega_{3dB} \quad A(j\omega) \approx \frac{A_0}{j(\omega/\omega_b)}$$

$$|A(j\omega)| \rightarrow \left| \frac{A_0 \omega_b}{j\omega} \right| \equiv 1$$
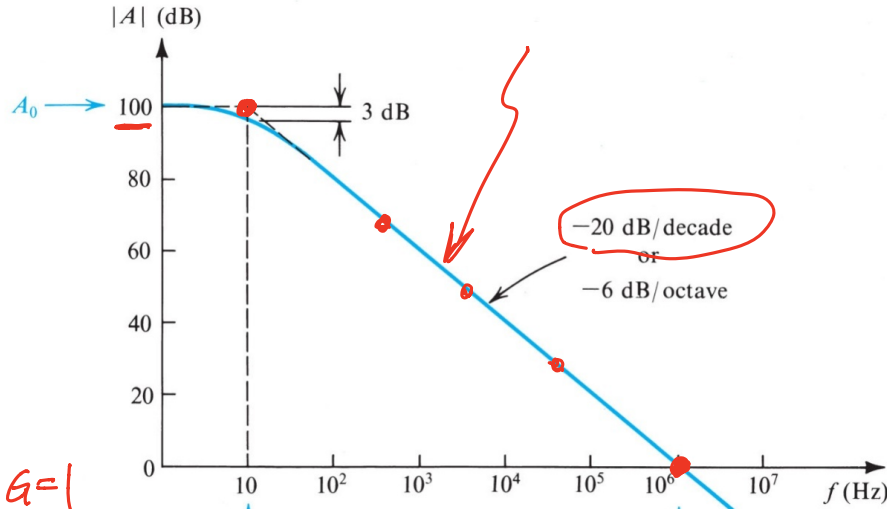
$$\omega = \omega_t = A_0 \cdot \omega_b = \text{Gain} \times \text{BW}$$




G=1

$$\frac{1}{2\pi} \omega_b = \frac{1}{2\pi} \omega_{3dB} = \frac{1}{2\pi R_x C_x} \quad \frac{1}{2\pi} \omega_t$$

Single pole response with a dominant pole at ω_b

Bandwidth Extension with Feedback

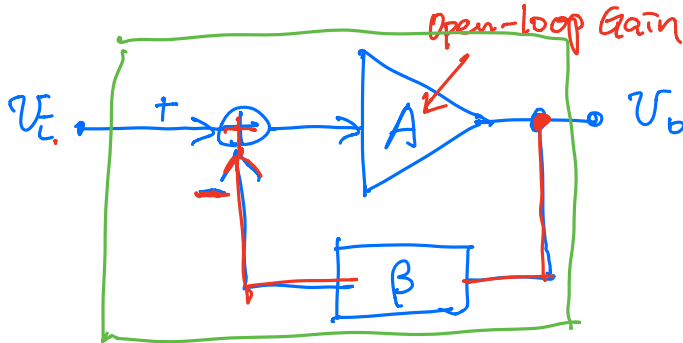- Overall transfer function with feedback:



$$v_o = A(v_E - \beta v_o)$$

$$G = \frac{v_o}{v_E} = \left(\frac{A}{1 + A\beta} \right)$$

↑ close-loop gain


$$A(j\omega) = \frac{A_o}{1 + j \frac{\omega}{\omega_b}}$$

$$v_o = A(j\omega)(v_i - \beta v_o);$$

$$G(j\omega) = \frac{\frac{A_o}{1 + j \frac{\omega}{\omega_b}}}{1 + \frac{A_o \beta}{1 + j \frac{\omega}{\omega_b}}} = \frac{A_o}{1 + j \frac{\omega}{\omega_b} + A_o \beta}$$

$$= \left(\frac{A_o}{1 + A_o \beta} \right) \cdot \frac{1}{1 + j \frac{\omega}{(1 + A_o \beta) \omega_b}}$$
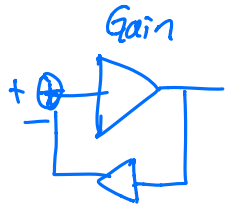
$$\omega_{3dB} = (1 + A_o \beta) \cdot \omega_b$$



Bandwidth Extension and Gain Reduction

extension

- Bandwidth increase:

$$BW = \underline{(1 + A_o\beta)\omega_b}$$

- Gain reduces:

$$G = \frac{A_o}{1 + A_o\beta}$$



- Gain-Bandwidth Product remains constant:

$$G \times BW = \underline{A_o\omega_b}$$

Gain – Bandwidth Trade-off

Unity Gain Feedback Amplifier

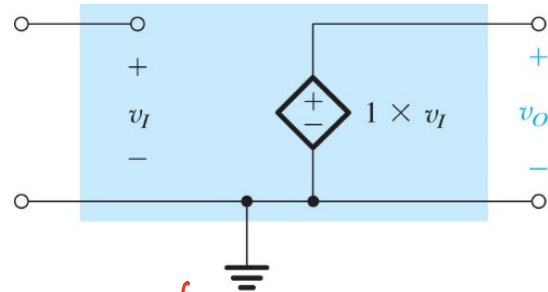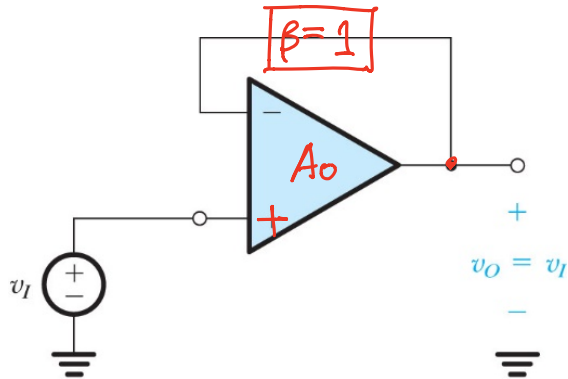- An amplifier that has a feedback factor $\beta = 1$, such as a unity gain buffer, has the full GBW product frequency range




think $A_o \sim 10^6$

$$G = \frac{A_o}{1 + A_o \beta} = \frac{A_o}{1 + A_o} \approx 1$$

$$BW = (1 + A_o \beta) \omega_b = (1 + A_o) \omega_b \approx \underline{A_o \omega_b}$$

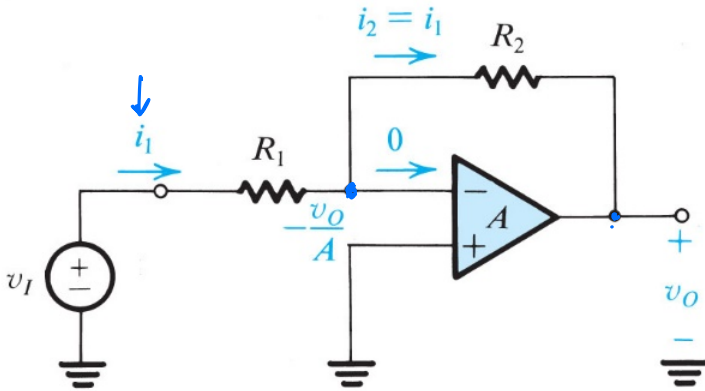Voltage Gain of Inverting Amplifier with Finite Open-Loop Gain



$$v_+ \neq v_- \neq 0$$

$$\rightarrow v_o = A(v_+ - v_-) = -A(v_-) = -Av_-$$

$$v_- = [v_i - (-\frac{v_o}{A})] / R_1$$

$$v_- = v_+ = \frac{v_i - v_o}{R_2}$$

$$\frac{v_i + \frac{v_o}{A}}{R_1} = \frac{-\frac{v_o}{A} - v_o}{R_2}$$

$$(v_i + \frac{v_o}{A}) \frac{1}{R_1} = (-\frac{v_o}{A} - v_o) \frac{1}{R_2}$$

$$v_o + \frac{v_o}{A} = (-\frac{R_2}{R_1}) (\frac{v_o}{A} + v_i)$$

$$v_o + \frac{1}{A} + (\frac{R_2}{R_1}) \frac{1}{A} = (-\frac{R_2}{R_1}) v_i$$

$$\frac{v_o}{v_i} = \frac{1}{1 + \frac{1}{A}(1 + \frac{R_2}{R_1})} (-\frac{R_2}{R_1})$$


$$G = \frac{v_o}{v_i} = (-\frac{R_2}{R_1}) \frac{1}{1 + \frac{1}{A}(1 + \frac{R_2}{R_1})}$$

$$A \rightarrow \infty$$

$$G \rightarrow -\frac{R_2}{R_1} \text{ Same Ideal Op Amp}$$

Frequency Response of Closed-Loop Op Amp

$A < \infty$
 $v_o = A(v_+ - v_-)$

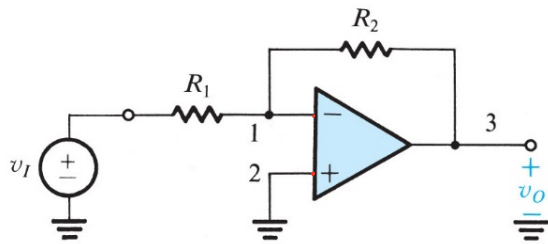

Steps to find frequency response of closed-loop amplifiers:

1. Find the transfer function with finite open-loop gain. For example, for inverting amplifier:

$$G = \frac{v_o}{v_I} = \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + \frac{(1 + R_2 / R_1)}{A}} \quad A_0 \sim 10^6$$

2. Substitute A with $A(j\omega) = \frac{A_0}{1 + j\omega / \omega_b}$

3. Simplify the expression

$$G(\omega) = \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + (1 + R_2 / R_1) \frac{1 + j\omega / \omega_b}{A_0}} \quad \leftarrow$$

$$= \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + \frac{(1 + R_2 / R_1)}{A_0} + \frac{j\omega}{\left(\frac{A_0 \omega_b}{1 + R_2 / R_1} \right)}}$$

Frequency Response of Closed-Loop Inverting Amplifier Example

Example

$A_0 = 100\text{dB}$
 $= 10^5$

$\left| \frac{R_2}{R_1} \right| \sim 30\text{dB} \rightarrow 10^{1.5} \sim 30$

$\frac{f_{3dB}}{f_b} = \frac{A_0}{\left(\frac{R_2}{R_1} \right)} = 70\text{dB} \sim 10^{3.5} \sim 3,000 \times$

$$G(\omega) \approx \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + \frac{j\omega}{\omega_{3dB}}} \quad \text{where } \omega_{3dB} = \frac{A_0 \omega_b}{1 + R_2 / R_1}$$

Note:


- (1) 3-dB frequency is higher than open-loop bandwidth, ω_b
- (2) Gain-bandwidth product remains unchanged:

$$G \times BW = \frac{R_2}{R_1} \frac{A_0 \omega_b}{1 + R_2 / R_1} \approx \frac{R_2}{R_1} \frac{A_0 \omega_b}{R_2 / R_1} = A_0 \omega_b = \omega_t$$

Same unity-gain frequency: f_t

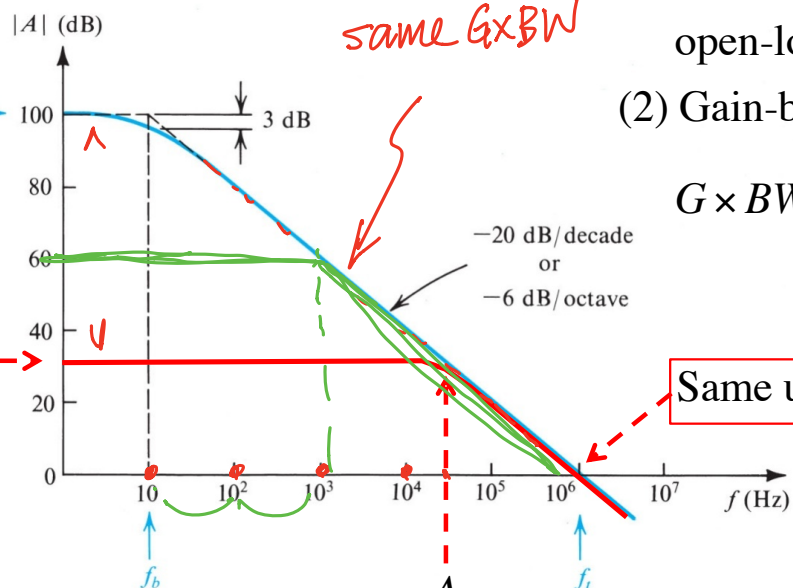Example 2: $\left(\frac{R_2}{R_1} \right) = 1000 \rightarrow 60\text{dB}$

$\frac{A_0}{\left(\frac{R_2}{R_1} \right)} = 100\text{dB} - 60\text{dB} = 40\text{dB}$
 $\rightarrow 100 \times$



$$f_{3dB} \approx \frac{A_0}{R_2 / R_1} f_b$$

