

EE105

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu


511 Sutardja Dai Hall (SDH)




Practical Op-Amps

- Linear Imperfections:
 - Finite open-loop gain ($A_0 < \infty$)
 - Finite input resistance ($R_i < \infty$)
 - Non-zero output resistance ($R_o > 0$)
 - Finite bandwidth / Gain-BW Trade-off
- Other (non-linear) imperfections:
 - Slew rate limitations
 - Finite swing
 - Offset voltage
 - Input bias and offset currents
 - Noise and distortion

Offset Voltage




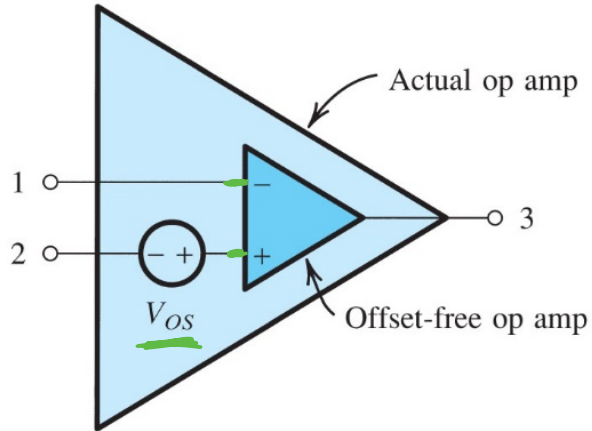


slope = A_o

 

$$\frac{10}{10^5} = 10^{-4}$$


Trimming of Offset Voltage

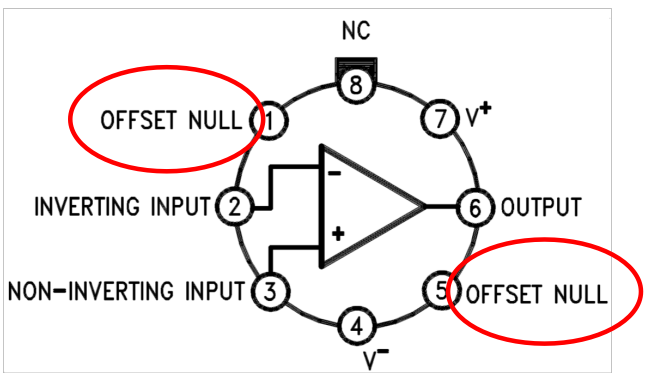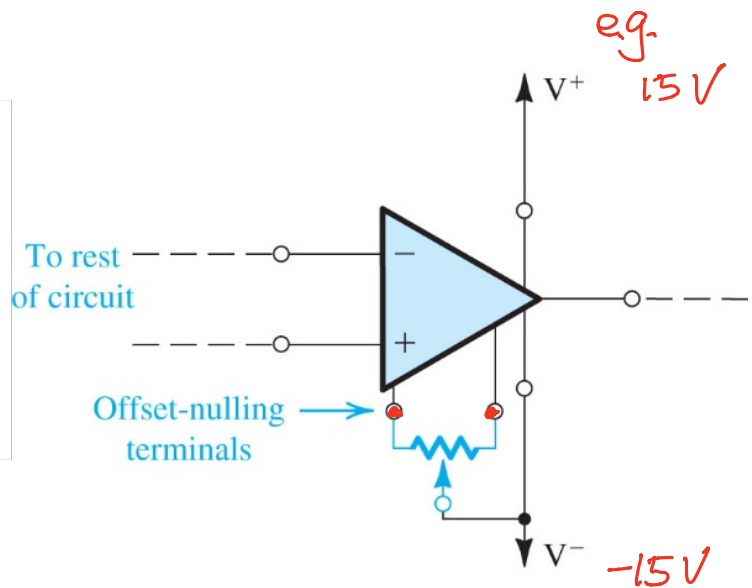  

The output dc offset voltage of an op amp can be trimmed to zero by connecting a potentiometer to the two offset-nulling terminals. The wiper of the potentiometer is connected to the negative supply of the op amp.

Input Bias Currents and Offset Currents

BJT = Bipolar Junction Transistor

 


$I_{B1} \approx I_{B2} \sim 100 \text{ nA}$
not identical

- Some op-amps (bipolar) have input bias currents that need to flow for the op-amp to function properly
- They are typically very small, $\sim 100 \text{ nA}$, but may differ slightly (by 10 nA)

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

$$\underline{I_{OS} = |I_{B1} - I_{B2}| \sim 10 \text{ nA}}$$

 Effect of Input Bias Current in Amplifier Circuit




In the absence of input voltage, the output should be zero for ideal Op Amp. However, with non-zero I_B ,

$$V_o = I_{B1} R_2 \approx I_B R_2$$

Ideal, $V_i = 0$, $V_o = 0$

$$V_i = 0, I_{B1} = \frac{V_o - 0}{R_2} \Rightarrow V_o = I_{B1} R_2$$

 Reducing the Effect of Input Bias Currents



$$\left. \begin{aligned} I_{B1} &= I_B + \frac{I_{os}}{2} \\ I_{B2} &= I_B - \frac{I_{os}}{2} \end{aligned} \right\} \rightarrow$$

$$V_+ = 0 - I_{B2} \cdot R_3 = -I_{B2} \cdot R_3$$

$$V_o = -I_{B2} \cdot R_3 + \underbrace{\left(\frac{0 - (-I_{B2} R_3)}{R_1} - I_{B1} \right)}_{\text{current } R_2} \cdot R_2$$

Let $I_{B1} = I_{B2}$

$$V_o = I_B \cdot \left(R_2 - R_3 \cdot \left(1 + \frac{R_2}{R_1} \right) \right)$$


Set $R_3 = \frac{R_2}{1 + \frac{R_2}{R_1}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$

$$\Rightarrow V_o = 0$$


$$V_o = I_{os} R_2$$

↑ 10% of I_B


Output Saturation

 

 
- The output voltage swing is limited by
 1. Saturation voltage (usually a volt or two lower than power supply voltage)
 2. Maximum output current (in case of small load resistance)
- Output waveform appears to be **“clipped”** when either condition happens



(a)

 

(b)

 

Slew Rate

Amplifier output is limited by "slew rate":
 maximum rate of change possible at output

$$SR = \left. \frac{dv_o}{dt} \right|_{\max}$$


SR is specified in datasheet in $[V/\mu s]$

Note

SR limit is different from bandwidth limit:


- Limited bandwidth is a linear phenomenon, it does not change the shape of input sinusoid
- SR limitation can cause nonlinear distortion to input sinusoidal signal

Input step

 


(b)

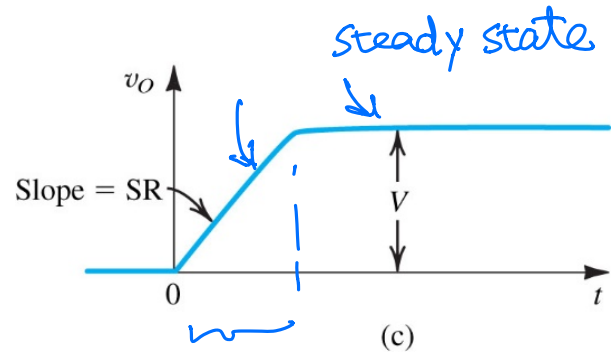**Output not able to follow input;
 Slope limited by SR**




(c)

 
Comparison of Slew Rate and Bandwidth Limits



 For step function input waveform, both SR and bandwidth limits cause the output to rise with a finite slope, but there is an important difference:



Slew rate limited output:
Slope = SR

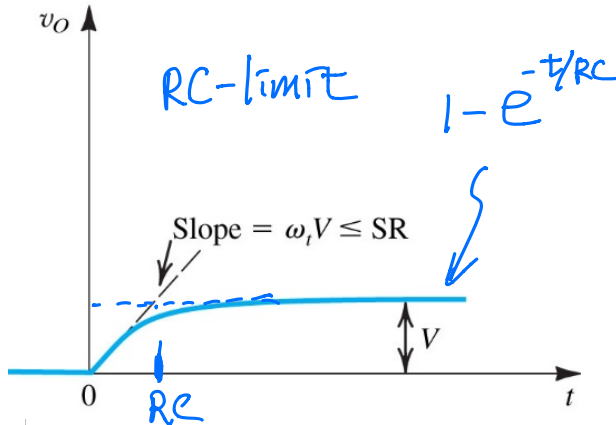

Bandwidth limited output:
Slope = $\omega_t V < SR$
(V is the steady state output voltage)

Full-Power Bandwidth

For ideal sinusoidal output

$$v_o = V_o \sin \omega t$$

Rate of change cannot exceed SR:



$$\frac{dv_o}{dt} = V_o \omega \cdot \cos \omega t \leq SR$$

Full-power bandwidth:

The frequency at which SR-limited distortion starts to occur for an output sinusoid with maximum rated output voltage, $V_{o\max}$,

$$\omega_M V_{o\max} = SR$$

$$f_M = \frac{SR}{2\pi V_{o\max}}$$

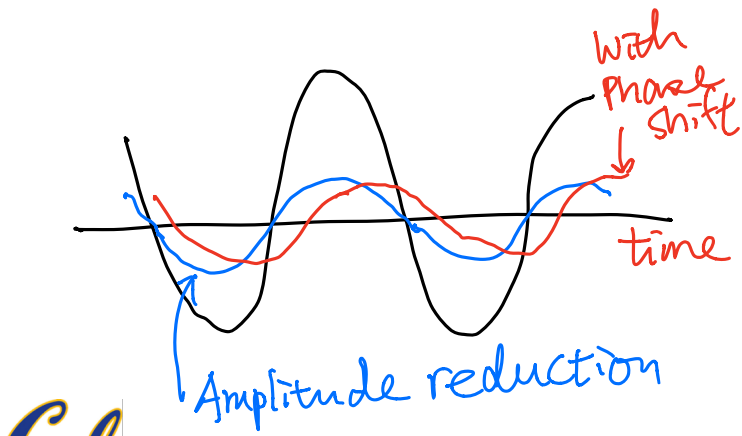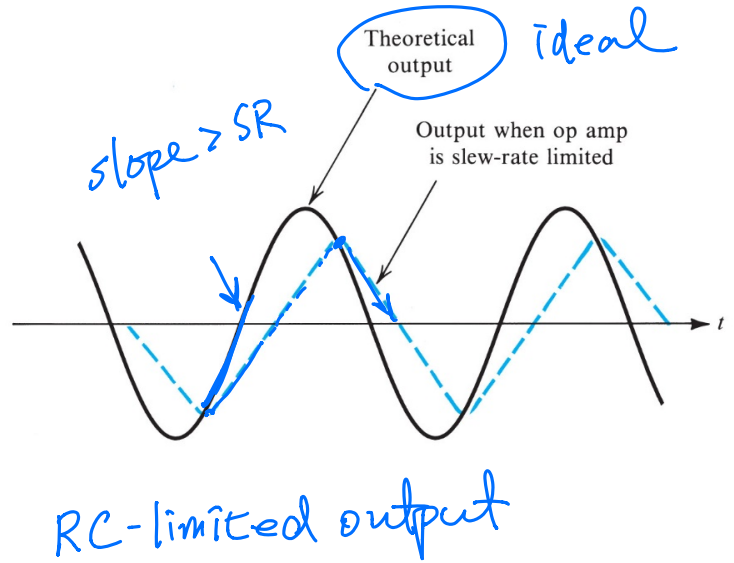

Op Amp Catalog (ti.com)

<https://www.ti.com/amplifier-circuit/op-amps/products.html#>

Hide filters Reset **1468** total parts Email Download to Excel

Number of Channels (#) ≤ 1468 total parts

Total Supply Voltage (Min) (+5V=5, +/-5V=10) ≥ ≤ 1468 total parts

Total Supply Voltage (Max) (+5V=5, +/-5V=10) ≥ ≤ 1468 total parts

GBW (Typ) (MHz) Slew Rate (Typ) (V/us) Rail-to-Rail Vos (Offset Voltage @ 25C) (Max) (mV) Iq per channel (Typ) (mA) Rating

Compare	Part Number	Number of Channels (#)	Total Supply Voltage (Min) (+5V=5, +/-5V=10)	Total Supply Voltage (Max) (+5V=5, +/-5V=10)	GBW (Typ) (MHz)	Slew Rate (Typ) (V/us)	Rail-to-Rail	Vos (Offset Voltage @ 25C) (Max) (mV)	Iq per channel (Typ) (mA)	Rating	Operating Temperature Range (C)	Package Group	Approx. Price (US\$)
<input type="checkbox"/>	ACF2101 - <u>Low Noise, Dual Switched Integrator</u>	2	14.5	36	2	3	No	2	15.5	Catalog	-40 to 125	SOIC	21.06 1ku
<input type="checkbox"/>	AFE030 - Powerline Communications Analog Front-End	1	7	26	0.67	19	No	40	40	Catalog	-40 to 125	VQFN	1.75 1ku
<input type="checkbox"/>	AFE031 - Powerline Communications Analog Front End	1	7	26	0.67	19	No	49	49	Catalog	-40 to 125	VQFN	2.00 1ku
<input type="checkbox"/>	AFE032 - Power Line Communications Analog Front End	1	7	24	3.8	75	No	78	78	Catalog	-40 to 125	VQFN	3.50 1ku
<input type="checkbox"/>	ALM2402-Q1 - Dual Opamp with High Current Output	2	5	16	0.6	0.17	No	15	5	Automotive	-40 to 125	HTSSOP, SON	1.29 1ku
<input type="checkbox"/>	BUF602 - <u>High Speed, Closed Loop Buffer</u>	1	2.8	12.6	1000	8000	No	30	30	Catalog	-45 to 85	SOIC, SOT-23	0.93 1ku
<input type="checkbox"/>	BUF634 - 250mA High-Speed Buffer	1	5	36	180	2000	No	100	1.5	Catalog	-40 to 125	DDPAK/TO-263, PDIP, SOIC, TO-220	3.50 1ku
<input type="checkbox"/>	DRV2700 - DRV2700 High Voltage Driver with Integrated Boost Converter	1	15	105	0.550	0.6		25	13	Catalog	-40 to 85	QFN	4.95 1ku
<input type="checkbox"/>	ICL7652 - Precision Chopper-Stabilized Operational Amplifier	1	7	36	1.9	2.8	In to V-, Out	0.005	1.5	Catalog	0 to 70	PDIP	2.91 1ku
<input type="checkbox"/>	LF147 - Wide Bandwidth Quad JFET Input Operational Amplifiers - <u>Hi-Rel</u>	4	5	44	4	13	In to V+	5	1.8	Military	-55 to 125	CDIP	
<input type="checkbox"/>	LF156 - JFET Input Operational	1	10	44	5	12	In	2	5	Military	-55 to 125	TO-99	




LPF

$$\frac{1}{(1 + j\frac{\omega}{\omega_p})}$$

LP Amplifier
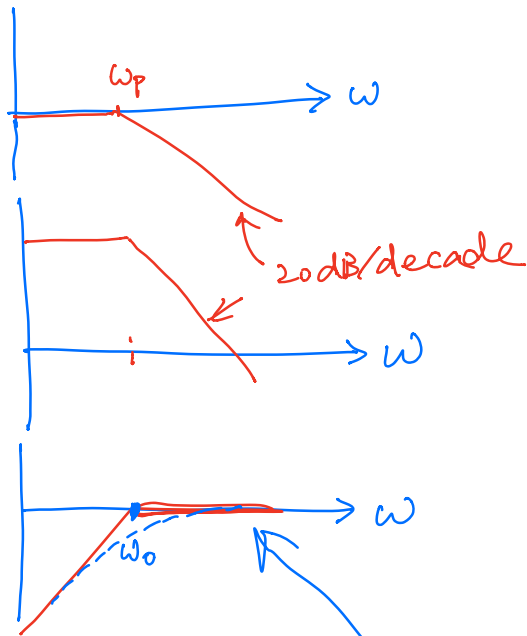
$$\frac{A_0}{1 + j\frac{\omega}{\omega_p}}$$



HPF

$$H(\omega) = \frac{1}{1 + \frac{\omega_0}{j\omega}}$$

$$\omega \ll \omega_0$$

$$H(\omega) \rightarrow \frac{1}{\frac{\omega_0}{j\omega}} = \frac{j\omega}{\omega_0} \propto \omega$$


$$\omega \gg \omega_0$$

$$H(\omega) \rightarrow 1 = 0 \text{ dB}$$


$$\omega = \omega_0, H(\omega) = \frac{1}{1 + j} \Rightarrow \begin{matrix} -3 \text{ dB} \\ \angle = -45^\circ \end{matrix}$$

$$\frac{j\omega}{j\omega + \omega_0} = \frac{s}{s + \omega_0}$$


$s = j\omega$

 
 
$$A \rightarrow A(j\omega) = \frac{A_0}{1 + j\frac{\omega}{\omega_b}}$$



Buffer, Low R_o

 

OTA \equiv load resistance of OTA + Input resistance of buffer

$$I = G_m (V_+ - V_-) = G_m V_{id}$$