

EE105
Microelectronic Devices and Circuits:
MOSFET


Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)

Simplest Model of MOSFET (from EE16B)

N-type MOSFET (NMOS)

 


$$V_{\text{gate}} = V_{\text{GS}}$$

$$V_{\text{DS}} > 0$$

$$I_{\text{DS}} > 0$$

P-type MOSFET (PMOS)

 


$$V_{\text{gate}} = V_{\text{SG}}$$


$$V_{\text{SD}} > 0$$

$$I_{\text{SD}} > 0$$


Case 1.
 $V_{\text{gate}} < V_{\text{th,N}}$

 


Case 2.
 $V_{\text{gate}} > V_{\text{th,N}}$

 


Case 1.
 $V_{\text{gate}} < V_{\text{th,P}}$

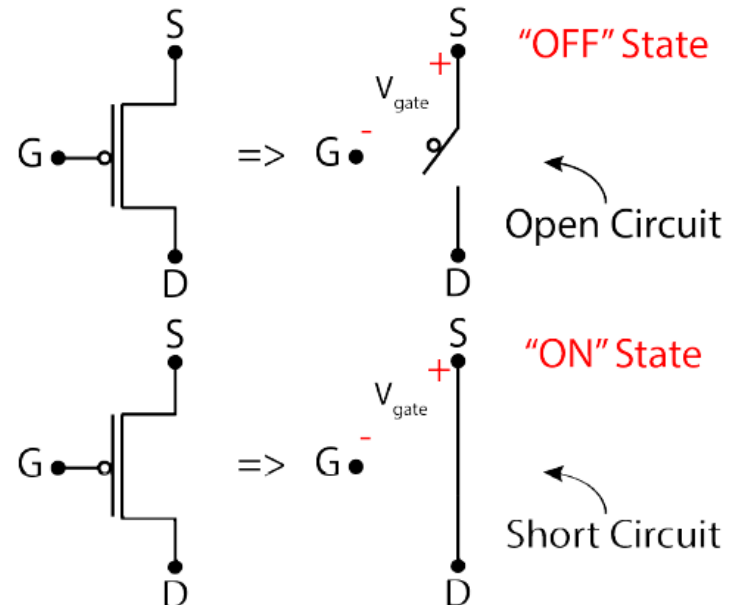

 
Case 2.
 $V_{\text{gate}} > V_{\text{th,P}}$




CMOS Inverter

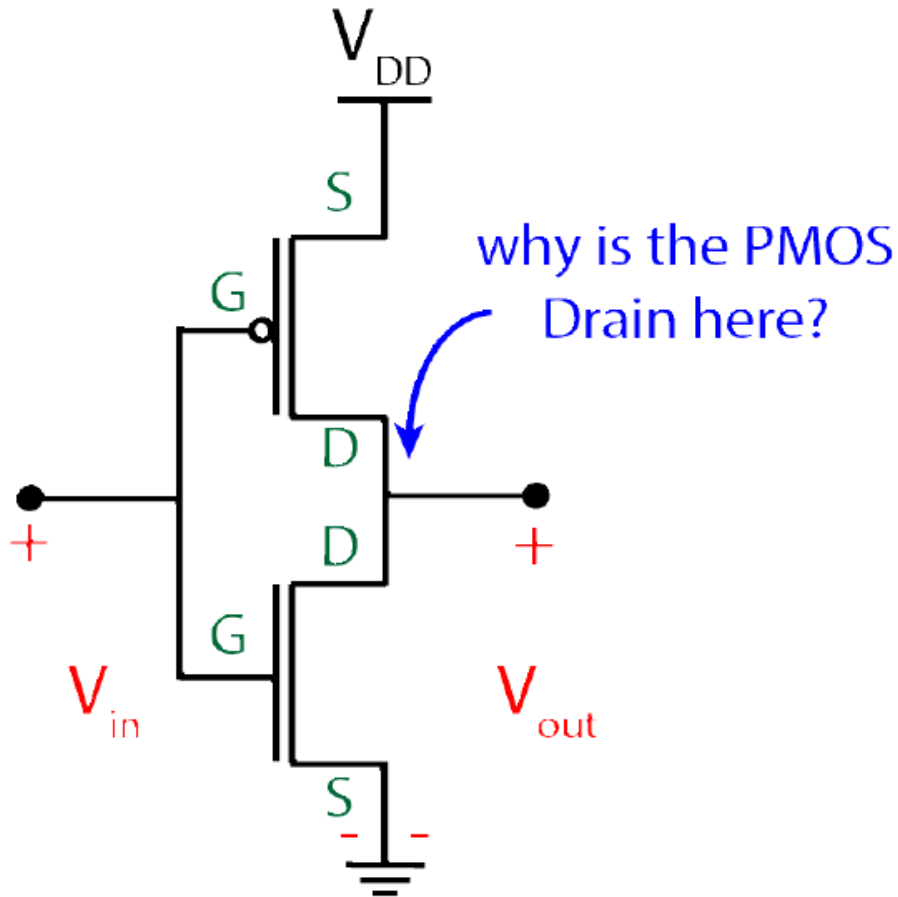


CMOS NAND Gate

 


More Circuit Symbol for NMOS

 

(a)

 

(b)

 

(c)

4 terminal including Body
(Arrow pointing to channel indicating substrate is p-type)


Modified circuit symbol with arrow on source
(Arrow indicating direction of current flow)

Simplified circuit symbol with body connected to source (or when the effect of the body on device operation is unimportant)


Note in NMOS

1. Drain voltage is always more positive than Source voltage
2. Current always flows from Drain to Source


More Circuit Symbol of PMOS

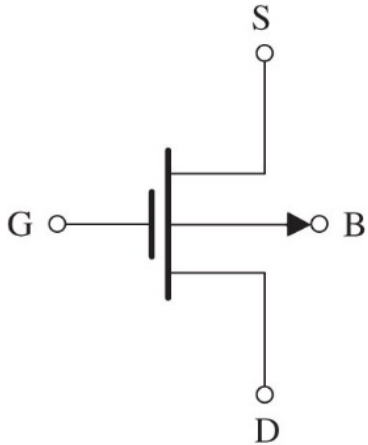

 4 terminal including Body
(Arrow pointing away from channel indicating substrate is n-type)



 Modified circuit symbol with arrow on source
(Arrow indicating direction of current flow)





Simplified circuit symbol with body connected to source (or when the effect of the body on device operation is unimportant)

Note in PMOS

1. Source voltage is always more positive than Drain voltage
2. Current always flows from Source to Drain
3. Source is usually drawn on top so current flows downward (convention)

Analog Voltage Amplifier

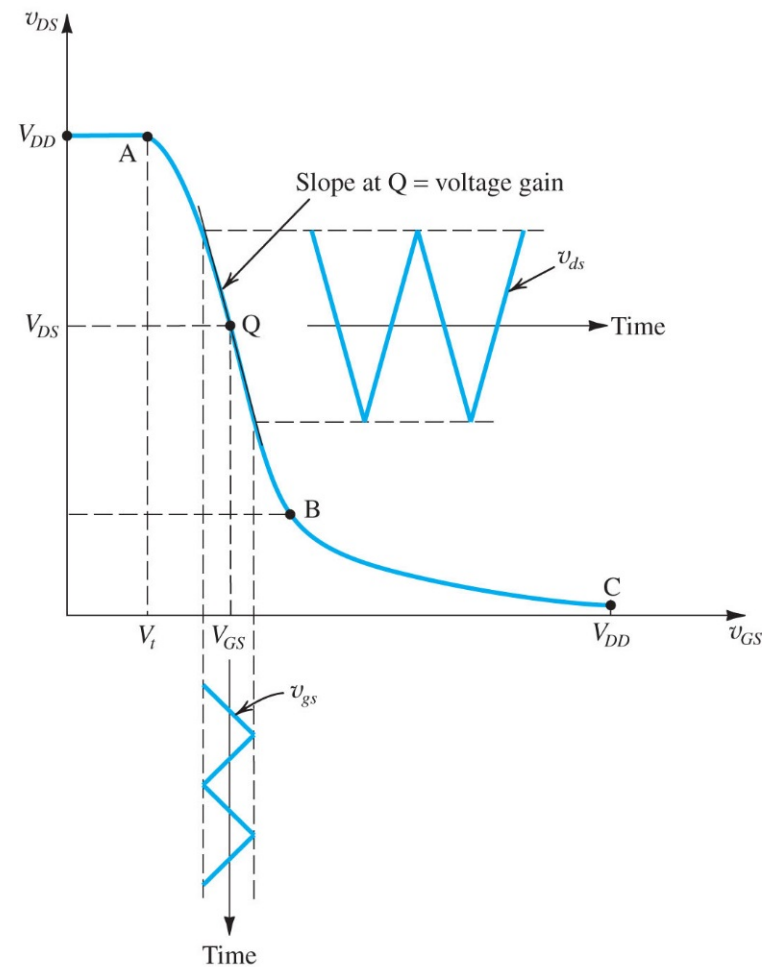 


- DC bias at Quiescent (Q) point
- Small-signal input superimposed on a DC bias voltage
- Symbol used in this course:


$$v_{GS} = V_{GS} + v_{gs}$$

- Need to know the transistor's I-V characteristics to find the voltage gain (and other properties of the amplifier)

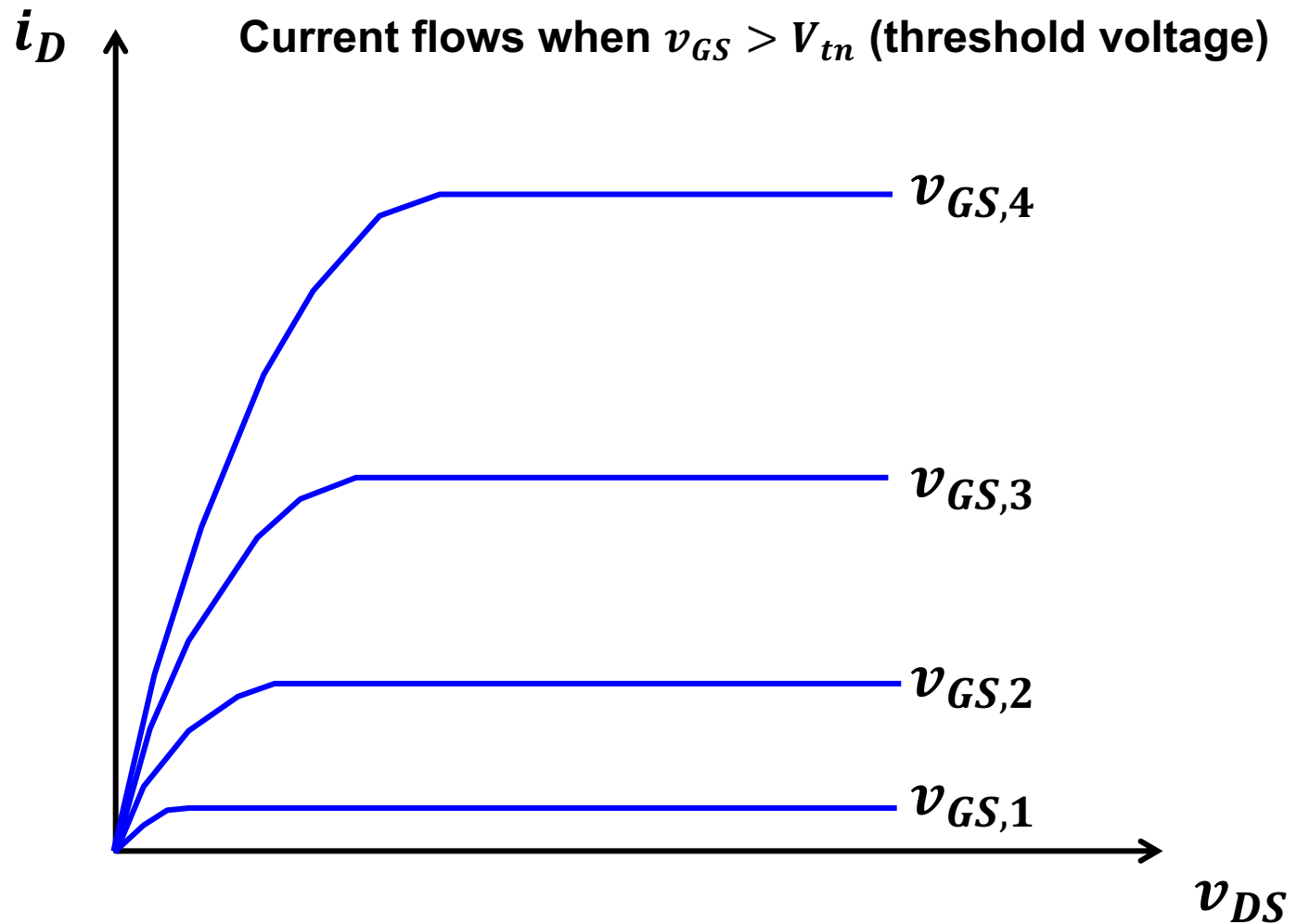I-V Curves of NMOS (for fixed Gate Voltage)




Drain Current vs Gate Voltage


 


$$i_D = \frac{1}{2} k_n (v_{GS} - V_{tn})^2$$

“Square Law”

 


MOSFET Device Structure

  


- **MOSFET: metal-oxide-semiconductor field effect transistor**
- **Typically**
 - Channel length: $L \sim < 10 \text{ nm to } 0.35 \mu\text{m}$,
 - Channel width: $W \sim 0.05 \mu\text{m to } 100 \mu\text{m}$,
 - Oxide thickness: $t_{ox} \sim 1 \text{ to } 10 \text{ nm}$

NMOSFET (or simply NMOS)

 

- **N-channel MOSFET**
 - Current conducted by electrons
- **3 terminal device**
 - Source (S): n+ (heavily n-type)
 - Drain (D): n+
 - Gate (G): metal deposited on insulator above channel
- **Substrate (called “Body”) is a 4th terminal**
 - Substrate is p-doped
- **Electrons is induced in channel when a positive gate voltage is applied**
- **Electrons moves from Source to Drain**
 - Current flows from D to S

Creating a "Channel" for Current Flow

 

MOS is a capacitor across an insulator (oxide)
 When a positive voltage is applied at Gate,
 electrons are induced under the gate.

At "threshold", sufficient number of electrons
 form a "channel" between Source and Drain,
 forming a conductive channel.

Total charge in the channel:

$$|Q| = C_{ox} \cdot WL \cdot (v_{GS} - V_t)$$

where $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$ is oxide capacitance

per unit area

$$\epsilon_{ox} = 3.9\epsilon_0 = 3.9 \times 8.854 \times 10^{-12} \text{ F/m}$$

W : gate width

L : gate length


V_t : Threshold voltage

$v_{GS} - V_t \equiv v_{OV}$ is called "Overdrive Voltage"

Large-Signal Model

(usually used to solve DC bias voltage and current)

Current at Small v_{DS}

 

When $v_{OV} = v_{GS} - V_t > 0$, a channel is formed between Source and Drain.

Linear charge density in channel:

$$\frac{|Q|}{L} = C_{ox} W \cdot v_{OV}$$

Electric field along the channel

$$|E| = \frac{v_{DS}}{L}$$


Drain current = charge density x velocity:

$$i_D = \frac{|Q|}{L} v_n = \frac{|Q|}{L} \mu_n |E| = C_{ox} W \cdot v_{OV} \mu_n \frac{v_{DS}}{L}$$

$$i_D = \mu_n C_{ox} \frac{W}{L} v_{OV} v_{DS}$$

At small v_{DS} , the transistor is like a gate-controlled variable resistor

Current at Small v_{DS}

 

$$i_D = \mu_n C_{ox} \frac{W}{L} v_{OV} v_{DS}$$

$$= k'_n \frac{W}{L} v_{OV} v_{DS}$$

$$= k_n v_{OV} v_{DS}$$

where

$k'_n = \mu_n C_{ox}$: process transconductance parameter

$k_n = \mu_n C_{ox} \frac{W}{L}$: MOSFET transconductance parameter


MOSFET behaves like a linear resistor

$$r_{DS} = \frac{v_{DS}}{i_D} = \frac{1}{k_n v_{OV}}$$

Resistance value can be changed

by gate voltage (overdrive voltage)

Triode Region ($v_{DS} < v_{OV}$)

 

As v_{DS} increases, the potential in the channel is no longer a constant. Assume the channel is $v(x)$:

$$i_D = C_{ox} W (v_{GS} - v(x) - V_t) v_n(x)$$

$$v_n(x) = \mu_n |E(x)| = \mu_n \frac{dv(x)}{dx}$$

Note: i_D is still constant along the channel (think Kirchhoff's Current Law)

Integrate along the channel


$$\int_{x=0}^{x=L} i_D dx = \int_{x=0}^{x=L} \left(C_{ox} W (v_{GS} - v(x) - V_t) \mu_n \frac{dv(x)}{dx} \right) dx$$

Change of variable on right-hand side: $x \rightarrow v$

$$i_D L = \int_{v=0}^{v=v_{DS}} (C_{ox} W (v_{OV} - v) \mu_n) dv$$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left(v_{OV} v_{DS} - \frac{1}{2} v_{DS}^2 \right)$$

Triode Region ($v_{DS} < v_{OV}$)

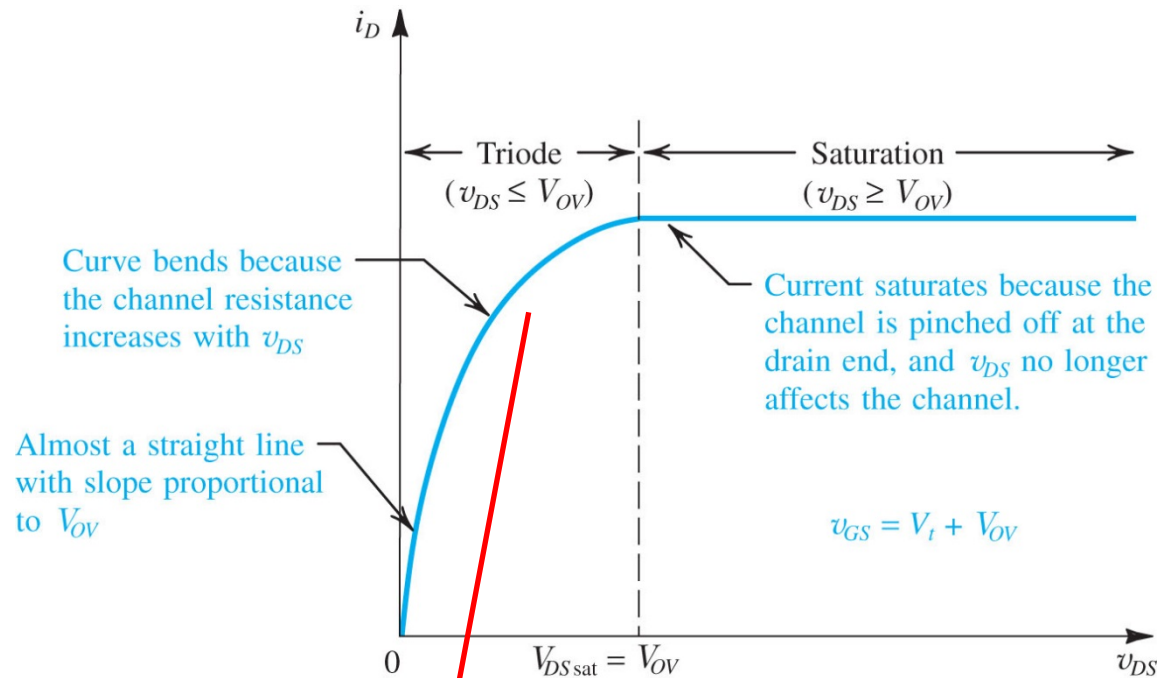


When $0 \leq v_{DS} \leq v_{OV}$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left(v_{OV} v_{DS} - \frac{1}{2} v_{DS}^2 \right)$$

This is called the "Triode Region"

Pinch-Off

 

The channel potential at the drain side is v_{DS} .

When $v_{DS} = v_{OV}$, the local charge density there

$$\frac{|Q|}{\text{area}} = C_{ox} (v_{GS} - v_{DS} - V_t) = C_{ox} (v_{OV} - v_{DS}) = 0$$


So the channel is "pinched off" near the Drain.

Once the channel is pinched off, the drain current remains constant:

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2$$

This region, $v_{DS} > v_{OV}$, is called "Saturation"

Saturation Region ($v_{DS} > v_{OV}$)

 

When $0 \leq v_{DS} \leq v_{OV}$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left(v_{OV} v_{DS} - \frac{1}{2} v_{DS}^2 \right)$$


This is called the "Triode Region"

When $v_{DS} > v_{OV}$,

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2$$


This is called "Saturation Region"

Full I-V Curves of NMOSFET

 

V_{tn} : threshold voltage of NMOS

Drain Current vs Gate Voltage

 

In Saturation Region

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2$$
$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{tn})^2$$



To experimentally determine V_{tn} :

Measure and plot $\sqrt{i_D}$ versus v_{GS}

$$\sqrt{i_D} = \sqrt{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} (v_{GS} - V_{tn})$$


V_{tn} = intercept with horizontal axis

PMOSFET (or simply PMOS)

  

- **P-channel MOSFET**
 - Current conducted by holes
- **3 terminal device**
 - Source (S): p+ (heavily p-type)
 - Drain (D): p+
 - Gate (G): metal deposited on insulator above channel
- **Substrate (called “Body”) is a 4th terminal**
 - Substrate is n-doped
- **Holes is induced in channel when a negative gate voltage is applied**
- **Holes moves from Source to Drain**
 - Current flows from S to D

CMOS (Complementary MOS)

 

- **CMOS is the prevalent IC technology today**
- **Since NMOS and PMOS are formed on oppositely doped substrates, one of the transistor needs to be placed in a “well”**
- **PMOS is placed in an “n well” here.**
- **Alternatively, NMOS can be placed in p well**