

**EE105**

**Microelectronic Devices and Circuits:  
MOS Large Signal Model and Bias Circuits**


**Prof. Ming C. Wu**

**wu@eecs.berkeley.edu**

**511 Sutardja Dai Hall (SDH)**


 
# Saturation Region ( $v_{DS} > v_{OV}$ )



When  $0 \leq v_{DS} \leq v_{OV}$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left( v_{OV} v_{DS} - \frac{1}{2} v_{DS}^2 \right)$$


This is called the "Triode Region"

When  $v_{DS} > v_{OV}$ ,

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2$$

This is called "Saturation Region"

# Drain Current vs Gate Voltage

 

In Saturation Region

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2$$
$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{tn})^2$$



To experimentally determine  $V_{tn}$  :

Measure and plot  $\sqrt{i_D}$  versus  $v_{GS}$

$$\sqrt{i_D} = \sqrt{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} (v_{GS} - V_{tn})$$

$V_{tn}$  = intercept with horizontal axis

# Analog Voltage Amplifier

  


- DC bias at Quiescent (Q) point
- Small-signal input superimposed on a DC bias voltage
- Symbol used in this course:

$$v_{GS} = V_{GS} + v_{gs}$$

- Need to know the transistor's I-V characteristics to find the voltage gain (and other properties of the amplifier)

# Diode-Connected Transistor

 

With Gate connected to Drain, it becomes a 2-terminal device.

This is called "diode-connected transistor"

In this configuration, the transistor is always in "Saturation".

Its I-V relationship is:

$$i = I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2$$

$$v_{GS} = v_{DS} = v$$


$$v_{OV} = v_{GS} - V_{tn} = v - V_{tn}$$

$$i = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v - V_{tn})^2$$
 
# Example Circuit (1)

Design Problem:

Determine  $R_S$  and  $R_D$  such that the NMOS is biased at  $I_D = 0.4\text{mA}$  and  $V_D = 0.5\text{V}$ . The NMOS has  $V_t = 0.7\text{V}$ ,  $\mu_n C_{ox} = 100\mu\text{A}/\text{V}^2$ ,  $L = 1\mu\text{m}$  and  $W = 32\mu\text{m}$ .



Solution:

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4} = 5\text{k}\Omega$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2 = 0.4\text{mA} \rightarrow v_{OV} = 0.5\text{V}$$



(channel length modulation can usually be ignored when solving DC bias)

$$v_{GS} = V_t + v_{OV} = 0.7 + 0.5 = 1.2\text{V}$$

$$V_G = 0 \text{ (grounded)} \rightarrow V_S = -1.2\text{V}$$

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{-1.2 - (-2.5)}{0.4} = 3.25\text{k}\Omega$$

# Example Circuit (2)

  

(b)

The resistor divider is a common bias circuit.

To solve the DC bias condition, it means to solve  $I_D, V_{DS}, V_{GS}$

The NMOS has  $V_{tn} = 1\text{ V}$ ,  $k_n = \mu_n C_{ox} \frac{W}{L} = 1\text{ mA/V}^2$

First, solve  $V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}} = 10 \frac{5}{5+5} = 5\text{ V}$

$V_{GS} = 5 - I_D R_S = 5 - 6I_D$  (with  $I_D$  in mA)

Next, assume the transistor is in saturation:

$$I_D = \frac{1}{2} k_n v_{OV}^2 = 0.5 (V_{GS} - V_{tn})^2 = 0.5 (5 - 6I_D - 1)^2$$

$$18I_D^2 - 25I_D + 8 = 0 \quad \rightarrow \quad I_D = 0.89\text{ mA or } 0.5\text{ mA}$$

If  $I_D = 0.89\text{ mA}$ ,  $V_{GS} = -0.34\text{ V}$ , NMOS will be cut-off



$\rightarrow$  not a physical solution.

If  $I_D = 0.5\text{ mA}$ ,  $V_{GS} = 2\text{ V}$ ,  $V_{OV} = 2 - 1 = 1\text{ V}$

$V_{DS} = V_{DD} - I_D (R_D + R_S) = 10 - 6 = 4\text{ V} > V_{OV}$

Saturation assumption verified !



# PMOS I-V Curves

  





# Right Side Up!

$$I_{SD} = |I_{DS}|$$

  

# PMOS I-V Equations

  

## Triode Region:

$$i_D = \mu_p C_{ox} \frac{W}{L} \left( |v_{OV}| |v_{DS}| - \frac{1}{2} v_{DS}^2 \right)$$

$$v_{OV} = |v_{SG}| - |V_{tp}|$$

Use same equation as NMOS but add absolute sign on all voltages

since most voltages are negative:

$$V_{tp} < 0, v_{DS} < 0, v_{GS} < 0$$

So either use  $v_{SD}$  or  $|v_{DS}|$

## Saturation Region:

$$i_D = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right) \left( |v_{GS}| - |V_{tp}| \right)^2$$

$$= \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right) v_{OV}^2$$

# Example Circuit (3)

## Design Problem:

Design the circuit such that  $I_D = 0.5\text{mA}$  and  $V_D = 3\text{V}$ .

PMOS has  $V_{tp} = -1\text{V}$ ,  $\mu_p C_{ox} (W/L) = 1\text{mA/V}^2$ .

Also find the maximum  $R_D$  for PMOS to remain in Saturation

## Solution:

$$I_D = \frac{1}{2} k_p V_{OV}^2 = 0.5\text{mA} \rightarrow |V_{OV}| = 1\text{V}$$


$$|V_{GS}| = |V_{tp}| + |V_{OV}| = 1 + 1 = 2\text{V}$$

$$V_S = 5\text{V} \rightarrow V_G = 3\text{V}$$

We can choose  $R_{G1} = 2\text{M}\Omega$  and  $R_{G2} = 3\text{M}\Omega$

Saturation:  $V_D \leq 5 - |V_{OV}| = 4\text{V}$
 
$$R_{D,\text{max}} = \frac{V_{D,\text{max}}}{I_D} = \frac{4}{0.5} = 8\text{k}\Omega$$




# Finite Output Resistance due to Channel Length Modulation

When  $v_{DS} = v_{OV}$ , the channel pinch off of near the Drain. With further increase in  $v_{DS}$ , the pinch off point moves slowly towards the source, effectively reducing the channel length from  $L$  to  $L - \Delta L$  (this is called "channel length modulation"):

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L - \Delta L} (v_{GS} - V_{tn})^2$$

The continual increase of  $i_D$  with  $v_{DS}$  is modeled by
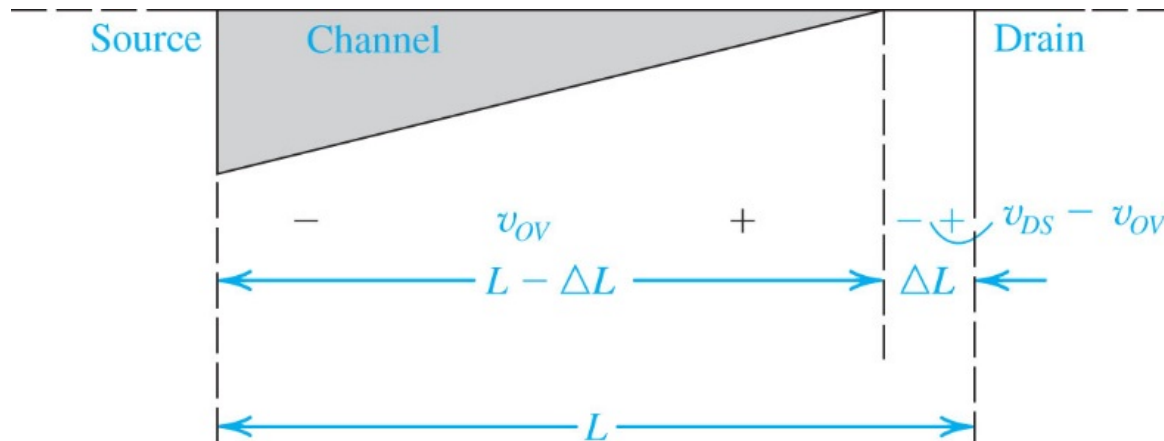
$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{tn})^2 (1 + \lambda v_{DS})$$



# Output Resistance of MOSFET

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{tn})^2 (1 + \lambda v_{DS})$$

$$r_o = \left( \frac{\partial v_{DS}}{\partial i_D} \right)_{v_{GS}=V_{GS}} = \left( \frac{\partial i_D}{\partial v_{DS}} \right)_{v_{GS}=V_{GS}}^{-1} = \frac{1}{\lambda \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{tn})^2 \right)} \approx \frac{1}{\lambda I_D}$$

$r_o = \frac{1}{\lambda I_D}$  where  $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{tn})^2$  is the DC bias current at Drain.

