 


NMOS, $V_{t,n} = 0.7V$, $\mu_n C_{ox} = k'_n = 100 \mu A/V^2$
 $W/L = 32 \mu m / 1 \mu m$
 $\Rightarrow k_n = k'_n \left(\frac{W}{L}\right) = 3.2 \text{ mA/V}^2$

Assume M_1 is in saturation

$$I_D = \frac{1}{2} k_n V_{ov}^2$$

Design: \rightarrow set I_D, V_{DS} (DC)



\rightarrow Amplifier gain

$$\propto \sqrt{I_D}$$

Power consumption

$$(V_{DD} - V_{SS}) \times I_D$$

V_{DS} : Output swing

\uparrow
Peak-to-peak

Goal: $I_D = 0.4 \text{ mA}$, $V_D = 0.5V$

$$I_D = \frac{1}{2} k_n V_{ov}^2 = 0.4 \text{ mA} = (1.6 \text{ mA/V}^2) \cdot V_{ov}^2$$

$$V_{ov}^2 = \frac{1}{4} \Rightarrow V_{ov} = \frac{1}{2} = \underline{0.5V} = V_{GS} - V_{t,n}$$

$$\Rightarrow V_{GS} = 0.5 + 0.7 = 1.2V = \underset{0}{V_G - V_S}$$

$$\Rightarrow V_S = -1.2V$$



$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{(2.5 - 0.5)V}{0.4 \text{ mA}} = 5 \text{ k}\Omega$$

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{(-1.2 - (-2.5))V}{0.4 \text{ mA}} = \frac{1.3}{0.4} = 3.25 \text{ k}\Omega \#$$

$$V_{DS} = V_D - V_S = 0.5 - (-1.2) = 1.7V > V_{ov} = 0.5V$$

Assumption is valid #

Example Circuit (2)

  

(b)

The resistor divider is a common bias circuit.

To solve the DC bias condition, it means to solve

$$I_D, V_{DS}, V_{GS}$$

The NMOS has $V_m = 1V$, $k_n = \mu_n C_{ox} \frac{W}{L} = 1mA/V^2$

$$\text{First, solve } V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}} = 10 \frac{5}{5+5} = 5V$$

$$V_{GS} = 5 - I_D R_S = 5 - 6I_D \quad (\text{with } I_D \text{ in mA})$$

Next, assume the transistor is in saturation:

$$I_D = \frac{1}{2} k_n v_{OV}^2 = 0.5 (V_{GS} - V_m)^2 = 0.5 (5 - 6I_D - 1)^2$$

$$18I_D^2 - 25I_D + 8 = 0 \quad \rightarrow I_D = 0.89mA \text{ or } 0.5mA$$

If $I_D = 0.89mA$, $V_{GS} = -0.34V$, NMOS will be cut-off


--> not a physical solution.

If $I_D = 0.5mA$, $V_{GS} = 2V$, $V_{OV} = 2 - 1 = 1V$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 10 - 6 = 4V > V_{OV}$$

Saturation assumption verified !

As a design problem

 

$$V_{ov} = V_{gs} - V_{t,n}$$

$$V_{gs} = V_{ov} + V_{t,n}$$

NMOS. $V_{t,n} = 1V$, $k_n = 1 \text{ mA/V}^2$

Design goal $I_D = 0.5 \text{ mA}$

Assume M_1 is saturation

$$I_D = \frac{1}{2} k_n V_{ov}^2 = 0.5 \text{ mA} \leftarrow$$

$$V_{ov}^2 = 1 \Rightarrow V_{ov} = 1V$$

$$V_{gs} = V_{ov} + V_{t,n} = 1 + 1 = 2V$$

Design rule of thumb:

$\approx 1/3$ voltage drop to each element

$$V_{gs} = 3V \rightarrow > V_{ov} = 1V$$

verify M_1 is indeed in saturation

$$R_D = \frac{4V}{0.5 \text{ mA}} = 8 \text{ k}\Omega$$

$$R_S = \frac{3V}{0.5 \text{ mA}} = 6 \text{ k}\Omega$$


$$V_G = 3 + 2 = 5V$$

$$R_{G1} = R_{G2}, V_G = \frac{R_{G2} V_{DD}}{R_{G1} + R_{G2}} = 5V$$

What do we choose $R_{G1} = R_{G2} = ?$

Choose large R_G to minimize power consumption



 
eg. $R_{G1} = R_{G2} = 1 \text{ M}\Omega$ or $10 \text{ M}\Omega$



RC time



\Rightarrow Bandwidth

PMOS I-V Curves

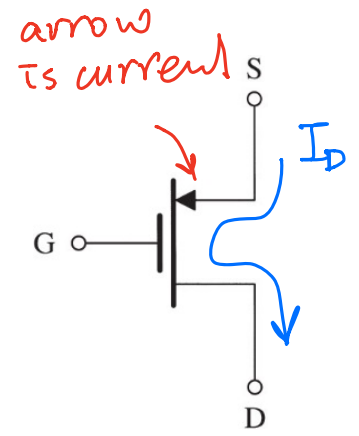  



Right Side Up!

$$I_{SD} = |I_{DS}|$$

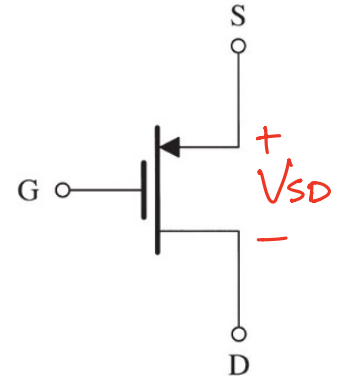 

$$\underline{V_{SD}} = |V_{DS}|$$

PMOS I-V Equations

  

Triode Region:

$$i_D = \mu_p C_{ox} \frac{W}{L} \left(|v_{OV}| |v_{DS}| - \frac{1}{2} v_{DS}^2 \right)$$

$$v_{OV} = |v_{SG}| - |V_{tp}|$$

Use same equation as NMOS but add absolute sign on all voltages

since most voltages are negative:

$$V_{tp} < 0, v_{DS} < 0, v_{GS} < 0$$

So either use v_{SD} or $|v_{DS}|$


Saturation Region:

$$i_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) \left(|v_{GS}| - |V_{tp}| \right)^2$$

$$= \frac{1}{2} \underbrace{\mu_p C_{ox} \left(\frac{W}{L} \right)}_{k_p} v_{OV}^2$$

k_p

Example Circuit (3)

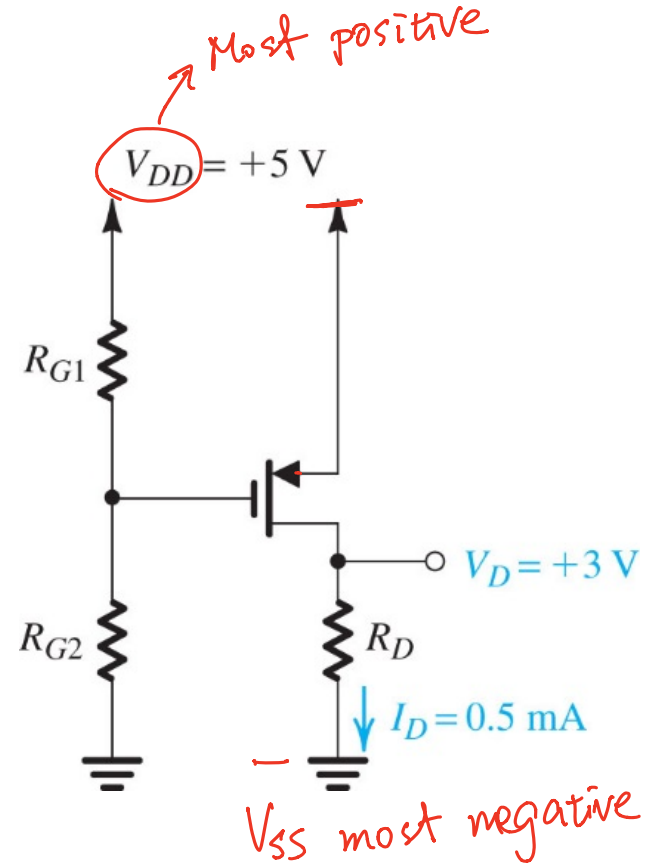

Design Problem:

Design the circuit such that $I_D = 0.5\text{ mA}$ and $V_D = 3\text{ V}$.

PMOS has $V_{tp} = -1\text{ V}$, $\mu_p C_{ox}(W/L) = 1\text{ mA/V}^2$.

Also find the maximum R_D for PMOS to remain in Saturation

Solution:

$$I_D = \frac{1}{2} k_p V_{OV}^2 = 0.5\text{ mA} \quad \rightarrow \quad |V_{OV}| = 1\text{ V}$$


$$|V_{GS}| = |V_{tp}| + |V_{OV}| = 1 + 1 = 2\text{ V}$$

$$V_S = 5\text{ V} \quad \rightarrow \quad V_G = 3\text{ V}$$

We can choose $R_{G1} = 2\text{ M}\Omega$ and $R_{G2} = 3\text{ M}\Omega$

Saturation: $V_D \leq 5 - |V_{OV}| = 4\text{ V}$
 
$$R_{D,\text{max}} = \frac{V_{D,\text{max}}}{I_D} = \frac{4}{0.5} = 8\text{ k}\Omega$$



Design example

PMOS: $V_{tp} = -1V$, $k_p = 1 \text{ mA/V}^2$

Design goal $I_D = 0.5 \text{ V}$

M_1 in saturation

$$I_D = \frac{1}{2} k_p V_{ov}^2 = 0.5 \text{ mA}$$

↑
1 mA/V²

$$\Rightarrow V_{ov}^2 = 1 \text{ V} \Rightarrow \underline{|V_{ov}| = 1}$$

$$|V_{GS}| = |V_{ov}| + |V_{t,p}| = 1 + 1 = 2 \text{ V}$$

$$\text{Choose } V_D = \frac{1}{2} V_{DD} = 2.5 \text{ V}$$

$$\Rightarrow |V_{DS}| = |V_{DD} - V_D| = 2.5 \text{ V} > |V_{ov}| \checkmark$$

M_1 indeed in saturation

R_{G1} , R_{G2} ,

$$\text{Choose } R_{G1} = 2 \text{ M}\Omega, R_{G2} = 3 \text{ M}\Omega$$

$$V_G = V_{DD} \cdot \frac{R_{G2}}{R_{G1} + R_{G2}} = 3 \text{ V}$$

Consider channel length modulation

$$\frac{1}{2} k_p V_{ov}^2 (1 + \lambda |V_{DS}|) = 0.5 \text{ mA}$$

\Rightarrow Solving Bias (DC) Problem by hand, Ignore λ


Finite Output Resistance due to Channel Length Modulation


When $v_{DS} = v_{OV}$, the channel pinch off near the Drain. With further increase in v_{DS} , the pinch off point moves slowly towards the source, effectively reducing the channel length from L to $L - \Delta L$ (this is called "channel length modulation"):

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L - \Delta L} (v_{GS} - V_m)^2$$


The continual increase of i_D with v_{DS} is modeled by
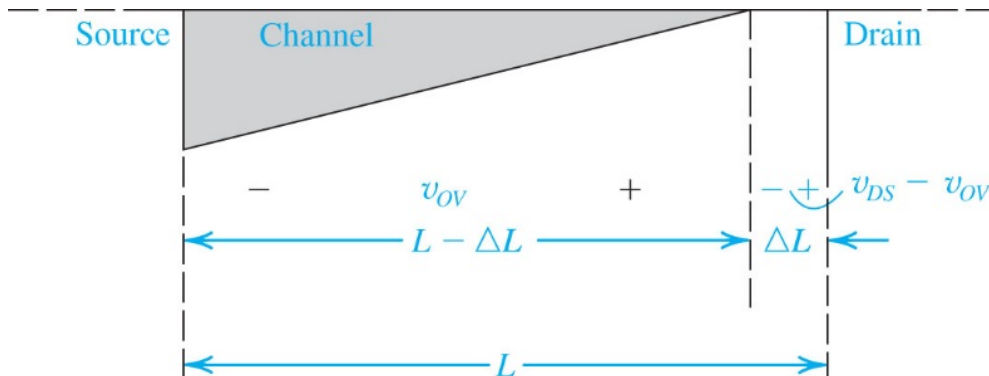
$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_m)^2 (1 + \lambda v_{DS})$$



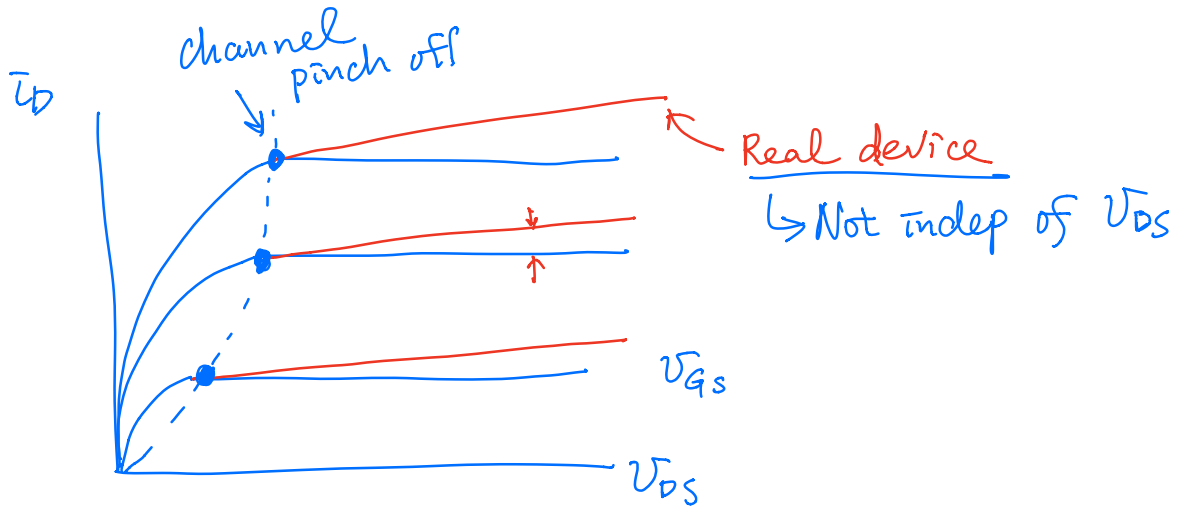
 
$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot V_{ov}^2 \quad \text{indep of } V_{DS}$$



Channel length modulation

$$V_{DS} = V_{ov} = V_{GS} - V_{thn}$$

Increase V_{DS} further

$$\Delta L \propto V_{DS}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L - \Delta L}\right) \cdot V_{ov}^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) V_{ov}^2 \cdot \left(\frac{1}{1 - \frac{\Delta L}{L}}\right)$$

$$\frac{\Delta L}{L} \ll 1 \quad \left(1 - \frac{\Delta L}{L}\right)^{-1} \approx 1 + \frac{\Delta L}{L} = 1 + \lambda V_{DS}$$

$$\frac{1}{1 - \epsilon} \approx 1 + \epsilon$$


Consider channel length modulation

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot V_{ov}^2 (1 + \lambda V_{DS})$$

Output Resistance of MOSFET

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_m)^2 (1 + \lambda v_{DS})$$
 
$$r_o = \left(\frac{\partial v_{DS}}{\partial i_D} \right)_{v_{GS}=V_{GS}} = \left(\frac{\partial i_D}{\partial v_{DS}} \right)_{v_{GS}=V_{GS}}^{-1} = \frac{1}{\lambda \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_m)^2 \right)} \approx \frac{1}{\lambda I_D}$$




$$r_o = \frac{1}{\lambda I_D} \text{ where } I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_m)^2 \text{ is the DC bias current at Drain.}$$

$$r_o = \frac{\Delta v_{DS}}{\Delta i_{DS}} = \frac{1}{\frac{\partial i_D}{\partial v_{DS}}}$$

$$= \frac{1}{\left(\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) v_{ov}^2 \right) \lambda} = \frac{1}{\lambda I_D}$$

$= I_D$

 

Ignore λ
 $(\lambda=0)$
 $r_o = \frac{1}{\lambda I_D} \rightarrow \infty$
 Fine for DC
 For AC
 consider λ

To find V_A

$$I_D = 0 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) v_{ov}^2 [1 + \lambda(-V_A)]$$

$$\Rightarrow 1 - \lambda V_A = 0 \Rightarrow V_A = \frac{1}{\lambda} \quad (\text{"Early" Voltage})$$

$$\lambda: [V^{-1}]$$

↑
Name derive from
BJT terminology