

EE105

Microelectronic Devices and Circuits:

MOS Small-Signal Model


Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)




Voltage Transfer Curves

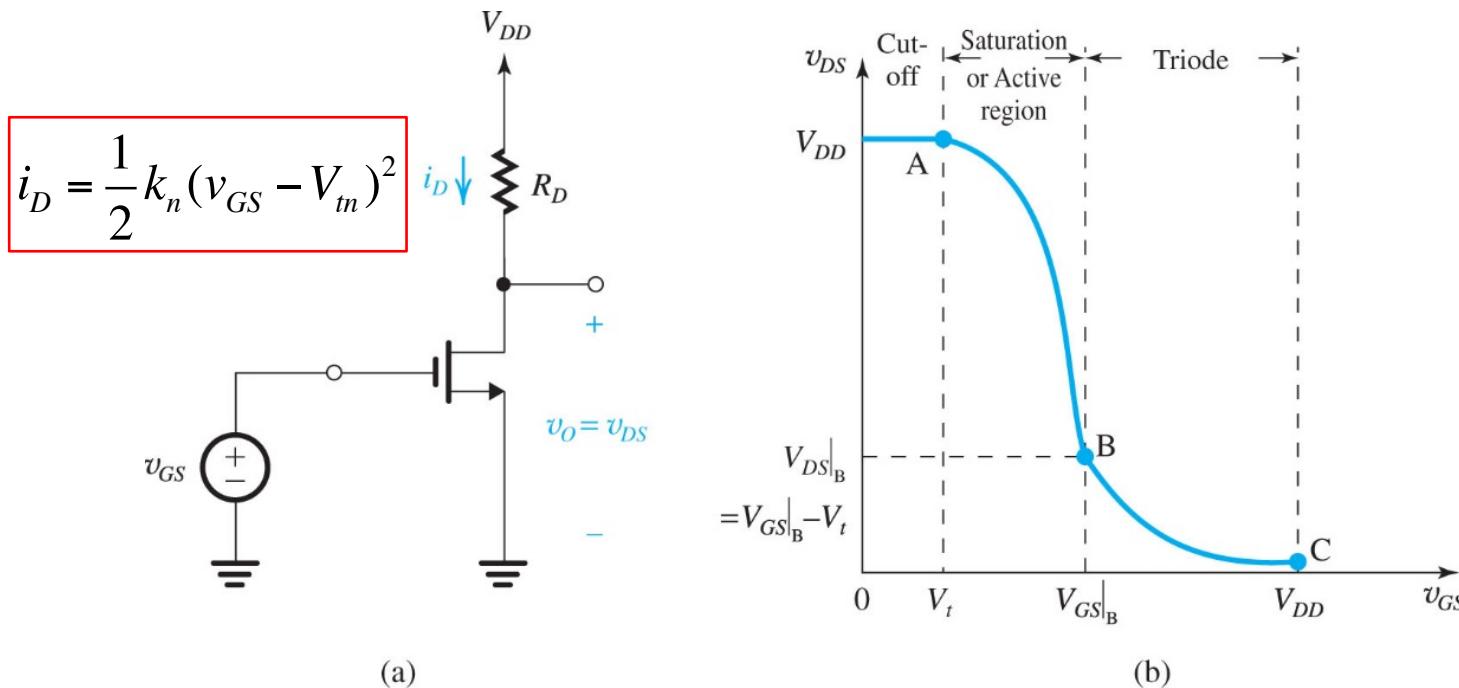


- Transistors are transimpedance amplifiers
 - MOSFET: v_{GS} controls i_D
- Adding load resistors converts current to voltage → voltage amplifiers
 - Drain voltage free to change in saturation mode

Voltage Amplifier

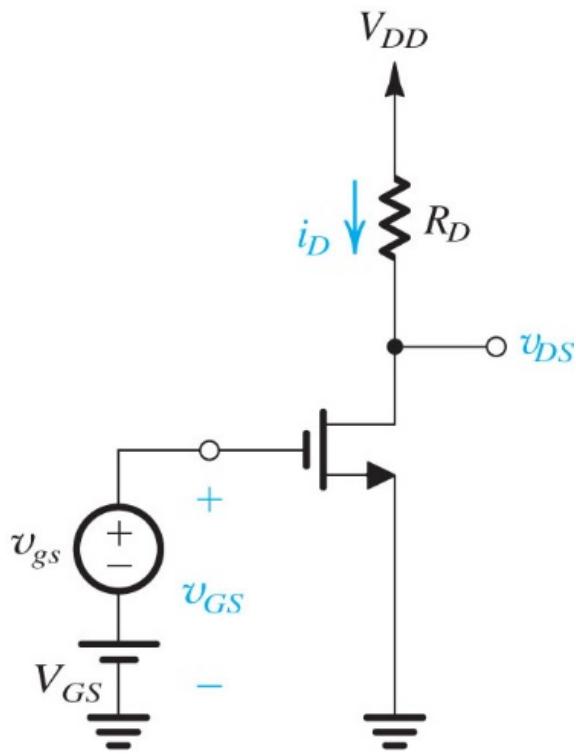

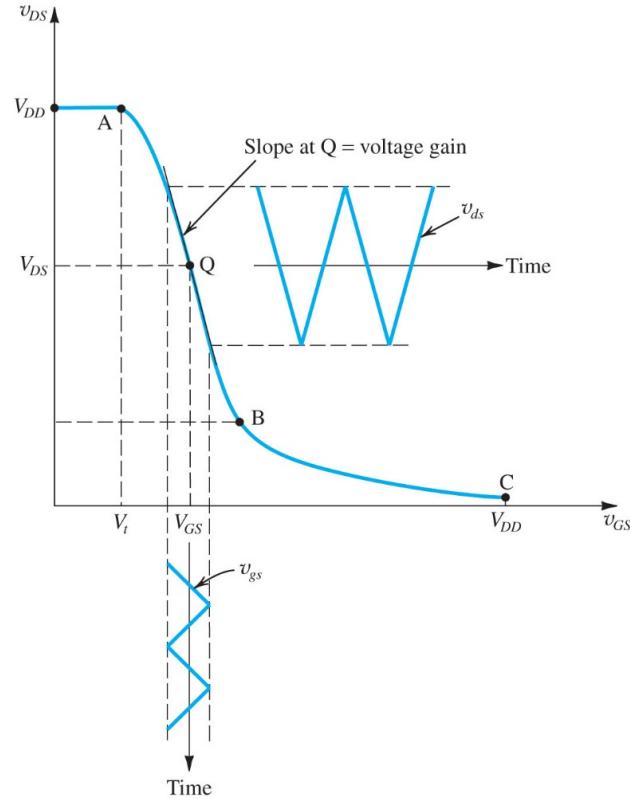- DC bias at Q point (Quiescent point)**
- Small-signal input superimposed on DC bias voltage**





$$v_{DS} = V_{DD} - \frac{1}{2} k_n (v_{GS} - V_t)^2 R_D$$

$$A_V = \left. \frac{dv_{DS}}{dv_{GS}} \right|_Q = -k_n (v_{GS} - V_t) R_D$$

$$\text{Voltage Gain: } A_V = -k_n V_{OV} R_D$$

Maximum Input Signal Amplitude

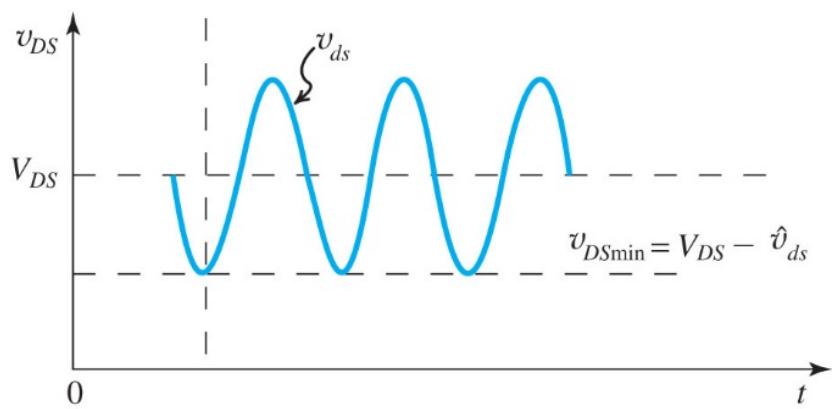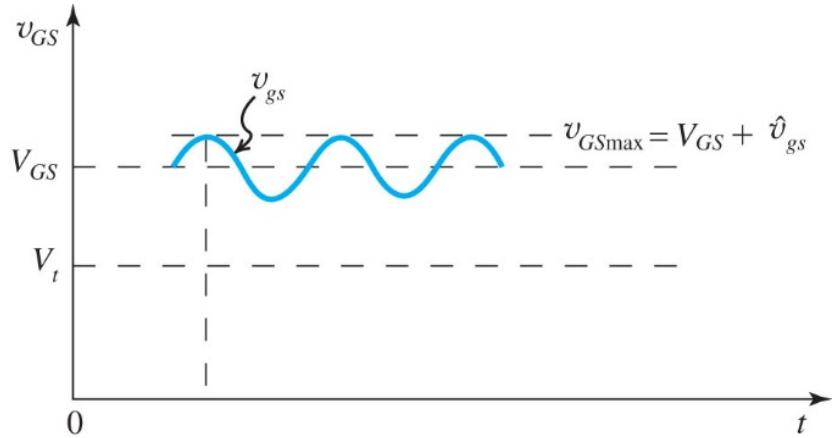

To keep the MOSFET in Saturation region
(linear part of I-V curve):

$$v_{DS} \geq v_{OV} = v_{GS} - V_t \text{ at all time.}$$

This condition is met if

$$v_{DS\min} = V_{DS} - v_{ds} \geq v_{GS\max} - V_t = V_{GS} + v_{gs} - V_t$$


$$\text{Since } v_{ds} = |A_V| v_{gs}$$

$$V_{DS} - |A_V| v_{gs} \geq V_{GS} + v_{gs} - V_t$$

$$v_{gs} \leq \frac{V_{DS} - V_{OV}}{1 + |A_V|}$$

The input amplitude must be smaller than this value to ensure MOSFET stays in Saturation

Graphical Analysis with Load Line

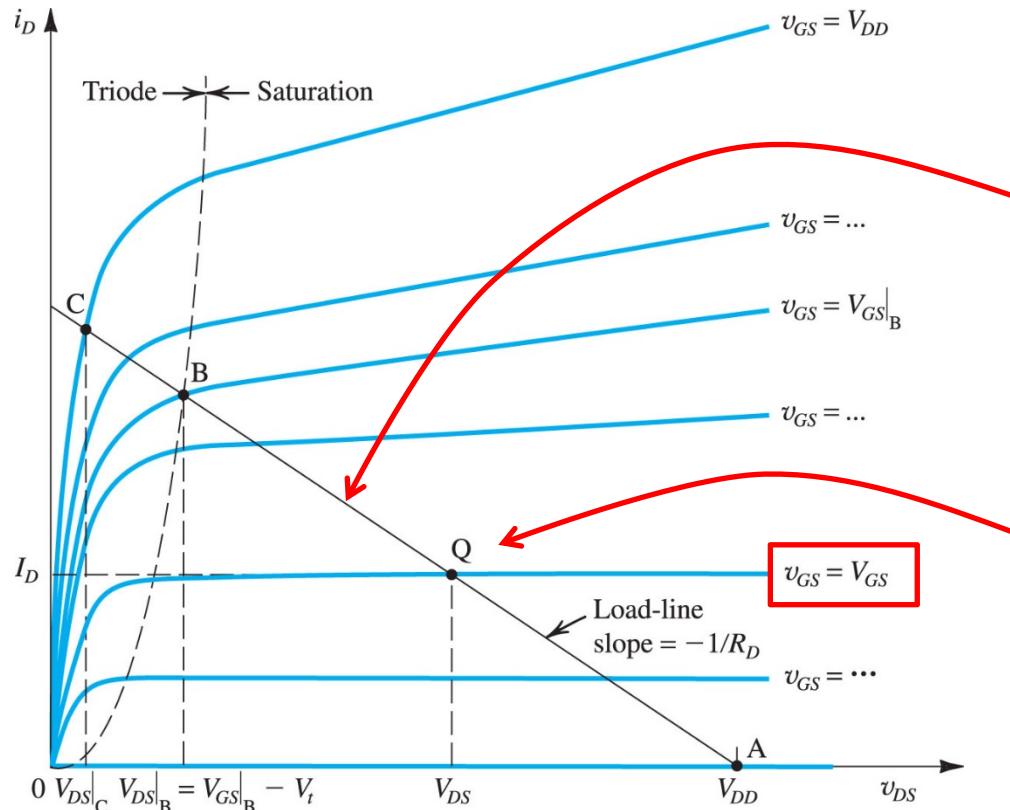


KVL:

$$V_{DD} = i_D R_D + v_{DS}$$

This is the equation for load line



The intersection of load line and MOSFET I-V (with a specific v_{GS}) defines the bias point (Q)

Consideration for Bias Point

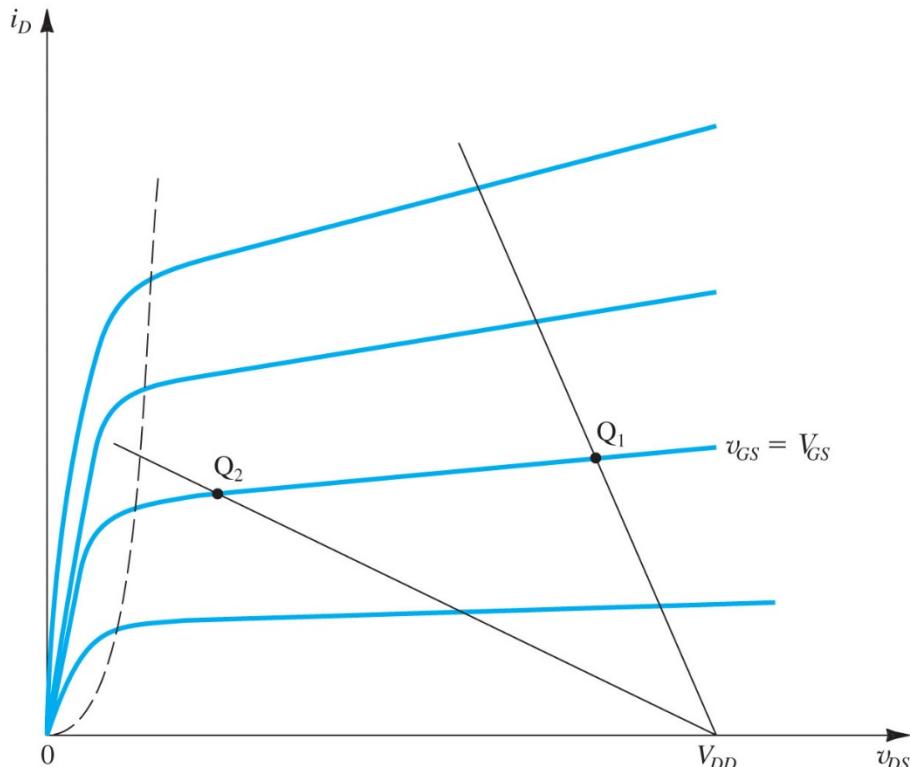


- **Q_1 : too close to V_{DD}**
 - Not enough room for positive signal swing
- **Q_2 : too close to Triode region**
 - Not enough room for negative voltage swing

MOS as Voltage-Controlled Current Source

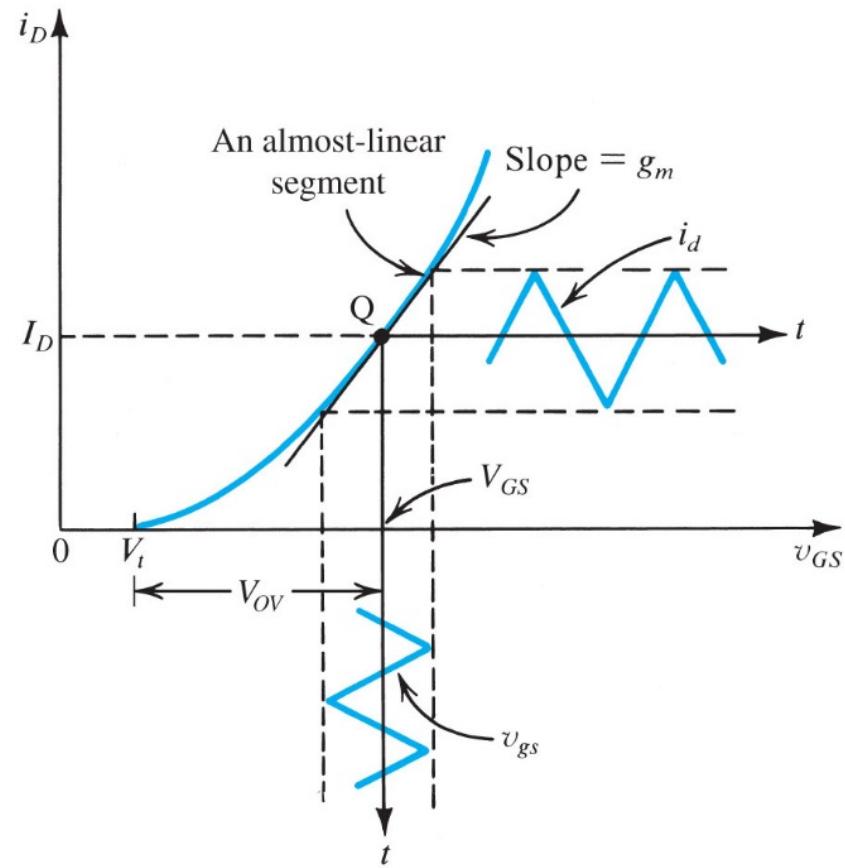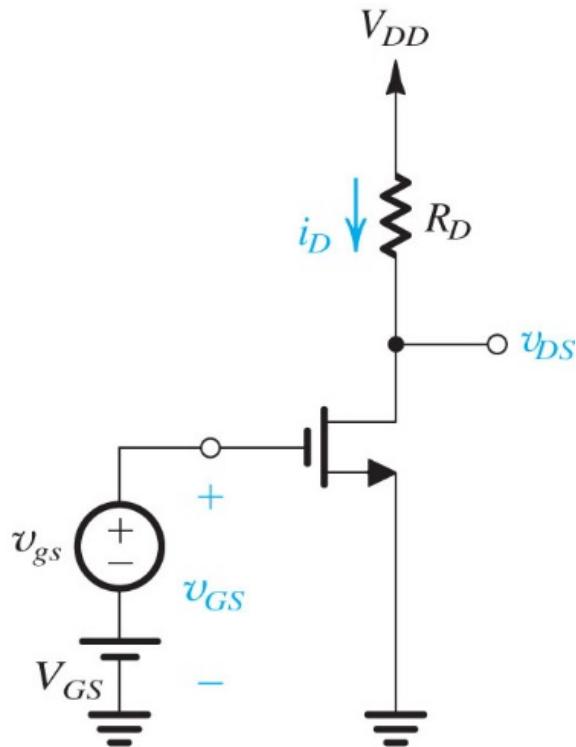

Simplified Small-Signal Model of MOSFET

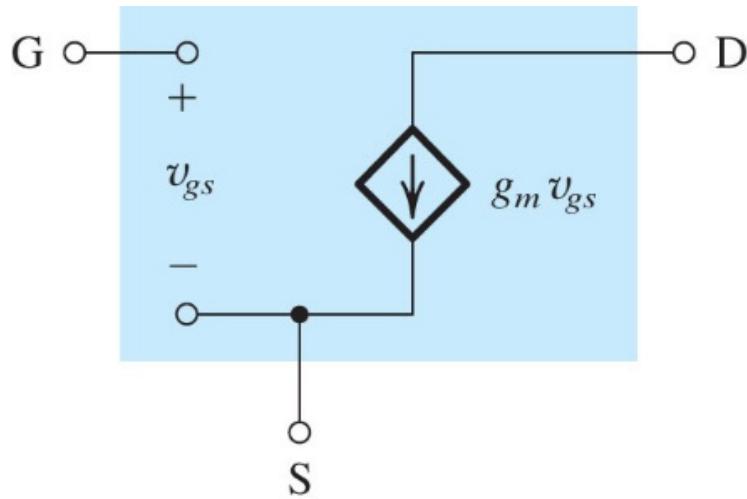

$$i_D(v_{GS}, v_{DS}) = \frac{1}{2} k_n (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

$$\approx \frac{1}{2} k_n (v_{GS} - V_t)^2$$

At DC bias point, Q

$$i_D = I_D + \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q v_{gs} = I_D + g_m v_{gs}$$

Transconductance:


$$g_m = k_n (v_{GS} - V_t) = k_n V_{ov}$$

Alternative g_m expression:

$$g_m = \frac{2I_D}{V_{ov}} = \sqrt{2k_n I_D}$$

Small-Signal Model for MOSFET

Hybrid- π Model

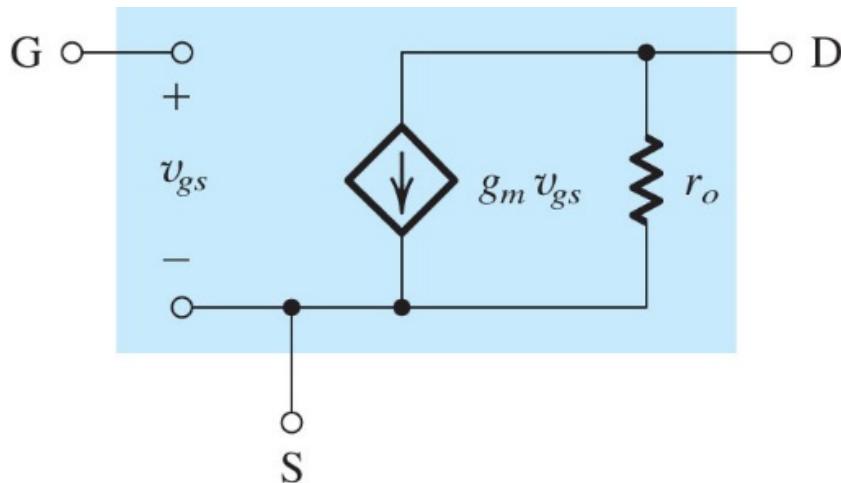

$$i_D(v_{GS}, v_{DS}) = \frac{1}{2} k_n (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

At DC bias point, Q



$$i_D = I_D + \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q v_{gs} + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q v_{ds}$$

$$i_D = I_D + g_m v_{gs} + \frac{1}{r_o} v_{ds}$$

Transconductance: $g_m = k_n V_{OV}$

Output Resistance: $r_o = \frac{1}{\lambda I_D}$

Applying Small-Signal Model

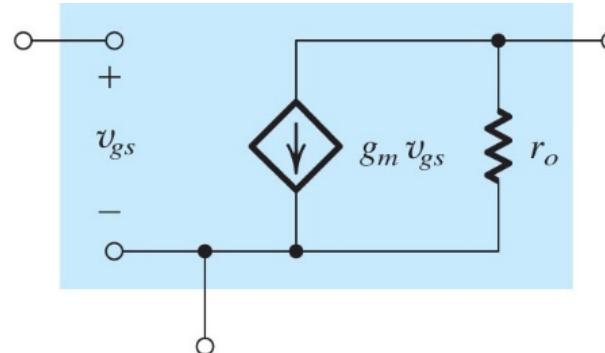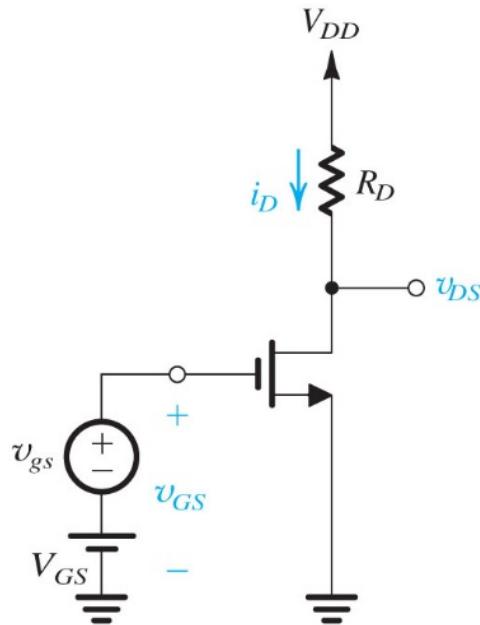

Previously, we used

$$v_{DS} = V_{DD} - \frac{1}{2} k_n (v_{GS} - V_t)^2 R_D$$

$$A_V = \left. \frac{dv_{DS}}{dv_{GS}} \right|_Q = -k_n (v_{GS} - V_t) R_D$$

Voltage Gain: $A_V = -k_n V_{OV} R_D$

With small-signal model, gain can be obtained much more easily:

$$v_{ds} = -g_m v_{gs} (r_o \parallel R_D)$$

$$A_V = \frac{v_{ds}}{v_{gs}} = -g_m (r_o \parallel R_D)$$


Usually $r_o \gg R_D$, $A_V \approx -g_m R_D$

Systematic Procedure for Transistor Amplifier Analysis

- 1. Perform DC analysis (ignore small signal source)**
- 2. Calculate small-signal parameters (g_m , r_o , etc)**
- 3. Generate AC small-signal equivalent circuit**
 - Replace DC voltage source by short circuit
 - Replace DC current source by open circuit
 - Replace transistor by hybrid- π model
- 4. Perform circuit analysis to determine voltage gain or other amplifier performance parameters**

MOSFET Amplifier Example:

(1) Solve DC Bias Point

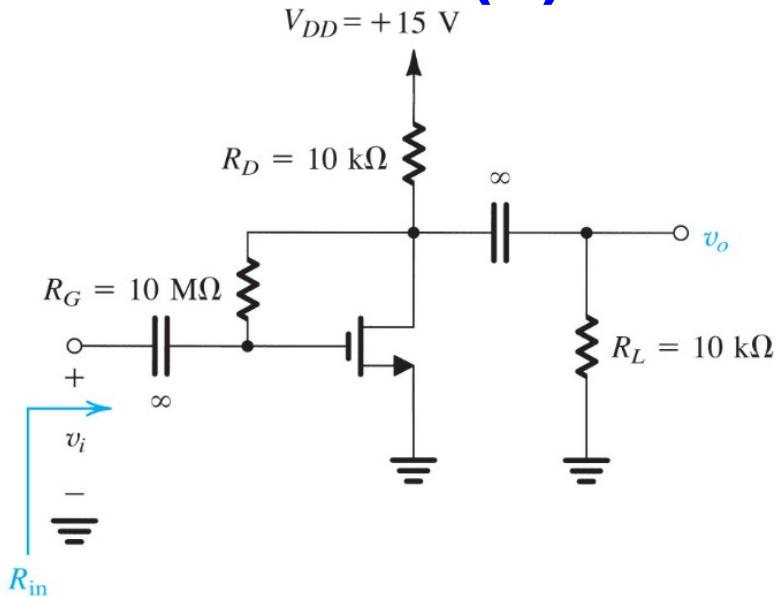

Find voltage gain for the amplifier. The MOSFET has $V_t = 1.5\text{V}$, $k_n = 0.25 \text{ mA/V}^2$ and $\lambda = (50\text{V})^{-1}$

Coupling capacitor is open circuit in DC, and short circuit for AC signal.

To solve DC bias point, replace coupling capacitor with V open circuit:


$$V_{GS} = V_{DS} \text{ from bias connection } R_G$$

$$V_{DD} = I_D R_D + V_{DS} = \frac{k_n}{2} (V_{GS} - V_t)^2 R_D + V_{DS}$$

$$15 = 1.25(V_{DS} - 1.5)^2 + V_{DS}$$




Solve quadratic equation: $V_{DS} = 4.4\text{V}$

$$I_D = 1.06 \text{ mA}$$

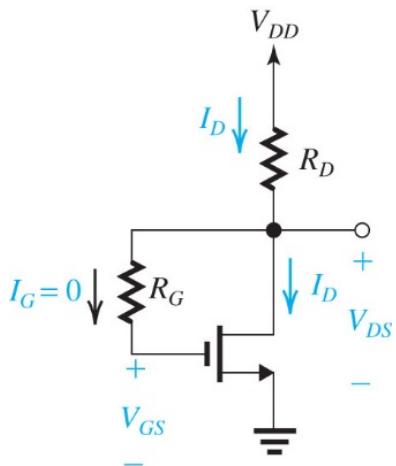

MOSFET Amplifier Example:

(2) Solve AC Small Signal Circuit

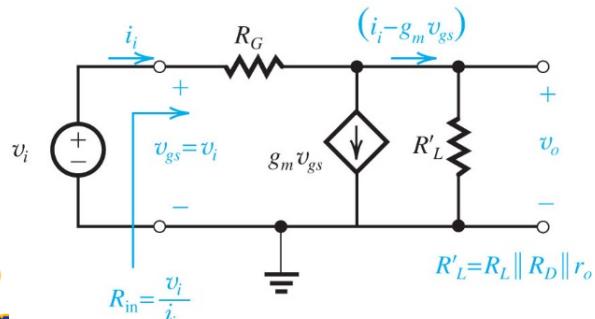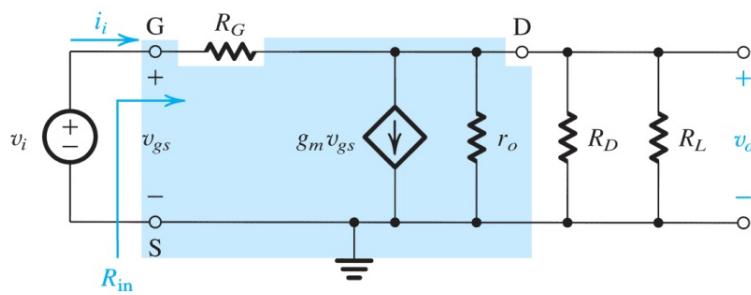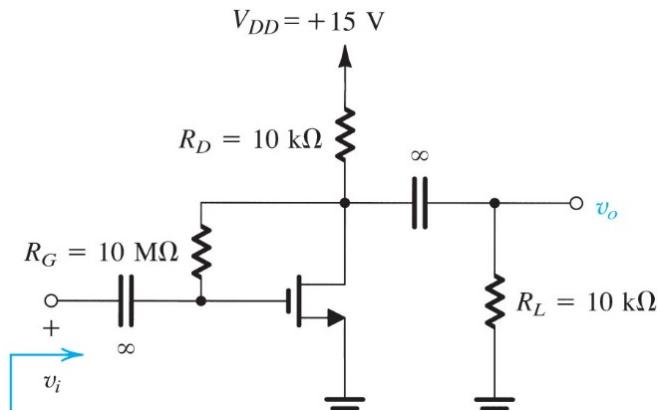

Now replace coupling capacitor with short circuit, and replace MOSFET with hybrid-pi model with $g_m = k_n V_{OV} = 0.25 \cdot (4.4 - 1.5) = 0.725 \text{ mA/V}$

$$r_0 = \frac{V_A}{I_D} = 47 \text{ k}\Omega$$

Next, simplify resistance at output to

$$R' = r_o \parallel R_D \parallel R_L = 4.5 \text{ k}\Omega$$

Do circuit analysis:




$$\begin{cases} v_o = (i_i - g_m v_{gs}) R' \\ i_i = \frac{v_i - v_o}{R_G} \end{cases}$$

$$A_v = -g_m R' \frac{1 - 1/g_m R_G}{1 + R'/R_G}$$

For large R_G , $A_v \approx -g_m R' = -0.725 * 4.5 = -3.3 \text{ V/V}$

MOSFET Amplifier Example:

(3) Additional Parameters of Interest

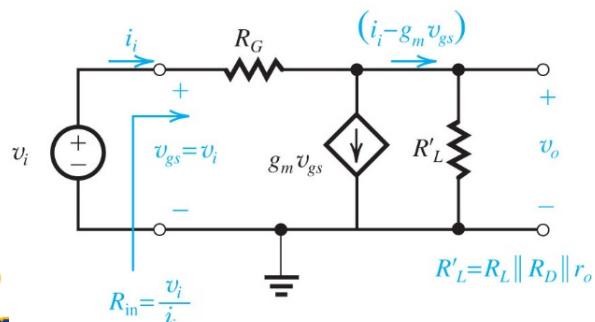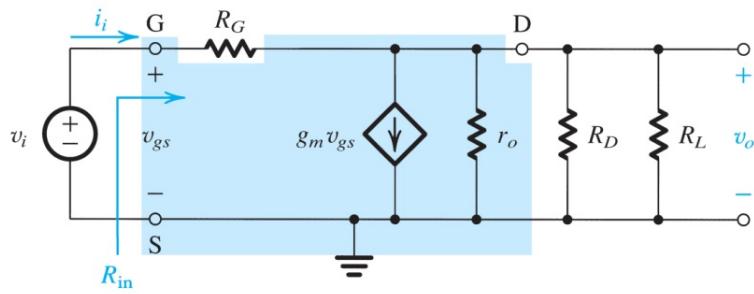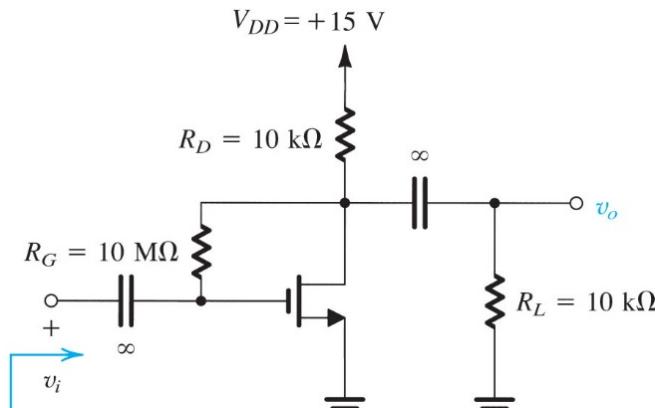

$$R_{in} = \frac{v_i}{i_i} = \frac{v_i}{\frac{v_i - v_o}{R_G}} = \frac{v_i}{\frac{v_i - A_v v_i}{R_G}} = \frac{R_G}{1 - A_v}$$

$$R_{in} = \frac{10 \text{ M}\Omega}{1 + 3.3} = 2.3 \text{ M}\Omega$$

Maximum signal that can be applied while keeping MOS in Saturation:

$$v_{DS\min} \geq v_{GS\max} - V$$

$$V_{DS} - |A_v| v_i \geq V_{GS} + v_i - V_t$$


$$v_i \leq \frac{V_{DS} - V_{GS} + V_t}{1 + |A_v|} = \frac{V_t}{1 + |A_v|}$$

$\therefore V_{DS} = V_{GS}$ here.

$$v_i \leq 0.35 \text{ V}$$

Small-Signal Model for PMOS

Hybrid- π Model

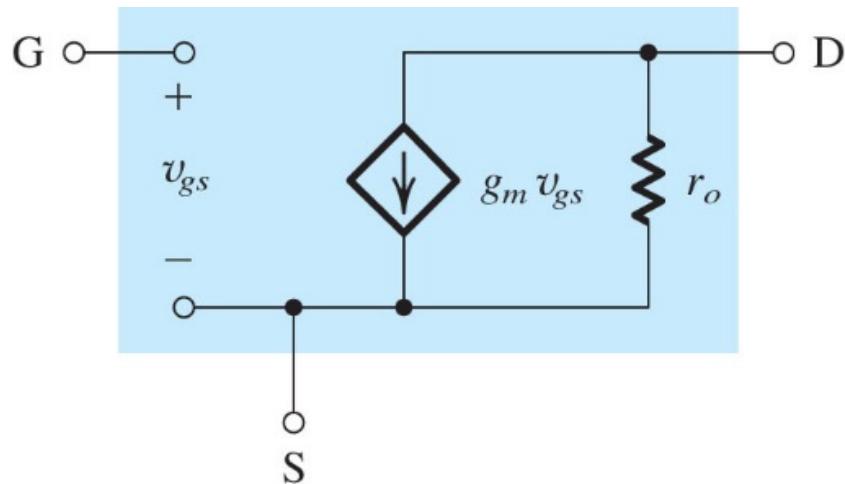

The equivalent circuit is valid for both NMOS and PMOS.

In PMOS, use absolute sign for all parameters:

$|V_{GS}|$, $|V_t|$, $|V_{OV}|$, $|V_A|$,
and replace k_n with k_p