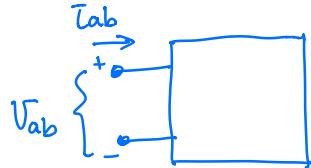



EE105 Midterm-2 : 4/9 (Next Tuesday) In class
 Same format as Midterm-1
 Sample midterms posted
 practice, Solution posted Wed.
 4/4 class . Q&A
 Topics in midterm, up to today's lectures
 Emphasis on materials after Midterm 1

Single Stage Amplifier
 ↓
 Transistor


From 1bA/B: Circuit model of "one port" circuit



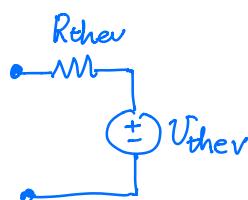
Thevenin Equivalent circuit (small signal)



Norton Equivalent circuit

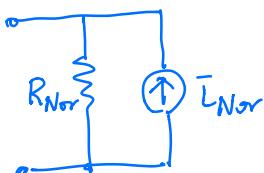


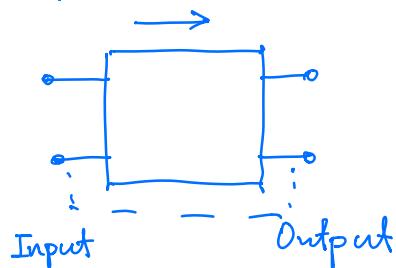
Two-Port Equivalent Circuit (Small Signal)





For amplifiers:


- Linear
- Unilateral: output dep. on input. but
input is not affect by output.
General true.

Input	Type	Output	Transfer fx
Voltage	Voltage Amp	Voltage	$\frac{V_o}{V_i}$
Current	Current Amp	Current	$\frac{I_o}{I_i}$
Voltage	Transconductance Amp.	Current	$\frac{I_o}{V_i} [S]$
Current	Transresistance Amp (Transimpedance Amp)	Voltage	$\frac{V_o}{I_i} [\Omega]$

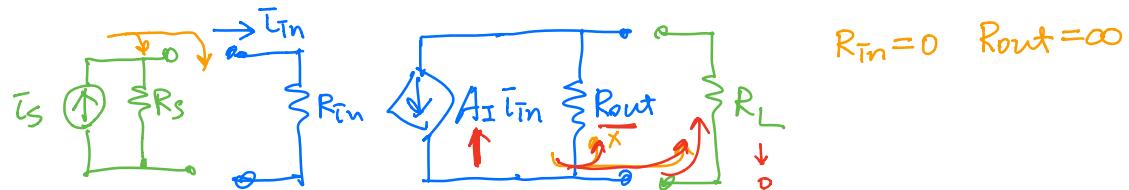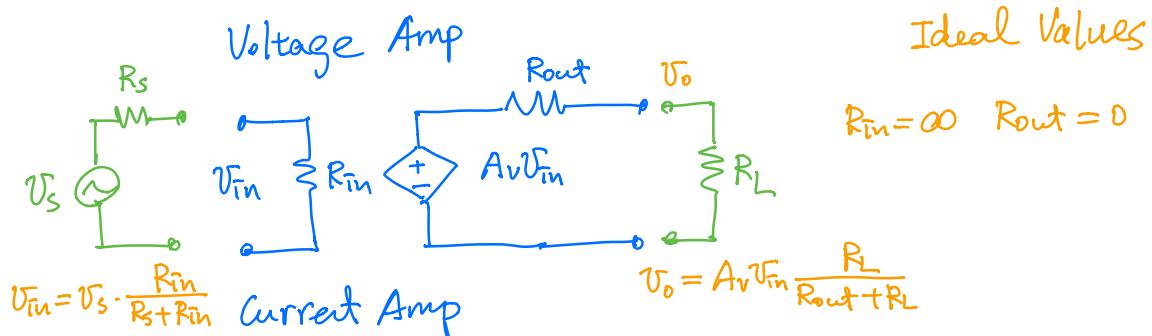


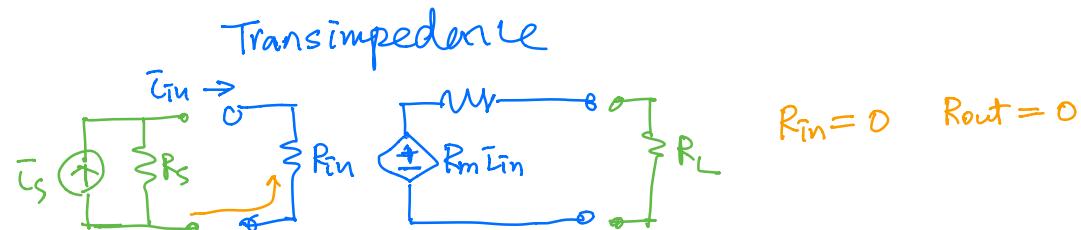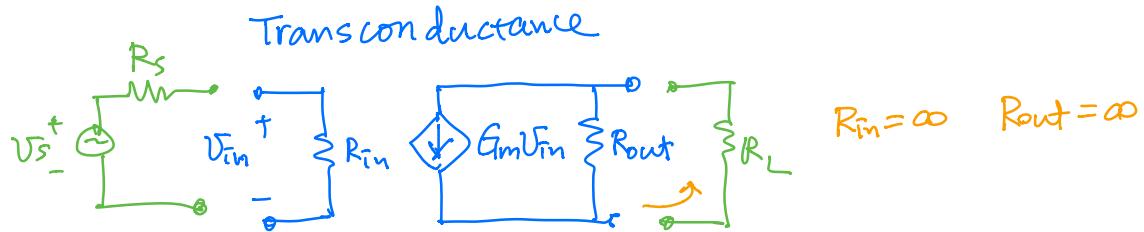

How do we calculate R_{in} ?

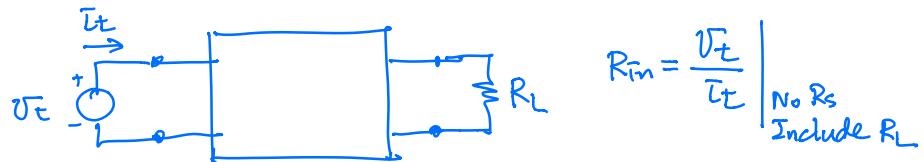

R_{out} ?

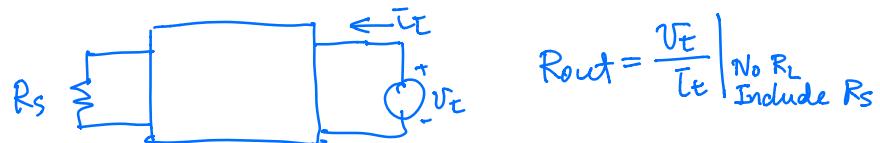


Single Transistor Circuit. 3 terminals (S,D,G)
2-port circuit 4 "


One terminal is used in both input and output

C common


Common Source Amp

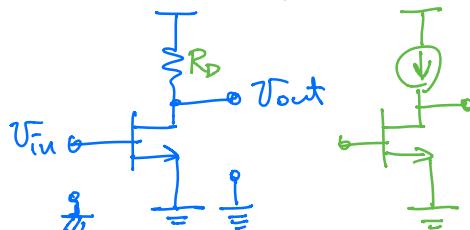



PMOS

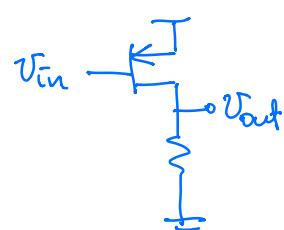


Common Gate

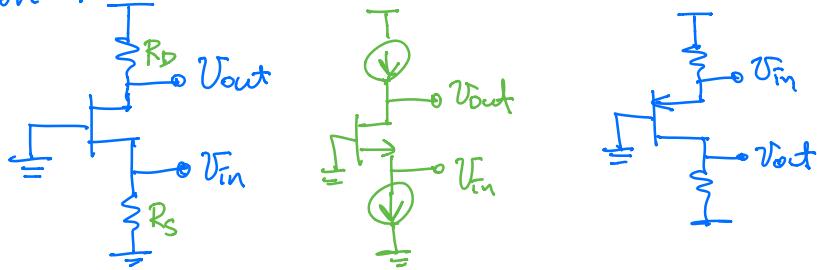

Common Drain

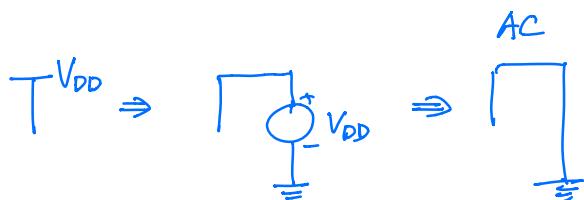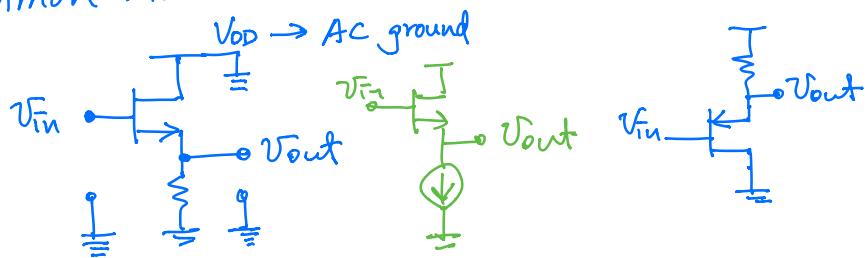


Common Source

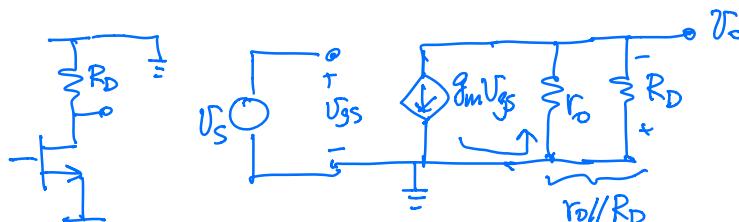


$$V_o = -g_m V_{gs} (r_o // R_D) = -g_m V_s (r_o // R_D)$$

$$A_v = \frac{V_o}{V_s} = -g_m (r_o // R_D)$$

$$R_{in} = \infty$$

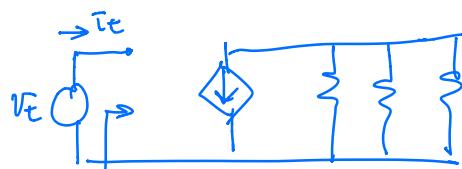

$$R_{out} = r_o // R_D$$

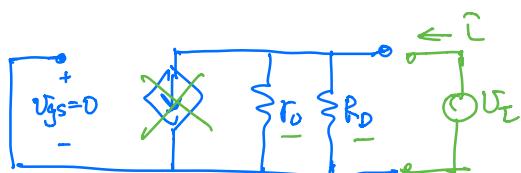

Typical values.


$$r_o \sim 200k\Omega, R_D = \text{a few } k\Omega$$

$$\Rightarrow r_o // R_D \approx R_D$$

Replace R_D by \downarrow $R_D \rightarrow \infty$

$$R_{out} = r_o // \infty = r_o$$

Common Gate

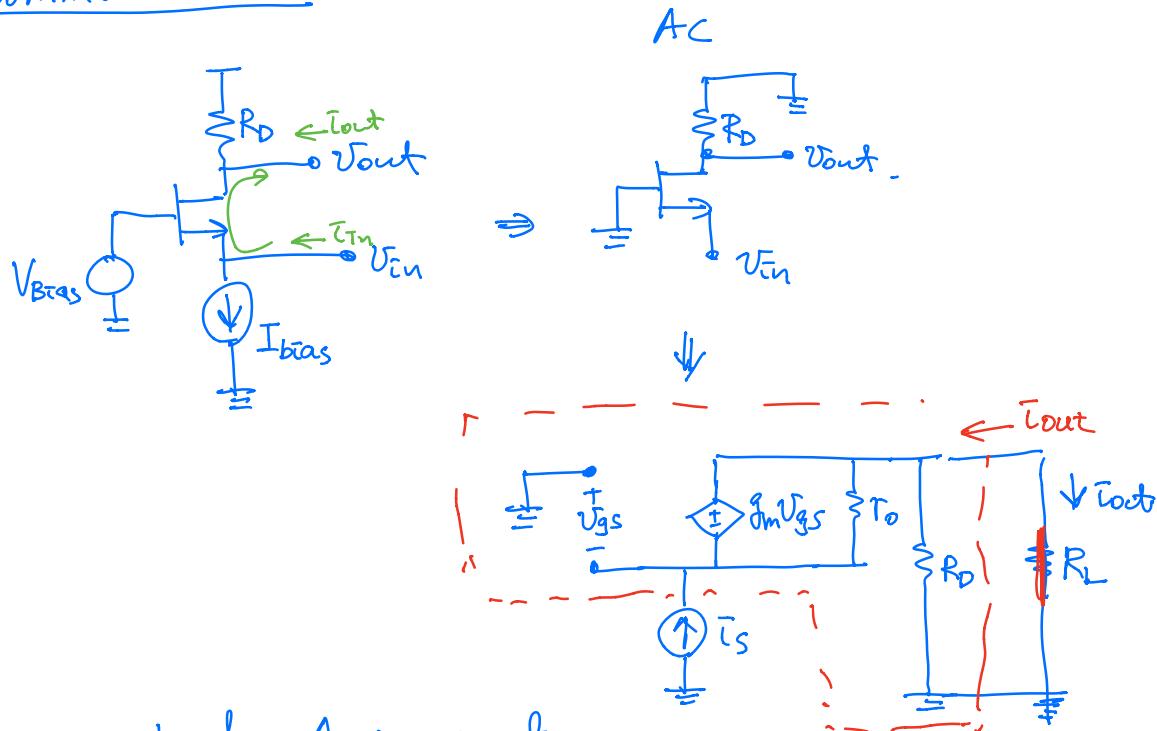


To evaluate $A_I = \text{current gain}$


Make $R_L = 0$

$$i_{out} = -i_s$$


$$A_I = \frac{i_{out}}{i_s} = -1$$

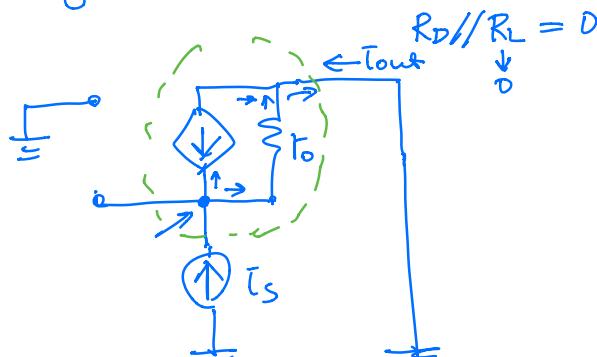

R_{in} :

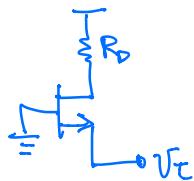

\Rightarrow

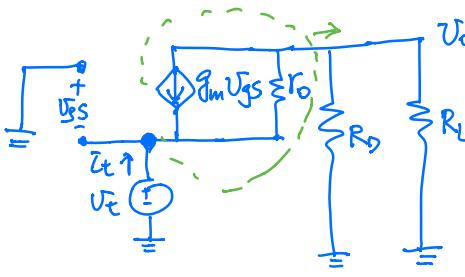

$$R' = R_D \parallel R_L$$

KCL at Source

$$\begin{aligned} \bar{I}_t + g_m V_{gs} &= \frac{V_T - V_o}{r_o} \\ \left\{ \begin{array}{l} V_{gs} = 0 - V_T = -V_T \\ V_o = \bar{I}_t \cdot R' \end{array} \right. \end{aligned}$$

$$\bar{I}_t - g_m V_T = \frac{V_T}{r_o} - \bar{I}_t R' \frac{1}{r_o}$$

$$\bar{I}_t \left(1 + \frac{R'}{r_o} \right) = \left(g_m + \frac{1}{r_o} \right) V_T$$

$$R_{in} = \frac{V_T}{\bar{I}_t} = \frac{1 + \frac{R'}{r_o}}{g_m + \frac{1}{r_o}} \approx \frac{1}{g_m}$$

Typical values

$$g_m \sim 0.5 \text{ mS}$$

$$r_o \sim 200 \text{ k}\Omega \quad \frac{1}{r_o} = \frac{1}{2 \times 10^5} = 5 \mu\Omega$$



$$R' = R_D \parallel R_L$$

$\hookrightarrow \sim \text{k}\Omega$

$$R' \ll r_o$$

↑ Small input resistance

R_{out} :

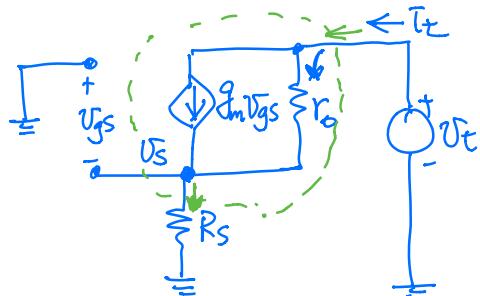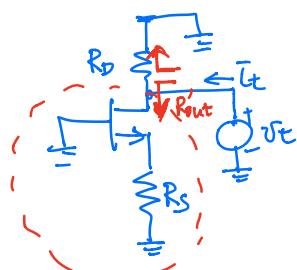

KCL at Drain

$$\bar{I}_t = g_m V_{gs} + \frac{V_T - V_S}{r_o}$$

$$\left\{ \begin{array}{l} V_{gs} = 0 - V_S = -V_S \\ V_S = \bar{I}_t \cdot R_S \end{array} \right.$$


$$\bar{I}_t = -g_m \bar{I}_t \cdot R_S + \frac{V_T - \bar{I}_t R_S}{r_o}$$

$$\bar{I}_t \left(1 + g_m R_S + \frac{R_S}{r_o} \right) = \frac{V_T}{r_o} \Rightarrow R_{out} = \frac{V_T}{\bar{I}_t} = r_o + \underline{g_m R_S r_o + R_S}$$

$$\left. \begin{array}{l} r_o \sim 200k\Omega \\ g_m \sim 0.5 \text{ mS} \\ R_s \sim k\Omega (\text{?}) \end{array} \right\} g_m r_o \sim 100 \Rightarrow 1$$

$$R'_{out} = r_o + g_m r_o \cdot R_s \Rightarrow \text{Very large out resistance}$$

2-Port for CG:

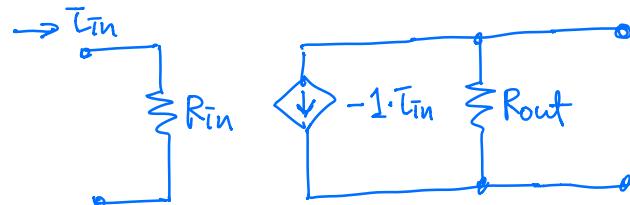


$$R_{in} = \frac{1}{g_m} \text{ small}$$

$$R'_{out} = r_o + g_m r_o \cdot R_s \text{ large}$$


$$R_{out} = R'_{out} // R_D = R_D // (r_o + g_m r_o R_s)$$

$$R_D \sim k\Omega \ll r_o$$

$$R_{out} \approx R_D$$

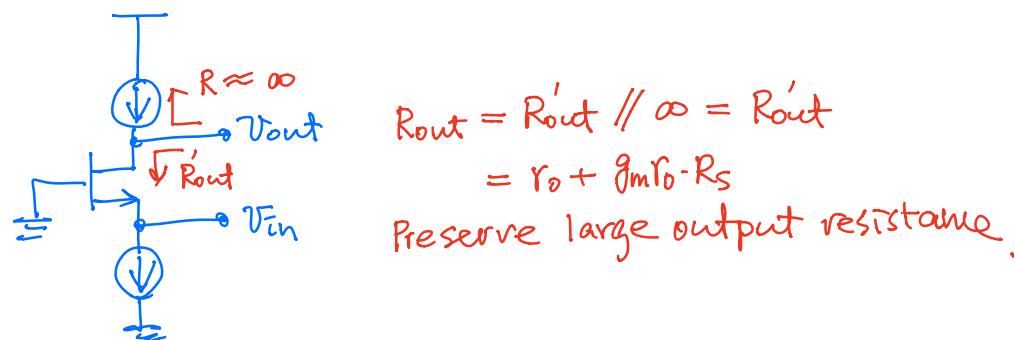

CG as a voltage amplifier

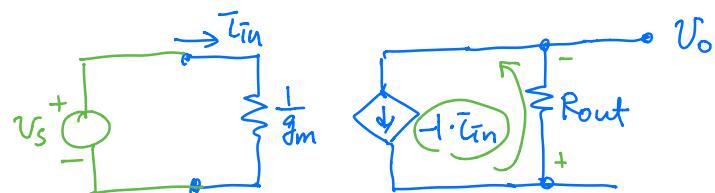

$$V_o = -(-1 \cdot I_{in}) \cdot R_{out} \Rightarrow V_o = I_{in} \cdot R_{out} = g_m V_s \cdot R_{out}$$

$$I_{in} = \frac{V_s}{(\frac{1}{g_m})} = g_m V_s$$

$$A_v = \frac{V_o}{V_s} = g_m R_{out}$$

$$R_{out} = r_o + g_m r_o \cdot R_S \gg r_o$$

\Rightarrow higher gain in CG

Recall for CS amplifier. $A_v = g_m (r_o \parallel R_D)$

$$= -g_m r_o$$

$\downarrow \infty$ for 