

# **EE105**

## **Microelectronic Devices and Circuits**

### **Current Sources**


**Prof. Ming C. Wu**

**wu@eecs.berkeley.edu**


**511 Sutardja Dai Hall (SDH)**

# Load Impedance


Common Source

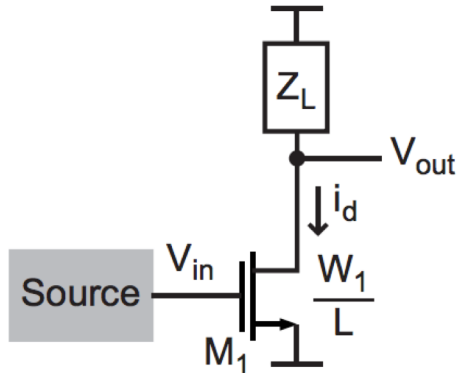


Common Gate

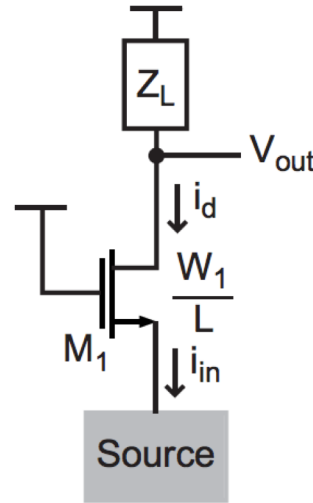

Source Follower

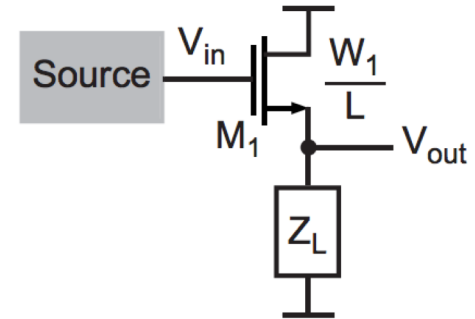


Common Source with Source Degeneration

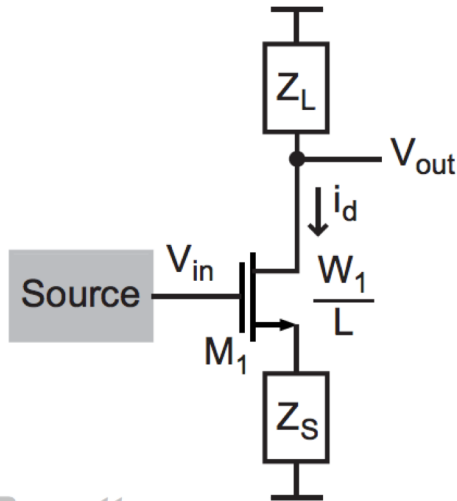

- To achieve high gain (or low attenuation in the case of a source follower), it is very desirable to achieve high load impedance,  $Z_L$ 
  - Unfortunately, using a simple resistor of high value has issues
    - What are these issues?

# Issue: Headroom Limitations

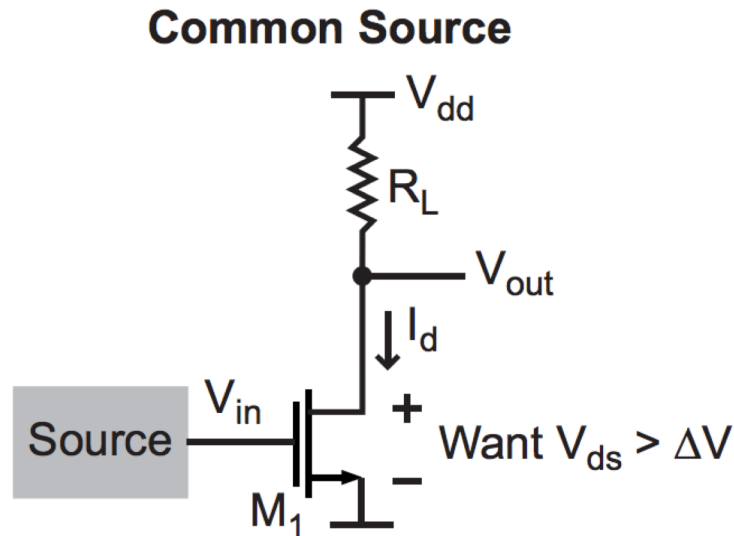

- The bias current of the device is a direct function of  $R_L$

$$I_d = \frac{V_{dd} - V_{ds}}{R_L}$$


- $V_{dd}$  is  $< 3.6V$  for most modern CMOS processes
- $V_{ds}$  must be greater than  $\Delta V$  to maintain device saturation

Large  $R_L$  implies small  $I_d$   
(implies small  $g_m$ , poor frequency response, etc.)



# Achieving High Gain


## Common Source

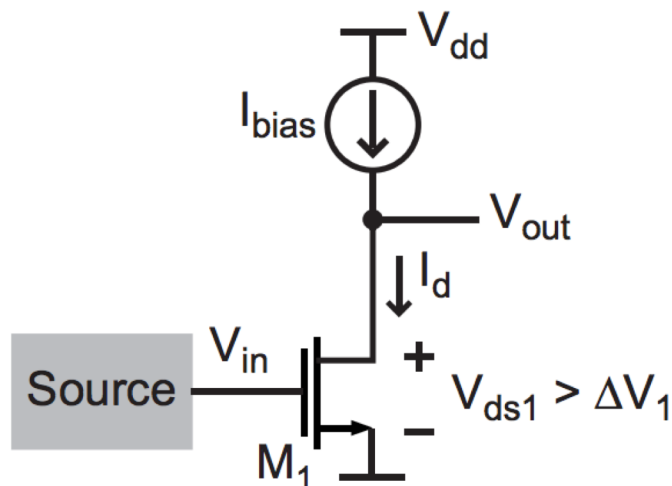

- Replacement of resistor load with a current source yields the highest possible DC gain out of the amplifier
  - Current source determines  $I_d$  of device
- We can make current sources out of transistors
  - Generally smaller area than polysilicon resistors


What is the small signal gain of the above circuit?

# Diode Connected Device

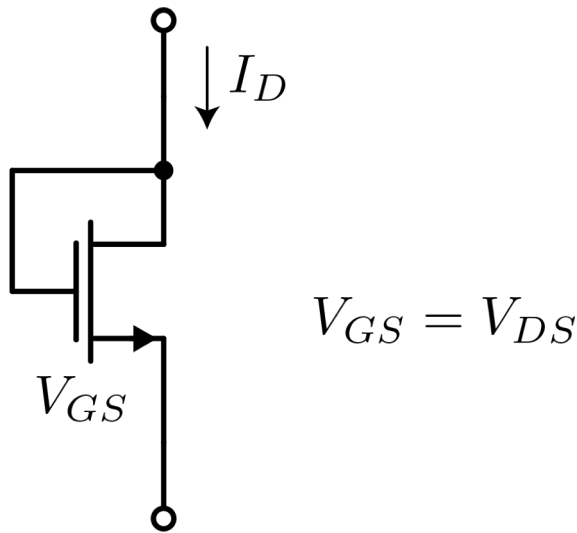


- How do we build current sources?
- Let's start with a “diode connected” device
- A MOS device with gate and drain shorted operates like a diode (but not exponential)

# Diode Connected -- SS Model

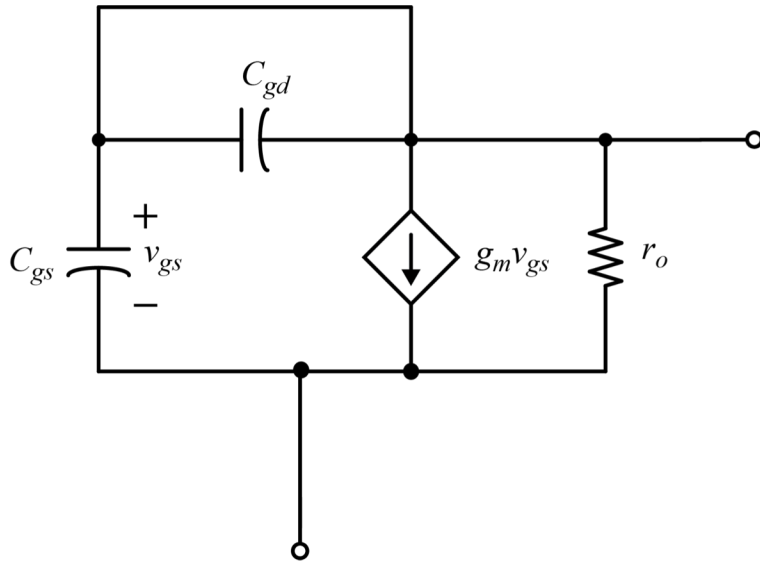


- We can derive the small-signal model by shorting out the hybrid-pi model
- Note that a  $G_m$  generator with its controlling terminals connected to the  $G_m$  is more simply a ...?

# The Integrated “Current Mirror”

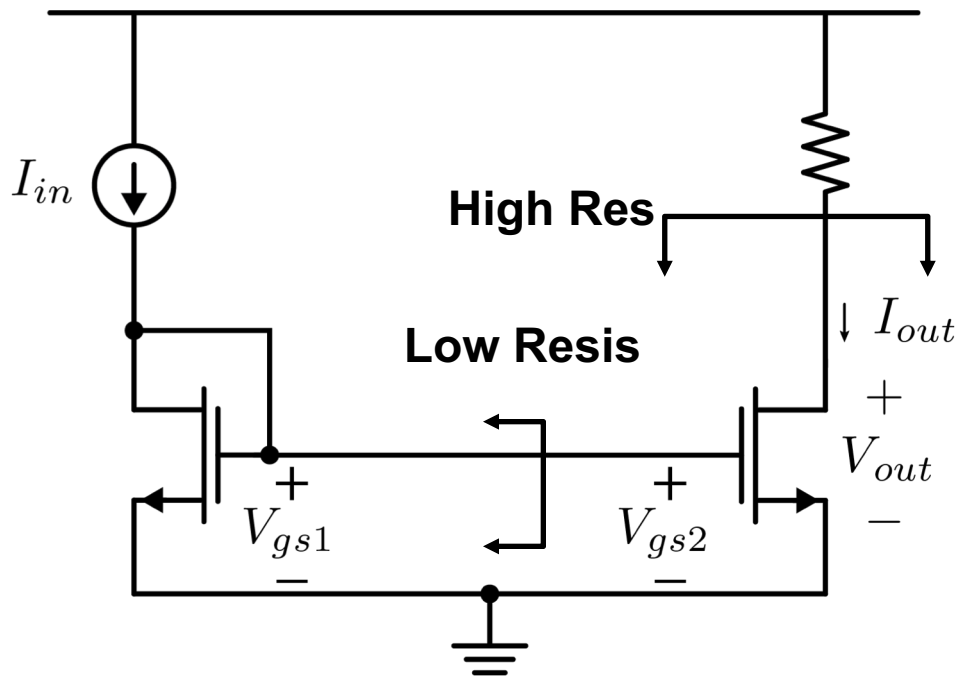

- $M_1$  and  $M_2$  have the same  $V_{GS}$
- If we neglect CLM ( $\lambda=0$ ), then the drain currents are equal
- Since  $\lambda$  is small, the currents will nearly mirror one another even if  $V_{out}$  is not equal to  $V_{GS1}$
- We say that the current  $I_{REF}$  is mirrored into  $i_{OUT}$
- Notice that the mirror works for small and large signals!

# Multiplication Ratio

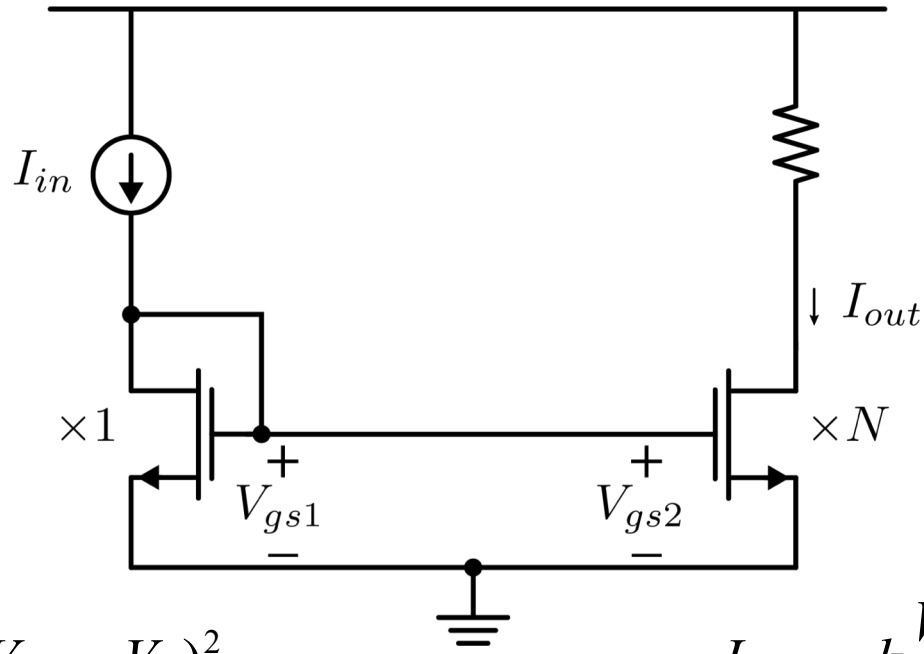

$$I_{IN} = k \frac{W_1}{L_1} (V_{GS1} - V_T)^2$$


$$I_{OUT} = k \frac{W_2}{L_2} (V_{GS2} - V_T)^2$$

$$V_{GS1} = V_{GS2}$$

$$I_{OUT} = k \frac{W_2}{L_2} (V_{GS2} - V_T)^2 = I_{IN} \frac{W_2 / L_2}{W_1 / L_1} = NI_{IN}$$




# Current Mirror as Current Source

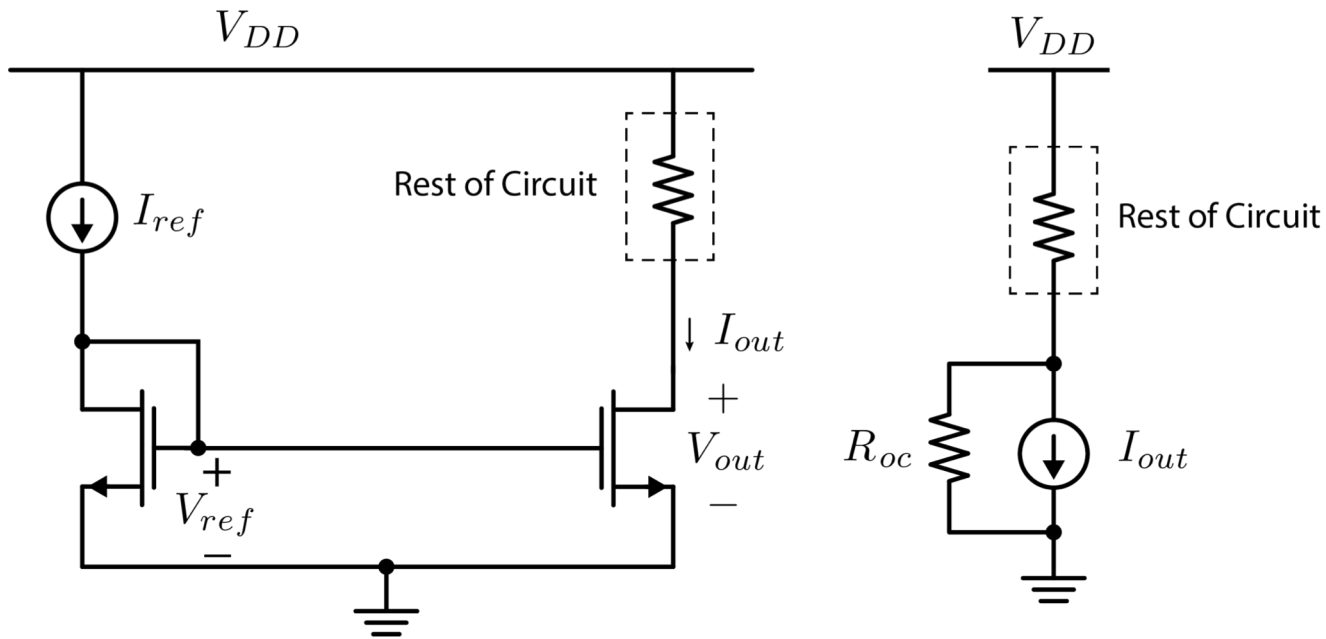

- The output current of  $M_2$  is only weakly dependent on  $v_{OUT}$  due to high output resistance of FET
- $M_2$  acts like a current source to the rest of the circuit
- For good current source behavior, what is the minimum  $v_{OUT}$ ?


# Small-Signal Resistance of $I$ -Source

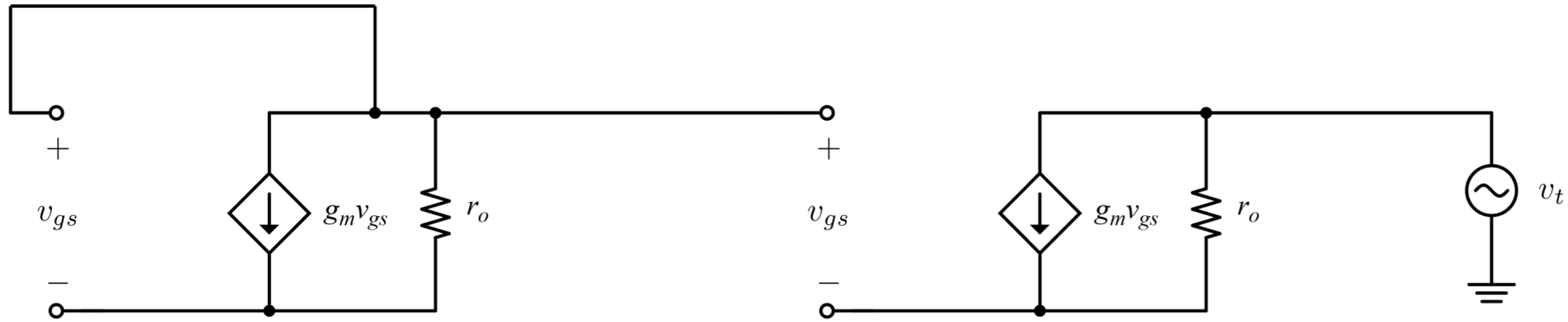

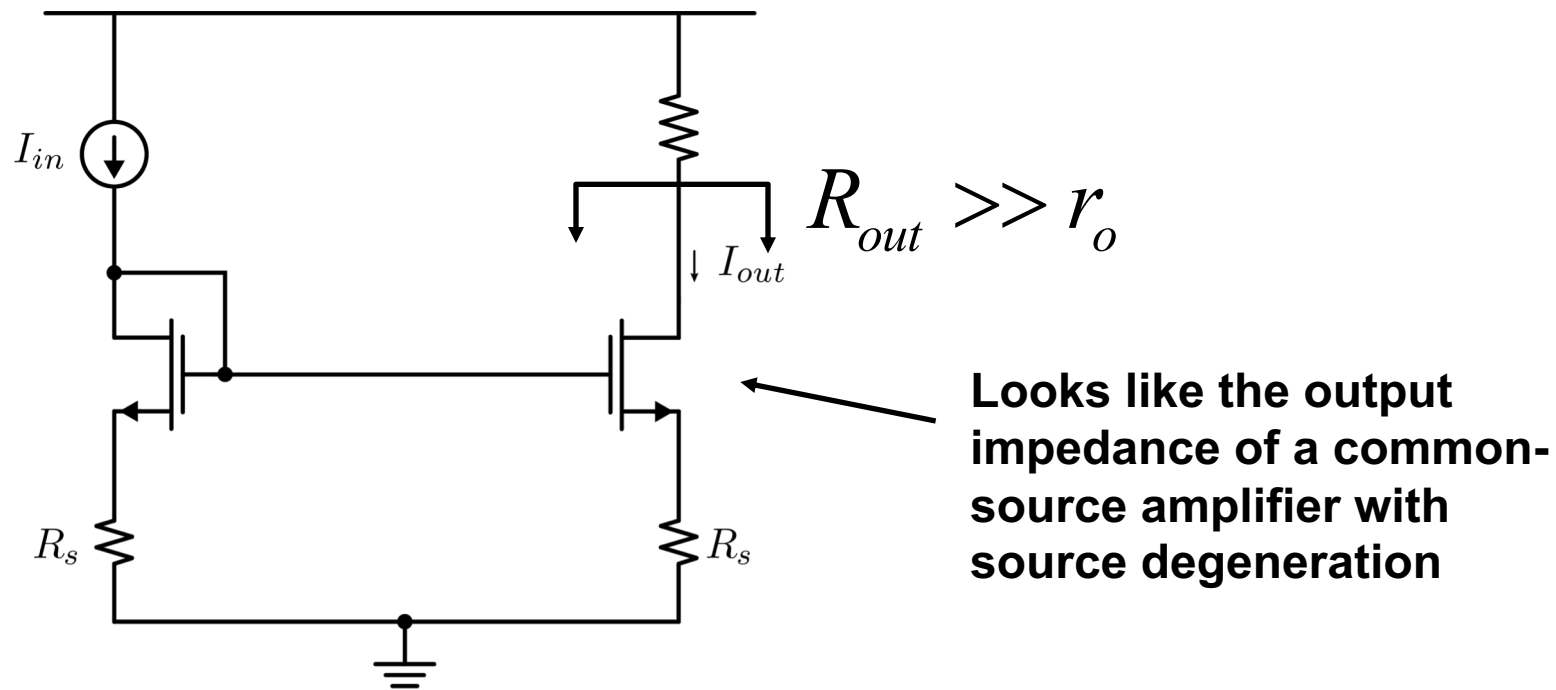
# Improved Current Sources

**Goal:** increase  $R_{o(ut)}$

**Approach:** look at *amplifier* output resistance results ... to see topologies that boost resistance



# Effect of Source Degeneration

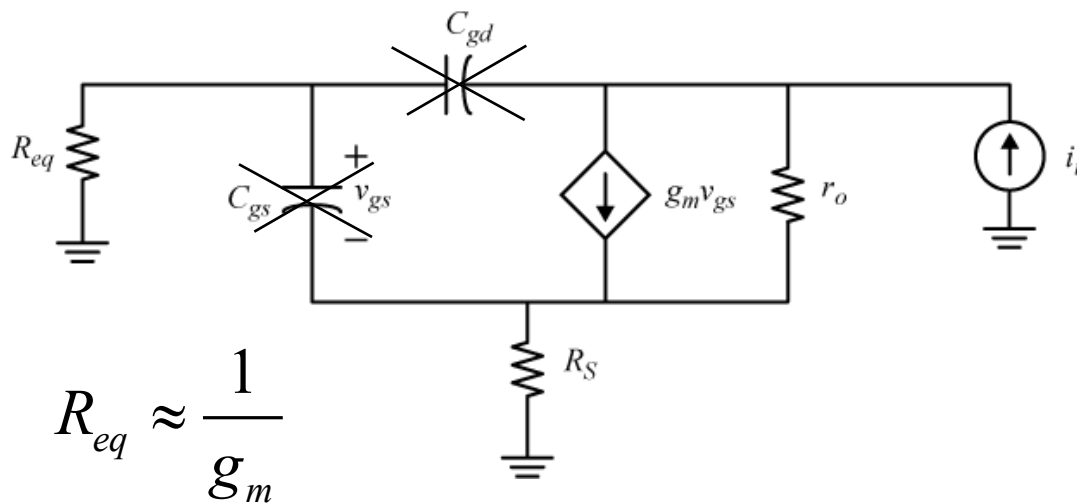

$$v_t = (i_t - g_m v_{gs}) r_o + v_{R_S}$$

$$v_{gs} \approx -v_{R_S}$$

$$v_{R_S} = i_t R_S$$


$$v_t = (i_t + g_m R_S i_t) r_o + i_t R_S$$

$$R_o = \frac{v_t}{i_t} \approx (1 + g_m R_S) r_o$$

- Equivalent resistance loading gate is dominated by the diode resistance ... assume this is a small impedance
- Output impedance is boosted by factor  $(1 + g_m R_S)$

# Improved Current Sources


How would you scale the output current?

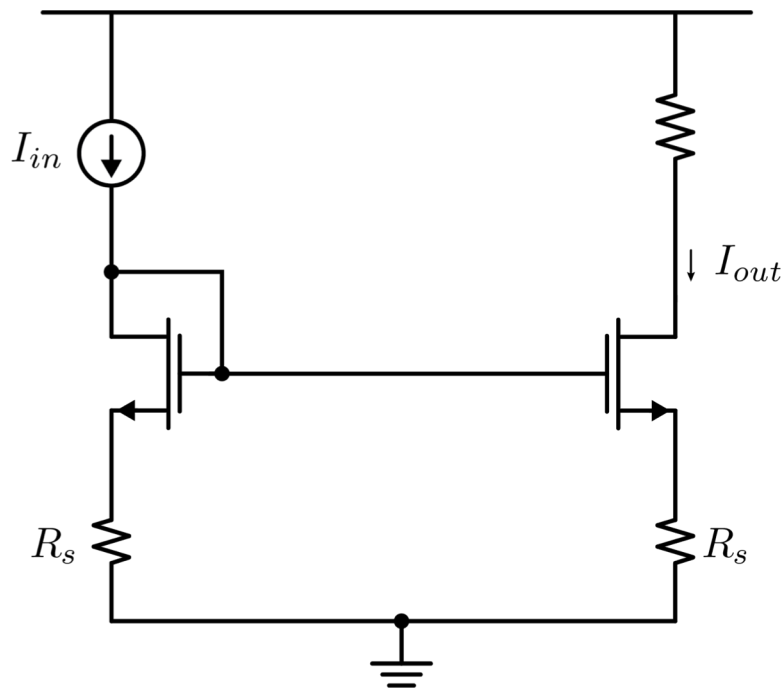

$$I_{IN} = k \frac{W_1}{L_1} (V_G - V_S - V_T)^2$$

$$V_S = I_{IN} R_S$$

# Cascode (or Stacked) Current Source

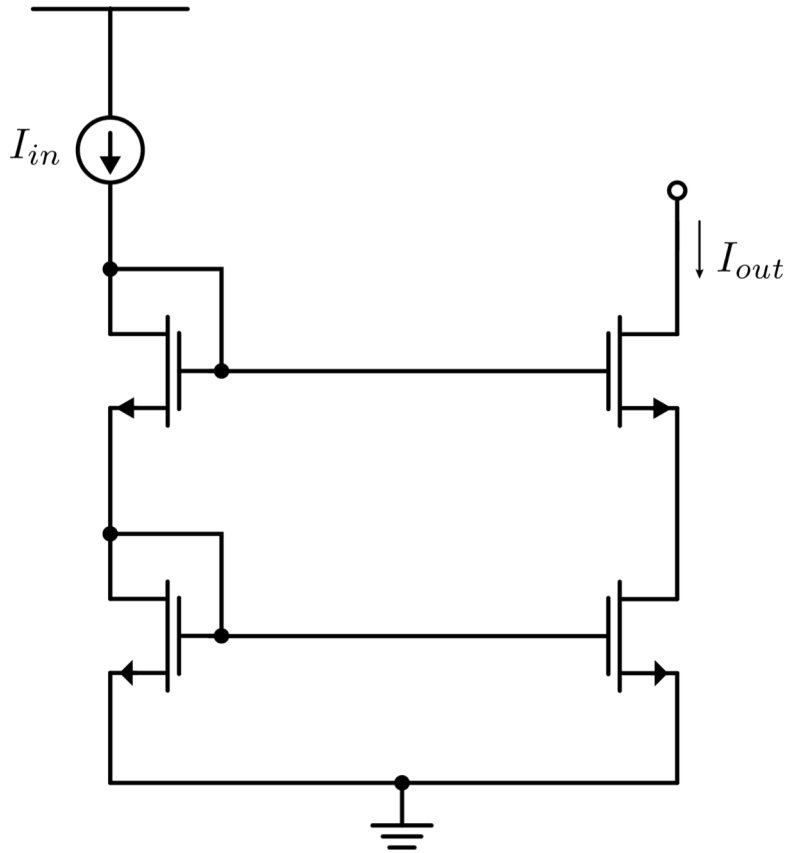

**Insight:**  $V_{GS2} = \text{constant}$  AND  
 $V_{DS2} = \text{constant}$

**Small-Signal Resistance  $R_o$ :**


$$R_o \approx (1 + g_m R_S) r_o$$

$$R_o \approx (1 + g_m r_o) r_o$$

$$R_o \approx g_m r_o^2 \gg r_o$$
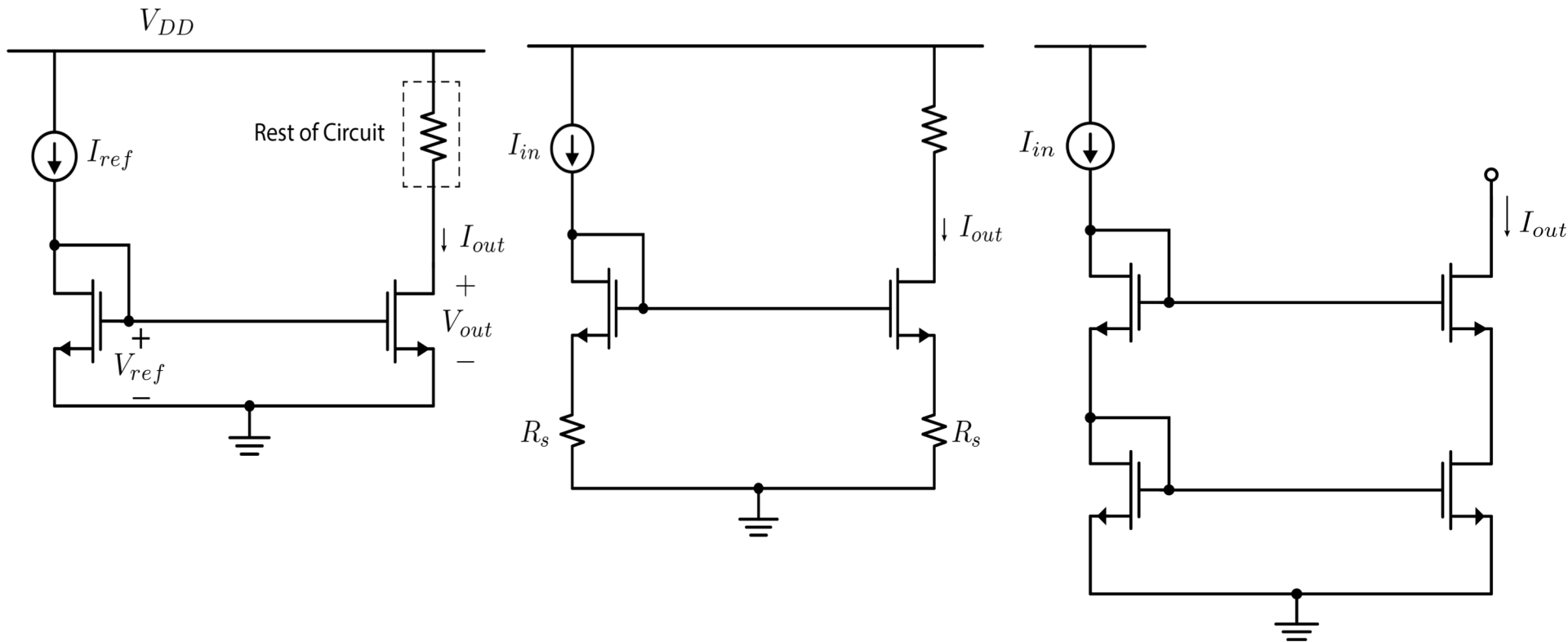
# Drawback of Cascode I-Source

What is the minimum output voltage to keep all transistors in saturation?




# Drawback of Cascode I-Source

Minimum output voltage to keep both transistors in saturation:


$$V_{OUT,MIN} = V_{DS4,MIN} + V_{DS2,MIN}$$

$$V_{DS2,MIN} > V_{GS2} - V_{T0} = V_{DSAT2}$$
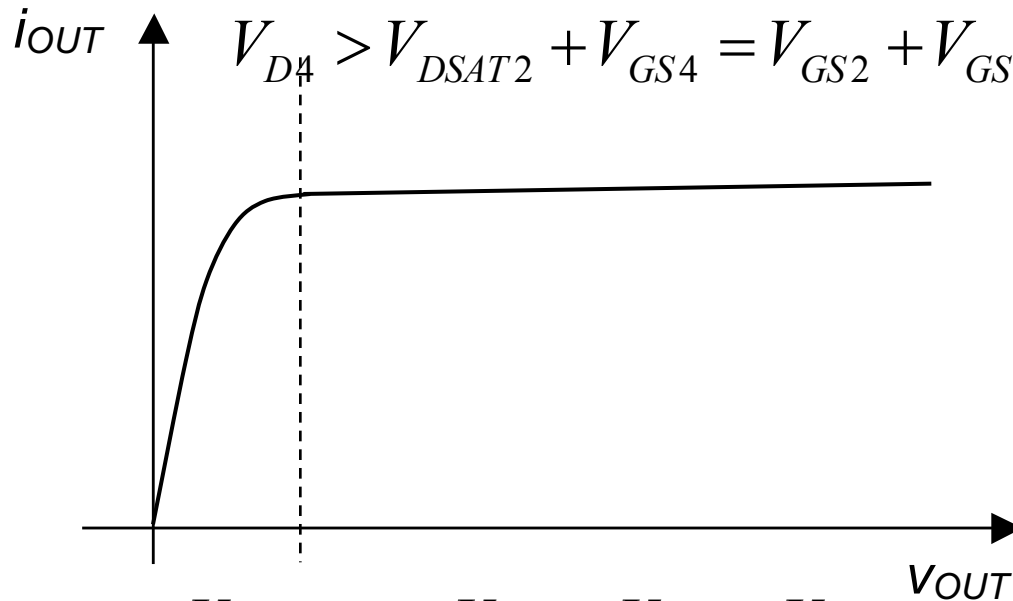
$$V_{D4} > V_{DSAT2} + V_{GS4} = V_{GS2} + V_{GS4} - V_{T0}$$


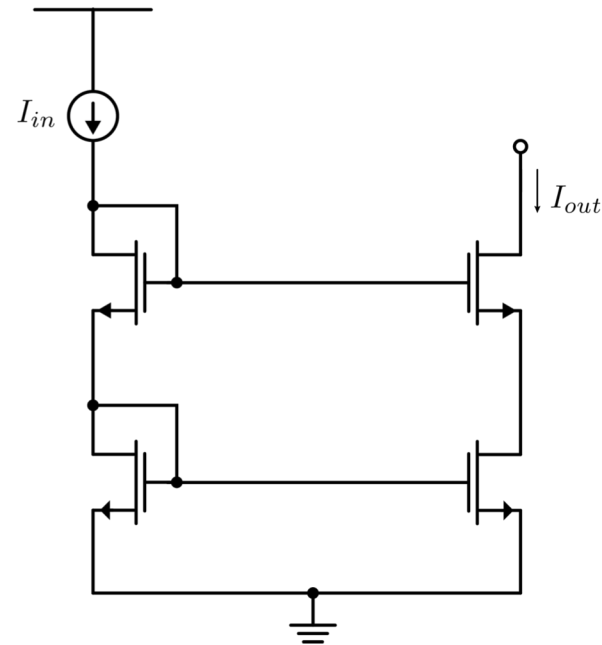
$$V_{OUT,MIN} = V_{GS2} + V_{GS4} - V_{T0}$$




In EE140 you will learn circuit tricks to overcome this problem!




# Current Sinks and Sources

**Sink:** output current goes to ground

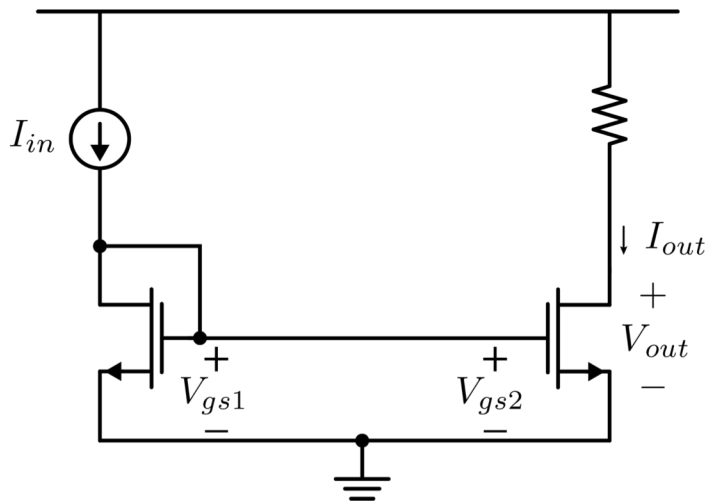


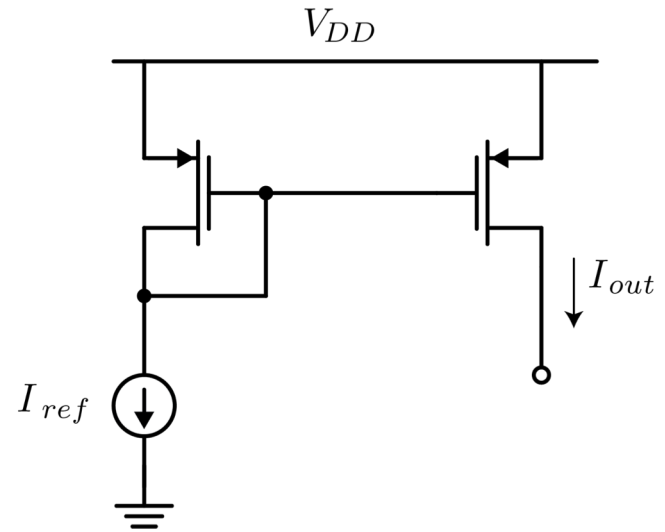**Source:** output current comes from voltage supply



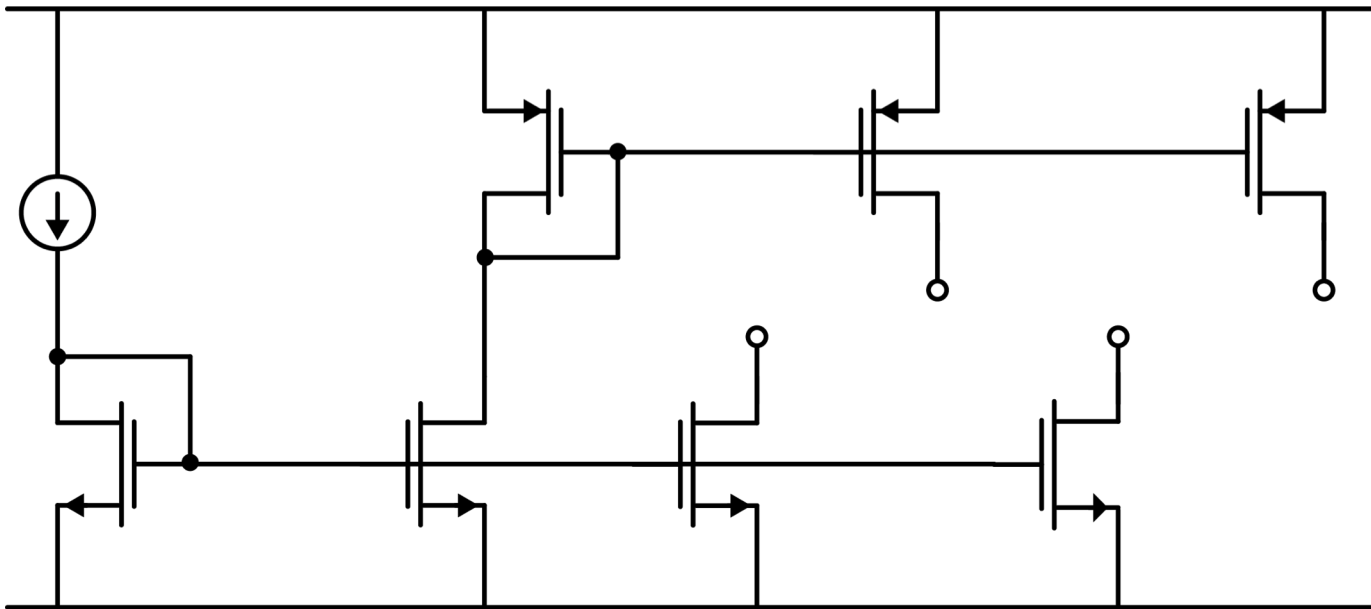
# Current Mirrors

**Idea:** we only need one reference current to set up all the current sources and sinks needed for a multistage amplifier.




# Example: Common-Drain Amplifier

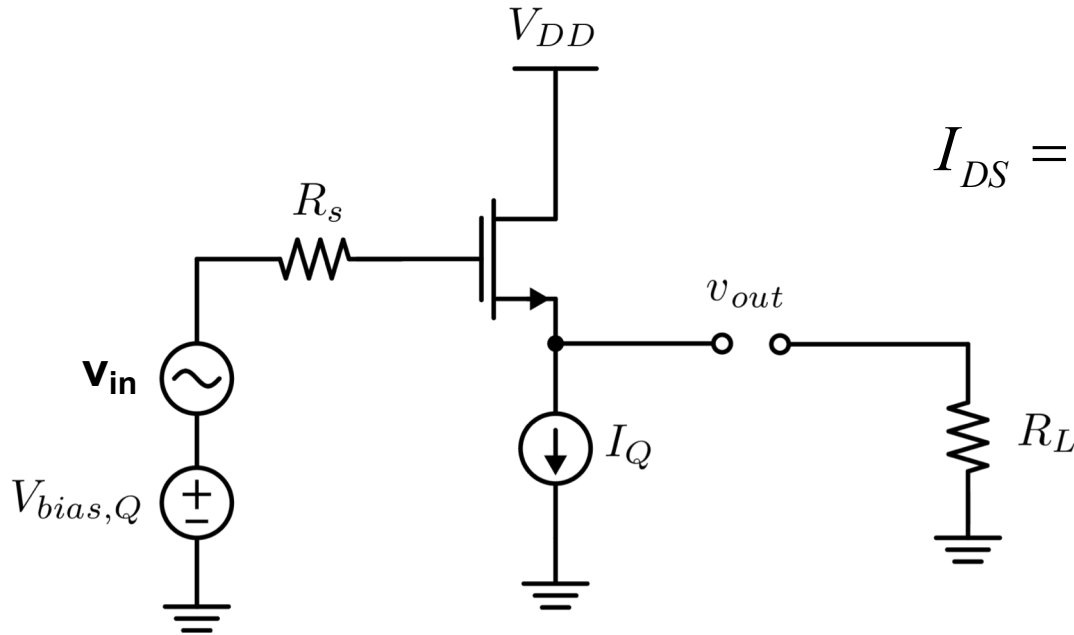


$$I_{DS} = \mu C_{ox} \frac{W}{L} \frac{1}{2} (V_{GS} - V_T)^2$$
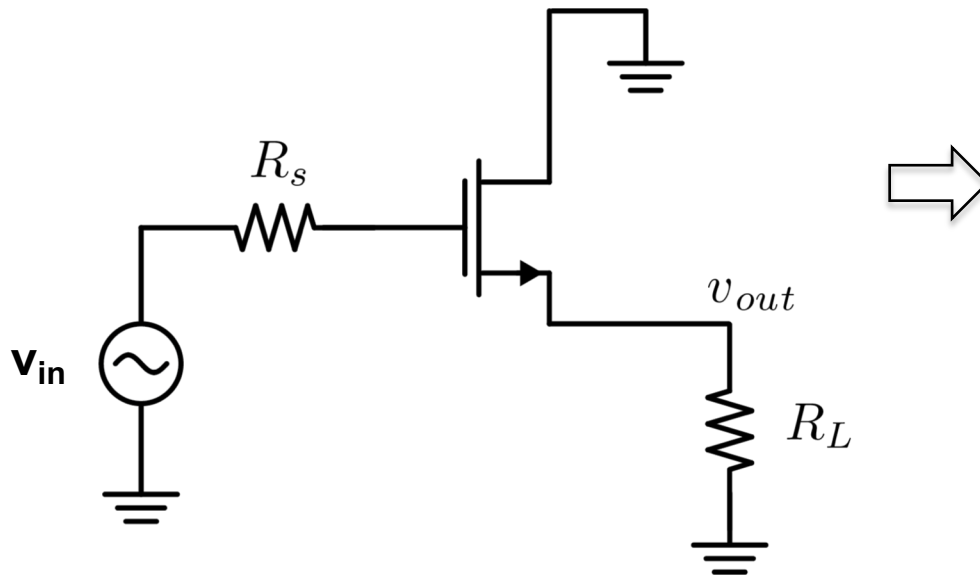
# Common Drain AC Schematic

How does a REAL current source fit in to the small-signal model?




# CD Voltage Gain With Real I-Source

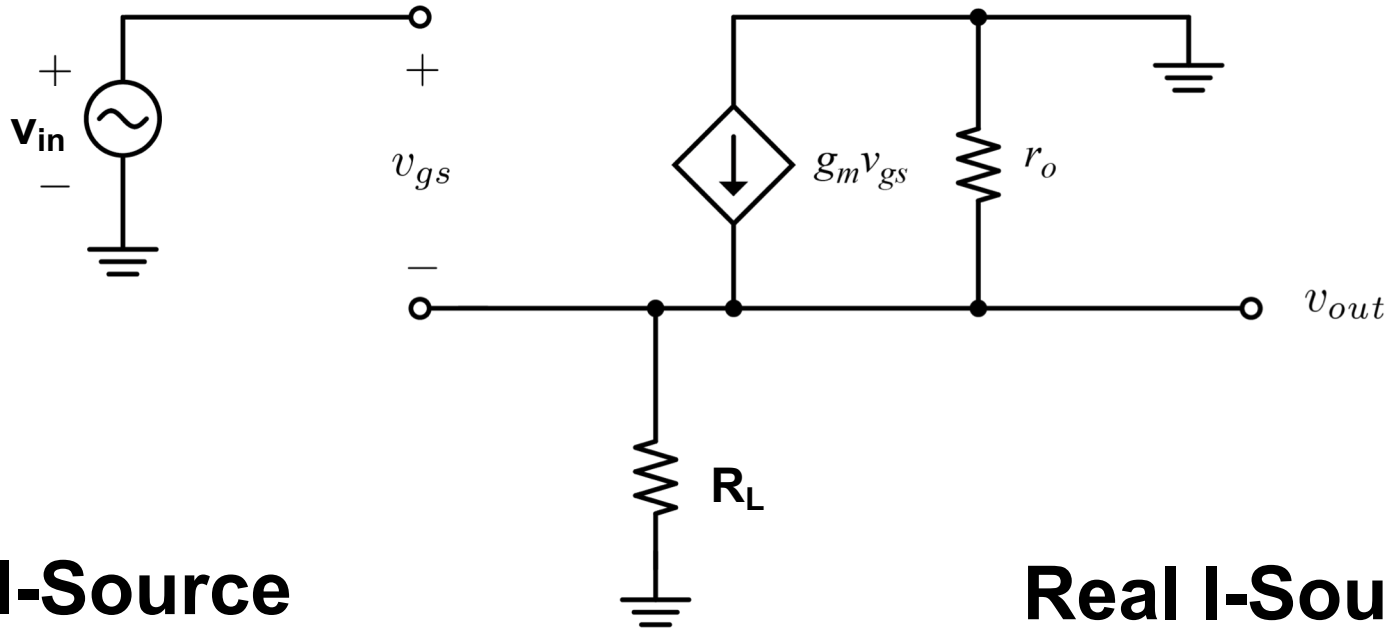

**Ideal I-Source**

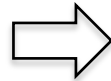**Real I-Source**

$$\frac{v_{out}}{R_L \parallel r_o} = g_m v_{gs}$$



$$\frac{v_{out}}{R_L \parallel r_o} = g_m (v_{in} - v_{out})$$