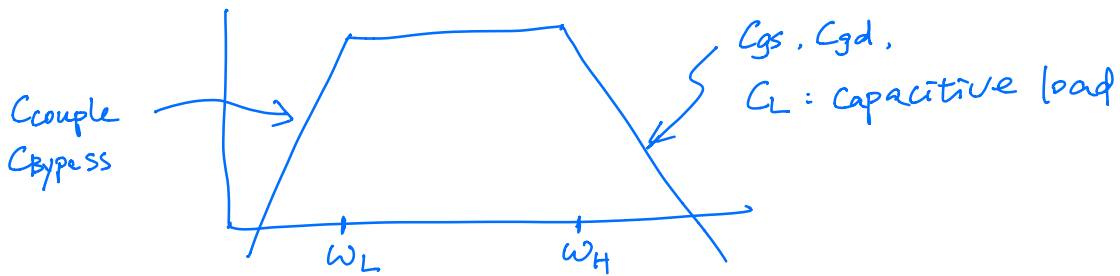


Summary of Frequency Response



SCTC $\rightarrow \omega_L$

\hookrightarrow AC equivalent
All other C's short-circuited
Find R_i seen by C_L


$$\omega_L = \sum_i \frac{1}{R_i C_L} = \sum_i \frac{1}{\tau_i}$$




OCTC $\rightarrow \omega_H$

\hookrightarrow AC eq det
All other C's open
Find R_i seen by C_L
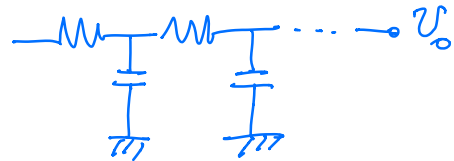
$$\omega_H = \frac{1}{\sum_i R_i C_L} = \frac{1}{\sum_i \tau_i}$$



Apply OCTC to CS amplifier:

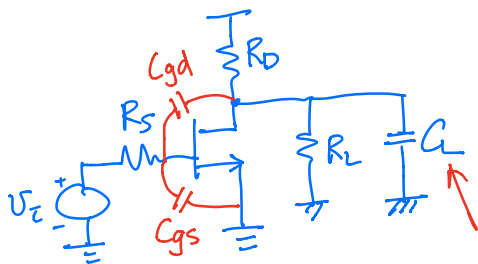


$$R'_{out} = R_D // R_L // r_o$$

Miller Approx

$$\frac{1}{\omega_L} = R_s [C_{gs} + (1 + g_m R'_{out}) C_{gd}]$$



Exact solution
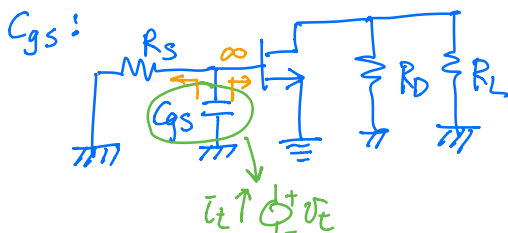
$$\frac{1}{\omega_L} = R_s [C_{gs} + (1 + g_m R'_{out}) C_{gd}] + R'_{out} (C_{gd} + C_L)$$



$$\left. \begin{array}{l} C_i = C_{gs} \\ R_i = R_s \end{array} \right\} \tau_i = R_s + C_{gs}$$

C_{gd}

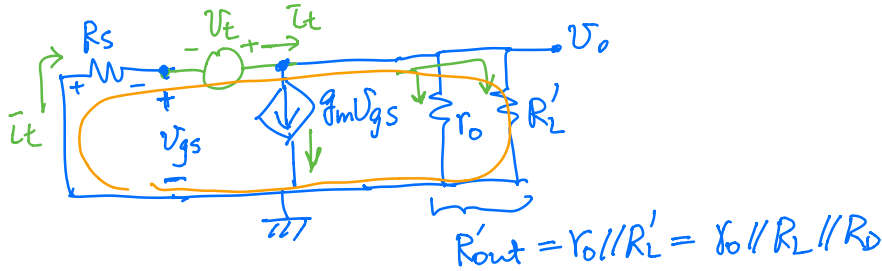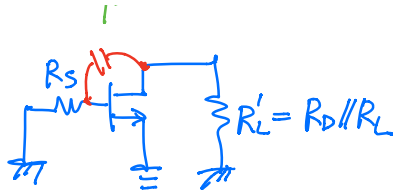

$$V_{gs} = -I_t R_s$$

KCL at Drain $I_t = g_m V_{gs} + \frac{V_o}{R_{out}}$

KLV

$$V_o = V_{gs} + V_t$$

$$I_t = g_m V_{gs} + \frac{V_{gs} + V_t}{R_{out}}$$

$$= (g_m + \frac{1}{R_{out}}) V_{gs} + \frac{1}{R_{out}} V_t$$

$$\downarrow$$

$$-I_t R_s$$


$$I_t (1 + R_s g_m + \frac{R_s}{R_{out}}) = \frac{V_t}{R_{out}}$$

$$R_{gd} = \frac{V_t}{I_t} = R_{out} + g_m R_s R_{out} + R_s$$

$$\tau_2 = R_{gd} C_{gd} = C_{gd} (R_{out} + g_m R_s R_{out} + R_s)$$

$$\approx C_{gd} \cdot (g_m R_s R_{out})$$

C_L :

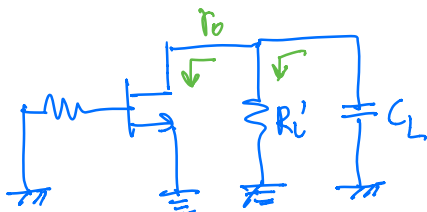

$$R_3 = R_L' \parallel R_D = R_{out}$$


$$\tau_3 = R_3 C_L = R_{out} C_L$$

OCTC $\frac{1}{\omega_H} = \sum_i R_i C_i = \underline{R_s} \cdot C_{gs} + C_{gd} (\underline{R_{out}} + \underline{j\omega R_s R_{out}} + \underline{R_s}) + \underline{R_{out}} \cdot C_L$

$$= R_s [C_{gs} + C_{gd} (1 + j\omega R_{out})] + R_{out} (C_{gd} + C_L)$$

Exact: $\frac{1}{\omega_H} = R_s [C_{gs} + C_{gd} (1 + j\omega R_{out})] + R_{out} (C_{gd} + C_L) \leftarrow$

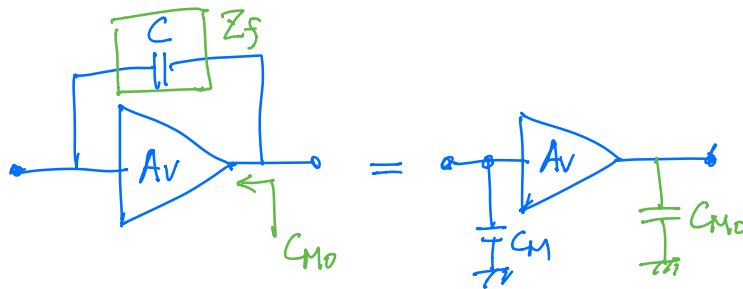Miller Approx $\frac{1}{\omega_H} = R_s [C_{gs} + C_{gd} (1 + j\omega R_{out})]$



$$C_M = (1 - A_v) C$$


$$Z_{M0} = \frac{V_o}{I_o} = \frac{V_o}{\frac{V_o - V_i}{Z_f}}$$

$$= \frac{Z_f}{1 - \frac{V_i}{V_o}} = \frac{Z_f}{1 - \frac{1}{A_v}}$$

$$Z_{M0} = \frac{1}{j\omega C_{M0}} = \frac{1}{j\omega C} \cdot \frac{1}{1 - \frac{1}{A_v}}$$

$$\Rightarrow C_{M0} = C \left(1 - \frac{1}{A_v}\right)$$

Refined Miller Approx.

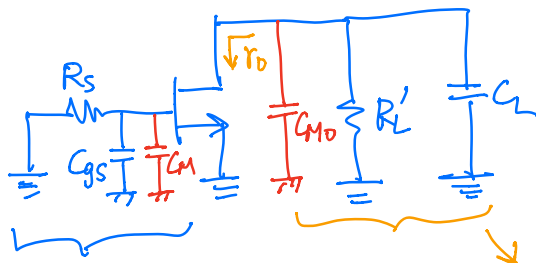


$$C_{M0} = \left(1 + \frac{1}{j\omega R_{out}}\right) \cdot C_{gd}$$


$$\approx C_{gd}$$

$$\frac{1}{\omega_H} \approx R_s [C_{gs} + C_{gd} (1 + j\omega R_{out})] + \underbrace{(R_L // R_o)}_{R_{out}} \cdot (C_L + C_{gd})$$

Apply OCTC to CG amplifier.

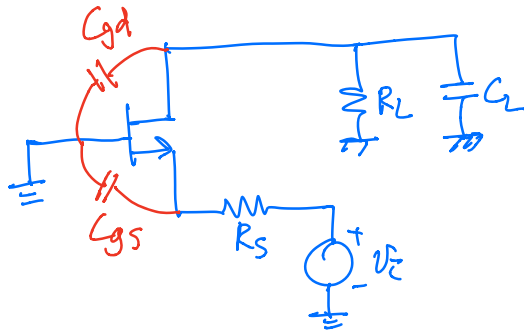

$$R_o' = r_o + (1 + g_m r_o) \cdot R_s$$

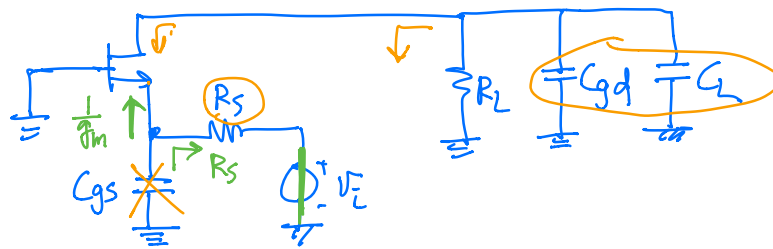

$$T_1 = C_{gs} \cdot \left(\frac{1}{g_m} \parallel R_s \right) \approx C_{gs} \cdot \frac{1}{g_m}$$

$$T_2 = (C_{gd} + C_L) \cdot (R_L \parallel R_o') \approx (C_{gd} + C_L) \cdot R_L$$

$$\omega_H = \frac{1}{\sum_i R_i C_i} = \frac{1}{T_1 + T_2} = \frac{1}{C_{gs} \cdot \frac{1}{g_m} + (C_{gd} + C_L) \cdot R_L} \rightarrow \text{large}$$

\uparrow small \uparrow small

Broadband Amplifier ,