

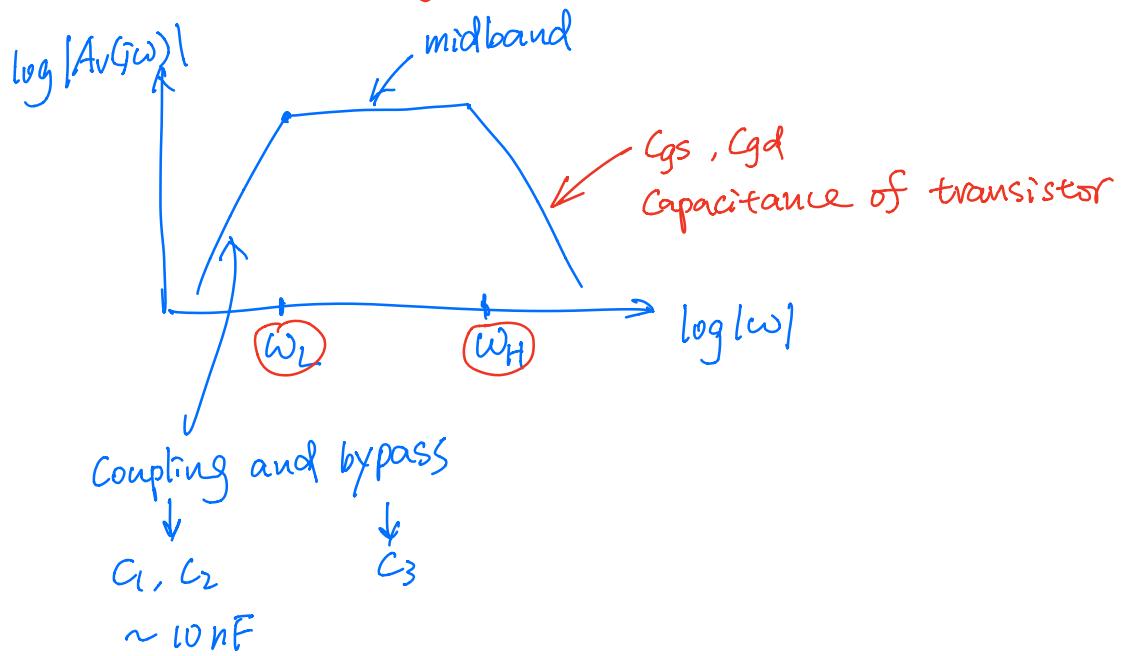


Frequency Response

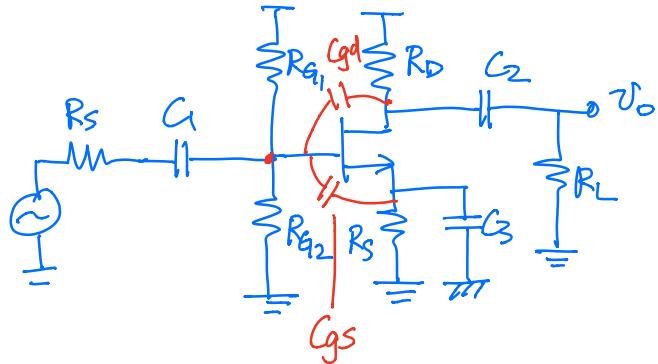

High-pass filter

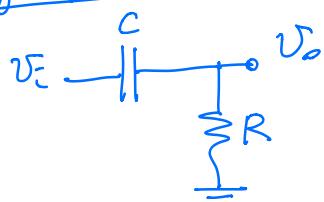

$$\frac{V_o}{V_i} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega}{\underbrace{\frac{1}{RC} + j\omega}_{\omega_L}}$$


$$s = j\omega$$

$$\frac{V_o}{V_i} = \frac{s}{s + \omega_L}$$

$$s \rightarrow 0 \quad \frac{V_o}{V_i} \rightarrow \frac{s}{\omega_L}$$

$$s = j\omega_L \quad \frac{V_o}{V_i} \rightarrow \left[\frac{1}{1+j} \right] = \frac{1}{\sqrt{2}}$$

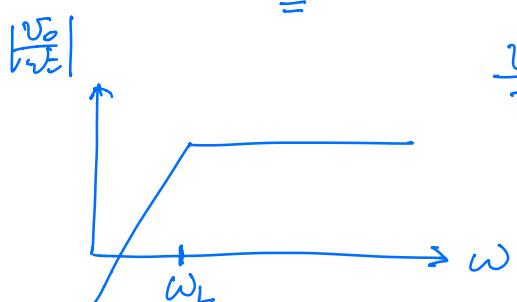
$$s \rightarrow \infty \quad \frac{V_o}{V_i} \rightarrow 1$$



General Expression

$$F(s) = \frac{s^{n_L} + d_1 s^{n_L-1} \dots}{s^{n_L} + e_1 s^{n_L-1} \dots} = \frac{(s+\omega_{p_1})(s+\omega_{p_2}) \dots}{(s+\omega_{p_1})(s+\omega_{p_2}) \dots}$$

n_L = # of poles = # of zeros

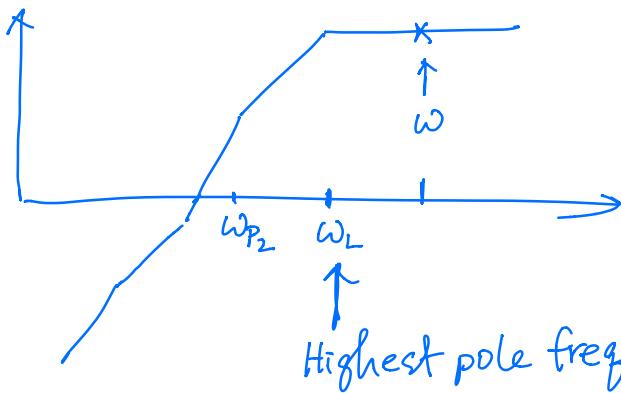

$$(s+\omega_{p_1})(s+\omega_{p_2}) \dots (s+\omega_{p_{n_L}})$$

$$= s^{n_L} + s^{n_L-1} (\underbrace{\omega_{p_1} + \omega_{p_2} + \dots + \omega_{p_{n_L}}}_{\text{Sum of poles}}) + s^{n_L-2} (\omega_{p_1} \omega_{p_2} + \dots)$$

$$s = |j\omega| \gg \omega_p$$

$$\approx (s + \underbrace{\sum_{i=1}^{n_L} (\omega_{p_i})}_{\text{Sum of poles}}) (s^{n_L-1} + \dots)$$

$$\omega_L = \sum_{i=1}^{n_L} \omega_i = \sum_{i=1}^{n_L} \frac{1}{R_i C_i} \quad C_i = \text{coupling or bypass caps.}$$

Short-Circuit Time Constant (SCTC) Method:

1. Find all coupling and bypass caps.
2. Solve one cap at a time,
Replace all other capacitor with short circuits
3. Replace indep voltage source by short circuit,

"current" by open "


4. Calculate resistance R_i that's in parallel with C_1

5. Find time constant associate with C_1

$$\frac{1}{R_i C_1}$$


6. $\omega_L = \sum_{i=1}^{n_L} \frac{1}{R_i C_i}$

Example:

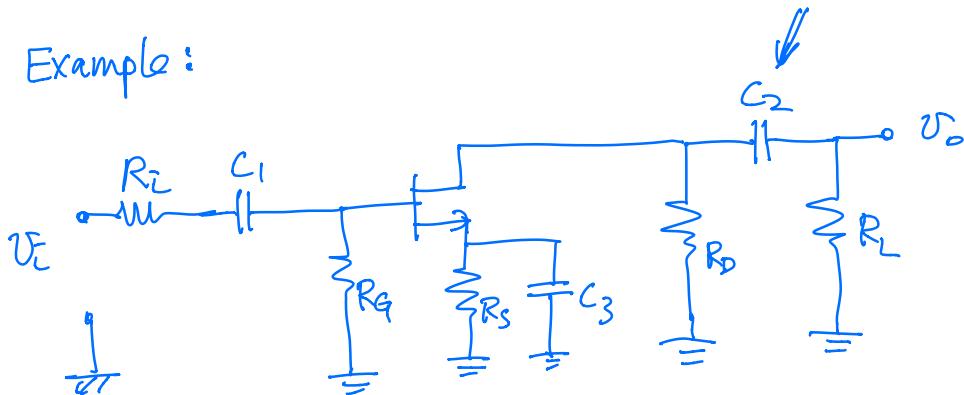

$$R_G = R_{G1} // R_{G2}$$

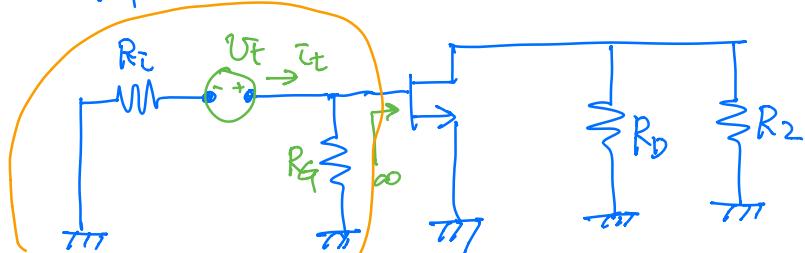
$$\tau_1 = \frac{1}{R_i C_1} \Rightarrow \text{Find } R_i$$



$$R_i = \frac{U_E}{I_E}$$

$$R_i = R_i + R_G$$

$$\tau_2 = \frac{1}{R_2 C_2}$$

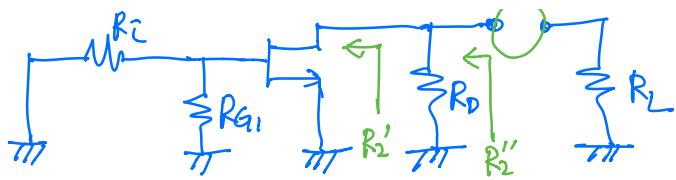


$$R'_z = r_o$$

$$R''_z = r_o \parallel R_D \approx R_D \quad \because r_o \gg R_D$$

$$R_z = R''_z + R_L = R_D + R_L$$

$$T_3 = \frac{1}{R_3 C_3}$$

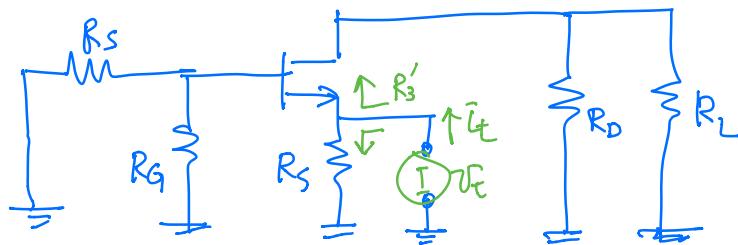

$$R'_z \approx \frac{1}{g_m}$$

$$R_3 = \left(\frac{1}{g_m}\right) \parallel R_z$$

$$\omega_L = \frac{1}{R_1 G} + \frac{1}{R_2 C_3} + \frac{1}{R_3 G} = \frac{1}{(R_z + R_g) G} + \frac{1}{(R_D + R_L) C_2} + \frac{1}{\left(\frac{1}{g_m}\right) \parallel R_S G_3}$$

Much simpler than solving small signal circuit with C_1, C_2, C_3

$\frac{1}{g_m}$ smallest resistance

As a designer, determine the minimum capacitance you need for C_1, C_2, C_3

$$\omega > \omega_L$$


$$\left| \frac{1}{j\omega C_1} \right| < R_1 = R_z + R_g \Rightarrow G \gg \frac{1}{\omega(R_z + R_g)}, \quad \omega = \text{operating freq.}$$

$$\left| \frac{1}{j\omega C_2} \right| < R_2 = R_D + R_L \Rightarrow C_2 \gg \frac{1}{\omega(R_D + R_L)}$$

$$\left| \frac{1}{j\omega C_3} \right| < R_3 = \left(\frac{1}{g_m} \right) // R_S \Rightarrow C_3 \gg \frac{1}{\omega \cdot \left(\frac{1}{g_m} // R_S \right)}$$

↑

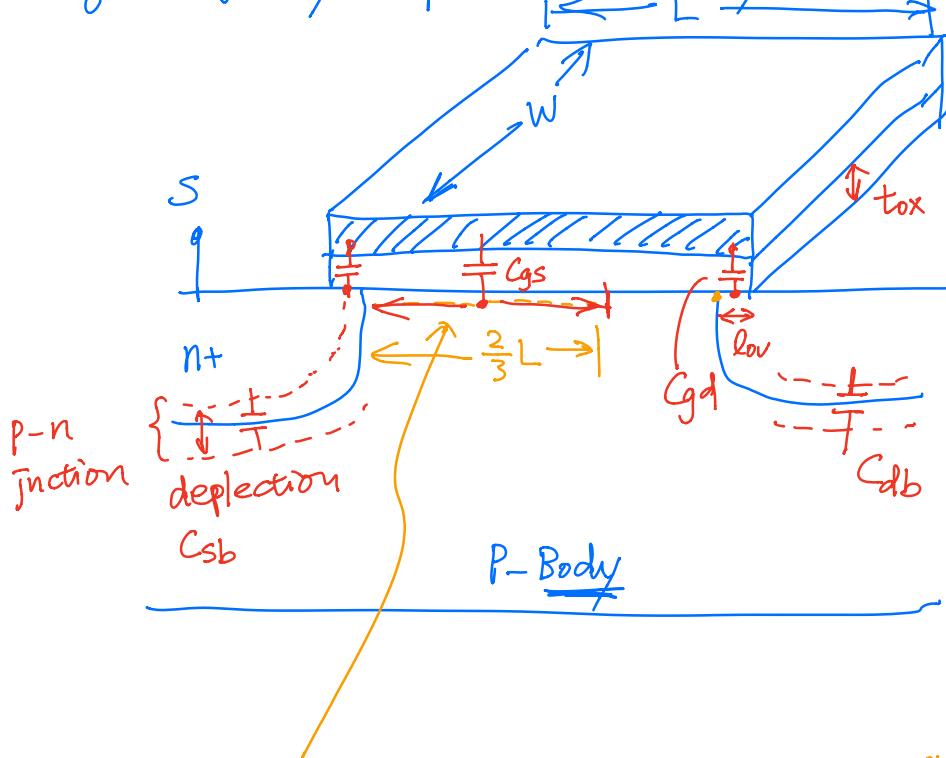High frequency Response limited by transistor cap.



electron inversion layer covers partially channel

$$C_{GS} = C_{OX} \left(\frac{2}{3} L \right) \cdot W = \frac{2}{3} W \cdot L \cdot C_{OX} ; \quad C_{OX} = \frac{\epsilon_{ox}}{t_{ox}}$$

\uparrow
 $\left[\frac{F}{cm^2} \right]$

usually the largest cap of MOSFET

$$C_{GD} = C_{Overlap} = C_{OX} \cdot l_{ov} \cdot W \quad l_{ov} \ll L$$

$$C_{GD} \ll C_{GS}$$

$$C_{sb} = C_{jsb} \cdot \text{area}$$

↑

$$\frac{C_{jo}}{\sqrt{1 + \frac{V_{bs}}{V_{bi}}}} \quad \text{junction cap.}$$

