
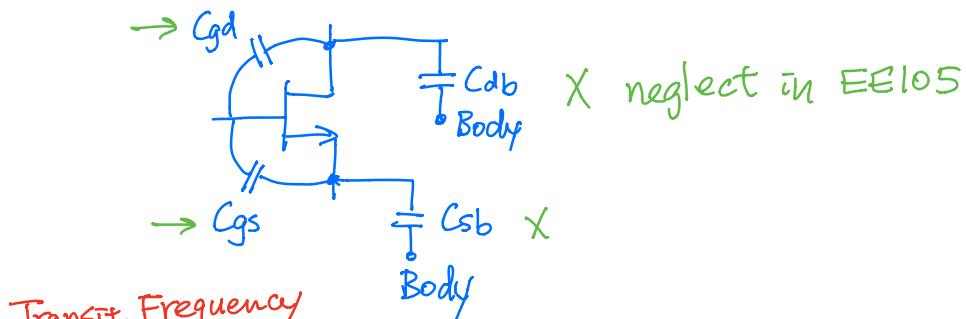



High Frequency Response

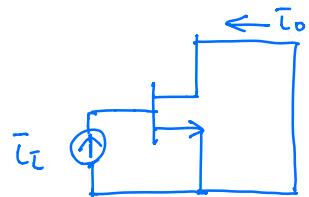

f_T of MOSFET = the freq at which current gain = 1
AC circuit for short circuit load.



Complete hybrid- π model:

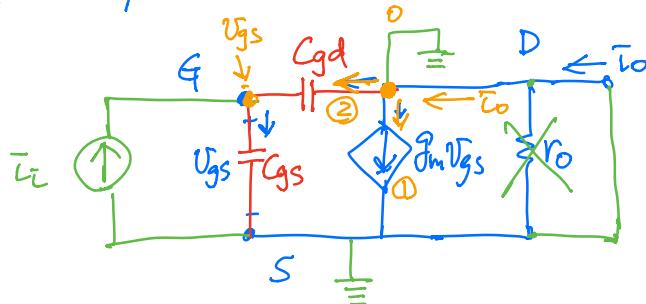


$$s = j\omega \quad C_{gd} \text{ Impedance} = \frac{1}{sC_{gd}} = \frac{1}{j\omega C_{gd}}$$

$$C_{gs} \quad " \quad = \frac{1}{sC_{gs}}$$



$$\text{KCL at } G: \quad \hat{I}_i = \frac{\hat{V}_{gs}}{sC_{gs}} + \frac{\hat{V}_{gs}}{sC_{gd}} = \hat{V}_{gs}(sC_{gs} + sC_{gd})$$

$$\text{KCL at } D: \quad \hat{I}_o = g_m \hat{V}_{gs} + \frac{(0 - \hat{V}_{gs})}{sC_{gd}} = g_m \hat{V}_{gs} - sC_{gd} \cdot \hat{V}_{gs}$$
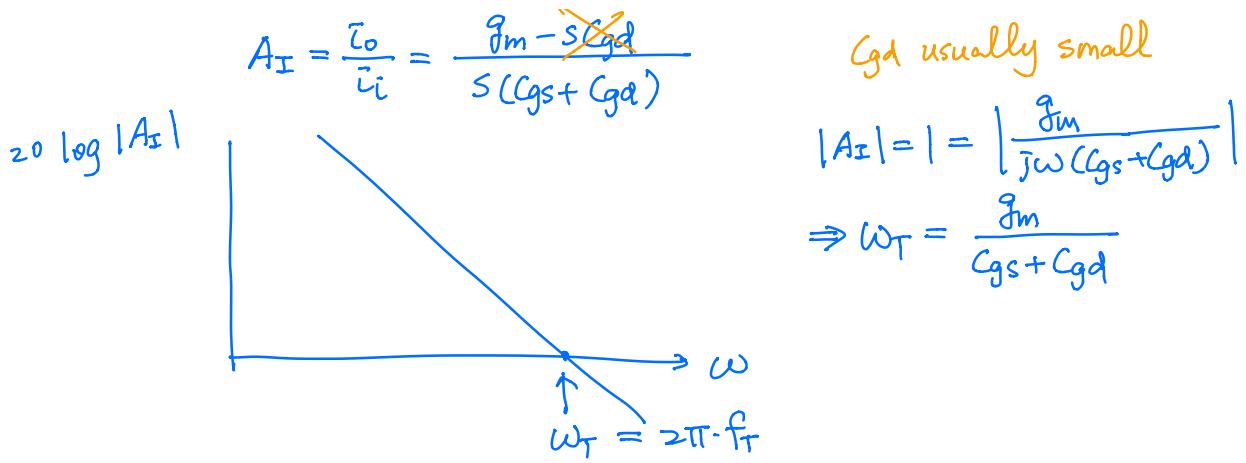
$$\hat{I}_o = \frac{\hat{I}_i}{sC_{gs} + sC_{gd}} (g_m - sC_{gd})$$




High freq Response of CS amp

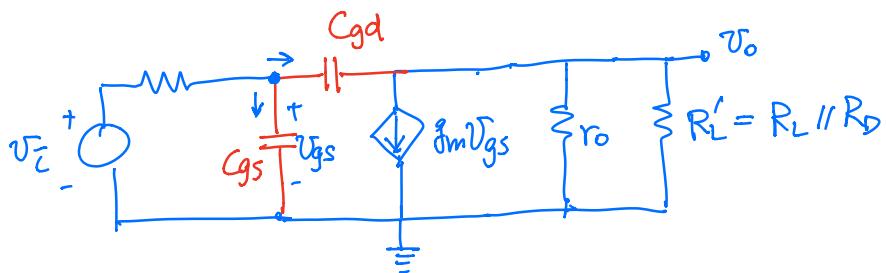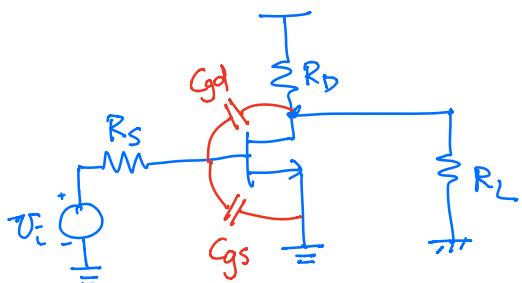

Solving using KCL, KVL still works, but tedious.

Simplified Method: Miller Effect

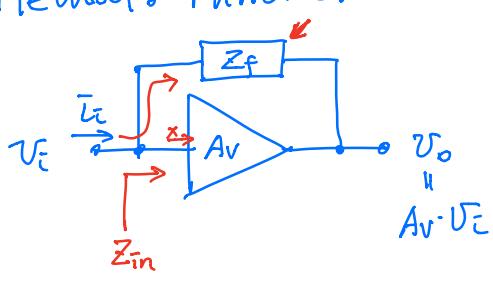

$$Z_{in} = \frac{V_E}{I_i} = \frac{V_E}{\frac{V_E - V_o}{Z_f}} = \frac{V_E}{\frac{V_E}{A_v} - \frac{V_o}{Z_f}}$$


$$Z_{in} = \frac{V_E}{V_E - A_v V_E} Z_f$$

$$Z_{in} = \frac{Z_f}{1 - A_v}$$


$$Z_f = \frac{1}{j\omega C}$$

$$Z_{in} = \frac{1}{j\omega C(1-A_v)} = \frac{1}{j\omega C_{Miller}}$$

$$C_{Miller} = C(1-A_v)$$

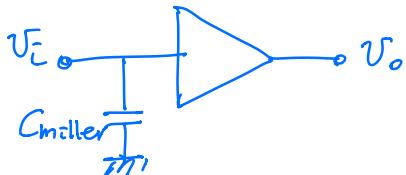


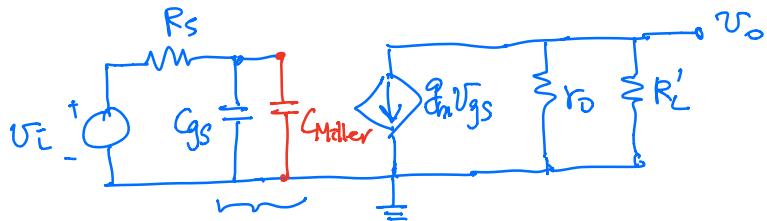CS Amp with Miller Cap replacing C_{gd} .



$$C_{in} = C_{gs} + (1-A_v) C_{gd} \quad \text{dc gain . } A_v = -g_m R''_L$$
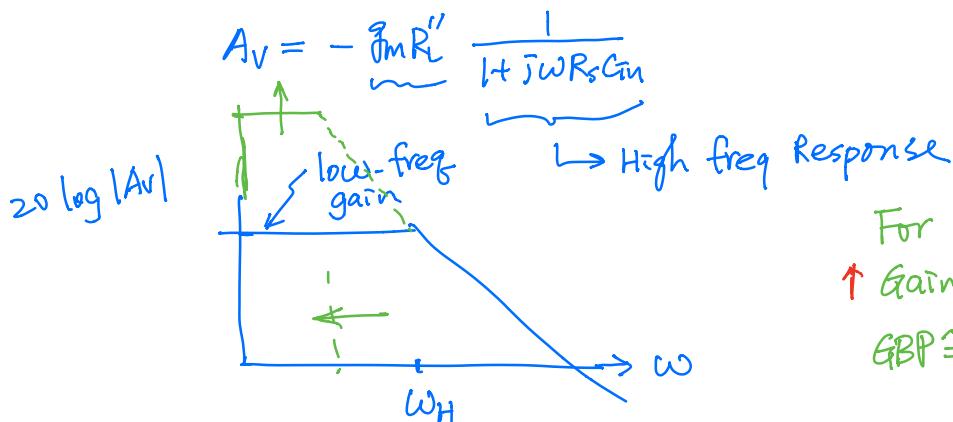
$$\begin{aligned} V_o &= -g_m V_{gs} (r_o \parallel R'_L) \\ &= -g_m V_i \cdot \frac{\frac{1}{j\omega C_{in}}}{R_s + \frac{1}{j\omega C_{in}}} \cdot R''_L \end{aligned}$$





For CS amp
↑ Gain × Bandwidth ↓
 $GFP \approx g_m R''_L \frac{1}{R_s C_{gd} \cdot g_m R''_L}$

$$\omega_H = \frac{1}{R_s C_{in}} = \frac{1}{R_s (C_{gs} + (1+g_m R''_L) C_{gd})} \quad \text{large}$$

$$= \frac{1}{R_s \cdot C_{gd}}$$




Typical Amp Freq Response

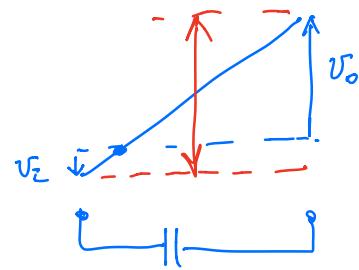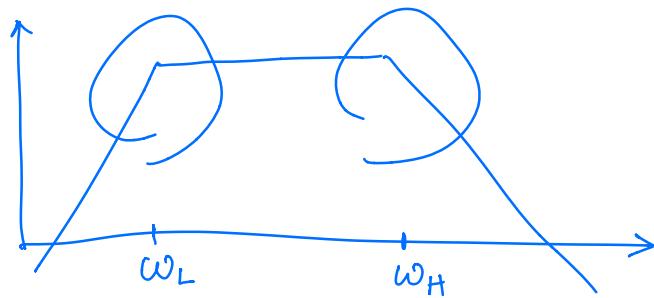

Full KCL, KVL

$$\omega_p = \frac{1}{R_s(C_{gs} + (1 + g_m R''_L) C_{gd}) + R''_L \cdot C_{gd}}$$

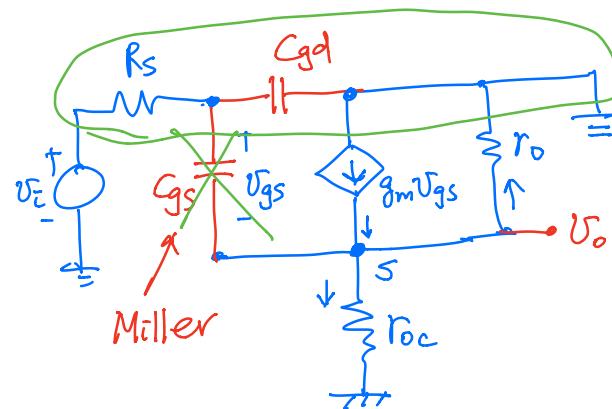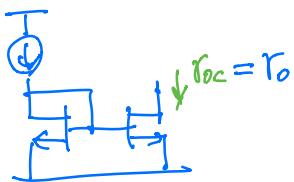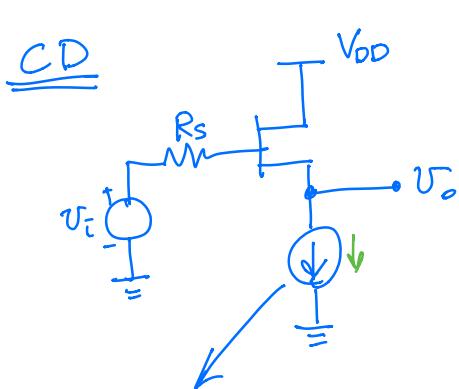⇒ Remember, Miller Cap is an Approximation



$$C_{Miller} = (1 - A_v) \cdot C_{gs}$$


$$A_v \approx 1 \text{ for CD}$$

$$C_{Miller} \rightarrow 0$$

KCL at S

$$g_m v_{gs} = \frac{v_o}{r_o \parallel R_{oc}}$$
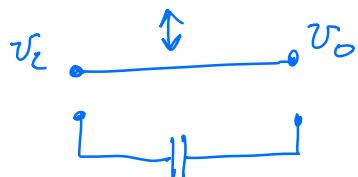
$$v_g = \frac{\frac{1}{sC_{gd}} v_i}{R_s + \frac{1}{sC_{gd}}} = \frac{1}{1 + sR_s C_{gd}} v_i$$




$$V_{gs} = V_g - V_o = V_g - V_0$$

$$g_m(V_g - V_0) = \frac{V_o}{r_o // r_{oc}}$$

$$V_o (g_m + \frac{1}{r_o // r_{oc}}) = g_m V_g = g_m \frac{1}{1 + s R_s C_{gd}} \cdot V_E$$

$$A_v = \frac{V_o}{V_E} = \underbrace{\frac{g_m}{g_m + \frac{1}{r_o // r_{oc}}}}_{\substack{\text{low freq} \\ \text{gain} \approx 1}} \cdot \underbrace{\frac{1}{1 + j\omega R_s C_{gd}}}_{\text{single pole}}$$

$$g_m \gg \frac{1}{r_o // r_{oc}}$$

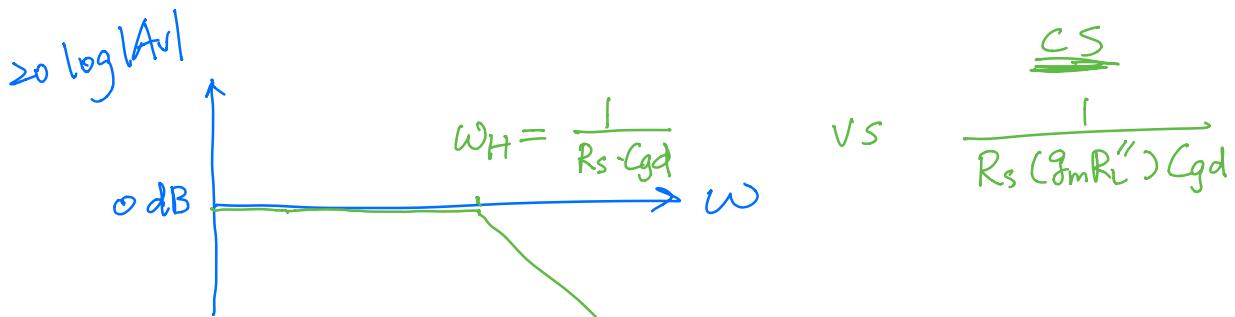


ω_L : Open-Circuit Time Constant (OCTC)

- Same small signal
- Consider one cap at a time, C_i
- Replace all other caps with OPEN circuit
- Find "R_i" seen by C_i


$$\Rightarrow \omega_H = \frac{1}{\sum_i R_i C_i} = \frac{1}{\sum_i T_i}$$

Compare SCTC
with
 ω_L

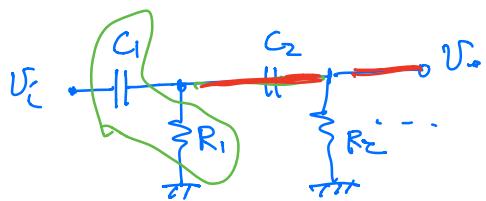

Replace $C_2 \dots$
by short circuit

OCTC
 \downarrow
 ω_H

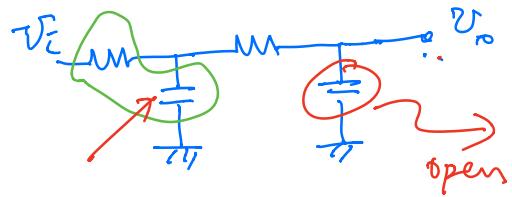

Replace $C_2 \dots$
with open circuit