

Common Source (CS)	CS with Degeneration	Common Drain (CD)	Common Gate (CG)
<ul style="list-style-type: none"> <li>✓ <math>A_{V,t} = -g_m R_L</math></li> <li>✓ <math>R_i = \infty</math></li> <li>✓ <math>R_o = r_o</math></li> <li>✓ <math>A_{I,t} = \infty</math></li> </ul>	$A_{V,t} = -\frac{g_m R_L}{1 + g_m R_S}$ $R_i = \infty$ $R_o = [r_o (1 + g_m R_E)]$ $A_{I,t} = \infty$ <p>Without degeneration: Simply set <math>R_S = 0</math></p>	$A_{V,t} = \frac{R_L}{\frac{1}{g_m} + R_L}$ $R_i = \infty$ $R_o = \frac{1}{g_m}$ $A_{I,t} = \infty$	<ul style="list-style-type: none"> <li>✓ <math>A_{V,t} = g_m R_L</math></li> <li><math>R_i = \frac{1}{g_m}</math></li> <li><math>R_o = [r_o (1 + g_m R_E)]</math></li> <li>✓ <math>A_{I,t} \approx 1</math></li> </ul>

MOS	Common Source (CS)	Common Source with Deg.	Common Drain (CD)	Common Gate (CG)
$R_i$	$\infty$	$\infty$	$\infty$	Small $\frac{1}{g_m}$
$R_o$	Large	Very Large	Small $\frac{1}{g_m}$	Large <u>very Large</u>
$A_V$	Moderate	Small	$\sim 1$	Moderate
$f_H$	<u>Small</u>	Moderate	Large ✓	Large ✓



### 2-Port Model

	Ideal $R_{in}$	Ideal $R_{out}$
Voltage Amplifier	$\infty$	0
Current Amplifier	0	$\infty$
Transconductance Amplifier	$\infty$	$\infty$
Transresistance Amplifier	0	0

$V_{in}$   $I_{out}$   
 $I_{in}$   $V_{out}$



### Multi-Stage Amplifiers.

\* 3 stages = input stage = match  $R_{in}$   
                   middle " = provide gain  
                   output " = match  $R_{out}$

\* Higher gain  
 \* Improve bandwidth

\* DC coupled amplifier → level shift

Example: 2 stage Amp: CS + CS

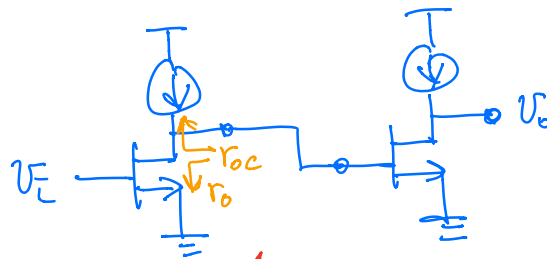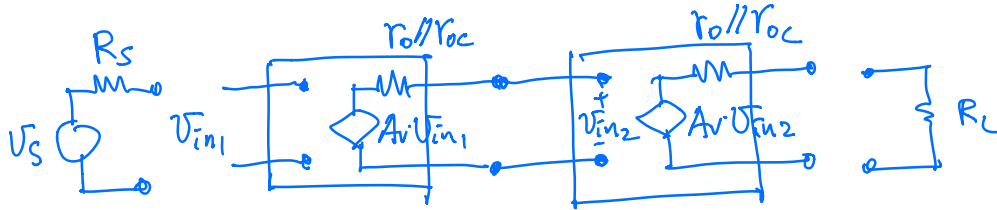

$$A_V = \left( \frac{R_{in1}}{R_s + R_{in1}} \right) \cdot A_{V1} \cdot \left( \frac{R_{in2}}{R_{out1} + R_{in2}} \right) \cdot A_{V2} \cdot \left( \frac{R_L}{R_{out2} + R_L} \right)$$


$$A_{V1} = -g_{m1} \cdot (r_o // r_{oc} // R_{in2}) = -g_{m1} (r_o // r_{oc})$$

$$A_{V2} = -g_{m2} (r_o // r_{oc})$$

$$A_V = [g_{m1} (r_o // r_{oc})] [g_{m2} (r_o // r_{oc})] \left( \frac{R_L}{r_o // r_{oc} + R_L} \right)$$

small

Bandwidth: Hybrid- $\pi$

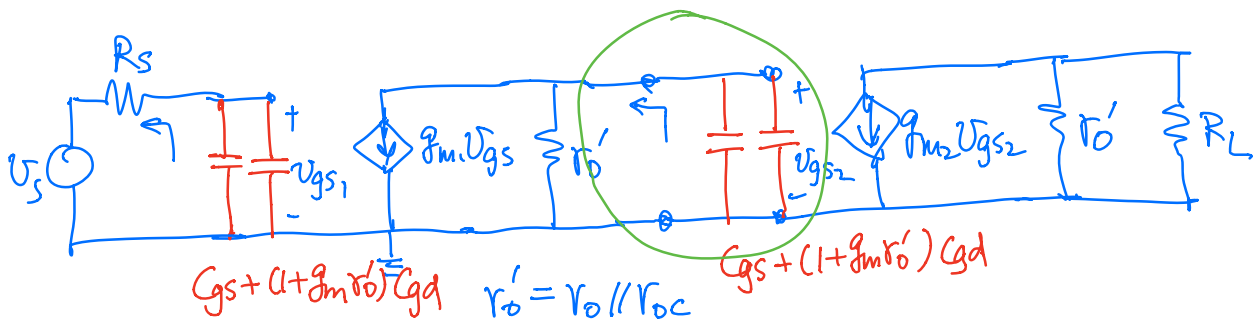

$$\tau_1 = [C_{gs} + (1 + g_{m1}r_o')C_{gd}] \cdot R_s \leftarrow$$

$$\tau_2 = [C_{gs} + (1 + g_{m2}r_o')C_{gd}] r_o' \rightarrow \text{super long}$$

$\uparrow$  large cap  
 $\uparrow r_{o1} // r_{o2} = \text{large resistance}$


$$\omega_H = \frac{1}{\tau_1 + \tau_2} = \text{super small}$$

2 disadvantages for CS+CS

- ① Large output resistance  $R_{out}$ ,  $\rightarrow$  lower gain
- ② Very Low Bandwidth

Solution: CS + CD + CS

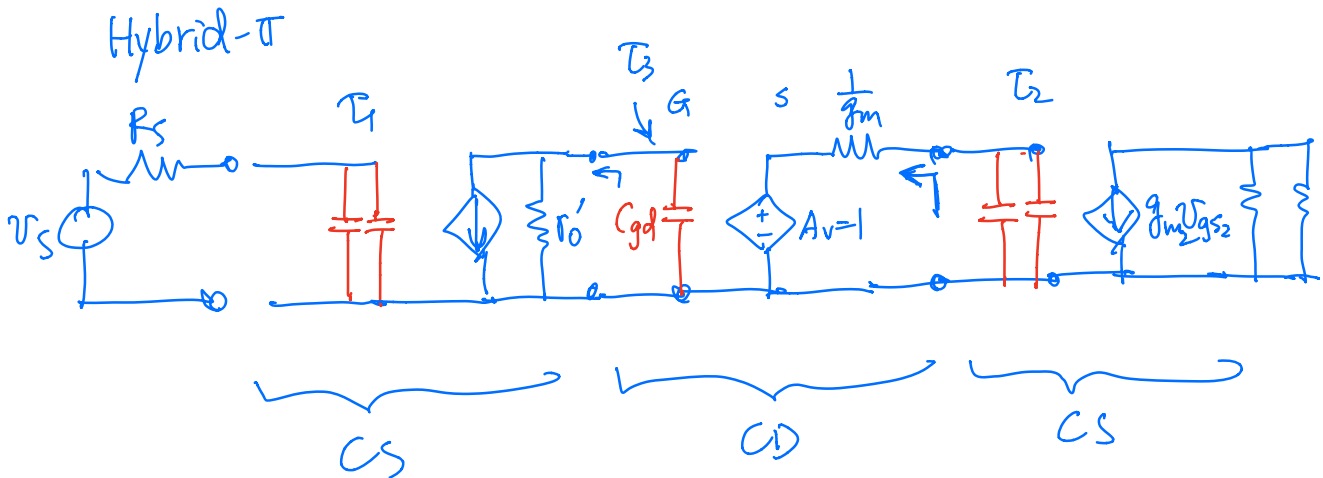$\uparrow$   
 unity gain  
 $R_{in} = \infty$   
 $R_{out} = \frac{1}{g_m}$



$$A_v = A_{v1} A_{v2} A_{v3} \frac{R_L}{R_{out} + R_L} \quad \text{same}$$

$\uparrow$   
 $= 1$

$$\tau_1 = R_s (C_{gs} + (1 + g_m r_{o1}') C_{gd}) \quad \text{same}$$

$$\tau_2 = \frac{1}{g_m} (C_{gs} + (1 + g_m r_{o1}') C_{gd}) \quad \text{substantially reduce}$$

$$\tau_3 = r_o' C_{gd} \quad \text{small,}$$

$\uparrow \quad \uparrow$   
 $\text{small}$

$$\omega_H = \frac{1}{\tau_1 + \tau_2 + \tau_3} > \omega_H \text{ of } CS + CS$$