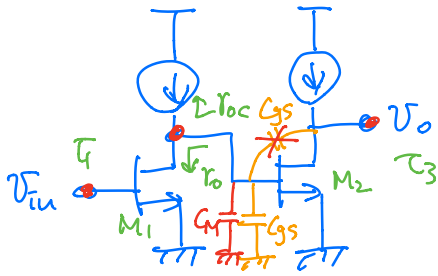


CS-CS



$$R = r_o \parallel r_{oc} \rightarrow \text{large } R$$


$$C = C_{gs} + C_M = C_{gs} + (1 - A_v) C_{gd} \rightarrow \text{large } C$$

$$T_2 = RC \rightarrow \text{Large}$$


$$T_3 = \frac{1}{\sum \tau_i} \approx \frac{1}{T_2}$$

$$C_{gs} + g_{m2} r_{o2} \cdot C_{gd} = C_{gs} + g_{m2} (R_L \parallel r_{oc} \parallel r_o)$$

CS-CD-CS

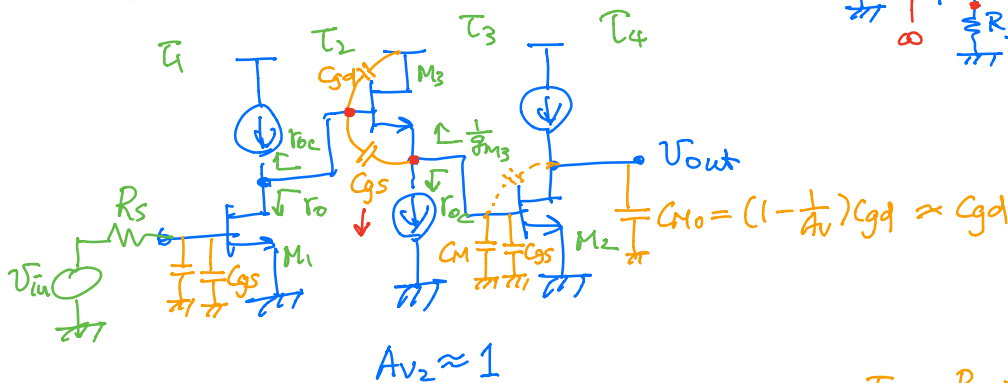

$$A_{v2} \approx 1$$

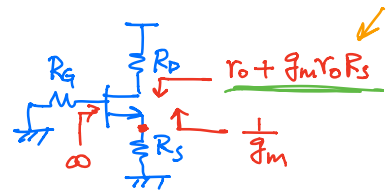

Total A_v unchange

$$T_2: R_2 = r_o \parallel r_{oc} \cdot C_2 = C_{gd} + (1 - A_{v2}) C_{gs} \approx C_{gd}$$

T_2 substantially¹ reduced.

$$T_3: R_3 = \frac{1}{g_{m3}} \parallel r_{oc} = \frac{1}{g_{m3}}$$

$$C_3 = C_{gs} + (1 - A_{v2}) C_{gd} \approx C_{gs} + g_{m2} (r_{o2} \parallel r_{oc} \parallel R_L) C_{gd}$$

T_3 substantially reduce

$$\omega_H = \frac{1}{\sum \tau_i} \approx \frac{1}{T_2 + T_3} \Rightarrow \text{Extended BW without lowering gain}$$

$$T_1 = R_s \cdot (C_{gs} + C_M) \rightarrow T_3$$

$$T_4 = (r_o \parallel r_{oc}) \cdot C_{gd} \sim T_2$$


Miller Cap C_f



$$C_M = (1 - A_v) \cdot C_f$$

$$C_{M0} = (1 - \frac{1}{A_v}) C_f$$


Example CS w/ Large C_L

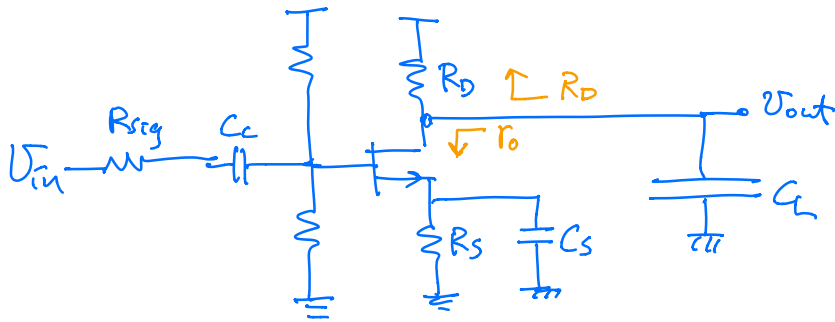

$$R = R_D \parallel r_o \approx R_D$$

$$C = C_L$$
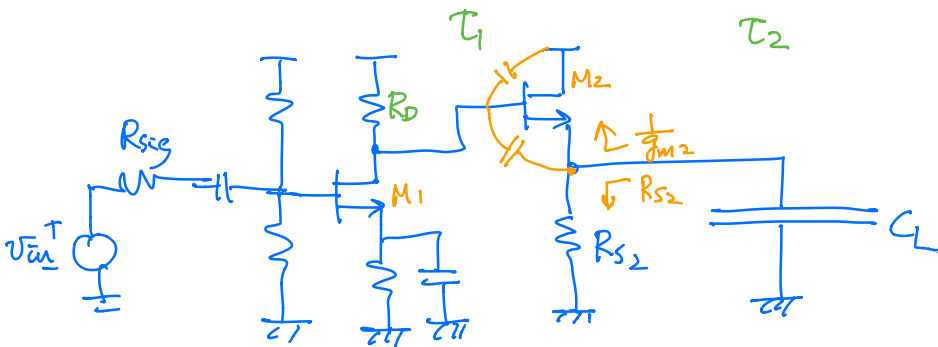
$$\omega_H = \frac{1}{RC} = \frac{1}{R_D C_L}$$



$$T_2: C \approx C_L$$

$$R = \frac{1}{g_{m2}} \parallel R_{S2} \approx \frac{1}{g_{m2}}$$




$T_2 = R \cdot C$ substantially reduce

$$T_1: R = R_D \parallel r_o = R_D$$

$$C = C_{gd} + (1 - A_{v1}) C_{gs} \approx C_{gd}$$

$$T_1 = R_D \cdot C_{gd} \ll \text{before}$$

Cascode Amplifier = CS + CG

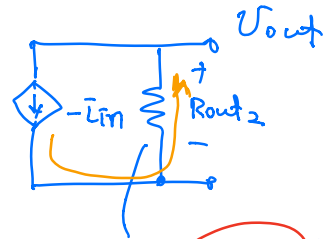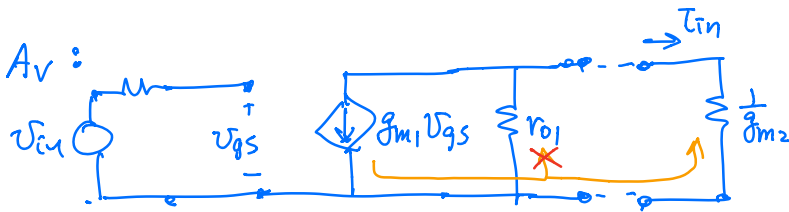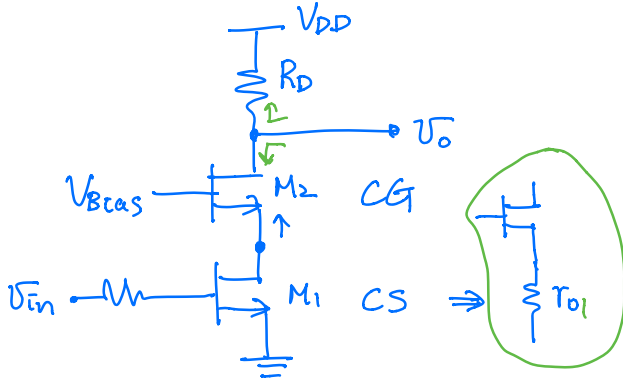

$$R_D \parallel (r_{o2} + g_{m2} r_{o2} r_{o1}) \approx R_D$$


$$V_{out} = -(-\bar{i}_{in}) \cdot R_{out2} = \bar{i}_{in} \cdot R_{out2} = \bar{i}_{in} \cdot R_D$$

$$\bar{i}_{in} = -g_{m1} V_{gs}$$

$$V_{out} = -g_{m1} V_{gs} \cdot R_D = V_{in} (-g_{m1} R_D)$$

$$A_v = -g_{m1} R_D$$

Cascode BW

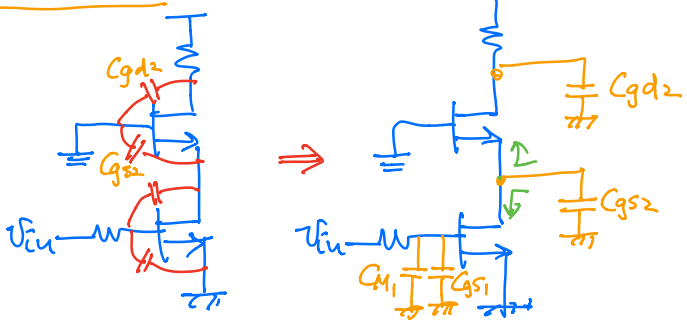

$$C_{M1} = (1 - A_{v1}) \cdot C_{gd1}$$

$$A_{v1} = -g_{m1} R_{out1}$$

$$R_{out1} = r_{o1} \parallel \frac{1}{g_{m2}} = \frac{1}{g_{m2}}$$

$$\left. \begin{array}{l} A_{v1} = -g_{m1} R_{out1} \\ R_{out1} = r_{o1} \parallel \frac{1}{g_{m2}} = \frac{1}{g_{m2}} \end{array} \right\} A_{v1} = -g_{m1} \cdot \left(\frac{1}{g_{m2}} \right) = -\frac{g_{m1}}{g_{m2}}$$

If M_1 and M_2 are the same (same $(\frac{W}{L})$)


$$\Rightarrow g_{m1} = g_{m2}$$

$$A_{v1} = -1$$

$$C_{M1} = (1 - (-1)) C_{gd} = 2C_{gd1}$$

$$\tau_f = R_{sig} \cdot (C_{gs1} + 2C_{gd1})$$

Cascode with cascode current mirror bias

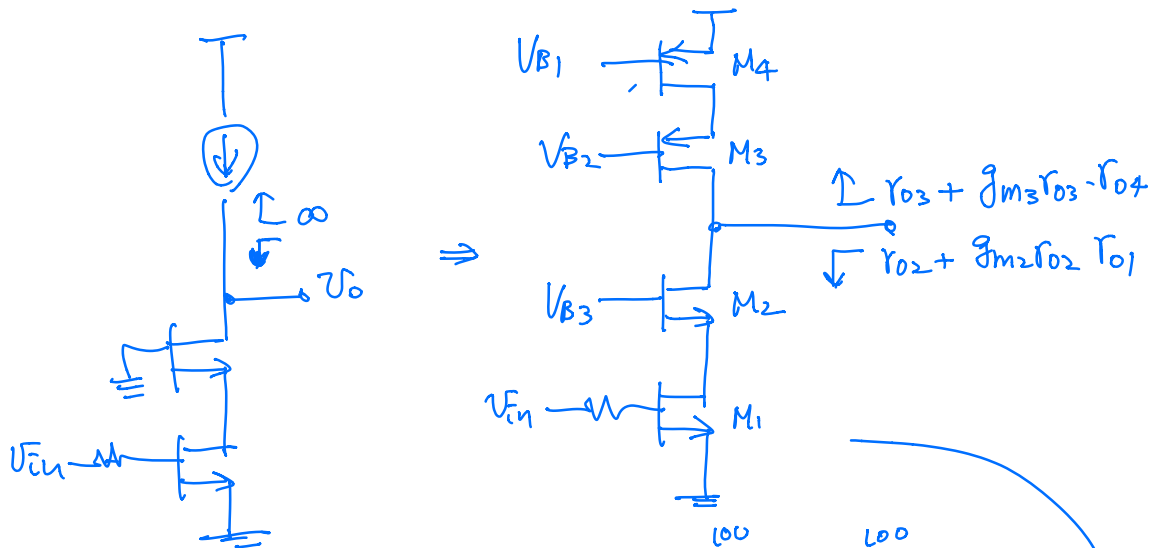

$$A_v = -g_{m1} \cdot (r_{o2} + \underline{g_{m2} r_{o2} r_{o1}}) \approx -(g_{m1} r_{o1}) (g_{m2} r_{o2})$$


super high gain

$$A_v = -g_{m1} \left[(r_{o2} + g_{m2} r_{o2} r_{o1}) \parallel (r_{o3} + g_{m3} r_{o3} r_{o4}) \right]$$

$$= -g_{m1} \left[(g_{m2} r_{o2} r_{o1}) \parallel (g_{m3} r_{o3} r_{o4}) \right]$$

If $r_{o1} \approx r_{o2} \approx r_{o3} \approx r_{o4}$ $g_{m2} \approx g_{m3}$
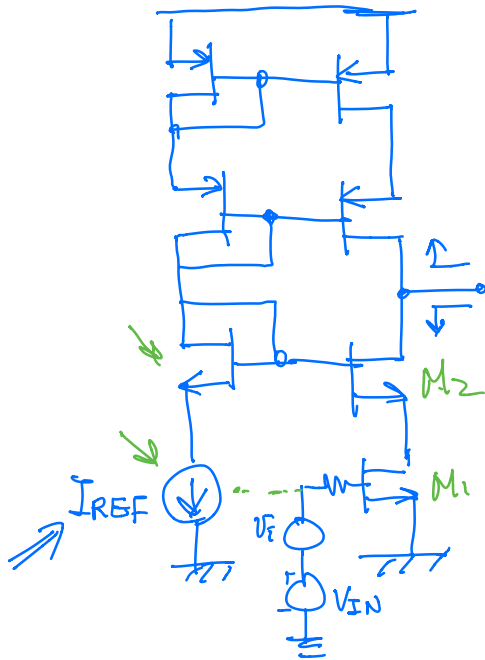
$$A_v = -\frac{1}{2} g_{m1} g_{m2} r_{o2} r_{o1}$$



Design Example

$$M_1, M_2: k_n' = 0.1 \text{ mA/V}^2$$

$$\lambda = 0.1 \text{ V}^{-1}$$

$$V_{tn} = 0.5 \text{ V}$$

$$\text{Goal: } g_{m1} = 1 \text{ mS}$$

$$R_{out} = 5 \text{ M}\Omega$$

$$\Rightarrow A_v = -g_{m1} R_{out} = -5000$$

Find $(\frac{W}{L})_1$

$$R_{out} = \frac{1}{2} g_m r_o^2 = 5 \times 10^6$$

For simplicity, all transistors have the g_m, r_o

$$g_m = 10^{-3}$$

$$r_o^2 = \frac{5 \times 10^6 \times 2}{10^{-3}} = 10^{10}$$

$$r_o = 100,000 \Omega = \frac{1}{\lambda I_{Ds}} = 10^5$$

$$I_{Ds} = \frac{1}{\lambda \cdot 10^5} = \frac{1}{0.1 \times 10^5} = \frac{1}{10^4} = 10^{-4} = 100 \mu\text{A}$$

$$g_m = k_n V_{ov} = \sqrt{2 \cdot k_n I_{Ds}}$$

$$2 \cdot k_n' \left(\frac{W}{L}\right) \cdot I_{Ds} = g_m^2 = 10^{-6}$$


$$\downarrow \quad \quad \downarrow$$

$$10^{-4} \quad 10^{-4}$$

$$\left(\frac{W}{L}\right) = \frac{10^{-6}}{10^{-4} \cdot 10^{-4} \cdot 2} = \frac{100}{2} = 50$$

$$I_{Ds} = \frac{1}{2} k_n V_{ov}^2$$
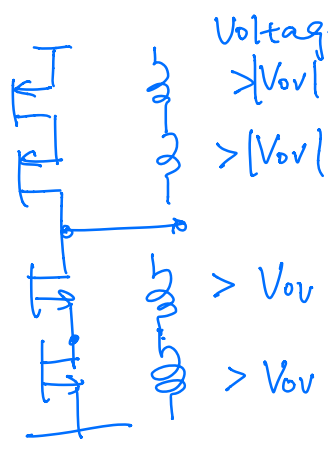
$$= \frac{1}{2} k_n' \left(\frac{W}{L}\right) V_{ov}^2$$



Voltage Swing?

$>|V_{ov}|$

$>|V_{ov}|$

$> V_{ov}$

$> V_{ov}$


$$g_m = V_{ov} \cdot k_n$$

$$V_{ov} = \frac{g_m}{k_n' \left(\frac{W}{L}\right)} = \frac{10^{-3}}{10^4 \cdot 50} = 0.2V$$

$$V_{out, min} = 2V_{ov} = 0.4V$$

$$V_{out, max} = V_{DD} - 2|V_{ov}| = V_{DD} - 0.4V$$

Lab 6 : Folded Cascode

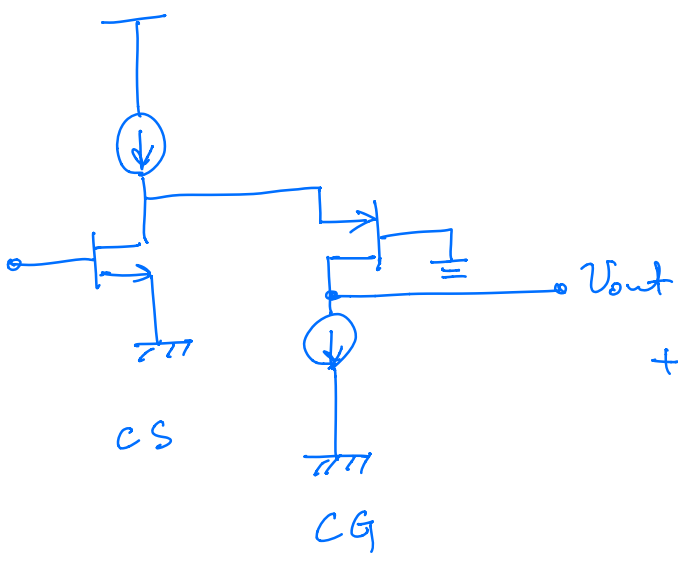

+ CD
to drive C_L