

EE105
Microelectronic Devices and Circuits
Multi-Stage Amplifiers





Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)



Terminal Gain and I/O Resistances of MOS Amplifiers

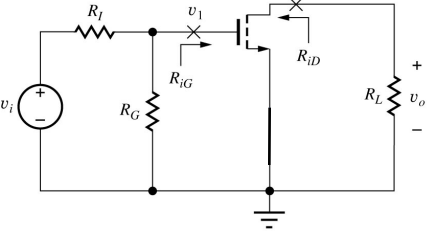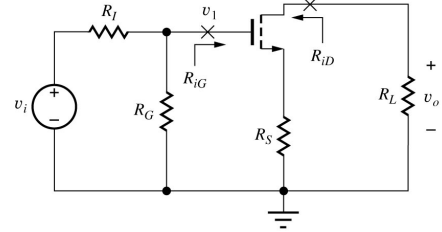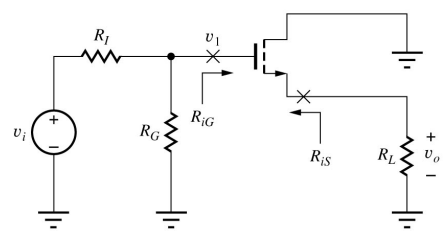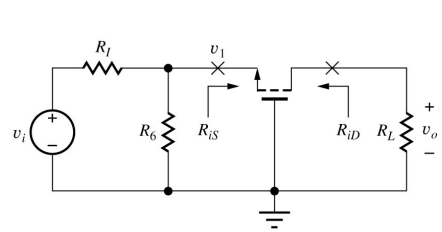Common Source (CS)	CS with Degeneration	Common Drain (CD)	Common Gate (CG)
 <p>(a)</p>	 <p>(a)</p>	 <p>(b)</p>	 <p>(c)</p>
$A_{V,t} = -g_m R_L$ $R_i = \infty$ $R_o = r_o$ $A_{I,t} = \infty$	$A_{V,t} = -\frac{g_m R_L}{1 + g_m R_S}$ $R_i = \infty$ $R_o = [r_o (1 + g_m R_E)]$ $A_{I,t} = \infty$ <p>Without degeneration: Simply set $R_S = 0$</p>	$A_{V,t} = \frac{R_L}{\frac{1}{g_m} + R_L}$ $R_i = \infty$ $R_o = \frac{1}{g_m}$ $A_{I,t} = \infty$	$A_{V,t} = g_m R_L$ $R_i = \frac{1}{g_m}$ $R_o = [r_o (1 + g_m R_E)]$ $A_{I,t} \approx 1$

For the gain, R_i , R_o of the whole amplifier, you need to include voltage/current dividers at input and output stages

Summary of MOS Single-Transistor Amplifiers

MOS	Common Source (CS)	Common Source with Deg.	Common Drain (CD)	Common Gate (CG)
R_i				Small
R_o	Large	Very Large	Small	Large
A_v	Moderate	Small	~ 1	Moderate
f_H	Small	Moderate	Large	Large

Single Stage Amplifier Cannot Meet All Requirements

- **For example, a general purpose operational amplifier requires**
 - High input resistance $\sim 1\text{M}\Omega$
 - Low output resistance $\sim 100\Omega$
 - High voltage gain $\sim 100,000$
- **No single transistor amplifier can satisfy all spec's**
- **Cascading multiple stages of amplifiers offers a path towards the design**

Multistage Amplifiers

- **Usually**
 - An input stage to provide required input resistance
 - Middle stage(s) to provide gain
 - An output stage to provide required output resistance or drive external loads
- **More gain !**
 - Gain/stage limited, especially in nanoscale devices
- **Improve Bandwidth**
 - De-couple high impedance nodes from large capacitors
- **DC coupling (no passive elements to block the signal)**
 - Use amplifiers to naturally “level shift” signal


Impedance “Match”

- On-chip circuits often use “voltage/current” matching to minimize loading
- Keep in mind the input resistance and output resistance of each type of stage so that the loading does not create an undesired effect

	Ideal R_{in}	Ideal R_{out}
Voltage Amplifier		0
Current Amplifier	0	
Transconductance Amplifier		
Transresistance Amplifier	0	0

Two-Stage Voltage Amplifier

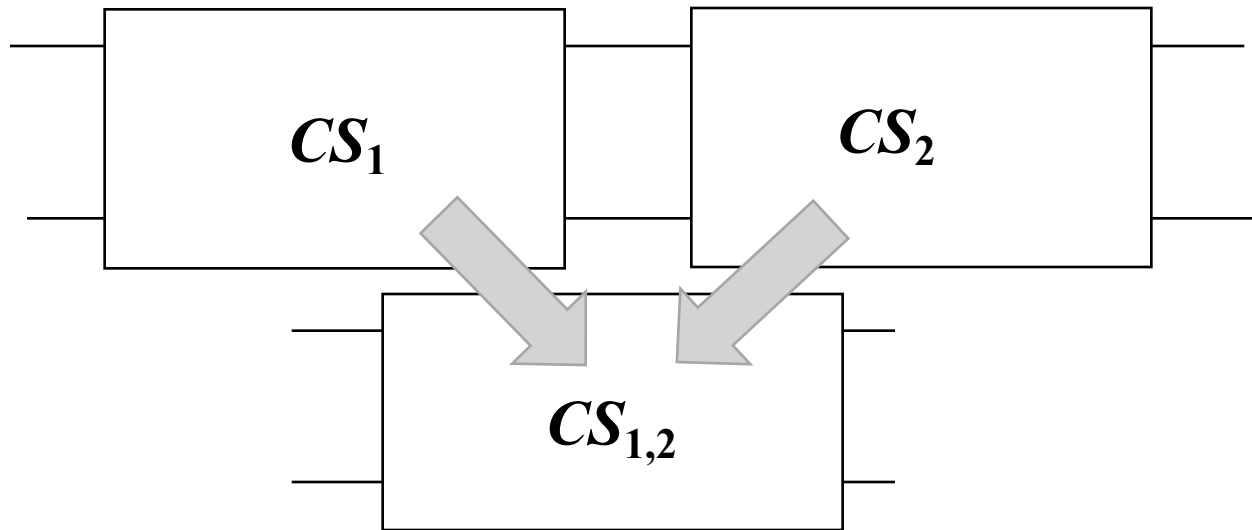
- Boost gain by cascading Common-Source stages



Can combine into a single 2-port model

Results of new 2-port: $R_{in} = R_{in1}$, $R_{out} = R_{out2}$

CS Cascade Analysis

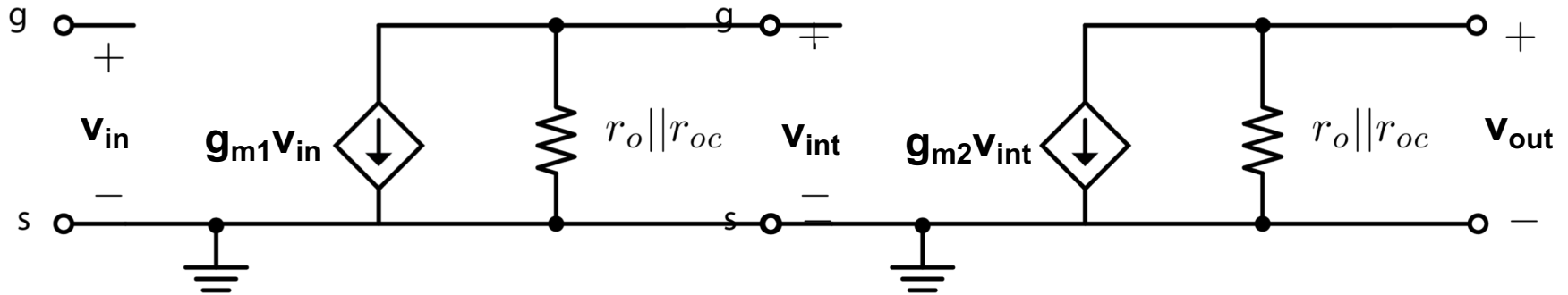


Results of new 2-port:

$$R_{in} = R_{in1} =$$

$$R_{out} = R_{out2} =$$

$$A_v = v_{out}/v_{in} =$$

CS Cascade Bandwidth

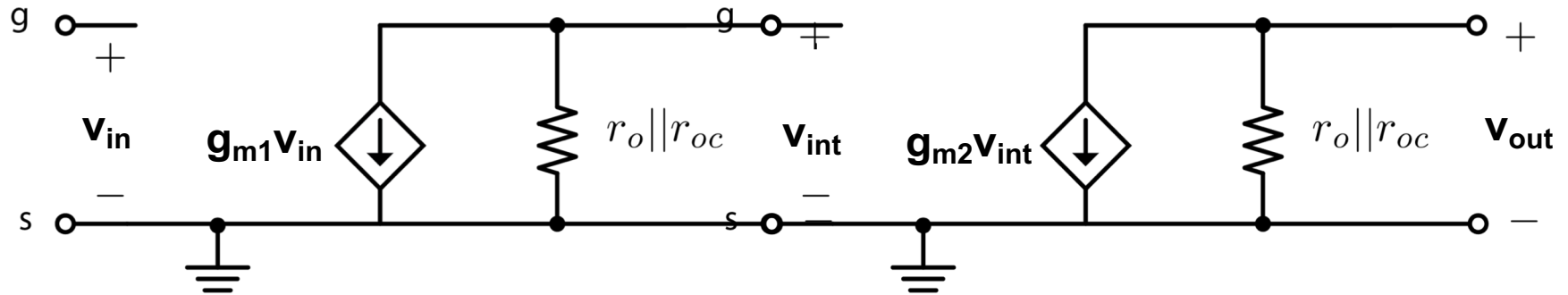

Two time constants:

$$\tau_1 =$$


$$\tau_2 =$$

Bandwidth Extension


- **Common Source stage has high gain, but low bandwidth**
- **Note that Miller effect is the culprit**
- **Follower stage can buffer source resistance from Miller cap**

Bandwidth Extension Using Source Follower (SF)

COMMON SOURCE

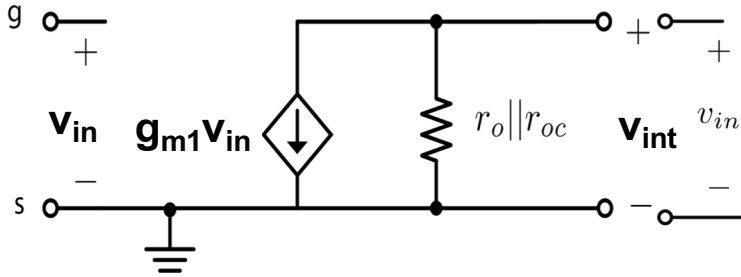

COMMON DRAIN

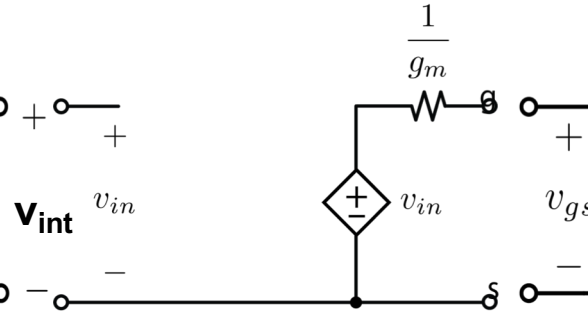

COMMON SOURCE

