
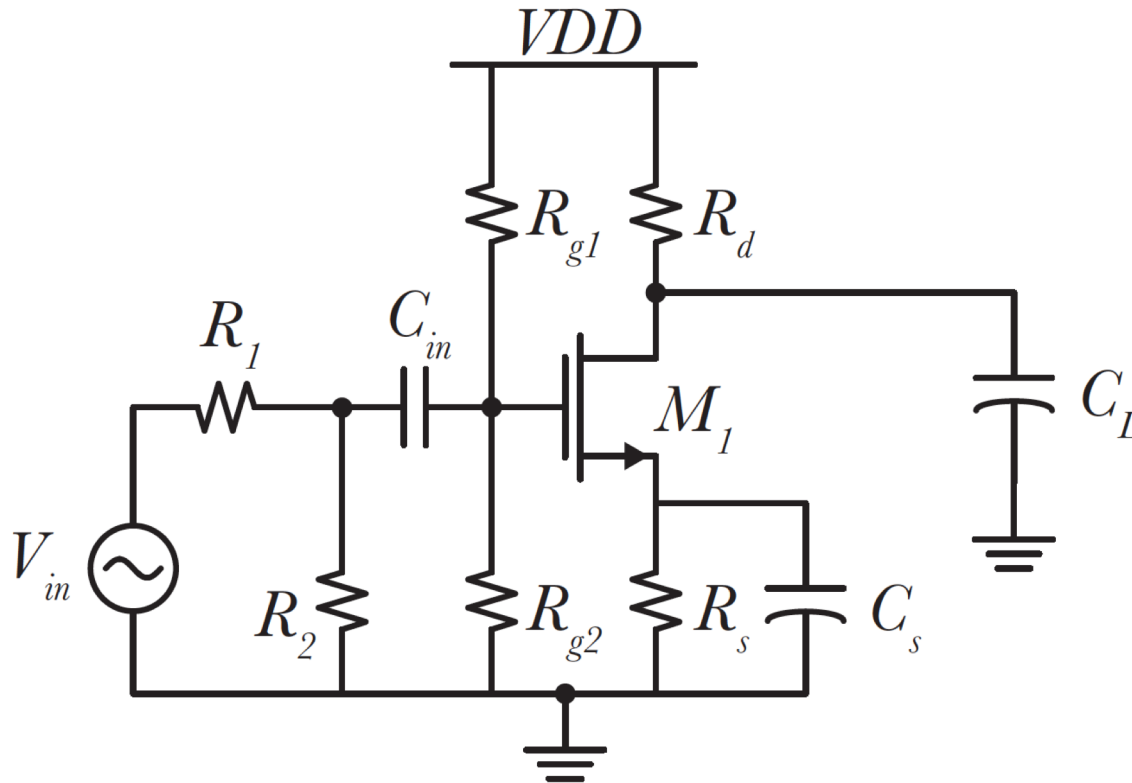


CS Example with Cap Load

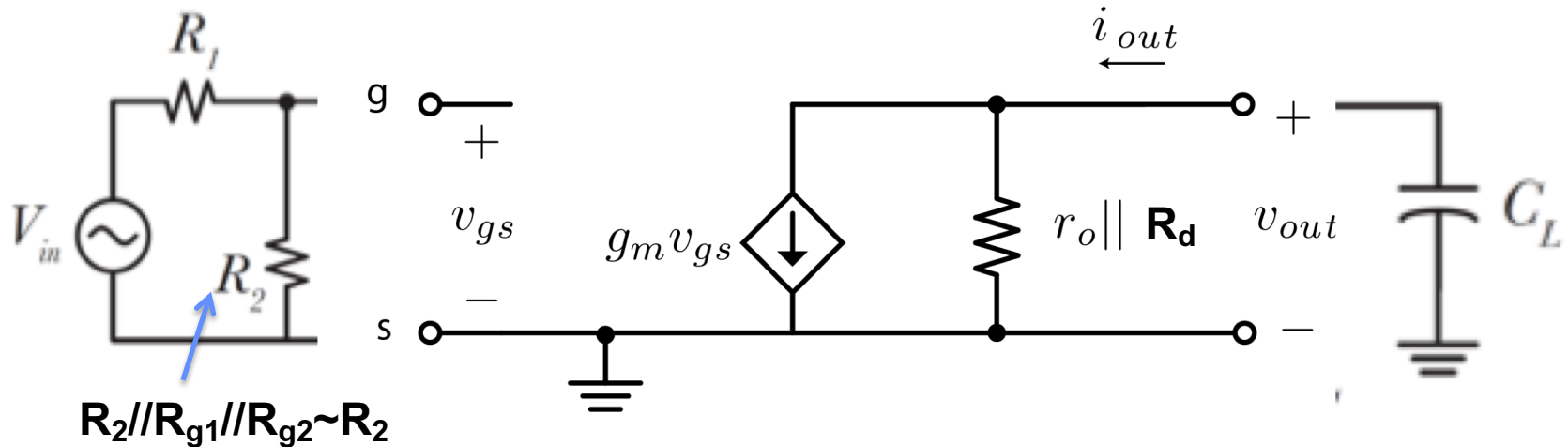


- C_{in} and C_s are very large, therefore they look like short circuits to the AC signal.
- If C_L is very large, its pole dominates, let's analyze

CS with Cap Load – Small Signal




- What are the time constants associated with the capacitors in this circuit?
- What can we do if we have to drive a large C_L ?

CS with Cap Load – Bandwidth

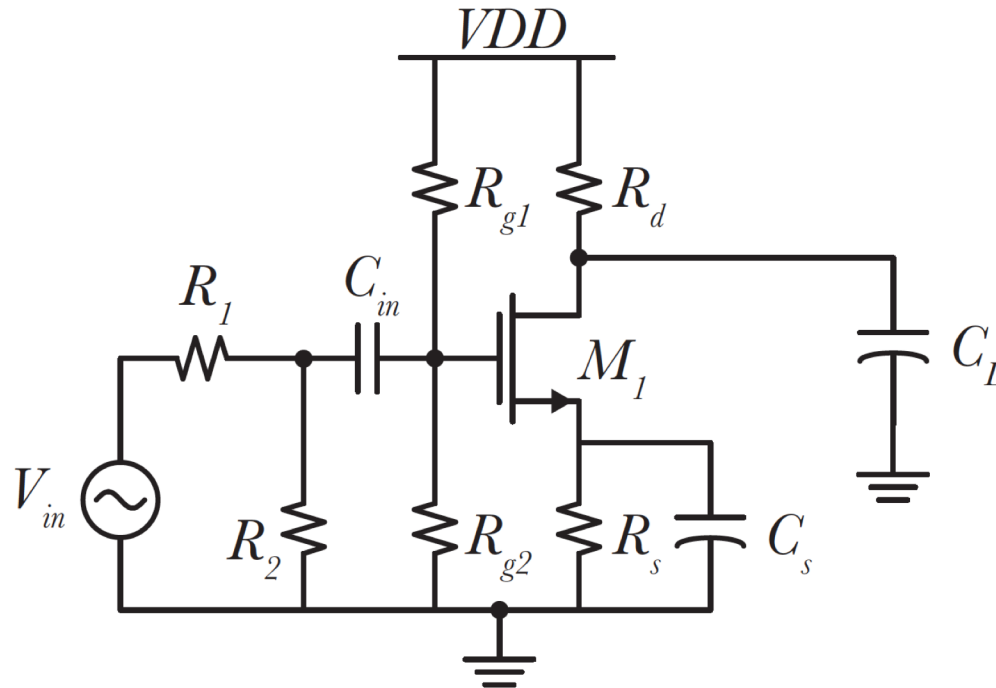


- How can we reduce the impact of C_L ?
- One way is to reduce the resistance R_d , but this reduces our low-frequency gain
- To recover the gain we can increase g_{m1} .
What does this cost us?

CS with Cap Load – BW Extension

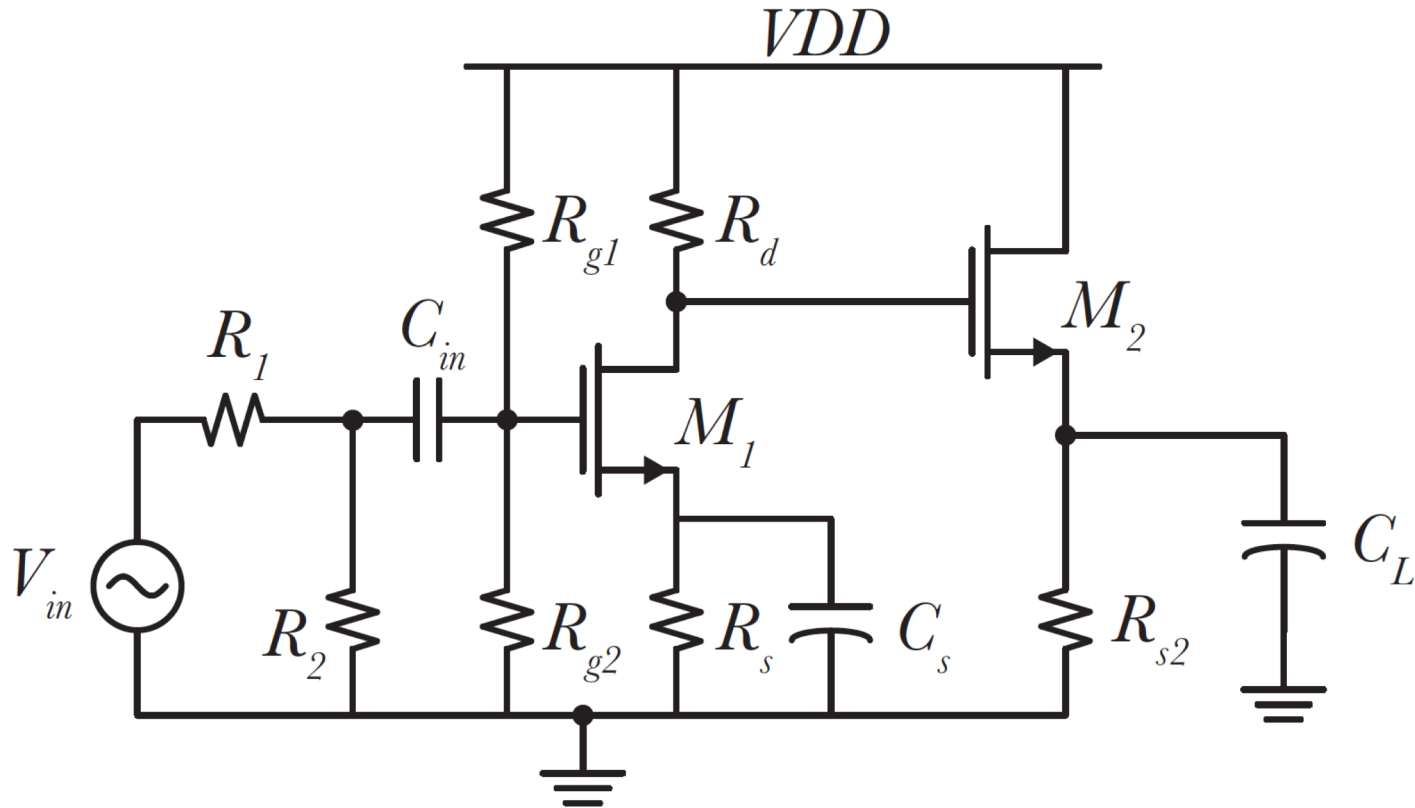

- A better way to extend the bandwidth is to add a source-follower stage.
- Similar to previous example


CS with Cap Load – BW Extension

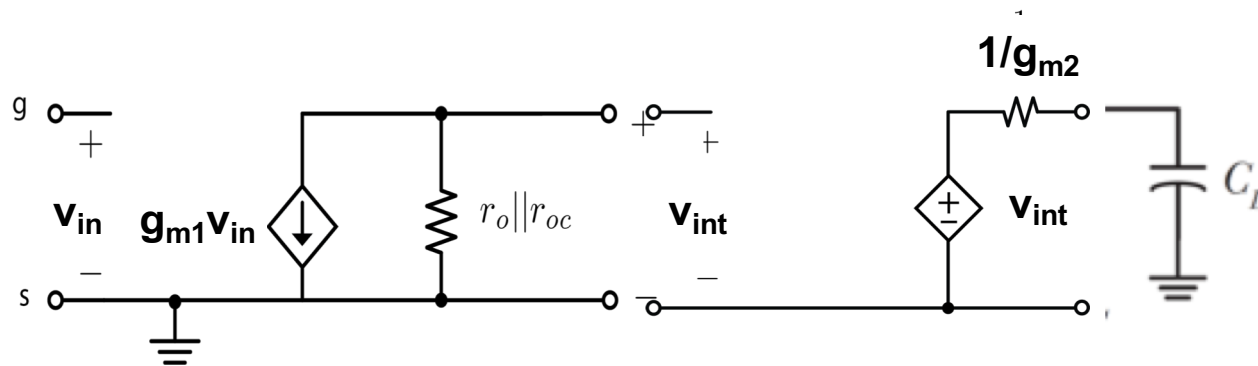

- By adding a CD (Source Follower) we can increase the bandwidth
- It costs us power for the CD stage
- Remember that increasing the BW by increasing g_{m1} costs us much more


CS + CG

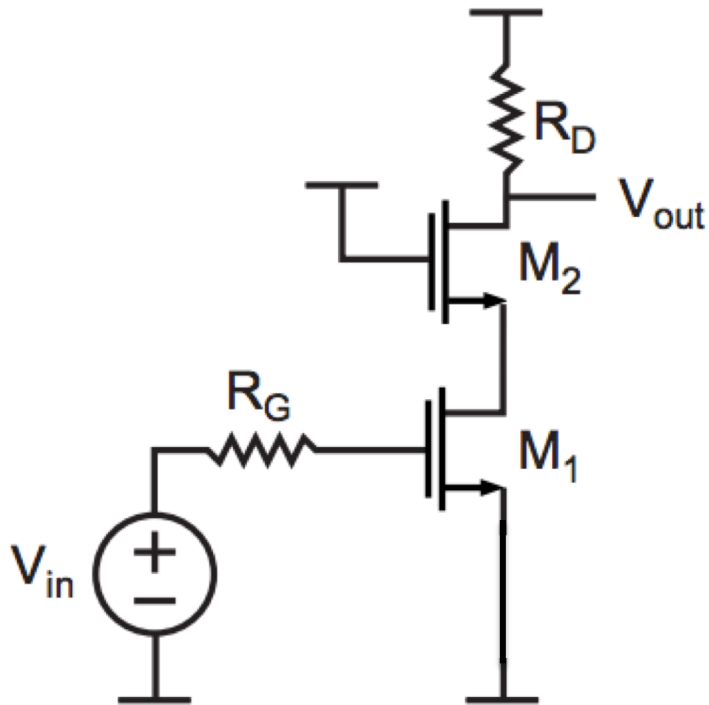- Common source provides gain, CG acts as a buffer, but is it even helping?
- How do you bias this circuit?



Merged CS + CG = Cascode

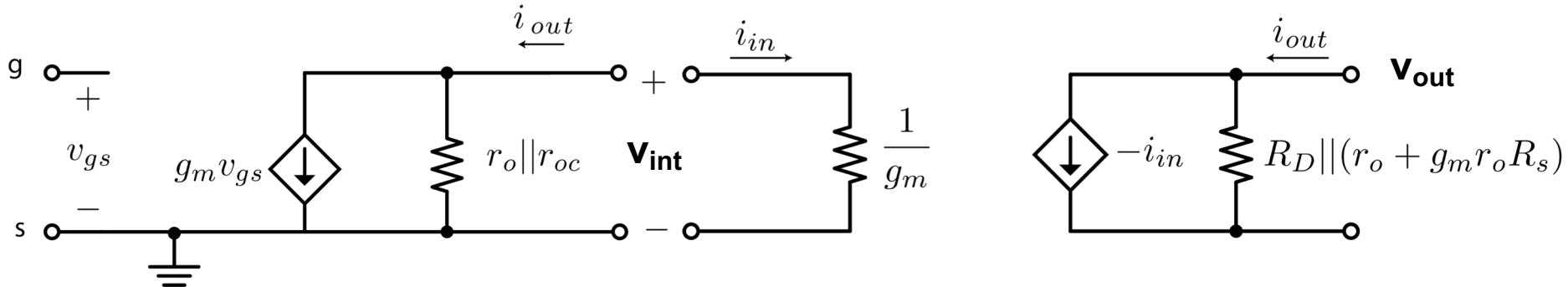
- Let's apply 2-port small-signal analysis



- In this case, we care about the *input current* to the second stage
- Note that the input resistance of the CG is low, therefore the majority of the CS current is fed to the CG
- $A_v =$


Cascode Bandwidth

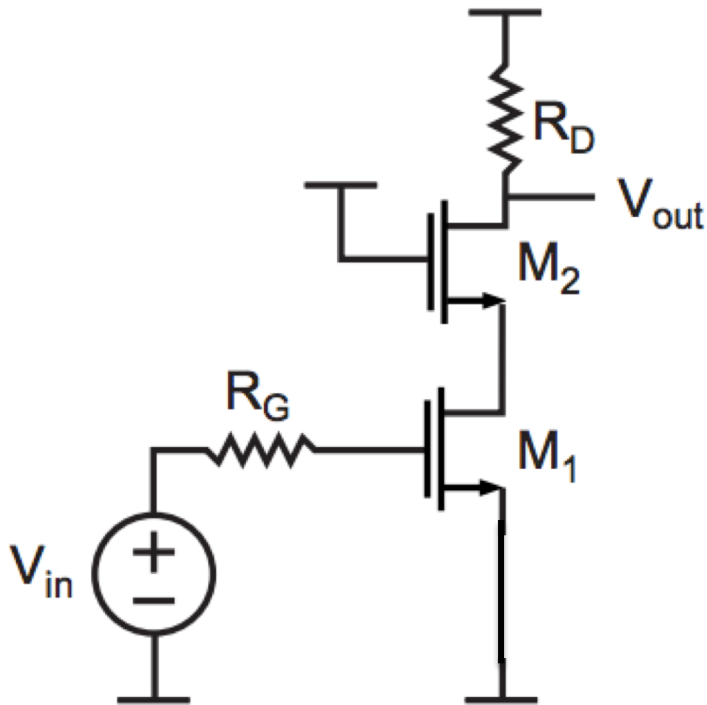- Draw in the C_{gs} and C_{gd} capacitors.
- Which ones are Miller effected?
- Is this better or worse than a CS without a CG?




Cascode Bandwidth

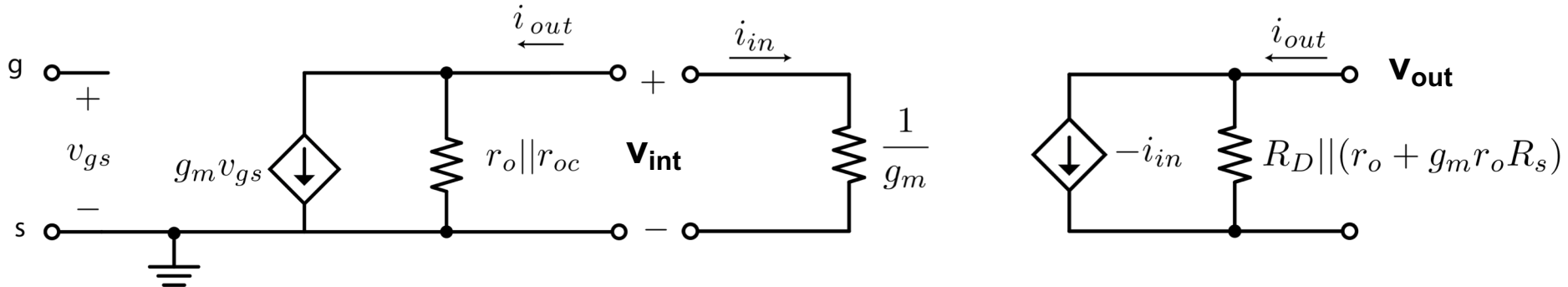- Draw in the capacitors and input resistance



Cascode Biasing

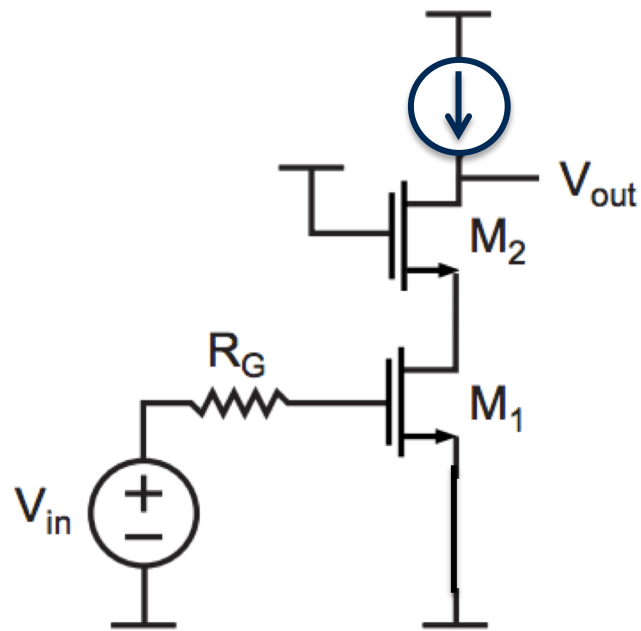- CG has a very large output resistance
- Loading it with R_D is likely to reduce the voltage gain
- We can increase the gain by using a current source load, but r_{oc} needs to be very large → Use a cascode current mirror!
- What is r_{oc} of cascode current mirror?



Cascode Design Problem

- Design goal:
 - Cascode amplifier with a gain of -5000 and $R_{out} = 5 \text{ M}\Omega$
- Transistor parameters
 - $k' = 100 \mu\text{A}/\text{V}^2$, $\lambda = 0.1 \text{ V}^{-1}$
- Find
 - Bias current
 - (W/L) of the transistors
(For simplicity, assume M_1 and M_2 are identical)
 - Voltage swing
 - Bias voltage at input

