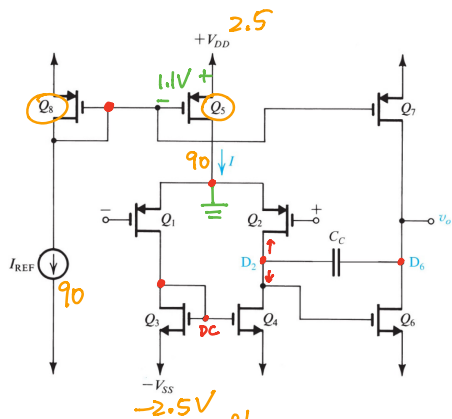


Q_3, Q_4 : active load
 \Rightarrow convert differential output to single-ended



	Q1	Q2	Q3	Q4
W/L in μm	20/0.8	20/0.8	5/0.8	5/0.8

	Q5	Q6	Q7	Q8
W/L in μm	40/0.8	10/0.8	40/0.8	40/0.8



$I_{REF} = 90 \mu A$, $V_{in} = 0.7V$, $V_{ip} = -0.8V$
 $\mu_n C_{ox} = 160 \mu A/V^2$, $\mu_p C_{ox} = 40 \mu A/V^2$ k_p'
 $|V_A| = 10V$ for all devices
 $V_{DD} = V_{SS} = 2.5V$

$|V_A| = \frac{1}{\lambda} \Rightarrow \lambda = 0.1 V^{-1}$

$I_1 = 45 \times 10^{-6} = \frac{1}{2} \times 40 \times 10^{-6} \left(\frac{20}{0.8}\right)^2 V_{ov1}^2$
 $V_{ov1}^2 = \frac{90 \times 0.8}{40 \times 20} = 0.09 \Rightarrow V_{ov1} = 0.3V$
 $V_{ov2} = 0.3V$
 $\left(\frac{W}{L}\right)_3 = \frac{1}{4} \left(\frac{W}{L}\right)_1$, $k_n' = 4 \times k_p'$
 $\Rightarrow V_{ov3} = V_{ov4} = 0.3V$
 $\left(\frac{W}{L}\right)_6 = 2 \left(\frac{W}{L}\right)_3$, $I_6 = 2 \times I_3$
 $\Rightarrow V_{ov6} = 0.3V$

Find I_D , $|V_{ov}|$, $|V_{GS}|$, g_m , r_o for all Q's,
voltage gain,
input common mode range,
output voltage range.

$\left(\frac{W}{L}\right)_7 = 2 \left(\frac{W}{L}\right)_1$, $I_7 = 2 \times I_1 \Rightarrow V_{ov7} = 0.3V$
 $V_{ov5} = V_{ov8} = 0.3V$
 $V_{GS3,4,6} = V_{ov} + V_{tn} = 0.3 + 0.7 = 1V$
 $|V_{GS1,2,5,7,8}| = |V_{ov}| + |V_{tp}| = 0.3 + 0.8 = 1.1V$

$A_{v1} = g_{m1} (r_{o2} // r_{o4})$

$A_v = -g_{m6} (r_{o6} // r_{o7})$

$g_{m1} = k_p V_{ov1} = k_p' \left(\frac{W}{L}\right)_1 V_{ov1} = 40 \times 10^{-6} \times \left(\frac{20}{0.8}\right) \cdot 0.3 = 0.3 \times 10^{-3}$

$g_{m6} = k_n V_{ov6} = 160 \times 10^{-6} \times \left(\frac{10}{0.8}\right) \cdot 0.3 = 0.6 \times 10^{-3}$

$r_{o2} = \frac{V_A}{I_2} = \frac{10}{45 \times 10^{-6}} = 220 \times 10^3$

$r_{o4} = 220 \times 10^3$

$r_{o6} = \frac{V_A}{I_6} = 110 \times 10^3 = r_{o7}$


$A_v = A_{v1} \cdot A_{v2} = \left(0.3 \times \frac{220}{2}\right) \times \left(-0.6 \frac{110}{2}\right) = -1.1 \times 10^3 \frac{V}{V}$

$20 \times \log |A_v| = 61 \text{ dB} \#$

$R_{out} = r_{o6} // r_{o7} = \frac{110 \text{ k}\Omega}{2} = 55 \text{ k}\Omega \#$

$D_2 \text{ node: } R_{D2} = r_{o2} // r_{o4} = 110 \text{ k}\Omega$

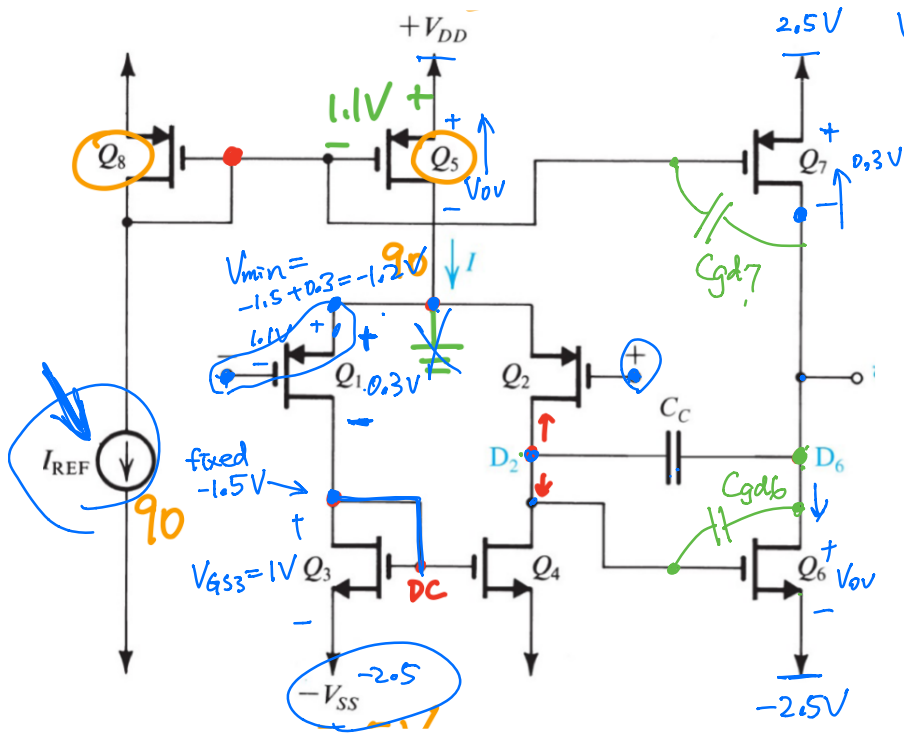$D_6 \text{ " : } R_{D6} = r_{o6} // r_{o7} = 55 \text{ k}\Omega$



$$V_{out, max} = 2.5 - 0.3 = 2.2V$$

$$V_{out, min} = -2.5V + 0.3 = -2.2V$$

Common Mode Input


$$V_{CM, max} = 2.5 - 0.3 - 1.1 = 1.1V$$

$$V_{CM, min} = -2.2 - 1.1 = -3.3V$$


$|V_{GS1}|$

Cap. at P6

$$C_6 = C_{gd7} + (C_{gd6} + C_c)$$

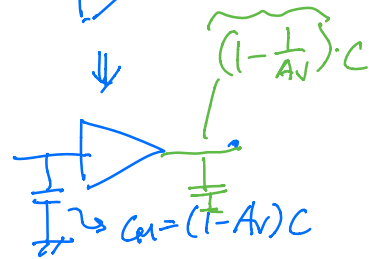


Cap at D2:

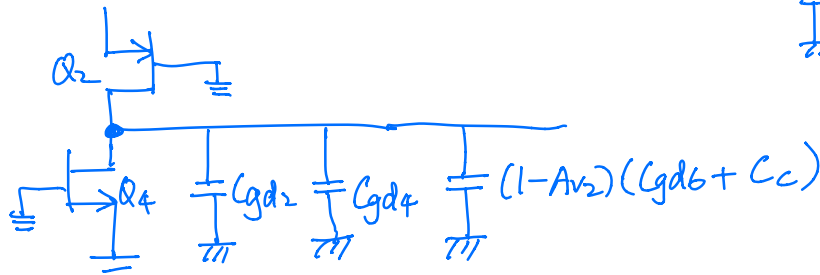

Dominant Pole is at D2

$$\tau \approx \tau_2 = (R_{o2} || R_{o4}) (C_{gd2} + C_{gd4} + (1 - A_{v2})(C_{gd6} + C_c))$$
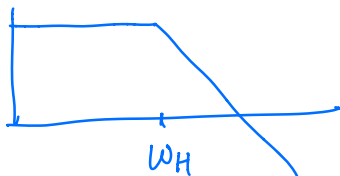
$$\omega_H = \frac{1}{\tau_2} \Rightarrow f_H = \frac{1}{2\pi} \omega_H$$



741 Op-Amp Circuit

