

* Linear time-invariant

Time response \longleftrightarrow Frequency Response
Fourier Transform


Phasor $I_D \rightarrow I_D e^{j\phi}$ ($= I_D e^{j\omega t + j\phi}$)

* Bode Plot

$$H(j\omega) = \frac{A (1 + j\omega \tau_1)}{B (1 + j\omega \tau_2)}$$

Pole $\omega_p = \frac{1}{\tau_2}$

Zero $\omega_z = \frac{1}{\tau_1}$

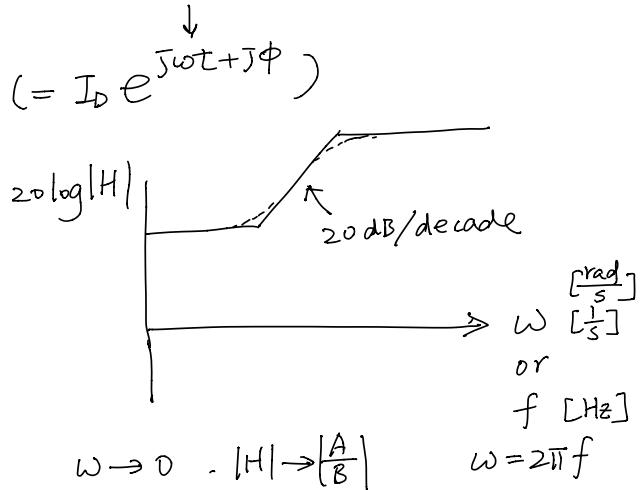

$$H(j\omega) = \frac{(j\omega \tau_1)}{(1 + j\omega \tau_2)}$$

$\omega \rightarrow 0 \quad H \rightarrow j\omega \tau_1$


e.g. $\omega_z > \omega_p$

$$\omega_z < \omega < \omega_p, |H| \rightarrow \left| \frac{A}{B} \right| \left| \frac{j\omega \tau_1}{1} \right|$$

$\omega_p < \omega$

$$|H| \rightarrow \left| \frac{A}{B} \right| \left| \frac{j\omega \tau_1}{j\omega \tau_2} \right|$$

$$= \left| \frac{A}{B} \right| \left(\frac{\tau_1}{\tau_2} \right)$$

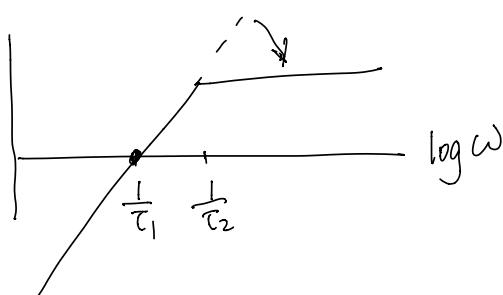


* Ideal Op-amp


* Non-Ideal Op-amp

$A_o < \infty$ Open-loop gain


ω_b Open-loop 3dB bandwidth

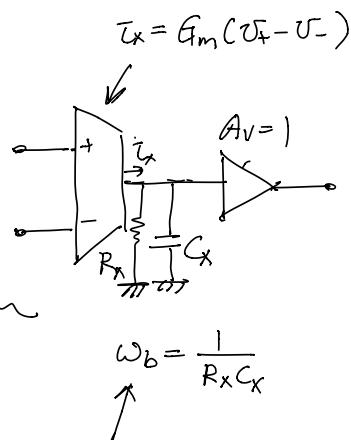$\omega_t = A_o \omega_b$ unity gain frequency



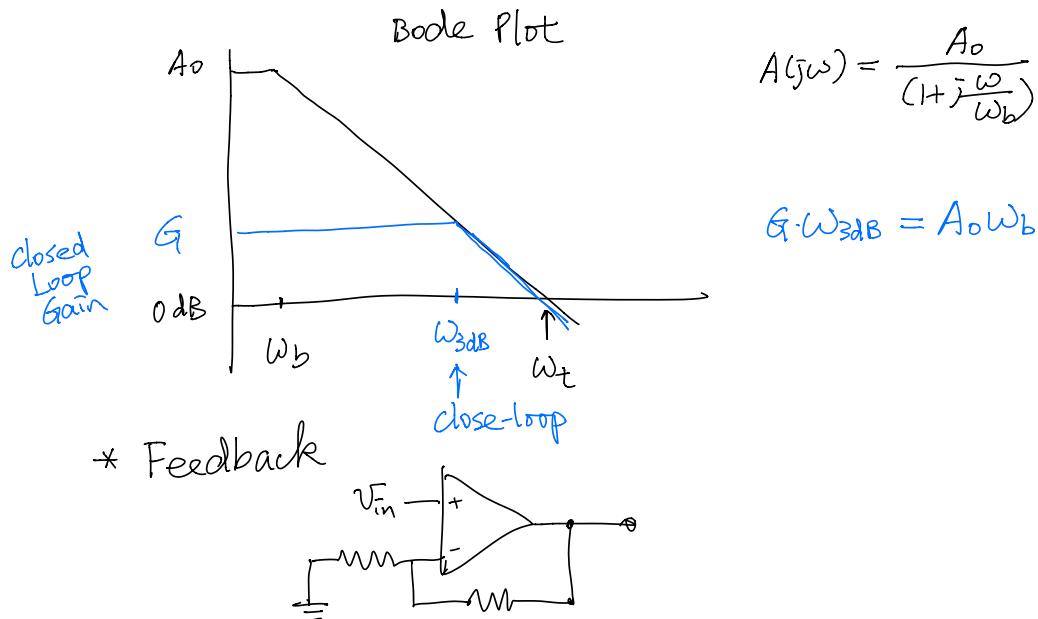

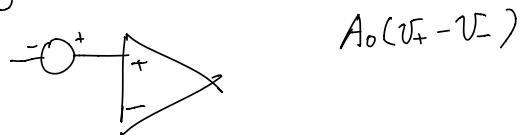* Offset voltage = Pay attention to polarity




$$V = \mu E$$

* Slew rate $V/\mu s$

$$\frac{cm}{s}/\mu s = \frac{cm^2}{s \cdot \mu s}$$

* Semiconductor = electron, hole

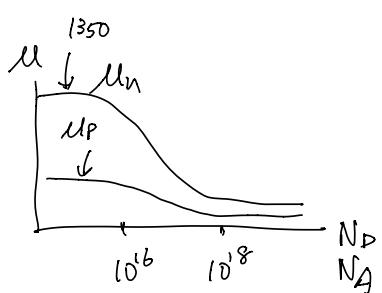Drift current $\left\{ \begin{array}{l} J = n q \mu_n \quad \text{for n-type} \\ J = p q \mu_p \quad \text{P-type} \end{array} \right.$



Diffusion current


$$J_p = -q D_p \frac{dp}{dx}$$



$$\frac{dp}{dx} < 0$$

$$J_n = q D_n \frac{dn}{dx}$$

* P-n junction \rightarrow Diode

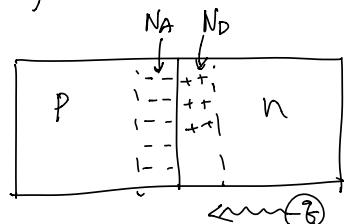

$$\leftarrow E \quad \check{\oplus} \rightarrow$$

$J_{p,\text{drift}} \leftarrow$ } cancel out at equilibrium, i.e. $V_{\text{Bias}} = 0$
 $J_{p,\text{diff}} \rightarrow$




$J_{n,\text{drift}} \leftarrow$ } cancel
 $J_{n,\text{diff}} \rightarrow$

Apply V_0

$$I_D = I_S (e^{\frac{V_D}{V_T}} - 1) \quad \text{Large-signal model}$$

* Rectifying circuit

$$\propto (1 - e^{-\frac{t}{RC}})$$

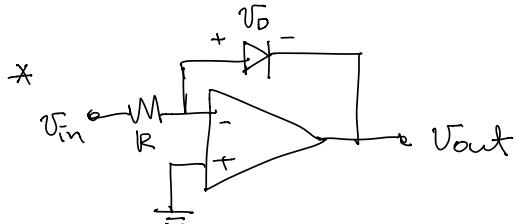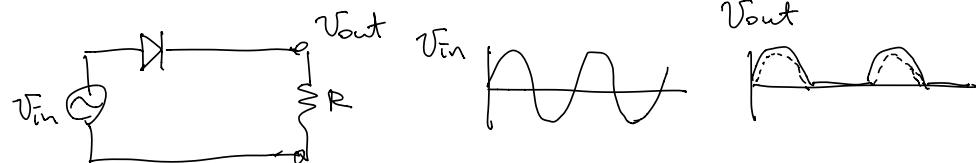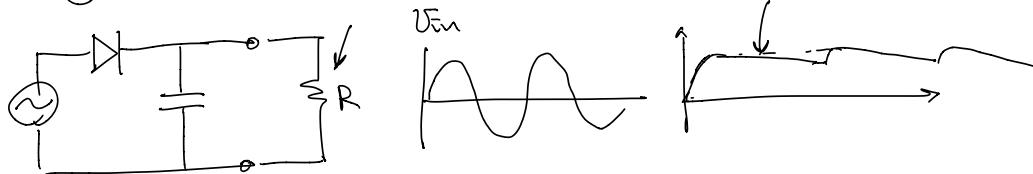

$$V_{\text{out}} = V_- - V_D = 0 - V_D = -V_D$$

||

V_T

||

0

$$I_D = I_S e^{\frac{V_D}{V_T}} = \frac{V_{\text{in}} - V_-}{R} = \frac{V_{\text{in}}}{R}$$



$$V_D = V_T \cdot \ln \frac{V_{\text{in}}}{I_S R}$$

$$V_{\text{out}} = -V_D = -V_T \ln \frac{V_{\text{in}}}{I_S R}$$

$H(j\omega)$




Bode

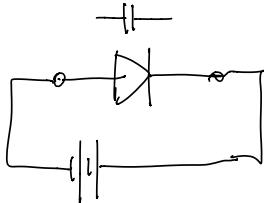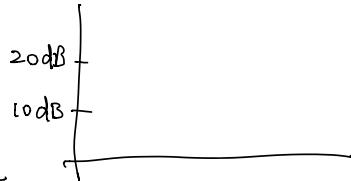

Reverse bias

$$I_D \rightarrow -I_S$$

$$C_{dep} = \frac{E_S \cdot A}{W} = \frac{C_0}{\sqrt{1 + \frac{|V_R|}{V_b}}}$$

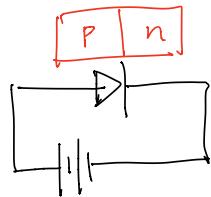

Forward bias

$$I_D = I_S e^{\frac{V_D}{V_T}}$$


2 capacitance

C_{dep}

C_{diff} (did not discuss)

\uparrow diffusion cap
= stored minority carriers

$$C_{dep} = \frac{E_S \cdot A}{W}$$

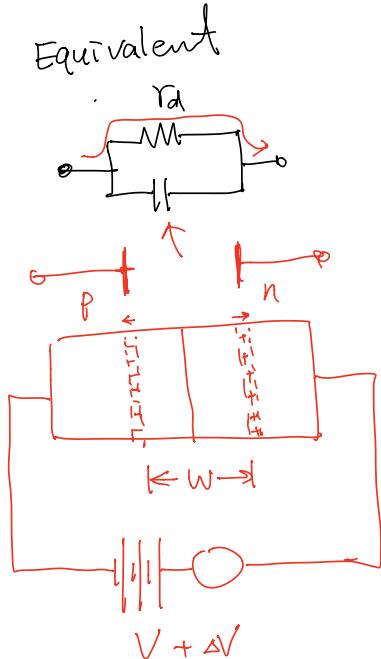

* Closed Book

2 pages

Calculator \rightarrow

$\times 3$ decimal
a few %

0.7

0.72

$$I \sim 1.1 \text{ mA}$$

$$1 \text{ mA}$$

$$1 + \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 100$$

$$1.0875$$

$$e^{\frac{2E}{V_F}}$$