

1. a)  $R_{out} = r_{o1} + r_{o2} + g_{m1} r_{o1} r_{o2}$

The "turn on" voltage is when the two right transistors are in saturation region.

It's set by  $V_{G4}$

$$\begin{aligned} V_{G4} &= V_{G3} + V_T + V_{DSAT} \\ &= 2(V_T + V_{DSAT}) \end{aligned}$$

$$\begin{aligned} V_{S2} &= V_{G2} - V_T - V_{DSAT} \\ &= V_{G4} - V_T - V_{DSAT} \\ &= V_T + V_{DSAT} \end{aligned}$$

$$\begin{aligned} V_{out} = V_{D2} &= V_{S2} + V_{DSAT} \quad (EOS) \\ &= V_T + 2V_{DSAT} = V_{min} \quad (\text{turn on voltage}) \end{aligned}$$

To find  $V_{DSAT}$ :

$$M3\&4: \frac{1}{2} k' \left(\frac{W}{L}\right) V_{DSAT}^2 \cdot (1 + \lambda(V_{DSAT} + V_T)) = 1 \text{ mA}$$

$$\therefore V_{DSAT} = 0.30423 \text{ V} \approx 0.304 \text{ V}$$

$$\therefore V_{min} = 1.108 \text{ V}$$

$$r_{o1} = \frac{1 + \lambda V_{DS1}}{\lambda I} = \frac{1 + \lambda(V_T + V_{DSAT})}{\lambda I} \doteq 10.8 \text{ k}\Omega$$

$$r_{o2} = \frac{1 + \lambda V_{DS2}}{\lambda I} = \frac{1 + \lambda(V_{DSAT} + V_T)}{\lambda I} \doteq 10.8 \text{ k}\Omega$$

$$g_{m1} = \frac{2I}{V_{DSAT}(1 + \lambda V_{DS})} \doteq 6.1 \text{ mS}$$

$$\begin{aligned} \therefore R_{out} &= g_{m1} r_{o1} r_{o2} + r_{o1} + r_{o2} \\ &= 732 \text{ k}\Omega \end{aligned}$$

Note: if you guys use  $r_o = \frac{1}{\lambda I}$ ,  $g_m = \frac{2I}{V_{DSAT}}$ ,  
you will end up with  $R_{out} = 678 \text{ k}\Omega$

(b) see SPICE deck and plots.

2. a)  $V_{BN}$  sets the source voltage of  $M_2$  and the drain voltage of  $M_1$ , so  $V_{BN}$  determines  $M_1$  in saturation region or not.

$$V_{D1} = V_{DSAT} \quad (\text{EOS of } M_1)$$

$$\begin{aligned} V_{BN, \min} &= V_{D1} + V_T + V_{DSAT} \\ &= 2V_{DSAT} + V_T \\ &= 1.108 \text{ V} \end{aligned}$$

Turn on voltage makes sure  $M_1$  &  $M_2$  are in saturation region.

$$\begin{aligned} V_{o, \min} &= V_{DSAT1} + V_{DSAT2} \\ &= 2V_{DSAT} \\ &= 0.608 \text{ V} \end{aligned}$$

$$R_{out} = r_{o1} + r_{o2} + g_{m1} r_{o1} r_{o2} \quad \text{the same as prob. 1}$$

b) see SPICE deck and plots.


$$r_o = \frac{1}{\lambda [I(\text{out}_2) - I(\text{out}_1)]} \quad \text{use expression builder}$$

c) cascode mirror w/  $V_{BN}$  is best.

Simulation should give very close results.

	$R_{out}$	$V_{o,min}$
Cascode Mirror	732 k $\Omega$	1.108V
Cascode Mirror w/ VBN	732 k $\Omega$	0.608V

3.

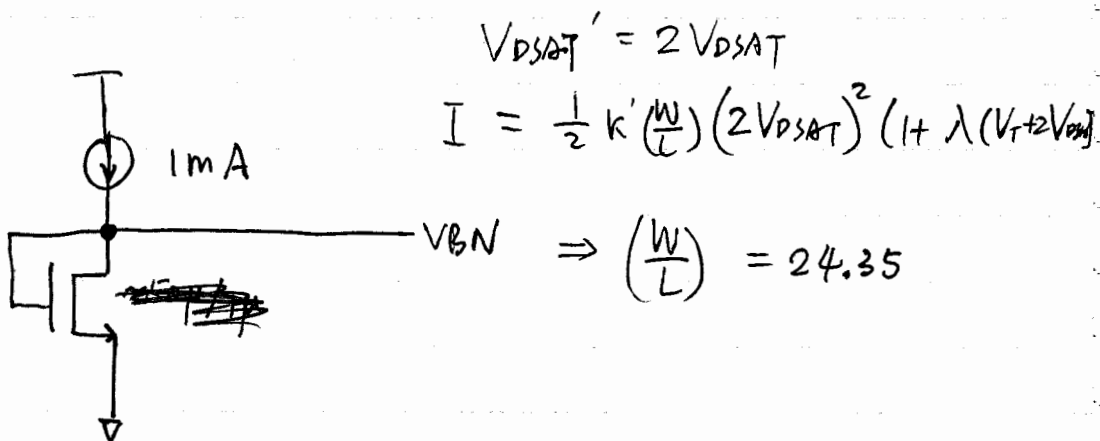

$$V_{DSAT}' = 2V_{DSAT}$$

$$I = \frac{1}{2} k' \left(\frac{W}{L}\right) (2V_{DSAT})^2 (1 + \lambda(V_T + 2V_{DSAT}'))$$

$$\Rightarrow \left(\frac{W}{L}\right) = 24.35$$

To verify, put this into SPICE and it works fine.

4. Assume  $g_m r_o \gg 1$ .

$$a) \frac{v_o}{v_i} = -(g_{m1} r_{o1} r_{o2} \parallel R_L) g_{m1} \quad (\text{cascode})$$

$$\frac{v_c}{v_i} = -g_{m1} R_{out}$$

$$= -g_{m1} \left( r_o \parallel \frac{R_L}{R_L \parallel r_o} \cdot \frac{1}{g_{m2}} \right) \quad (\text{CS})$$

$$\frac{v_o}{v_{BN}} = \text{CS w/ source degeneration}$$

$$\frac{v_o}{v_{BN}} = R_{out} \cdot G_m$$

$$= \left( [r_{o1} + r_{o2}(1 + g_{m2}r_{o1})] \parallel R_L \right) \cdot \frac{-g_{m2}}{1 + g_{m2}r_{o1}}$$

$$\frac{v_c}{v_{BN}} = \frac{g_{m2}}{1 + \frac{R_L}{r_o}} \left( r_{o1} \parallel \frac{R_L \cdot \frac{1}{g_m}}{R_L \parallel r_{o2}} \right) \quad \text{CD}$$

b)  $R_L = r_o$ .  $g_m = \frac{2I}{V_{DSAT}} \doteq 6.3 \text{ mS}$ ,  $r_o \doteq 10 \text{ k}\Omega$

$$\therefore \frac{v_o}{v_i} = -g_m (r_o \parallel g_m r_o^2) = -g_m r_o = -63$$

$$\frac{v_c}{v_{BN}} = -g_m \left( r_o \parallel \frac{r_o}{r_o \parallel r_o} \frac{1}{g_m} \right)$$

$$\approx -g_m \left( r_o \parallel \frac{2}{g_m} \right) \approx -g_m \cdot \frac{2}{g_m} = -2$$

$$\frac{v_o}{v_{BN}} \approx r_o \cdot \frac{-g_{m2}}{1 + g_{m2}r_{o1}} \approx -1$$

$$\frac{v_c}{v_{BN}} = \frac{g_m}{1 + \frac{r_o}{r_o}} \cdot \left( r_o \parallel \frac{r_o}{r_o \parallel r_o} \frac{1}{g_m} \right) \approx 1$$

Note: Assume  $g_m r_o \gg 1$  approximation.

c)  $R_L = g_m r_o^2$

$$\frac{v_o}{v_i} = -g_m (g_m r_o^2 \parallel g_m r_o^2) = -\frac{1}{2} g_m^2 r_o^2 = -1984.5$$

$$\frac{v_c}{v_i} = -g_m \cdot \left( r_o \parallel \frac{g_m r_o^2 / g_m}{r_o} \right) = -\frac{1}{2} g_m r_o = -31.5$$

$$\frac{v_o}{v_{in}} = \frac{g_m r_o^2}{2} \cdot \frac{-g_m}{1 + g_m r_o} \doteq -\frac{1}{2} g_m r_o = -31.5$$

$$\frac{v_c}{v_{in}} = \frac{g_m}{1 + g_m r_o} \cdot (r_o \parallel r_o) \doteq \frac{1}{r_o} \cdot \frac{r_o}{2} \doteq \frac{1}{2}$$

5. open end design problem, no solution.