PROBLEM SET #12

Issued: Tuesday, April 26^h, 2011

Due: Tuesday, May 3rd, 2011, 5:00 p.m. in the EE 140 homework box in 240 Cory

- 1. The ac schematic of a shunt-shunt feedback amplifier is shown in Fig. PS12.1. ("ac schematic" means that biasing is not shown, but that you should assume that all devices are biased appropriately.) All transistors have $I_D = 1$ mA, W/L = 100, $k' = 60 \mu A/V^2$, and $\lambda = 1/(50 \text{ V})$.
 - a. Calculate the overall gain v_o/i_i , the loop transmission, the input impedance, and the output impedance at low frequencies.
 - b. If the circuit is fed from a source resistance of $1 \text{ k}\Omega$ in parallel with i_i , what is the new output resistance of the circuit?



Fig. PS12.1

2. Assume the BiCMOS amplifier of Fig. PS12.2 is fed from a current source. Calculate the low-frequency small-signal transresistance v_o/i_i , the loop gain, and the input and output impedances of the circuit. Use the following parameters in your calculation: $I_S = 10^{-16}$ A, $\beta_F = 100$, $r_b = 0$, $V_A \rightarrow \infty$, $\mu_n C_{ox} = 200 \mu$ A/V², $V_t = 0.6$ V, and $\lambda = 0$.



Fig. PS12.2

3. A CMOS feedback amplifier is shown in Fig. PS12.3. If the dc input voltage is zero, calculate the overall voltage gain v_o/v_i and the output resistance. Compare your answer with a SPICE simulation. Use the following:

 $\mu_n C_{ox} = 60 \ \mu A/V^2, \ \mu_p C_{ox} = 30 \ \mu A/V^2, \ V_{tn} = 0.8 \ V, \ V_{tp} = -0.8 \ V, \ \lambda_n = |\lambda_p| = 0.03 \ V^{-1}, \ \text{and} \ \gamma_n = \gamma_p = 0.$



Fig. PS12.3