
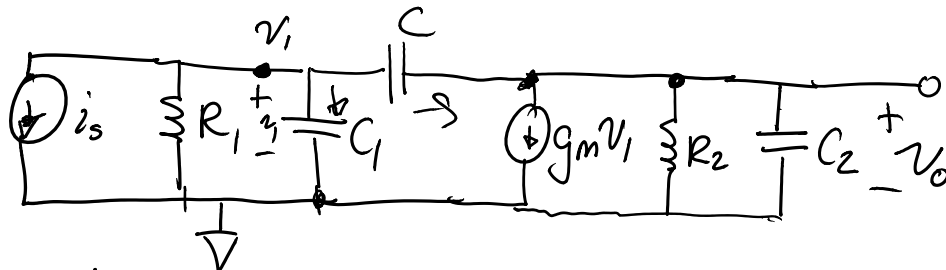


Pole Splitting

- G_m, R_1

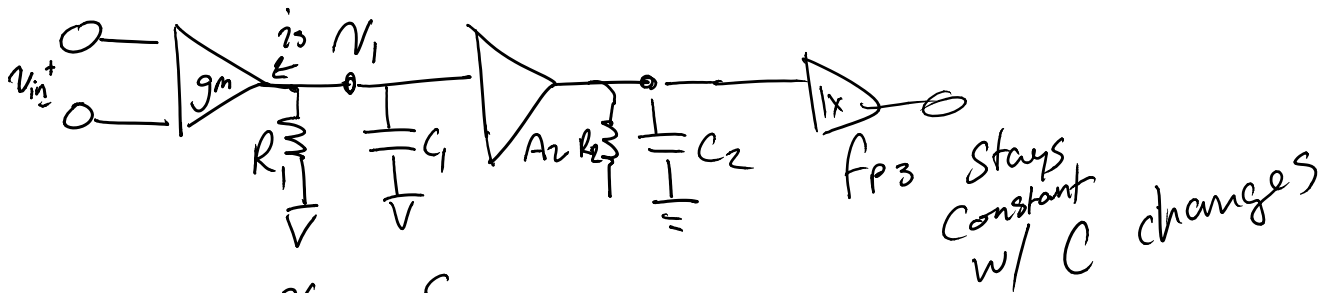

$$\frac{1}{\frac{1}{sC}} = \frac{1}{sC}$$

$$-i_s = \frac{v_1}{R_1} + v_1 C_1 s + (v_1 - v_0) \cdot C s$$

$$g_m v_1 + \frac{v_0}{R_2} + v_0 C_2 s + (v_0 - v_1) \cdot C s$$

$$\frac{v_0}{i_s} = \frac{(g_m - C s) R_2 R_1}{1 + s[(C_2 + C) R_2 + (C_1 + C) R_1 + g_m R_2 R_1 C] + s^2 R_2 R_1 (C_2 C_1 + C C_2 + C C_1)}$$

Zero @ g_m/C Pg. 640 of GNM

assume a two pole system

$$A(s) = \frac{A_0}{(1 - s/p_1)(1 - s/p_2)}$$

denom: does not look like this

$$D(s) = (1 - s/p_1)(1 - s/p_2)$$

$$= 1 - s/p_1 - s/p_2 + s^2$$

$$P_1, P_2, \overline{P_1 P_2}$$

assume $P_1 \ll P_2$

$$D(s) \approx \left[1 - \frac{s}{P_1} + \frac{s^2}{P_1 P_2} \right] \quad \Rightarrow P_2 = \frac{s^2}{P_1}$$

$$P_1 = \frac{-1}{(C_2 + C)R_2 + (C_1 + C)R_1 + g_m R_2 R_1 C}$$

this term is the biggest

$$P_1 = - \frac{1}{g_m R_2 R_1 C}$$

gain of 2nd stage

the same as miller multiplication

$$\frac{1}{RC} \rightarrow \frac{1}{R_1 C_m} = \frac{1}{R_1 C \cdot g_m R_2}$$

Now look @ P_2

$$P_2 = - \frac{g_m C}{C_2 C_1 + C(C_2 + C_1)}$$

increasing C will increase the pole

$$\frac{s^2 R_2 R_1 (C_2 C_1 + C C_2 + C C_1)}{P_1} = P_2$$

$$P_2 = - \frac{1}{\tau}$$

$$R_o \cdot C_T$$

↑ output resistance w/ negative feedback from C

C_T is total cap from V_o to gnd (through C)

$$R_o = \frac{R_2}{1 + T} \Rightarrow$$

$$T = g_m R_2 f$$

Open Loop


$$\text{Gain} = G_m R_{out}$$

open Loop

$$R = R_{out}$$

$$\text{Closed Loop Gain} = \frac{G_m R_{out}}{1 + G_m R_{out} f}$$
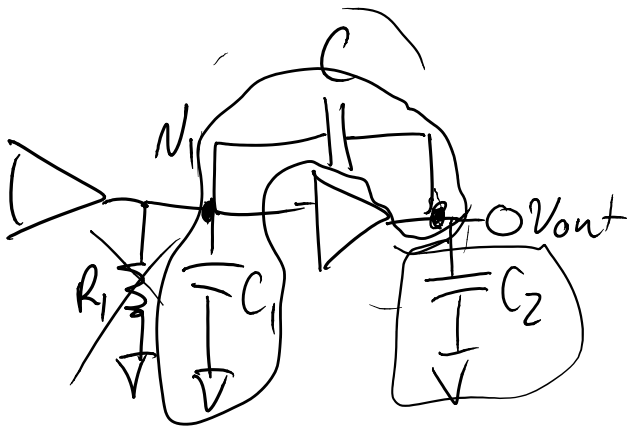
$$\text{Closed Loop } R = \frac{R_{out}}{1 + G_m R_{out} f}$$



how does V_{out} feedback to V_1

(a) HF $Z_{C1} \ll Z_{R1}$



$$f = \frac{C}{C + C_1}$$

$$R_o = \frac{R_2}{1 + \underbrace{g_m R_2 f}_{\text{Large}}} \approx \frac{1}{g_m f} = \boxed{\frac{C + C_1}{g_m C} = R_o}$$

$$R_o = \frac{K_2}{1 + \underbrace{g_m R_2 f}_{\text{Large}}} \approx \frac{1}{g_m f} = \boxed{\frac{C + C_1}{g_m C} = R_o}$$

$$C_T = C_2 + \frac{C \cdot C_1}{C + C_1} = \frac{C C_2 + C R_2 + C C_1}{C + C_1}$$
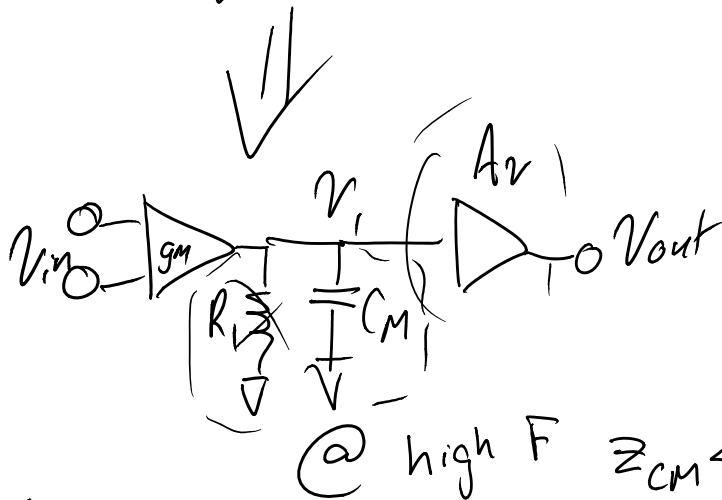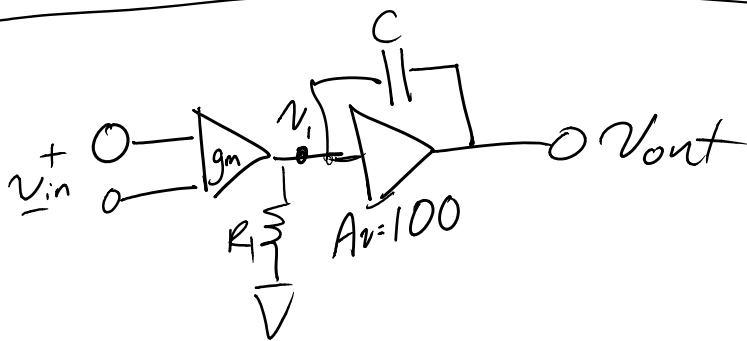
$$P_2 = -\frac{1}{R_o C_T} = \boxed{\frac{-g_m C}{C_2 C_1 + C(C_1 + C_2)}}$$



Approach:

- ① find open loop TF
- ② solve for ω_x where $|TF| = \frac{1}{f} : \omega_x$
- ③ plug ω_x into CL eqn $\frac{a(s)}{1 + a(s) \cdot f}$ and take magnitude @ ω_x

$$\frac{v_1}{v_{in}} = -\frac{g_m}{s C_M}$$

$$v_o = A_v v_1$$

$$v_1 \quad \overline{(1 - \frac{s}{\omega_2})}$$

$$C_m = A_v \cdot C$$

$$a(s) = \frac{v_{out}}{v_{in}} = \frac{-g_m A_v}{s \cdot A_v C (1 - s/\omega_2)} = \frac{-1}{\frac{sC}{g_m} (1 - s/\omega_2)}$$

$$\approx \frac{1}{(1 - \frac{sC}{g_m})(1 - s/\omega_2)}$$

$$\text{set } |a(s)| = \frac{1}{f} \quad \approx 1 @ \text{ GX freq.}$$

$$f|a(s)| = 1$$

↑ find freq that satisfies this

$$|a(s)| = \frac{1}{f}, \quad \angle(a(s)) = ?$$

$$|A(\omega_x)| = \left| \frac{a(s)}{1 + a(s)f} \right| = \left| \frac{\frac{1}{f} \angle ?}{1 + 1 \angle ?} \right| \left(\frac{1}{f} \cdot \text{factor} \right)$$

10.

Max
amplitude

