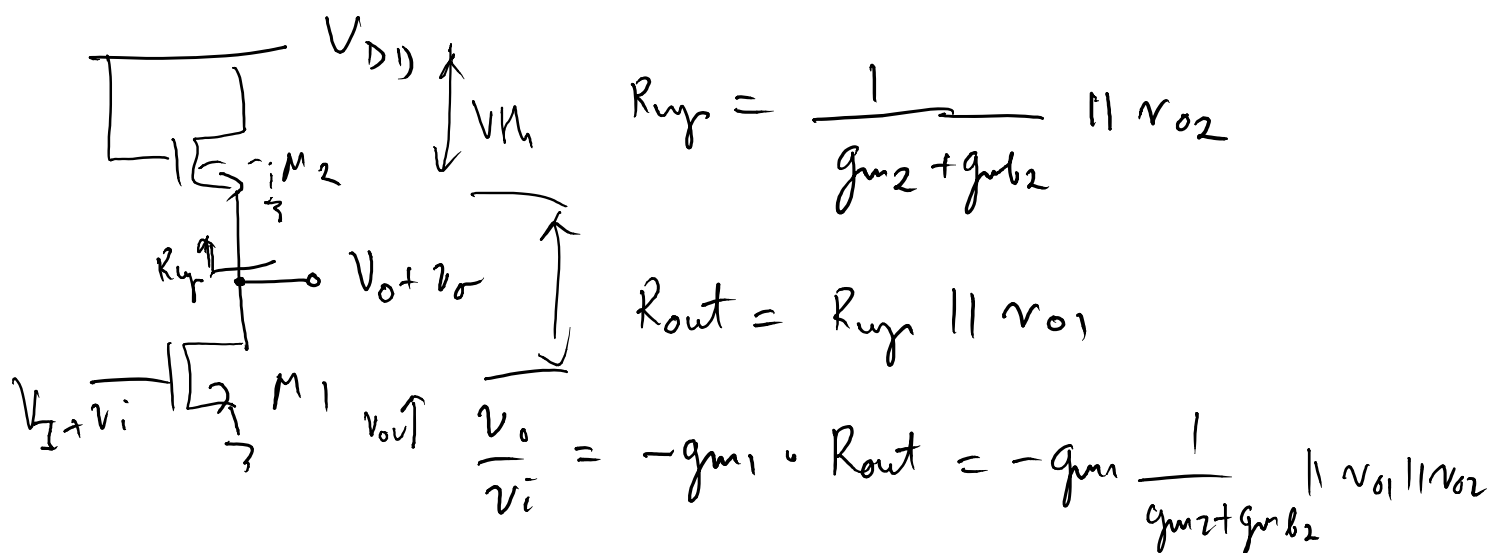


Active loads:C's with active diode load:

If $g_{mb2} = 0$
 $\frac{v_o}{v_i} \approx - \frac{g_{m1}}{g_{m2}} = - \sqrt{\frac{(\frac{W}{L})_1}{(\frac{W}{L})_2}}$


Conditions DC point:

M_2 saturation : $v_O < V_{DD} - V_{th}$

M_1 saturation : $v_I > V_{th}$

$v_O > v_I - V_{th} = v_{ov}$

b)

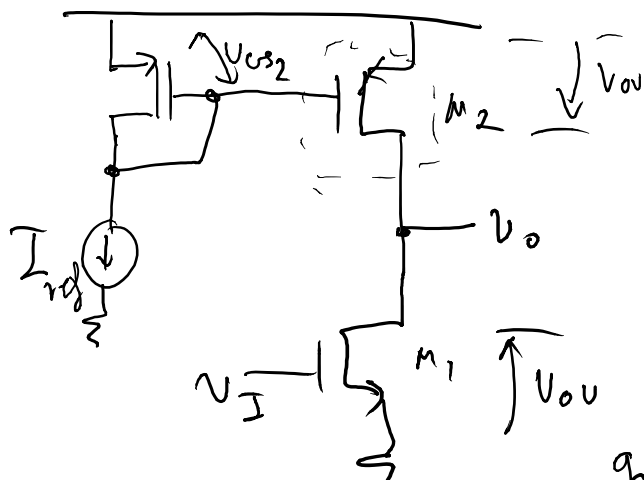

$$R_{out} = r_{o1} \parallel r_{o2}$$


$$\frac{v_o}{v_i} = -g_{m1} \cdot R_{out} = -g_{m1} \underbrace{r_{o1} \parallel r_{o2}}_{r_o}$$

$$g_m \sim \sqrt{I_D}, \quad r_o \sim \frac{1}{I_D}$$


BJTs:






$$\left. \begin{array}{l} g_m \sim I_c \\ r_o \sim \frac{1}{I_c} \end{array} \right\} g_m r_o \sim \text{cte.} \quad (1000)$$
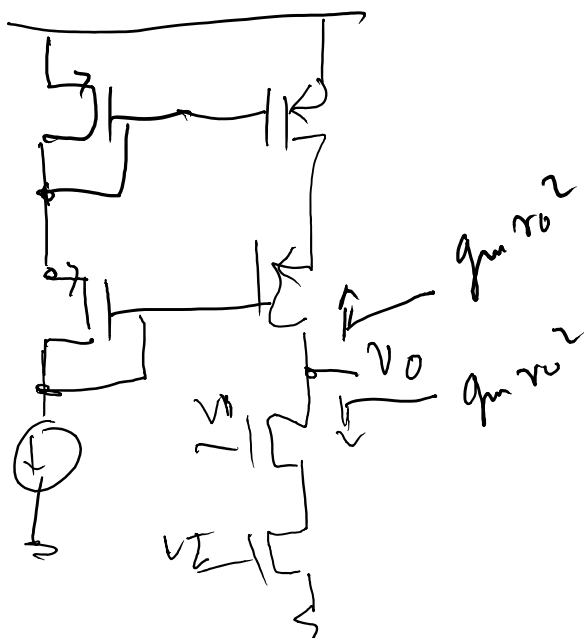
$$\frac{v_o}{v_i} \sim \frac{1}{\sqrt{I_D}} \quad (5-100)$$



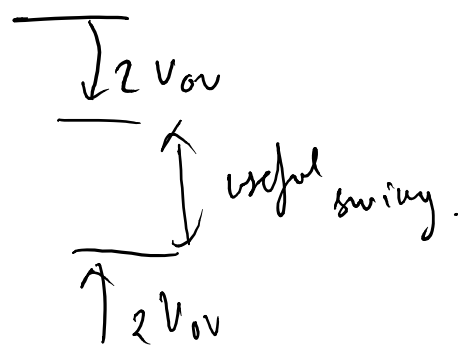
$$A_v = -g_m \cdot \left(\frac{g_m r_o^2}{2} \right) = -\frac{(g_m r_o)^2}{2}$$



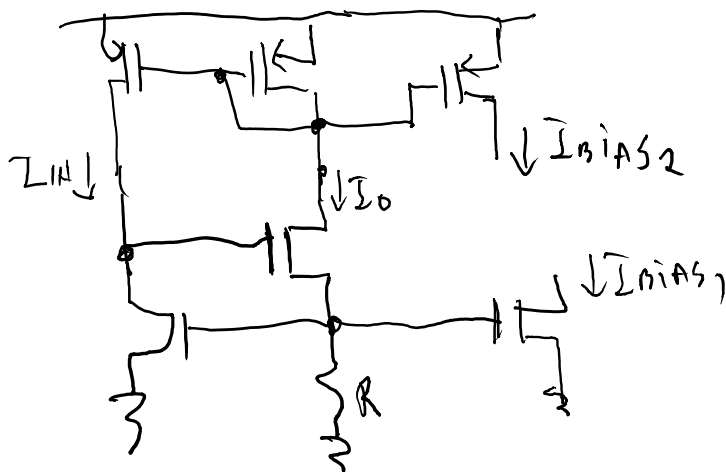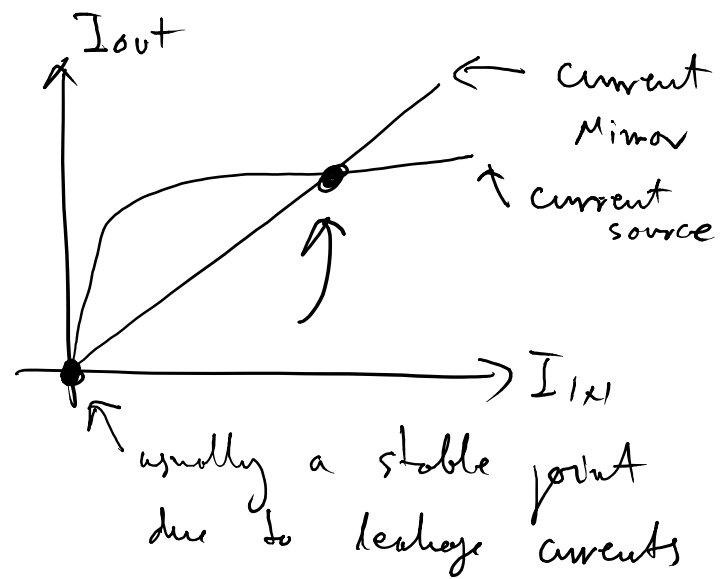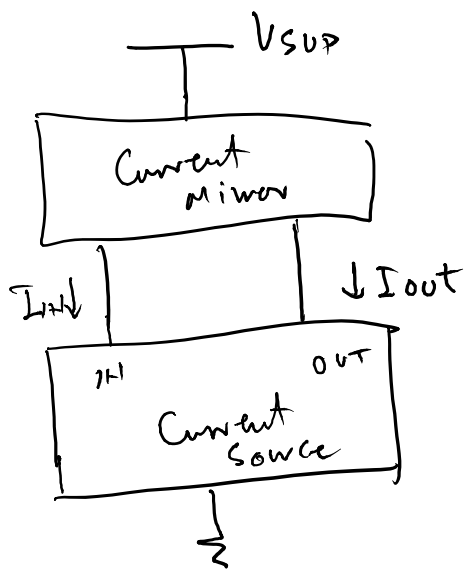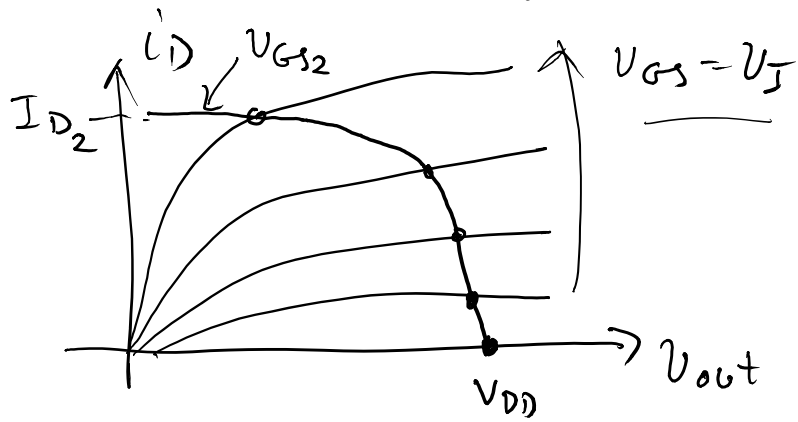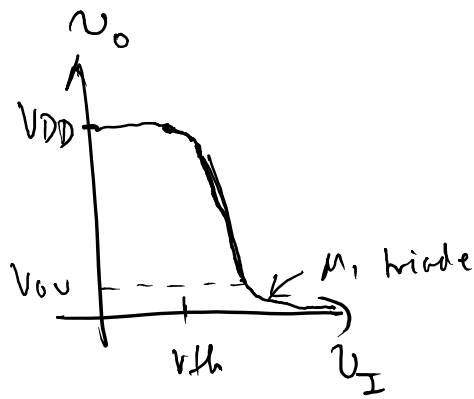

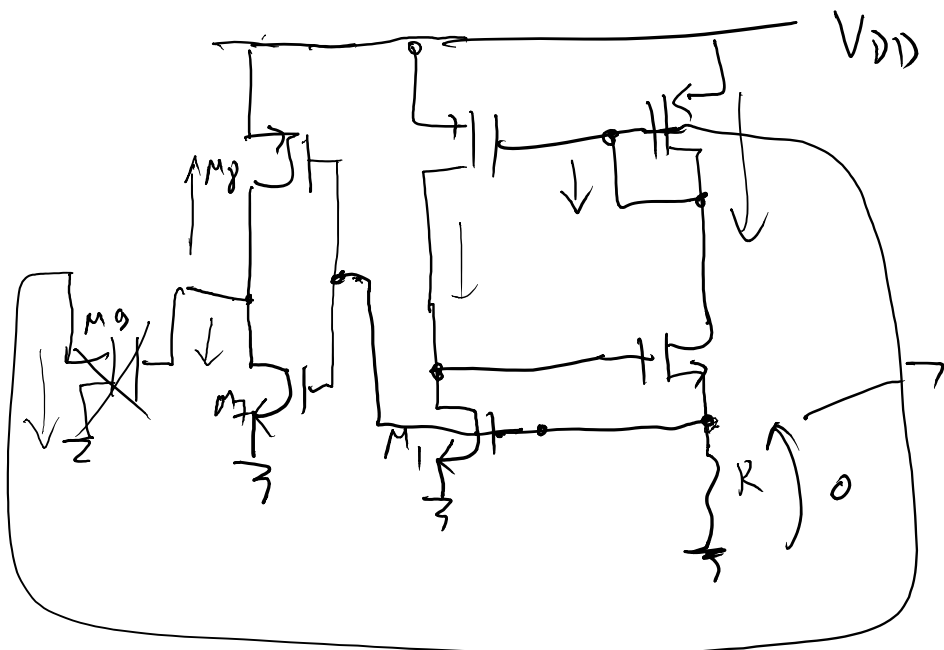$I_o \uparrow, I_{in} \uparrow \Rightarrow I_o \uparrow$
PFB loop
but stable as loop gain < 1




$I_0 R$


M_8 still on

$s_0 \left(\frac{w}{L} \right)_{M7} \gg \left(\frac{w}{L} \right)_{M8}$

V_{BE} - self-biased

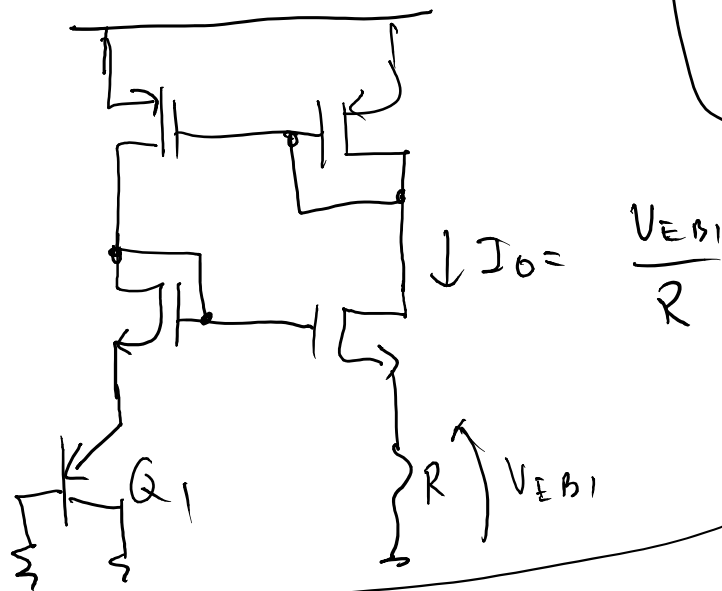

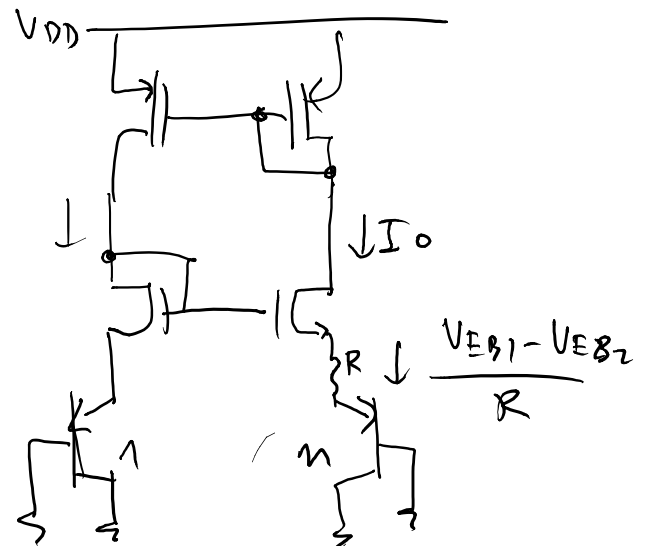
at stable point $I_0 \cdot R$
turns-off M_8 .



$$V_{EB1} - V_{EB2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$= V_T \ln \frac{I_{C1}}{I_{C2}} - \ln \left(\frac{I_{S2}}{I_{S1}} \right) = V_T \ln(n)$$

Copyright © 2014 Regents of the University of California

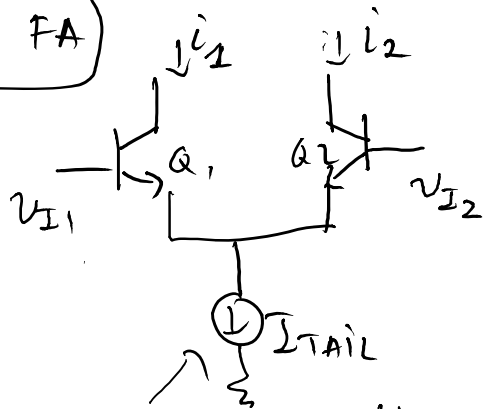BJT's:Diff: pairs Q_1, Q_2 FA

KVL: $v_{I1} - v_{BE1} + v_{BE2} - v_{I2} = 0$

$$v_{I1} - v_{I2} = v_{BE1} - v_{BE2}$$


$$V_T \ln \frac{i_{c1}}{I_{S1}} = V_T \ln \frac{i_{c2}}{I_{S2}}$$

$$v_{Id} = v_{I1} - v_{I2} = V_T \ln \frac{i_{c1}}{i_{c2}} - \frac{I_{S1}}{I_{S2}}$$


$$\frac{i_{c1}}{i_{c2}} = e^{\frac{v_{Id}}{V_T}}$$

KCL: $i_{E1} + i_{E2} = I_{TAIL} \Rightarrow i_{c1} + i_{c2} = \alpha_F I_{TAIL}$
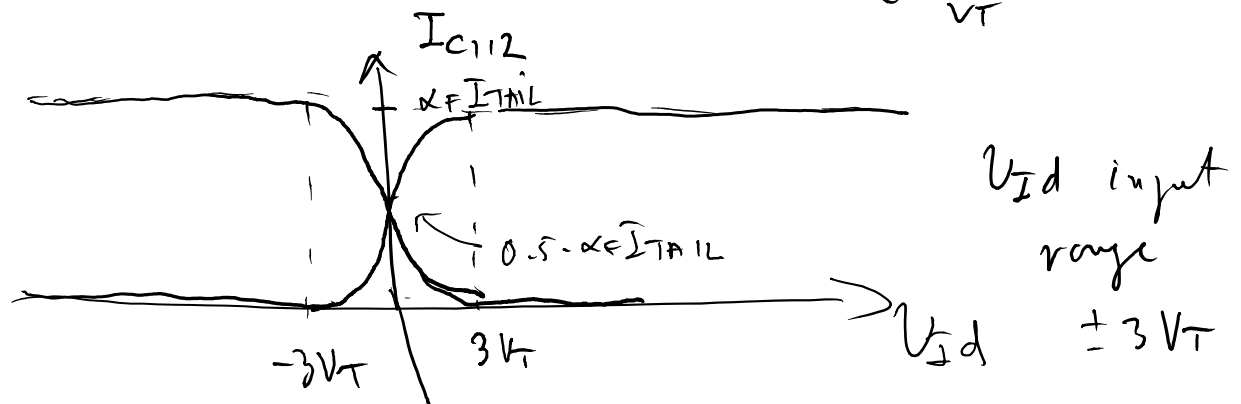
$$i_{c1} = \frac{\alpha_F I_{TAIL}}{1 + e^{\frac{v_{Id}}{V_T}}}, \quad i_{c2} = \frac{\alpha_F I_{TAIL}}{1 + e^{-\frac{v_{Id}}{V_T}}}$$



input range

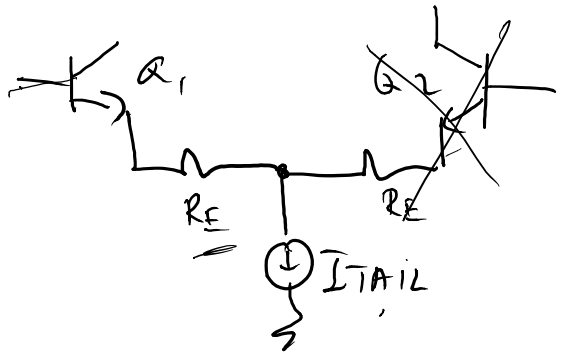

$$v_{Id} = \underline{V_{BE1}} - \underline{V_{BE2}} + \underline{I_{TAIL}} \cdot R_E$$

