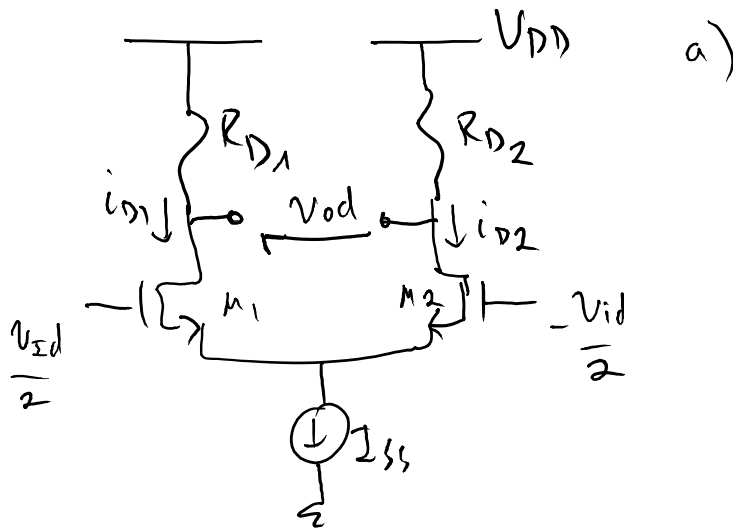


Offset : ① Systematic offset : even at zero mismatch
 ② Random - mismatch between $V_{th,1,2}$, μ_n, \dots
 $\frac{W}{L}, \dots$

Simple example:



$$V_{od} = V_{DD} - i_{D1} R_{D1} - (V_{DD} - i_{D2} R_{D2})$$

$$= i_{D2} R_{D2} - i_{D1} R_{D1}$$

Look for V_{os} vs v_{Id} for which $V_{od} = 0$

$$i_{D1} R_{D1} = i_{D2} R_{D2} \quad \Rightarrow \quad \sqrt{\frac{2 i_{D1}}{k'(\frac{W}{L})_1}} \quad \leftarrow i_{D1} \cdot \frac{R_{D1}}{R_{D2}} \quad \sqrt{\frac{2 i_{D2}}{k'(\frac{W}{L})_2}}$$

$$V_{os} = v_{Id} = V_{GS1} - V_{GS2} = V_{th1} + V_{ov1} - V_{th2} - V_{ov2}$$

$$= \underbrace{\Delta V_{th}}_{V_{th1} - V_{th2}} + \underbrace{\sqrt{\frac{2 i_{D1}}{k'(\frac{W}{L})_1}} \left(1 - \sqrt{\frac{R_{D1}}{R_{D2}}} \right)}_{\frac{1}{2} \frac{\Delta R}{R}} \quad \text{assumed } \left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2$$

Incorporate W, L mismatch :

$$V_{OS} = \Delta V_{th} + \frac{V_{OV}}{2} \cdot \left(-\frac{\Delta R}{R} - \frac{\Delta\left(\frac{W}{L}\right)}{\frac{W}{L}} \right)$$

\uparrow process & layout \uparrow process \uparrow process layout

Example: $V_{th1} - V_{th2} = 10 \text{ mV}$


$$\underbrace{V_{GS} - V_{th}}_{V_{OV}} = \sqrt{\frac{2I_{D1}}{k' \frac{W}{L}}} = 500 \text{ mV}$$

$$\frac{R_{D1}}{R_{D2}} = 1.02 \quad (2\% \text{ mismatch})$$

$$V_{OS} = 10 \text{ mV} + \underbrace{V_{OV} \cdot \left(1 - \frac{R_{D1}}{R_{D2}}\right)}_{\substack{2\% \rightarrow 1\%}} = 10 \text{ mV} + \cancel{10 \text{ mV}} \xrightarrow{5 \text{ mV}} 20 \text{ mV}$$

f_T of MOS $\sim V_{OV} \uparrow \Rightarrow V_{OS} \uparrow$

trade-off between accuracy & speed.

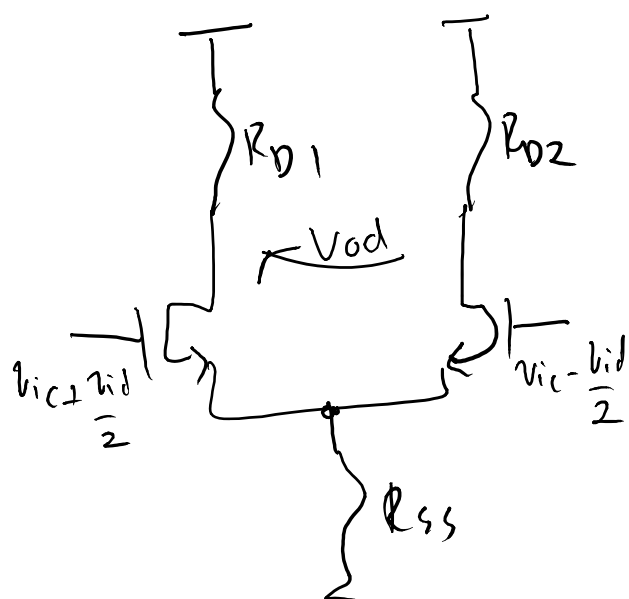

$$A_{dm-cm} =$$

$$A_{cm-dm} =$$

$$V_{od} \Big|_{v_{id}=0} = - \frac{g_{m1} R_{D1}}{1 + 2g_{m1} R_{SS}} v_{ic} + \frac{g_{m2} R_{D2}}{1 + 2g_{m2} R_{SS}} v_{ic}$$

$$V_{od} = V_{o1} - V_{o2}$$


$$V_{oc} = \frac{V_{o1} + V_{o2}}{2} = - \frac{g_{m1} R_{D1} - g_{m2} R_{D2}}{1 + 2g_{m1} R_{SS}}$$

$$= - \frac{(g_m + \frac{\Delta g_m}{2})(R + \frac{\Delta R}{2}) - (g_m - \frac{\Delta g_m}{2})(R + \frac{\Delta R}{2})}{1 + 2g_m R_{SS}} v_{ic}$$

$$A_{cm-dm} = - \frac{g_m \Delta R + \Delta g_m R}{1 + 2g_m R_{SS}} = \frac{V_{od}}{v_{ic}} \Big|_{v_{id}=0}$$

$$\underline{A_{dm-cm}} = V_{oc} \Big|_{v_{ic}=0} = \frac{V_{o1} + V_{o2}}{2} = \frac{A_1 \cdot \frac{v_{id}}{2} + A_2 \cdot (-\frac{v_{id}}{2})}{2} = \frac{A_1 - A_2}{4}$$

Diff - pair CM input range :

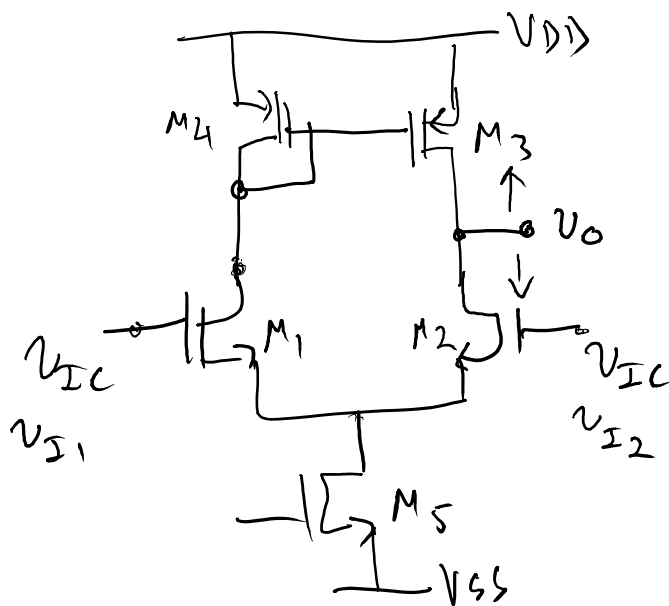

v_{IC} range :

M_1 SAT :

$$v_{IC} < V_{DD} - |V_{th4}| - |V_{ov4}| + V_{th1}$$

M_5 SAT :

$$v_{IC} > V_{SS} + V_{ov5} + V_{th1} + V_{ov1}$$

v_O range :

M_2 SAT :

$$v_{Omin} > v_{I2_max} - V_{th2}$$


M_3 SAT :

$$v_{Omax} < V_{DD} - |V_{ov3}|$$


Freq response of diff-pairs.

$$A(s) = A_0 \frac{\prod_j^n (1 - \frac{s}{z_j})}{\prod_i^m (1 - \frac{s}{p_i})}$$

$$m_p > n_z$$

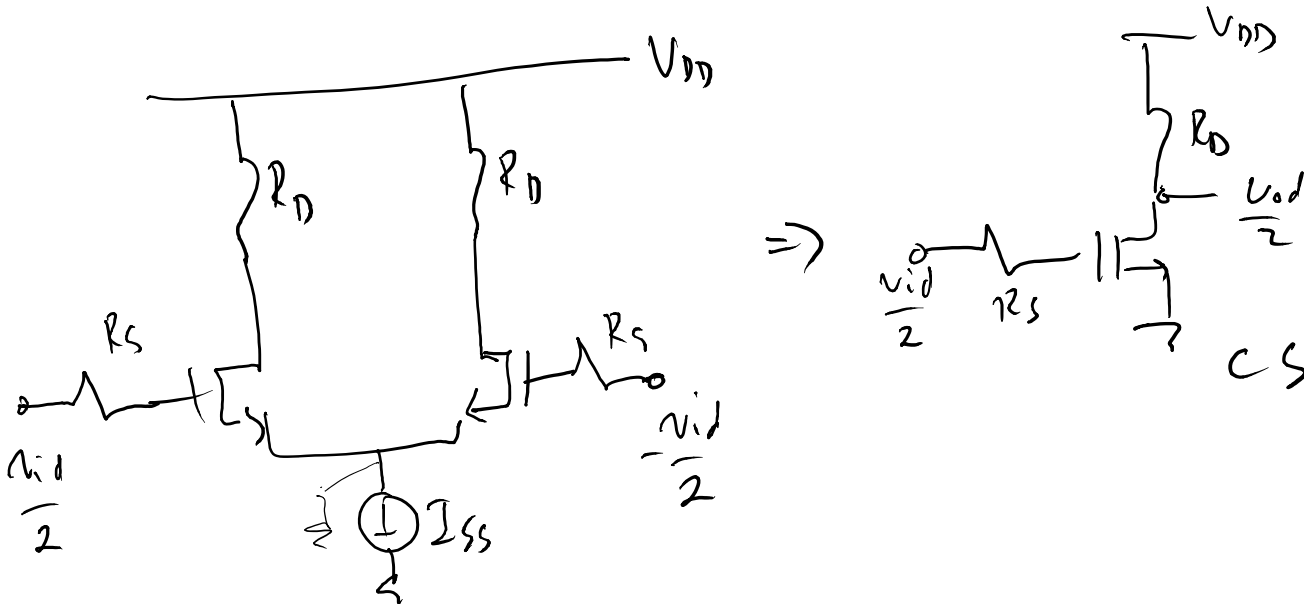

CS: small-signal.

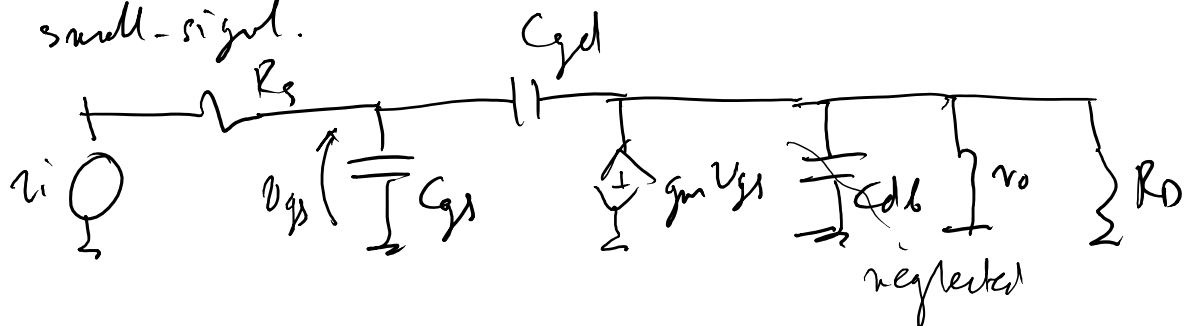

$$A_{vo} = -g_m R_D, \quad z_1 = + \frac{g_m}{C_{gd}}, \quad |z_1| \gg \omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$


$C_{gs} \gg C_{gd}$

poles OCTC:

$$p_1 = - \frac{1}{R_S (C_{gs} + C_{gd} (1 + g_m R_D))}$$

SCTC:

$$p_2 = - \left(\frac{1}{R_D C_{gd}} + \frac{1}{C_{gs}} \left(\frac{1}{R_S} + \frac{1}{R_D} + g_m \right) \right) \Rightarrow |p_2| > \omega_T$$

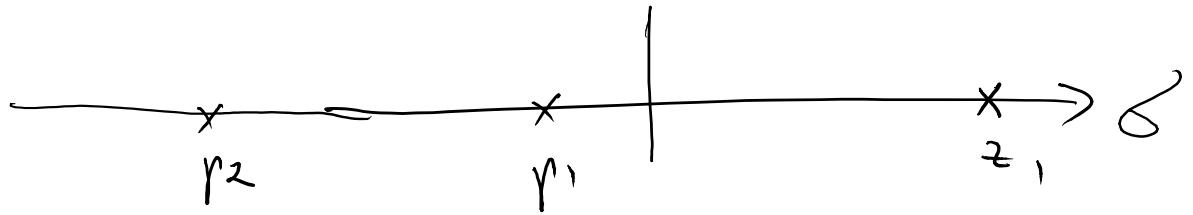


$$| \text{Gain} \times \text{BW} | = \frac{g_m R_D}{R_s \cdot g_m \cdot C_{gd} \cdot R_D} \approx \frac{1}{R_s C_{gd}}$$


no dependence
on R_D

in case
Miller effect
dominant.

CM response:

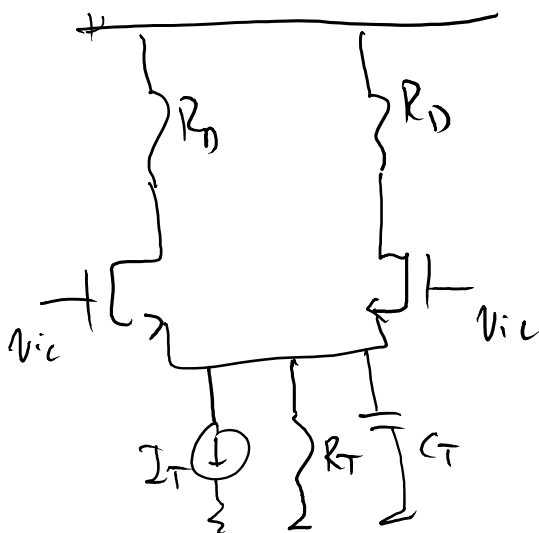

CM.
H.C.
 \Rightarrow

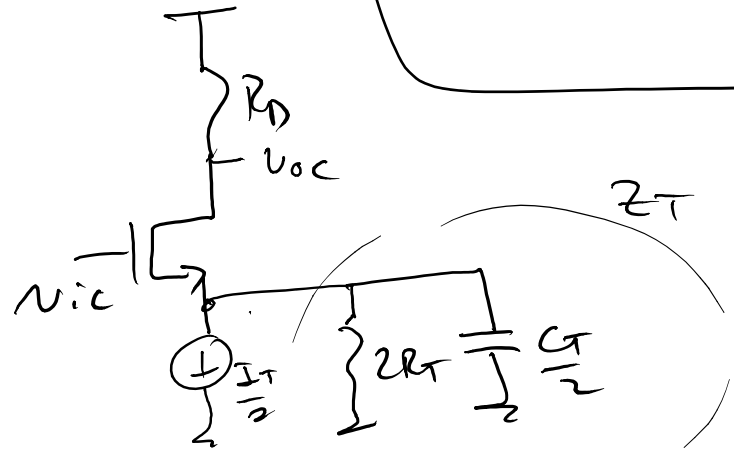

C_T dominates all other C_{gs} .

$$A_{cm}(s) = \frac{v_{oc}}{v_{ic}} = - \frac{g_m R_D}{1 + g_m Z_T} \approx - \frac{R_D}{Z_T}$$

$$Z_T = 2R_T \parallel \frac{1}{s C_T} = \frac{2R_T}{1 + s C_T R_T} \quad \nearrow A_{cm} \approx - \frac{R_D}{2R_T} \underbrace{(1 + s C_T R_T)}_{\text{zero}}$$

bad!

