
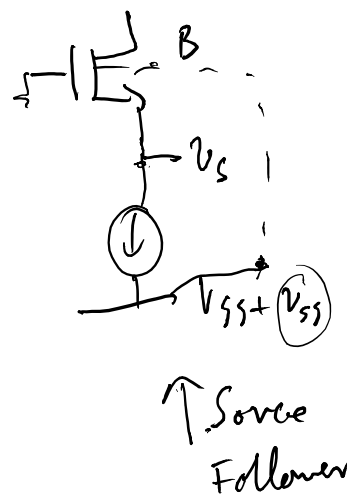
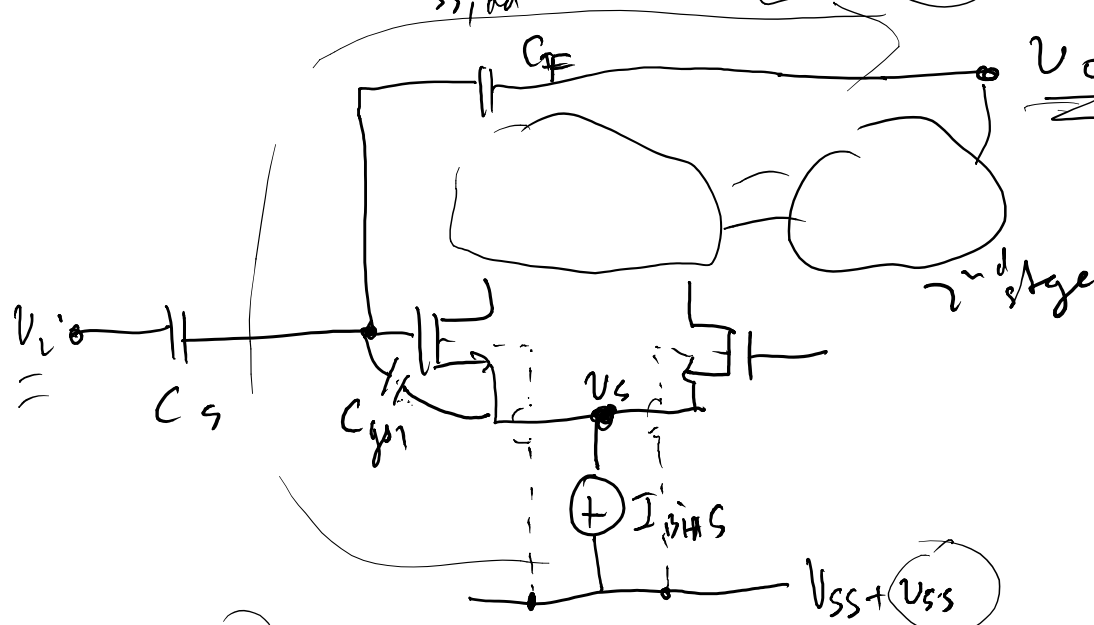


PSRR

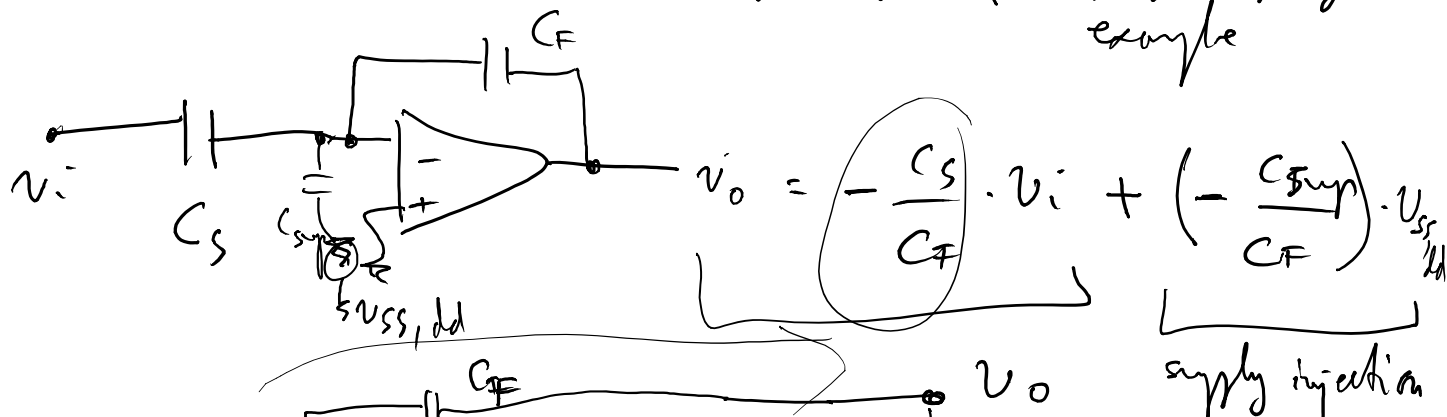2-stage diff. CMOS op-amp (Supply coupling)
example




$$\frac{v_o}{v_{ss}} = \left(\frac{v_o}{v_s} \right) \cdot \left(\frac{v_s}{v_{ss}} \right) = -\frac{C_{gs1}}{C_F} \cdot \frac{g_{mb}}{g_m + g_{mb}}$$

$$PSRR^- = \frac{-\frac{C_s}{C_F}}{-\frac{C_{gs1}}{C_F}} \cdot \frac{g_m + g_{mb}}{g_{mb}} = \left(\frac{C_s}{C_{gs1}} \right) \cdot \frac{g_m + g_{mb}}{g_{mb}}$$


* Make $\frac{C_s}{C_{gs1}}$ ↑ increased noise from M_1

* Tie M_1 B to S \Rightarrow affects CMR (↓)


PSRR for 2-stage CMOS op-amp

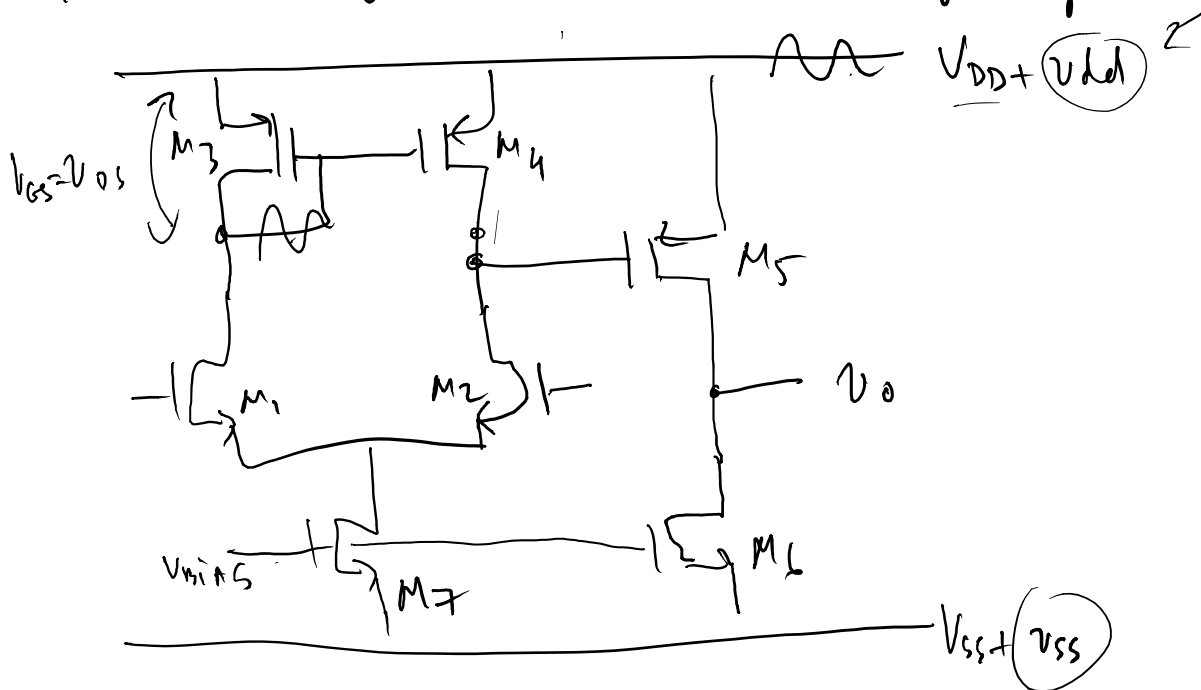

PSRR_v



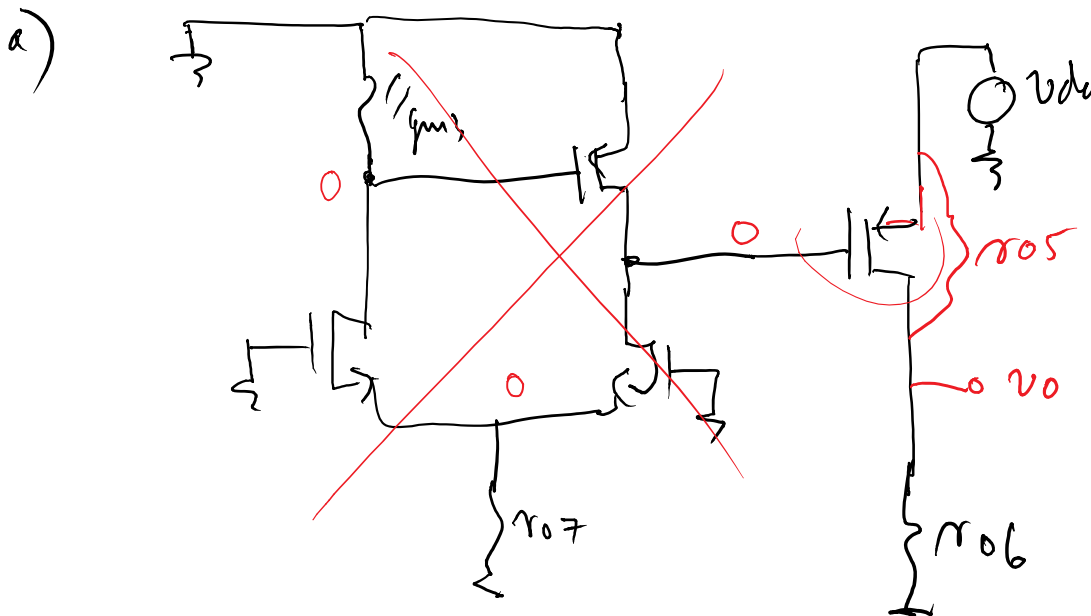

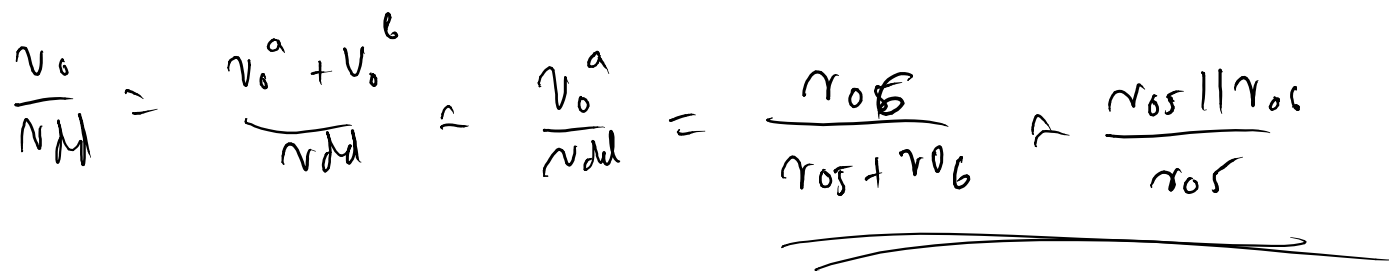
$$\frac{v_0}{v_{dd}} = \frac{r_{06}}{r_{05} + r_{06}}$$




PSRR⁻:

a) 2nd stage

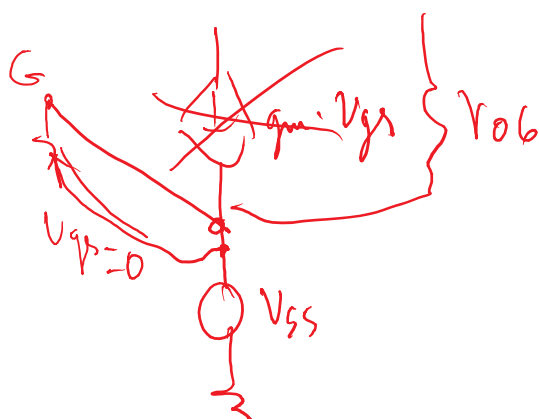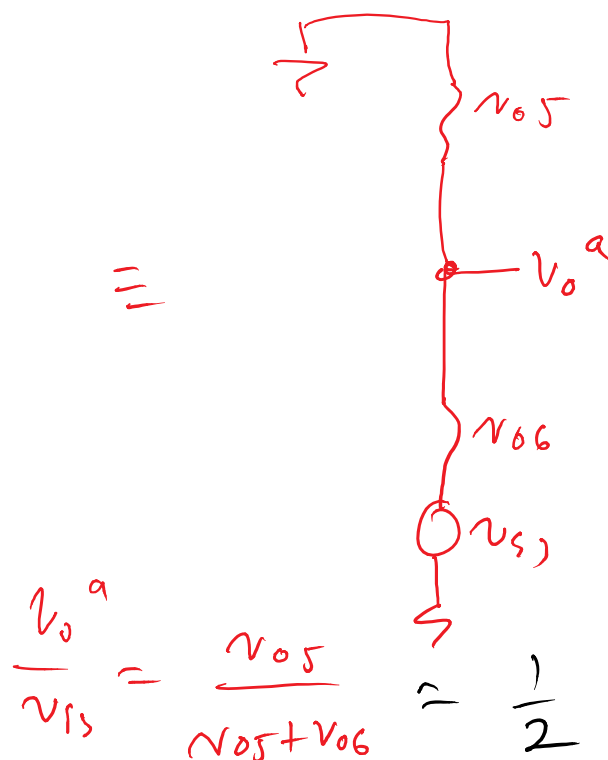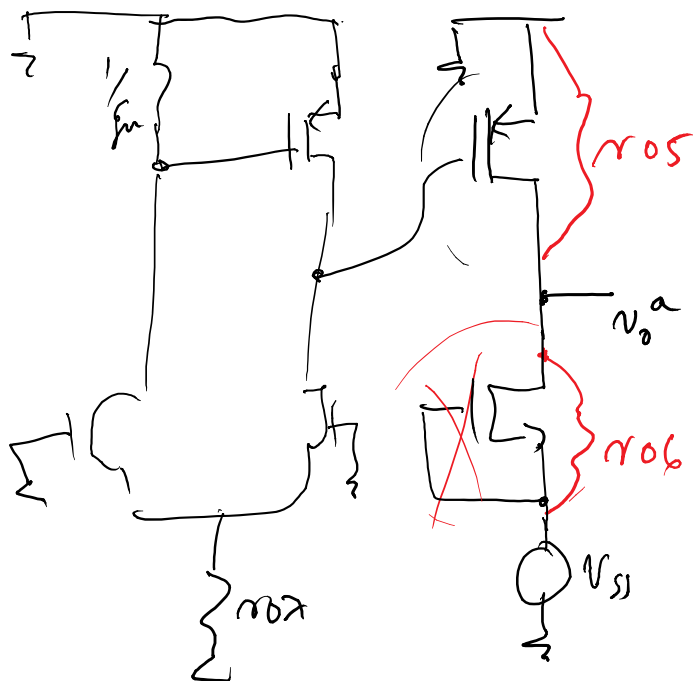

b) v_{ss} in 1st stage.

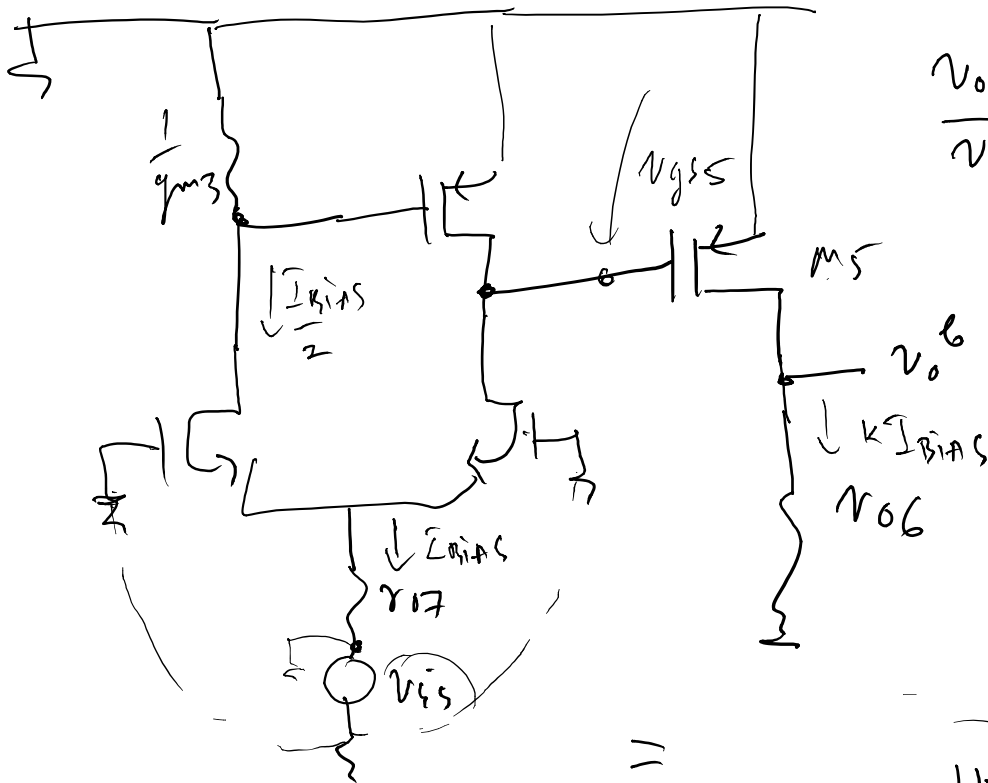


$$\frac{v_{ob}}{v_{ss}} = \frac{v_{gs5}}{v_{ss}} \cdot \frac{v_{ob}}{v_{gs5}}$$

$$\uparrow$$

$$- g_{m5} \cdot r_{05} || r_{06}$$

$$\frac{v_{gs5}}{v_{ss}} = \frac{g_{m3} (r_{02} || r_{04})}{2 g_{m2} \cdot r_{07} + g_{m3} (r_{01} || r_{03})}$$

$$\approx \frac{1}{2 g_{m3} r_{07}}$$

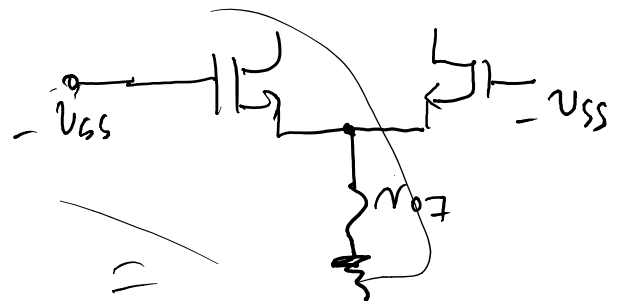

$$\frac{v_{ob}}{v_{ss}} = - \frac{g_{m5} \cdot r_{05} || r_{06}}{2 g_{m3} \cdot r_{07}} = - \frac{g_{m5}}{2 g_{m3}} \cdot \frac{r_{05} || r_{06}}{r_{07} \cdot \frac{V_A}{2 K I_{BIAS}}} \approx - \frac{1}{2}$$

$$\frac{v_o}{v_{ss}} \approx \frac{v_o^a + v_o^b}{v_{ss}} \approx 0$$

$V_{ov} \downarrow$ (reducing I_{Bias} for same $\frac{W}{L}$) \Rightarrow

$L \uparrow \Rightarrow \text{Adm} \uparrow, \text{CMRR} \uparrow, \text{PSRR} \uparrow$


Fundamental trade-off : speed vs. everything else

Increasing A_{dm} :

- cascode diff pair
- cascode mirror

} Telescopic cascode

$$A_{dm} \sim (g_m \cdot V_D)^2$$

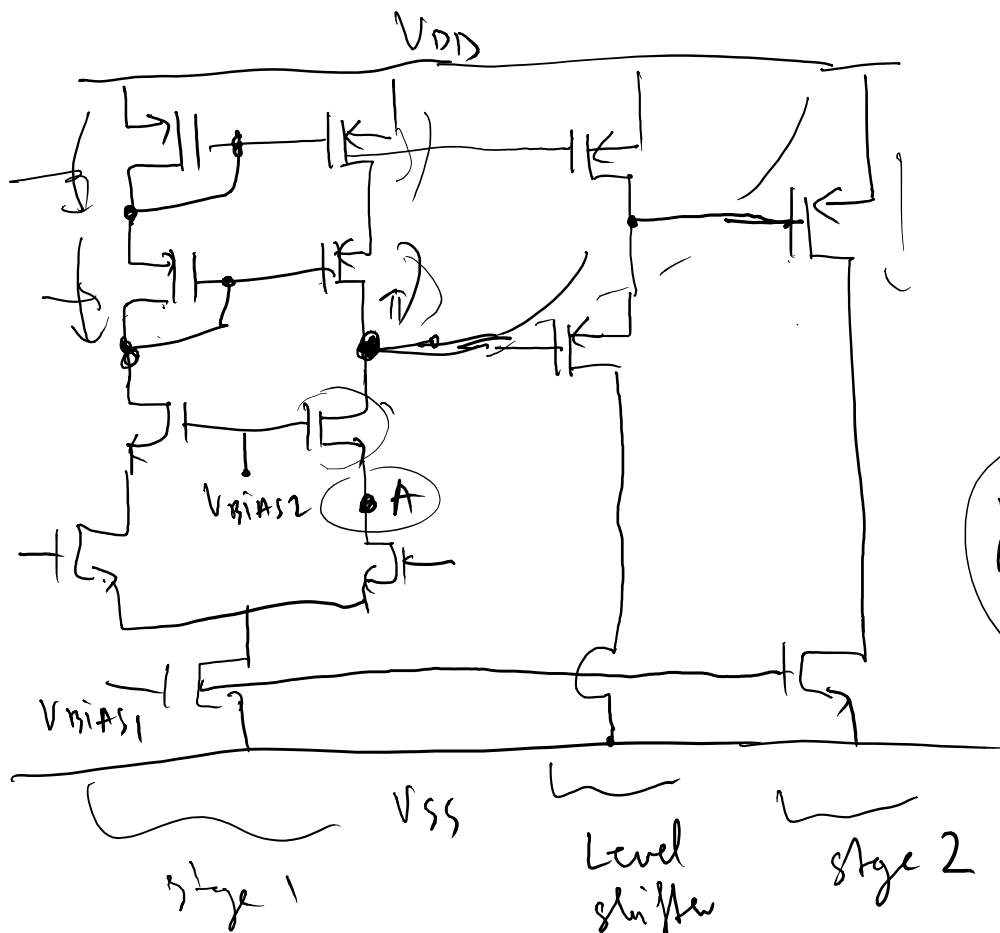

$$p_1^{1\text{-stage}} = \frac{1}{R_{outB} - C_B}$$

\uparrow
 $g_m r_o^2$

$$p_2^{1\text{-stage}} = \frac{1}{\frac{1}{g_{m2}} \cdot C_x}$$

negligible.

$$A_{dm} \approx g_m \cdot \underbrace{(g_m r_o) \cdot r_o}_{R_{outB}} \cdot \frac{g_m r_o \parallel r_{on}}{1 + g_m r_o \parallel r_{on}} \cdot g_{mF} \cdot (r_{of} \parallel r_{on})$$

\uparrow
 $G_{m, 1\text{-stage}}$

- level shift minimizes systematic offset