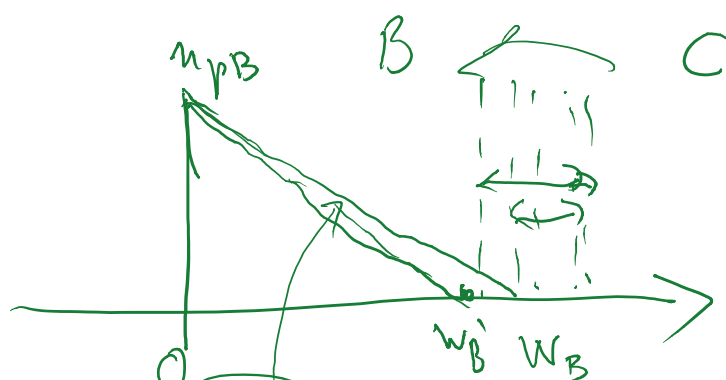


Early effect - effect of V_{CE}



V_{BC}

$V_{CE} \uparrow$

$$I_C = -AqD_{nB} \frac{dn_{pB}(x)}{dx}$$

$$= -\frac{n_i^2}{N_{AB} \cdot W_B} \cdot e^{\frac{V_{BE}}{V_T}}$$

$$V_{CE} = V_{BE} + V_{BC}$$

\uparrow

$0.7V$

\uparrow

$$\frac{\partial I_C}{\partial V_{CE}} = -\frac{I_C}{W_B} \cdot \frac{dW_B}{dV_{CE}}$$

Early

voltage:

$$V_A = \frac{I_C}{\frac{\partial I_C}{\partial V_{CE}}}$$

$$(V_A \approx 15-100V)$$

$V_{CE} \uparrow$

$W_B \downarrow$

$I_C \uparrow$

dV_{CE}

dV_{CB}

$\sim -W_B$

$$\frac{1}{\frac{\partial W_B}{\partial V_{CB}}}$$

$$V_A \approx 15-100V \quad \overline{2V_{CE}}$$


Copyright © 2014 Regents of the University of California

$$\overline{2V_{CE}}$$

Lecture 3 - BJT SSM and biasing

Friday, January 24, 2014

EE140 Spring 2014
Vladimir Stojanović

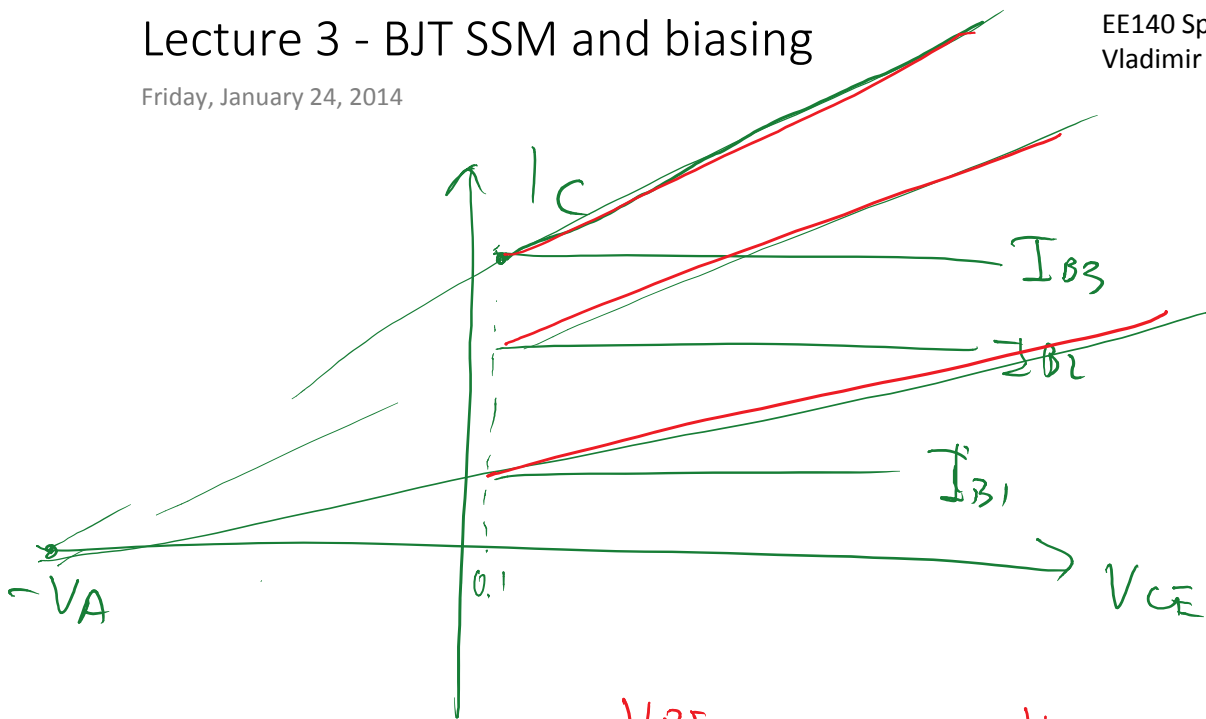

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A} \right)$$

Saturation :

B E	B C
F	F





$$V_{BE} \approx 0.7\text{ V}$$

$$V_{CE} \approx 0.1-0.2\text{ V}$$

currents set KVL

Small - signal :

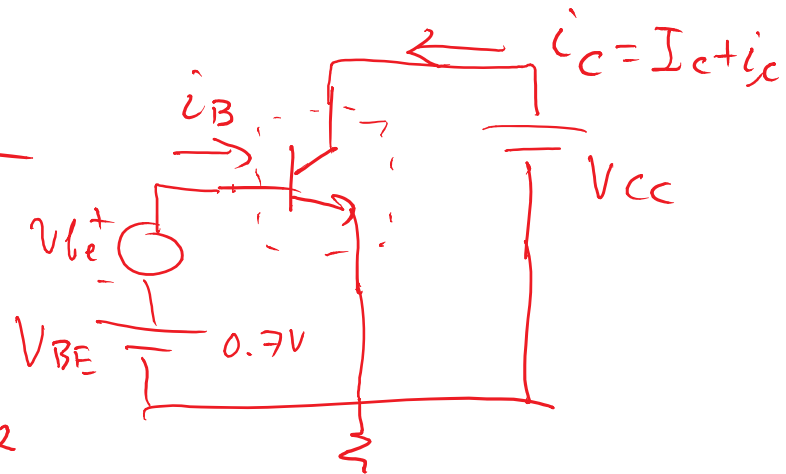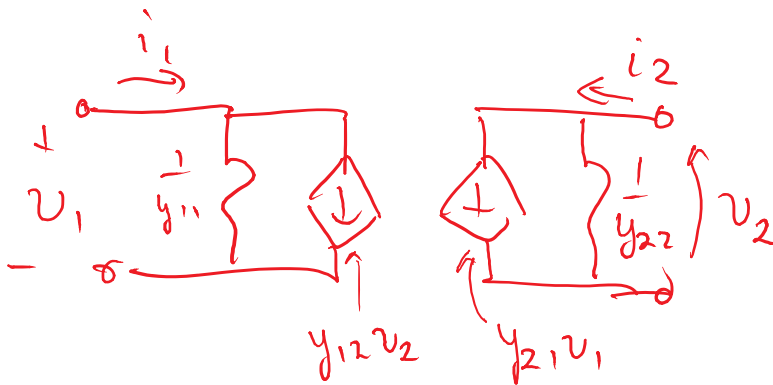


$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$

$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

h FA

π - model

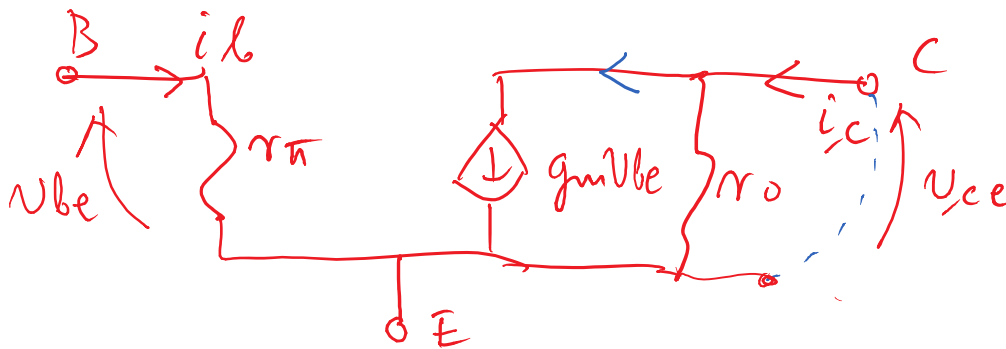

Model parameters:
 r_{π}, g_m, r_o

$$\textcircled{1} \quad g_m = \frac{i_c}{v_{be}} \Big|_{v_{ce}=0} \quad (y_{21})$$

$$g_m = \frac{\partial i_c}{\partial v_{BE}} = \frac{\partial}{\partial v_{BE}} \left(I_S e^{\frac{v_{BE}}{V_T}} \right) = \frac{I_S}{V_T} e^{\frac{v_{BE}}{V_T}} = \frac{I_C}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$

$$V_T = \frac{kT}{q}$$

$$| g_m = \frac{1}{V_T} \quad V_T = \frac{k}{q}$$

Copyright © 2014 Regents of the University of California

② input resistance r_{π} :

$$r_{\pi} = \left. \frac{v_{be}}{i_b} \right|_{v_{ce}=0} = \left. \frac{\partial v_{BE}}{\partial i_B} \right|_{V_{CE}=const, \beta_0} = \left. \frac{\partial v_{BE}}{\partial (\frac{i_c}{\beta_0})} \right|_{V_{CE}=const} = \frac{\beta_0}{g_m}$$

$$r_{\pi} = \frac{\beta_0}{g_m}$$

③ Output resistance :

$$r_o = \left. \frac{v_{ce}}{i_c} \right|_{v_{be}=0} = \left. \frac{\partial v_{CE}}{\partial i_c} \right|_{V_{BE}=const} = \frac{1}{\left. \frac{\partial i_c}{\partial v_{CE}} \right|_{V_{BE}=const}} = \frac{1}{\left. \frac{\partial}{\partial v_{CE}} \left(I_S e^{\frac{V_{BE}}{V_T}} \cdot \left(1 + \frac{v_{CE}}{V_A} \right) \right) \right|_{V_{BE}=const}} = \frac{V_A}{I_C}$$




$$r_o = \frac{V_A}{I_C}$$

Lecture 3 - BJT SSM and biasing

Friday, January 24, 2014

EE140 Spring 2014
Vladimir Stojanović

PNP

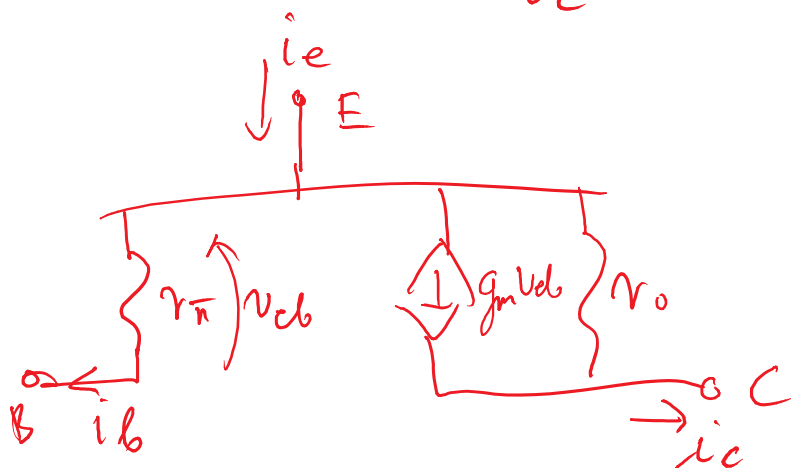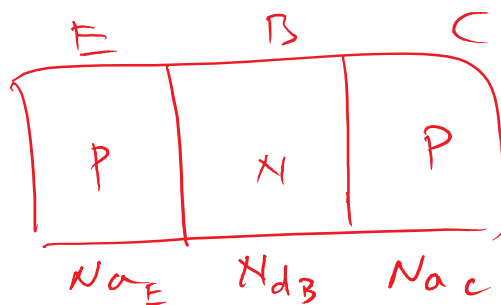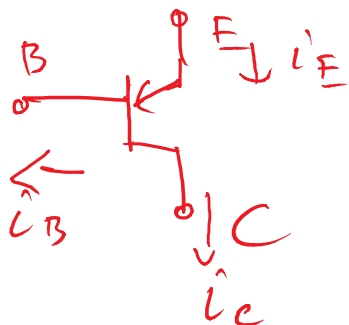


Summary:

$$g_m \cdot r_{\pi} = \beta_0$$

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A}{I_C}$$

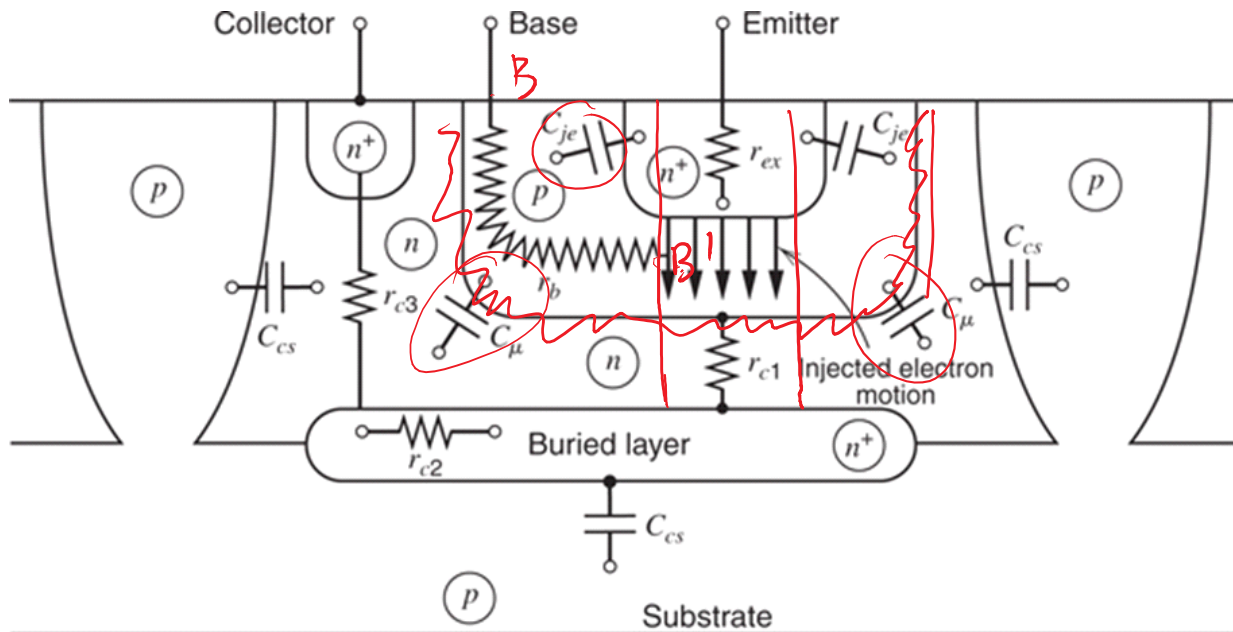


More complete model



C_μ - base-collector depletion cap

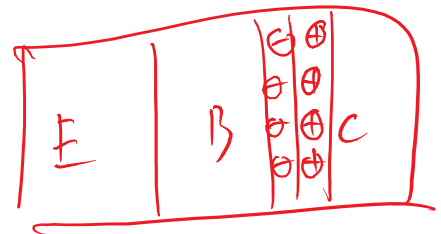
$$C_\mu = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CB}}{\psi_0}}}$$



ψ_0 - built-in potential

$$\psi_0 = V_T \ln \frac{N_{AB} N_{DC}}{n_i^2}$$
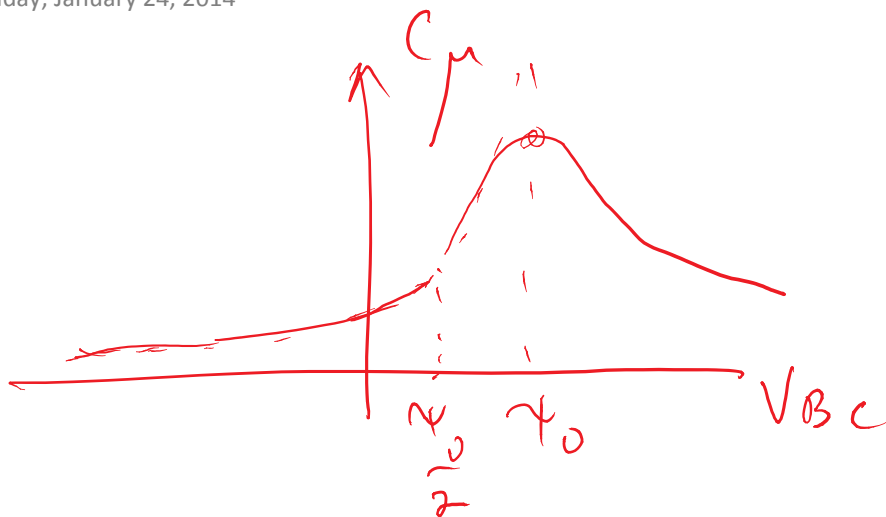
$$C_\mu = A \sqrt{\frac{\epsilon N_{AB} N_{DC}}{2(N_{AB} + N_{DC})}}$$



C_{in} : Base - Emitter

① junction - capacitance (C_{je})

② diffusion - capacitance

$\tau_F = \frac{Q_E}{i_C}$ ← charge in "transit"

$$= \frac{\Delta Q_E}{\Delta i_C} \Rightarrow q_e = \tau_F \cdot i_C = C_b \cdot v_{be}$$

$$C_b = \tau_F \left(\frac{i_C}{v_{be}} \right)^{gm} = \tau_F g_m$$


$$C_{in} \approx C_b \quad \text{since} \quad C_{je} \ll C_b$$

Collector - Base resistance





$$r_{\mu} = \frac{\Delta V_{CE}}{\Delta i_{rB}} = \underbrace{\frac{\Delta V_{CE}}{\Delta i_C}}_{r_o} \cdot \underbrace{\left(\frac{\Delta i_C}{\Delta i_{rB}} \right)}_{\approx 10/\beta_0} \approx 10\beta_0 r_o$$

E B C

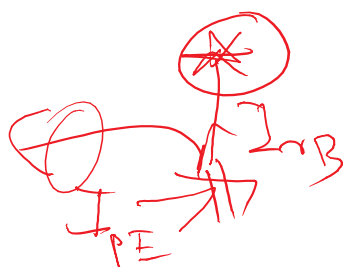


$$\frac{\Delta i_C}{\Delta i_B} \approx \beta_0$$

$$I_C \gg I_{rB}$$

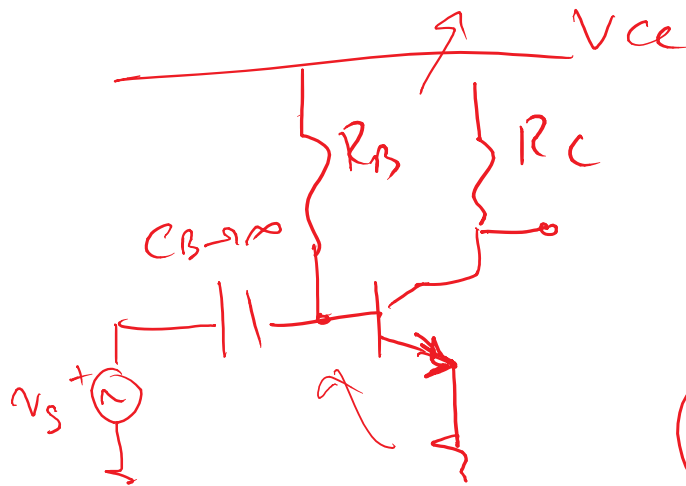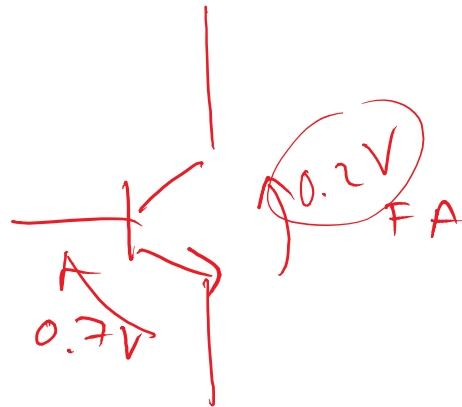


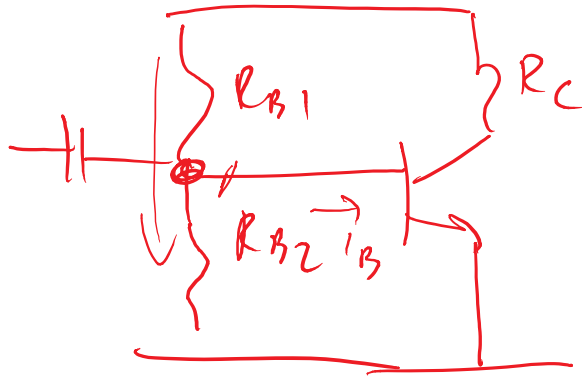Problems:

- ① β_F dependent
- ② V_{ce} dependent
- ③ Thermal runaway
 $T \uparrow, I_C \uparrow, T \uparrow, I_C \uparrow$



$$I_C \sim I_S e^{\frac{V_{BE}}{V_T}}$$

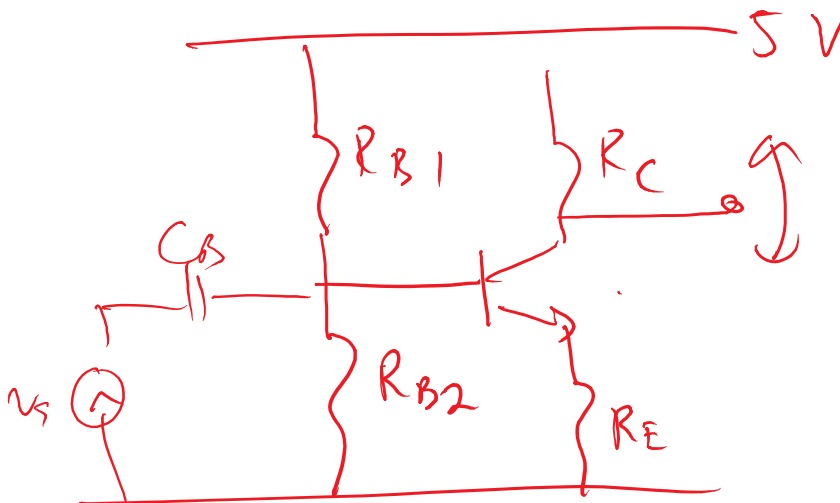

Challenge Problem.

Find R_{B1} , R_{B2} , R_C and R_E so that $I_C = 1\text{mA}$ and output voltage swing is maximized. Assume $V_{CES} = 0.1\text{V}$.

$I_C = 1\text{mA}$, max out swing

$\beta_F = 100$, $V_{CC} = 5\text{V}$, $V_A = 100\text{V}$