

$$\Delta V_{out} = \Delta I_o \cdot R_{out}$$

$\Delta I_o$  small, big, small

$$\Delta V_{out} = (A_{cL} \cdot \Delta V_r + PSRR_{cL} \cdot \Delta V_{DD})$$

$PSRR_{neg} \cdot \Delta V_{DD}$

$$R_{out} = R_{out}(a=0) \cdot \frac{1}{1+RR}$$

$$A_{c,L} = \frac{A_{eq}}{1+RR} + \frac{A_o}{1+RR} = \frac{V_o}{V_R}$$

$$\Rightarrow \frac{1}{1+RR} = \frac{V_o}{(A_{eq}+A_o) \cdot V_R}$$

$$R_{out} = R_{out}(a=0) \cdot \frac{V_o}{(A_{eq}+A_o) \cdot V_R}$$

$$\Delta V_o = R_{out} \cdot \Delta I_o$$

$$\Delta V_o = R_{out}(a=0) \cdot \frac{V_o}{(A_{eq}+A_o) V_R} \cdot \Delta I_o$$

$$\left| \frac{\Delta V_o}{V_o} = \frac{R_{out}(a=0)}{(A_{eq}+A_o) V_R} \cdot \Delta I_o \right|$$


Load regulation spec.

$$\frac{\Delta V_o}{V_o} = \hookrightarrow \cdot \frac{\Delta V_{dd}}{V_{dd}}$$

Line regulation spec.

# Wilson current source:

Type of feedback?

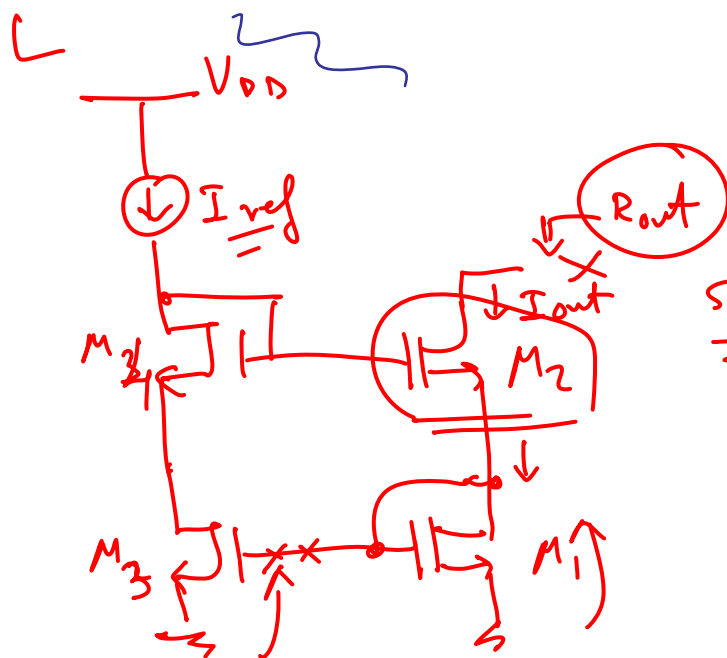


Series  $\Rightarrow$  current  $I_{out}$

$$R_{out}(g_{m2}=0) = r_{o2} + \frac{1}{g_{m1}} \approx r_{o2}$$

$$R_{out} \approx r_{o2} \cdot (1 + g_{m2} r_{o3})$$


$$RR(\text{output open}) = 0$$

$$RR(\text{output shorted}) = RR$$

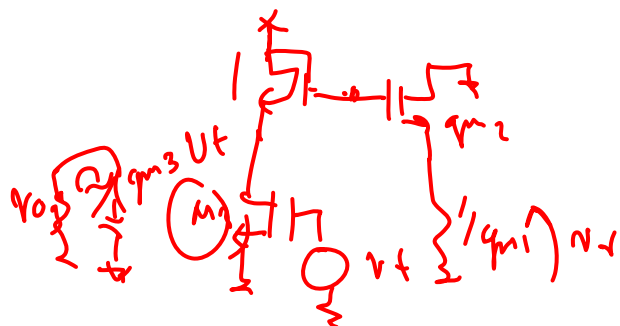

$$RR = g_{m3} \cdot r_{o3} \cdot \frac{1}{1 + g_{m2} \cdot \frac{1}{g_{m3}}} \approx g_{m2} \cdot r_{o3}$$

BJT version:

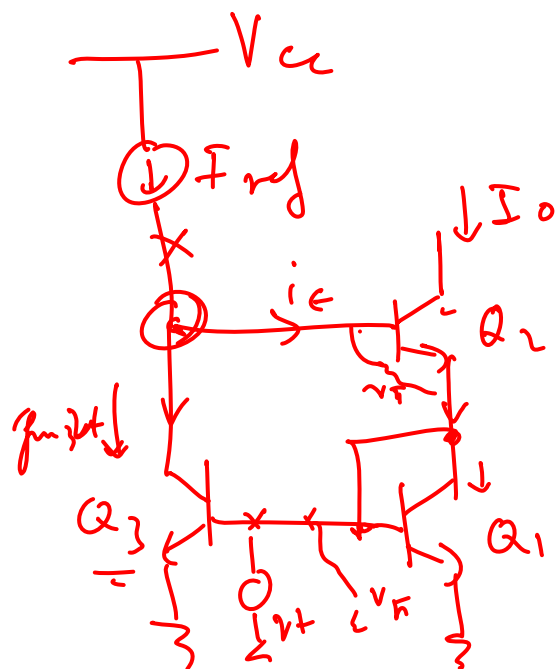

FB type:

shunt - series


$$R_{out} (=0) = r_{o2} + \frac{1}{g_{m1} || r_{\pi3}} \approx r_{o2}$$

$$RR (\text{open out}) = g_{m3} \cdot \frac{1}{g_{m1}} \approx 1$$

$$RR (\text{short out}) = g_{m3} \cdot (1 + \beta_0) \left( \frac{1}{g_{m1} || r_{\pi3}} \right) \approx \beta_0$$

$$R_{out} = r_{o2} \frac{1 + \beta_0}{1 + 1} = \frac{r_{o2} \cdot \beta_0}{2}$$

F<sub>ns</sub> type: Series-series

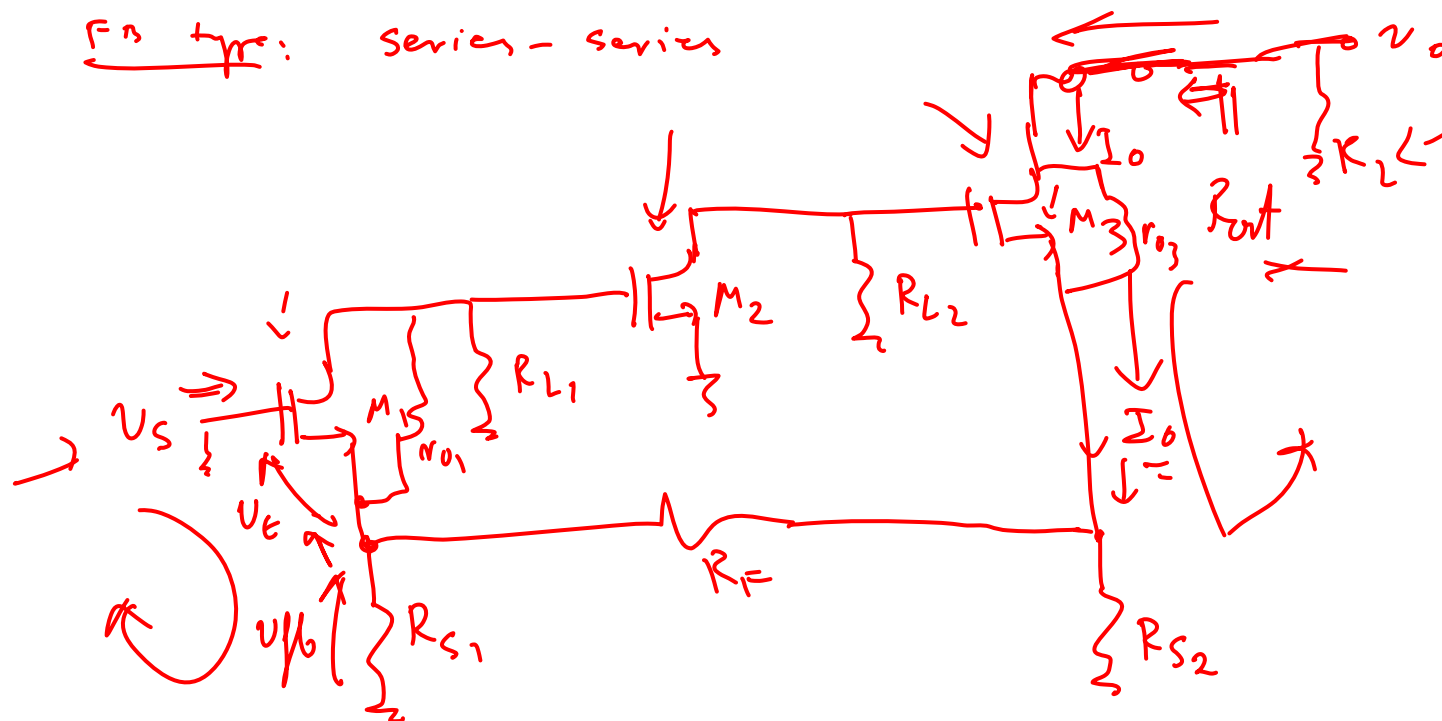


$$RR(\text{output open}) = 0$$

$$RR(\text{output shorted}) = RR$$

$$R_{out} = R_{out}(\dots = 0) \cdot (1 + RR)$$

$$R_{out}(\dots = 0) = r_{o3} + R_{s2} \parallel (R_f + R_{s1} \parallel (r_{o1} + R_{L1}))$$


RR:

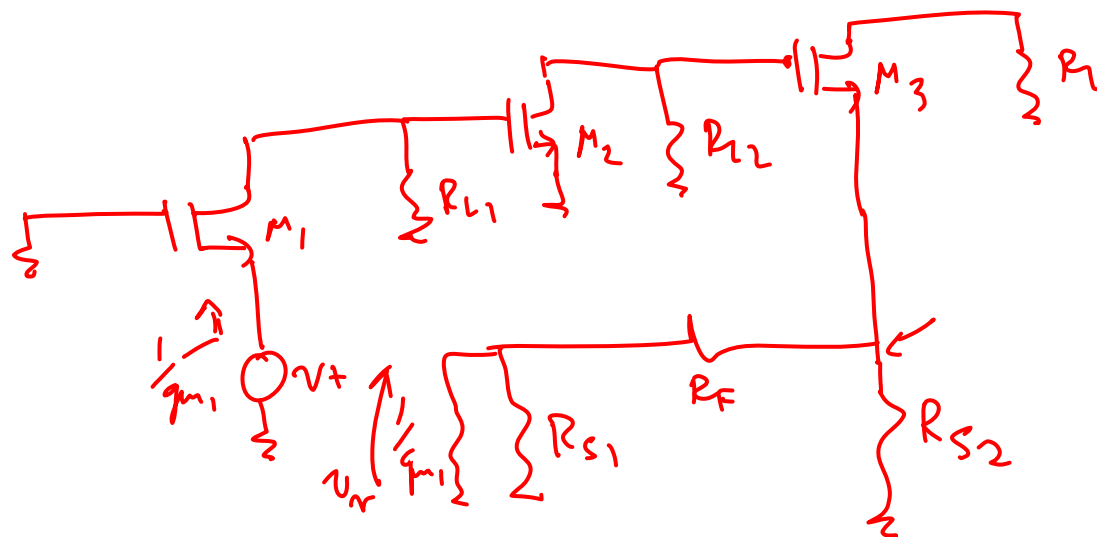

$$V_r = V_t \cdot g_{m1} \cdot R_{L1} \cdot (-g_{m2} R_{L2}) \cdot \frac{g_{m3} \cdot (R_{S2} \parallel (R_F + R_{S1} \parallel \frac{1}{g_{m1}}))}{1 + g_{m3} \cdot (R_{S2} \parallel (R_F + R_{S1} \parallel \frac{1}{g_{m1}}))} \cdot \frac{\frac{1}{g_{m1}} \parallel R_{S1}}{R_F + \frac{1}{g_{m1}} \parallel R_{S1}}$$

$$RR = -\frac{V_r}{V_t} ; A_0 = 0$$

Acy:

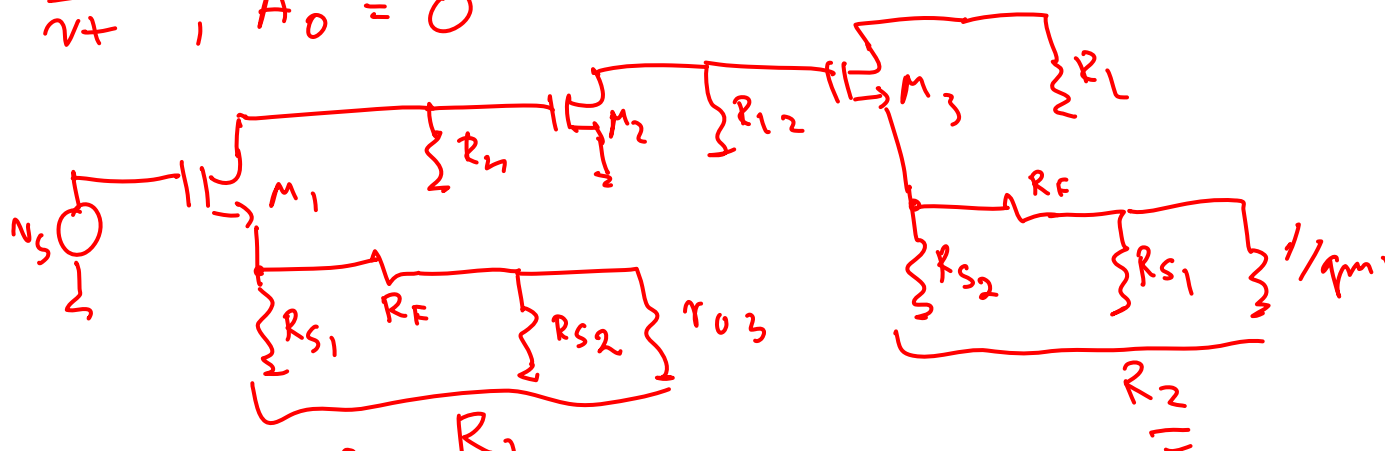

$$\frac{I_0}{V_s} = A_{cy} = \frac{-g_{m1} R_{L1}}{1 + g_{m1} R_{L1}} \cdot (-g_{m2} R_{L2}) \cdot (-\frac{g_{m3}}{1 + g_{m3} R_2}) = -RR \cdot \frac{R_L}{R_{S1} \parallel R_{S2}}$$

