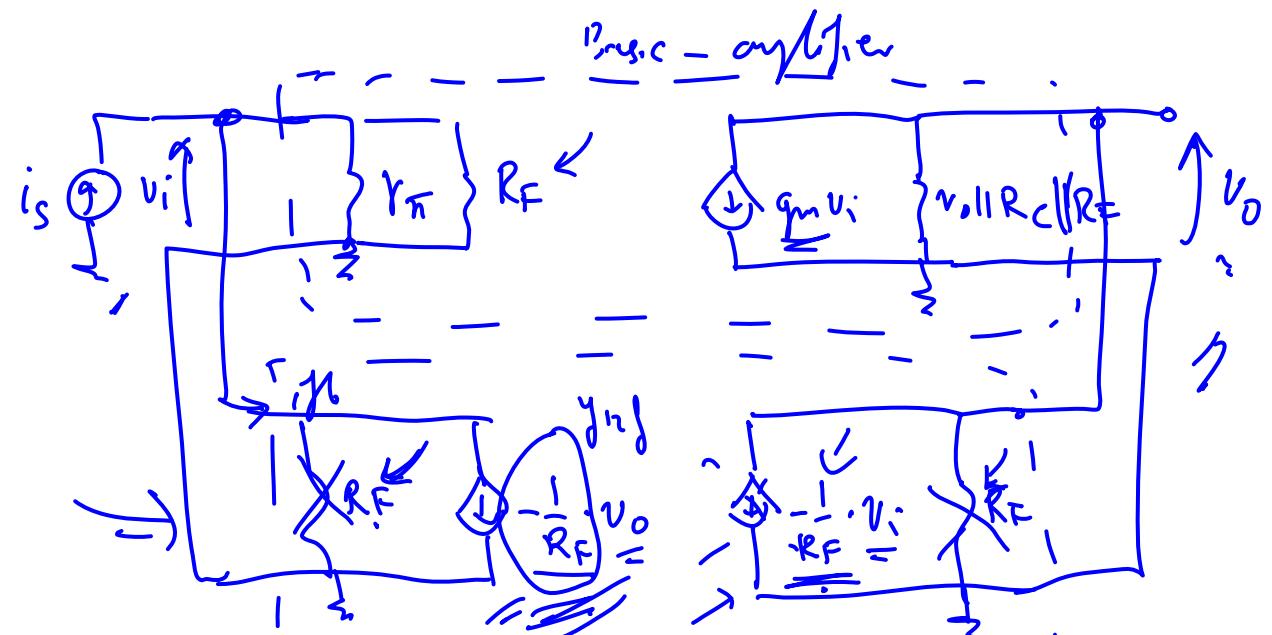



$$\alpha = -\frac{(y_{21a} + y_{21f})}{y_1 y_2}$$

$$= -\frac{\left(g_m - \frac{1}{R_F}\right)}{\left(\frac{1}{r_{\pi}} + \frac{1}{R_F}\right) \left(\frac{1}{r_0} + \frac{1}{R_F} + \frac{1}{R_E}\right)}$$



$$\alpha = -\frac{g_m}{r_{\pi} + R_F} \quad \text{Feedback block}$$

$$= -\left(g_m - \frac{1}{R_F}\right) \cdot \left(r_{\pi} || R_F\right) \cdot \left(r_0 || R_C || R_F\right)$$

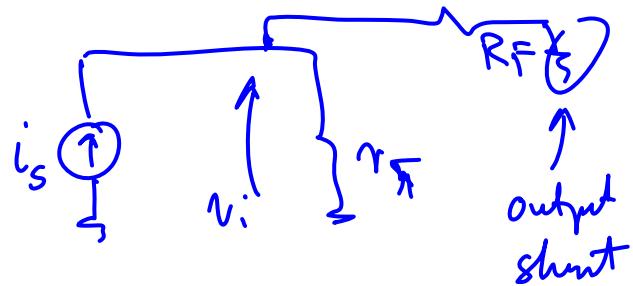

$$Z_{ia} = r_\pi \parallel R_F$$

$$Z_i = \frac{Z_{ia}}{1+T}$$





$$Z_{oa} = r_o \parallel R_C \parallel R_F$$

$$Z_o = \frac{Z_{oa}}{1+T}$$

$$A_{C,2} = \frac{a}{1+a-\underbrace{\frac{T}{T}}_1} = \frac{1}{\frac{1}{j} + \frac{1}{1+\frac{1}{j}}} = \frac{1}{\frac{1}{j}} \cdot \frac{\frac{1}{j}}{1+\frac{1}{j}}$$

Series - series fb. with 2-port analysis

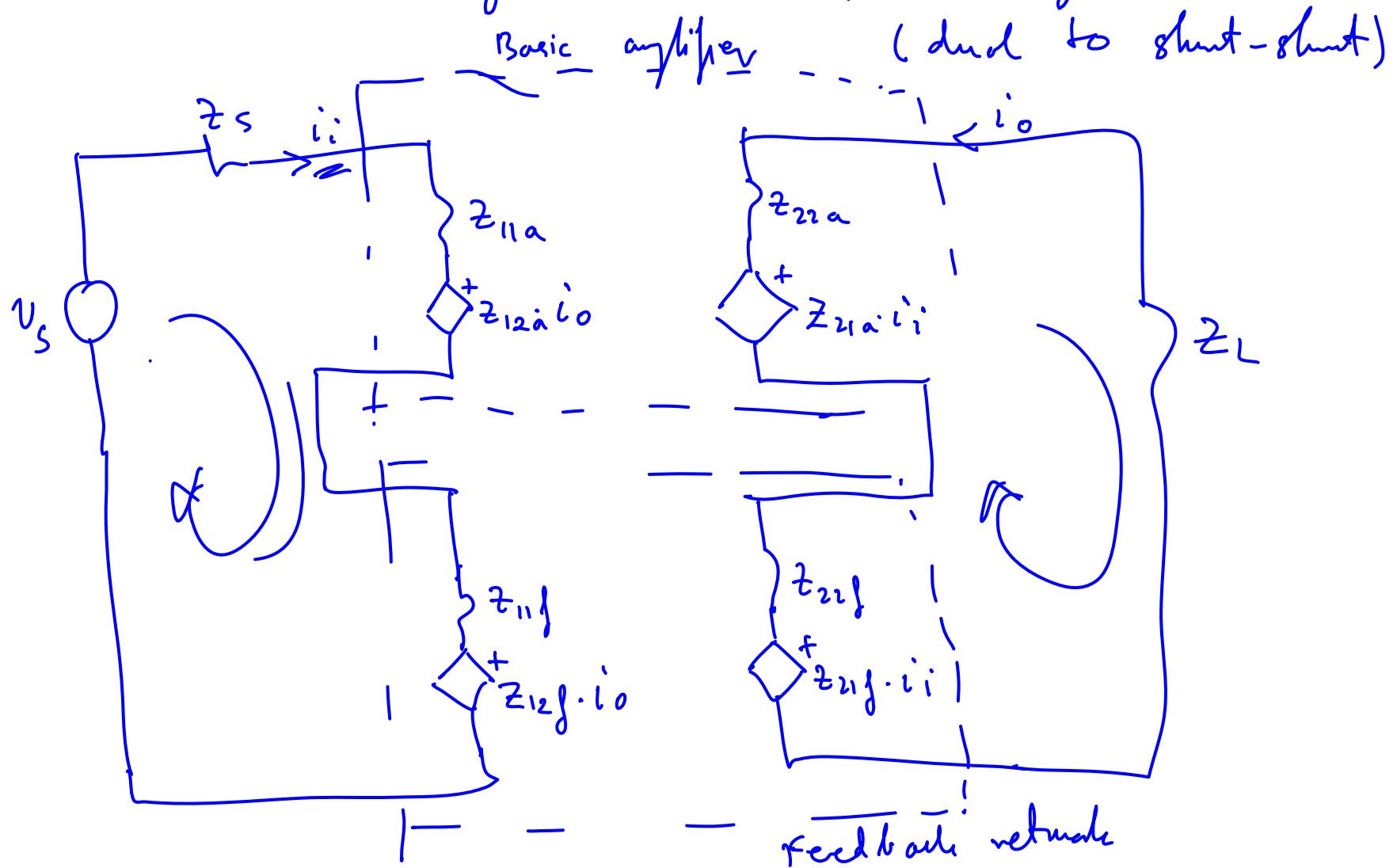

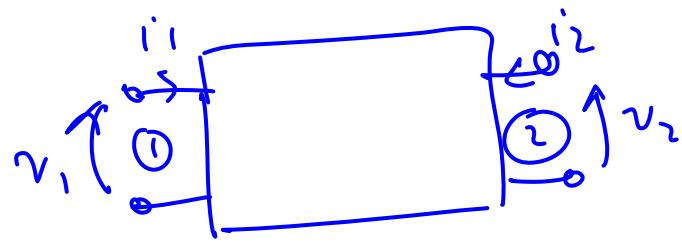

$$v_1 = z_{11} \cdot i_1 + z_{12} \cdot i_2$$

$$v_2 = z_{21} \cdot i_1 + z_{22} \cdot i_2$$

$$z_{11} = \frac{v_1}{i_1} \Big|_{i_2=0}$$

$$z_{21} = \frac{v_1}{i_2} \Big|_{i_1=0}$$

$$z_{22} = \frac{v_2}{i_1} \Big|_{v_2=0}$$

$$z_{12} = \frac{v_2}{i_2} \Big|_{i_1=0}$$

$$v_s = \underbrace{(z_s + z_{1a} + z_{1f})}_{z_i} \cdot i_i + (z_{na} + z_{nf}) \cdot i_o$$

$$0 = (z_{21a} + z_{2if}) \cdot i_i + \underbrace{(z_{22a} + z_{2if})}_{z_o} \cdot i_o$$

$$\hookrightarrow i_i = -\frac{z_o}{z_{21a} + z_{2if}} \cdot i_o$$

$$\frac{v_s}{i_o} = -\frac{z_i z_o}{z_{21a} + z_{2if}} + (z_{na} + z_{nf}) ; \quad A_{c,L} = \frac{i_o}{v_s}$$

$$A_{c,L} = \frac{- (z_{na} + z_{nf})}{z_i z_o - (z_{na} + z_{nf})(z_{na} + z_{nf})}$$


$$= \frac{- (z_{na} + z_{nf})}{z_i z_o} = a$$

$$= \frac{a}{1 + \frac{(z_{21a} + z_{2if})}{(z_{na} + z_{nf})}} = \frac{a}{1 + \alpha f}$$


Often:  $|z_{21a}| \ll |z_{21f}|$

$$|z_{21f}| \ll |z_{21a}|$$

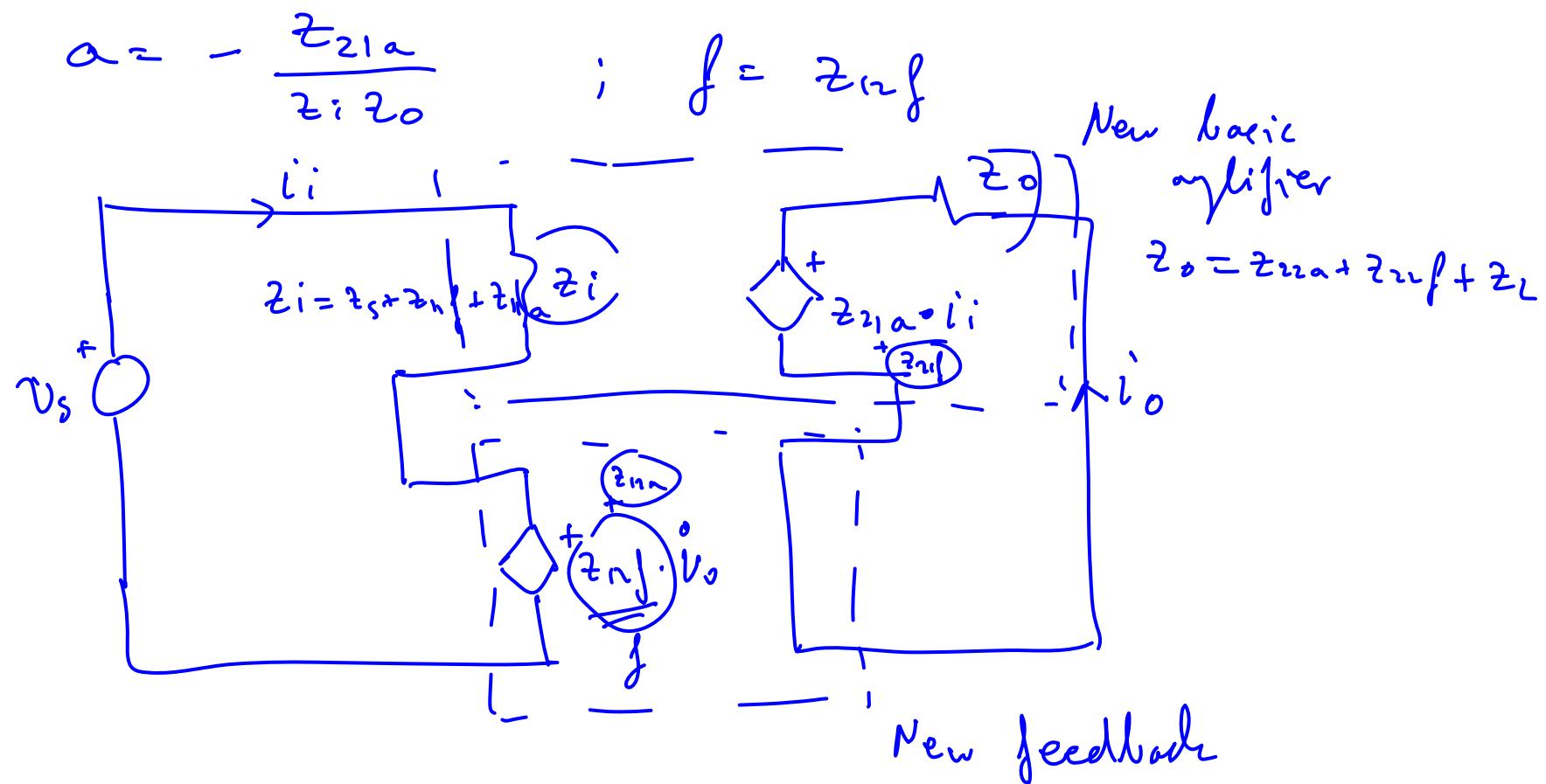
unilateral amplifier  
& feedback assumptions



In practice:

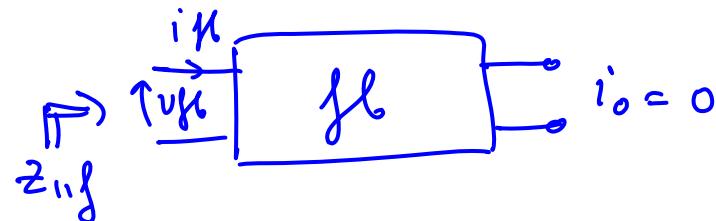


$$z_{11f} = \frac{v_{11f}}{i_1f} = \frac{v_t}{i_t} \quad |_{i_o = 0}$$

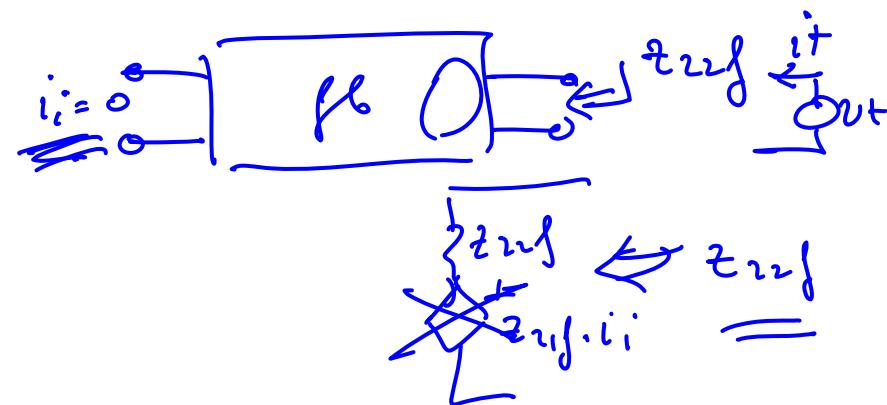


$$Z_i = z_i \cdot (1+T) \quad \text{✓ Series}$$
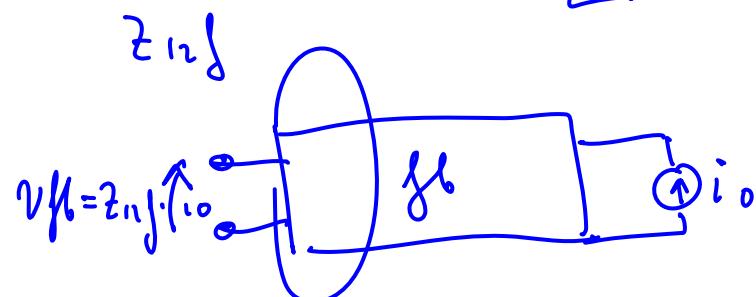
$$Z_o = z_o (1+T) \quad \text{✓ series}$$





$$z_{11f} = \frac{v_{11f}}{i_o} \quad |_{i_i = 0} = \infty$$

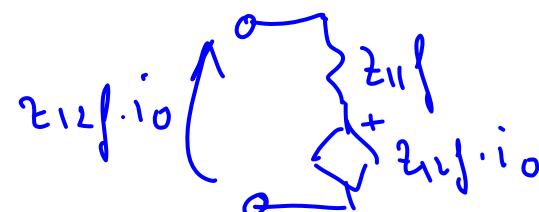

Example:


EE140 Spring 2014  
Vladimir Stojanović

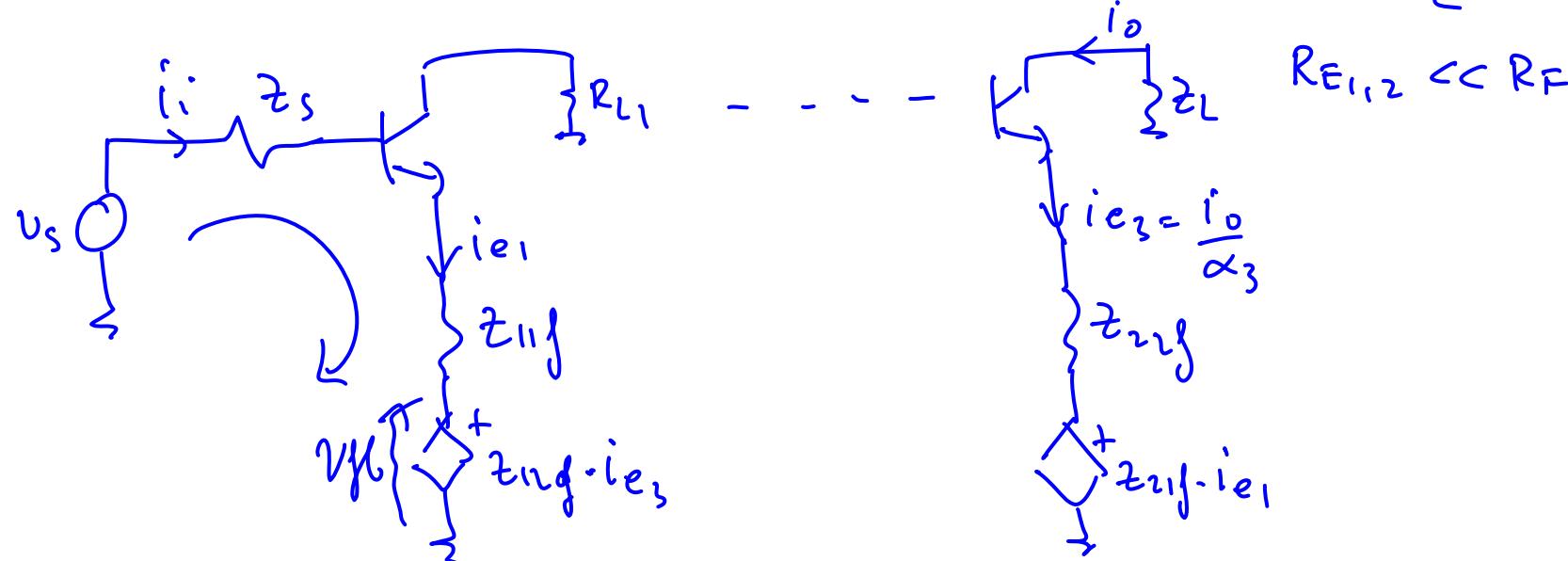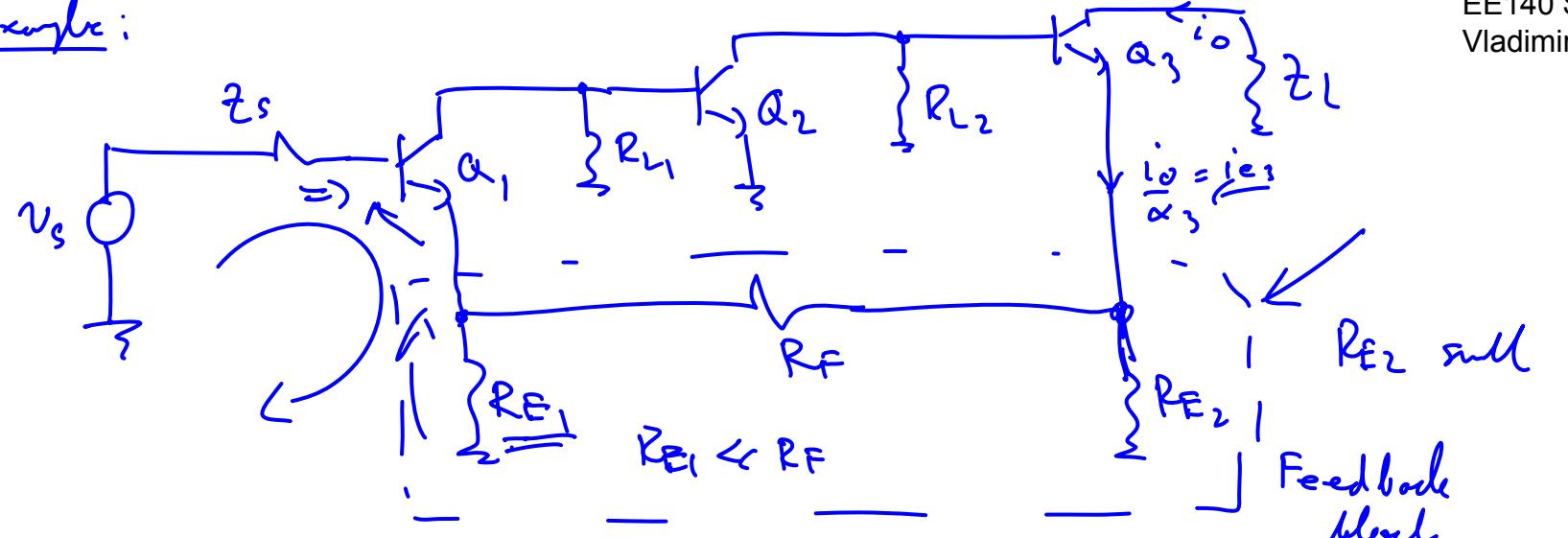

$$v_s = i_1 \cdot z_s + v_{be} + i_{e1} \cdot z_{11f} + z_{12f} \cdot i_{e3} \frac{i_o}{\alpha_3}$$

$$\rightarrow v_s - \frac{z_{11f}}{\alpha_1} \cdot i_o = i_1 z_s + v_{be} + i_{e1} \cdot z_{11f}$$

$$z_{12f} = \frac{v_1}{i_2} \Big|_{i_1=0} = \frac{R_{E2}}{R_{E1} + R_F + R_{E2}} \cdot R_{E1}$$

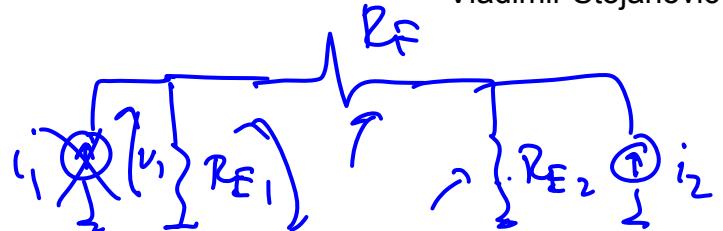

$$z_{22f} = \frac{v_2}{i_2} \Big|_{i_1=0} = R_{E2} \parallel (R_F + R_{E1})$$

$$z_{11f} = \frac{v_1}{i_1} \Big|_{i_2=0} = R_{E1} \parallel (R_F + R_{E2})$$

$$z_{21f} = \frac{v_2}{i_1} \Big|_{i_2=0} = \frac{R_{E1}}{R_{E1} + R_F + R_{E2}} \cdot R_{E2}$$

← can still neglect in feed-forward direction  
- - -  
open bc series fb.  
open bc series at input

