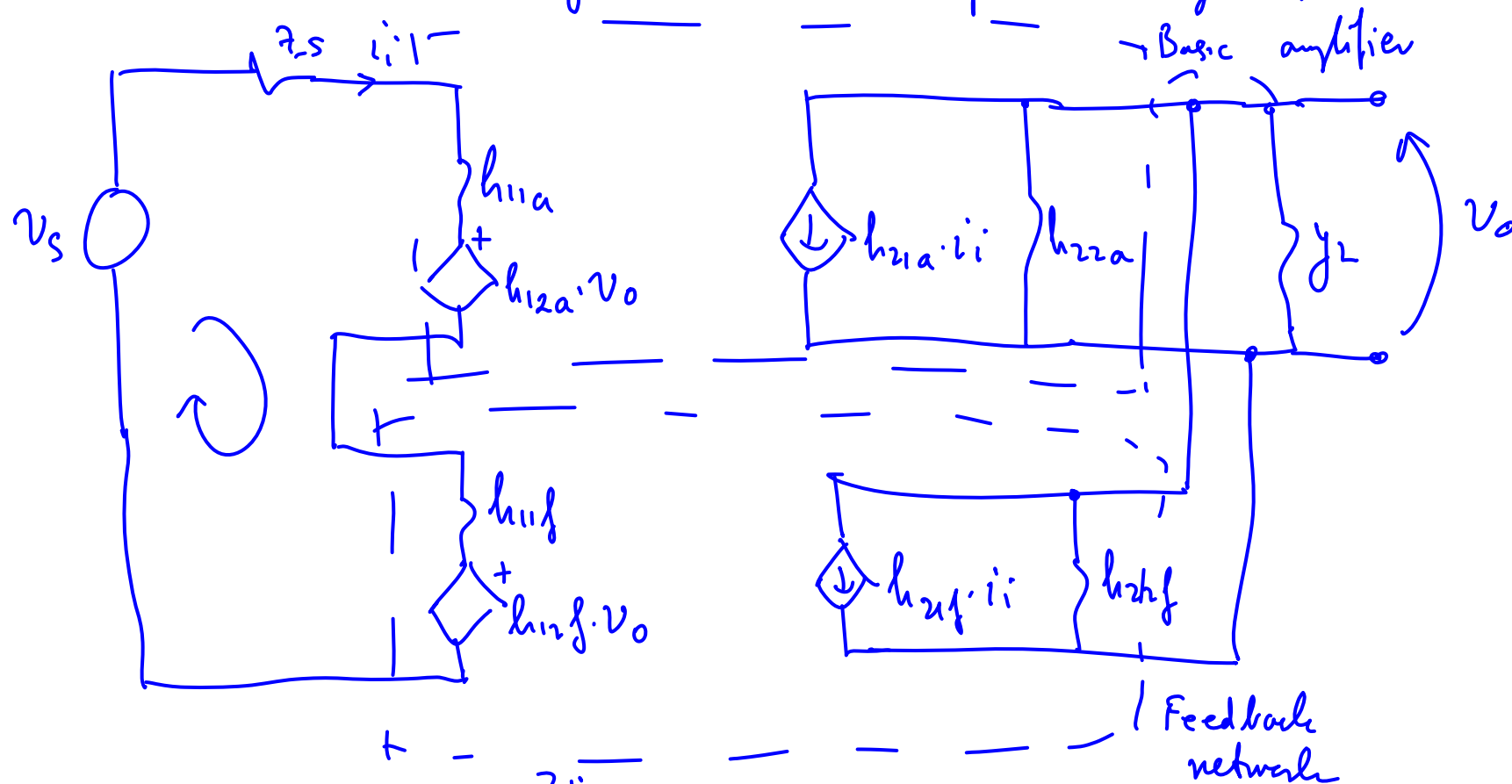


# Series-shunt feedback (2-port analysis)



$$v_s = \underbrace{(z_s + h_{11a} + h_{11f})}_{z_i} \cdot \underline{i_i} + (h_{12a} + h_{12f}) \cdot \underline{v_o}$$

$$0 = (h_{21a} + h_{21f}) \cdot \underline{i_i} + \underbrace{(y_L + h_{22a} + h_{22f})}_{y_o} \cdot \underline{v_o}$$

$$\underline{i_i} = \frac{-y_o}{h_{11a} + h_{11f}} \cdot \underline{v_o}$$

$$\frac{v_o}{v_s} = A_{vL} = \frac{-(h_{21a} + h_{21f})}{y_o z_i - (h_{21a} + h_{21f})(h_{12a} + h_{12f})}$$

$$= \frac{\left( \frac{-(h_{21a} + h_{21f})}{y_o z_i} \right) a}{1 + \underbrace{\frac{-(h_{21a} + h_{21f})}{y_o z_i}} \cdot \underbrace{(h_{12a} + h_{12f})}_f}$$



$$|h_{21a}| \gg |h_{21f}|$$

&

$$|h_{12a}| \ll |h_{12f}|$$





unilateral flow assumption.  $\Rightarrow$

$$a = -\frac{h_{21a}}{y_o z_i}, \quad f = h_{12f}$$



$$Z_i = z_{ia} \cdot (1+T) \quad , \quad Z_o = \frac{z_{oa}}{1+T} = \frac{1}{y_{oa}(1+T)}$$

Example:

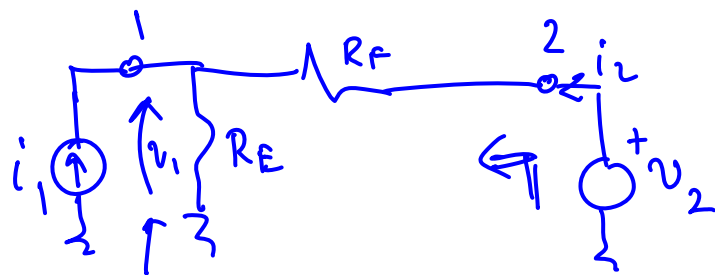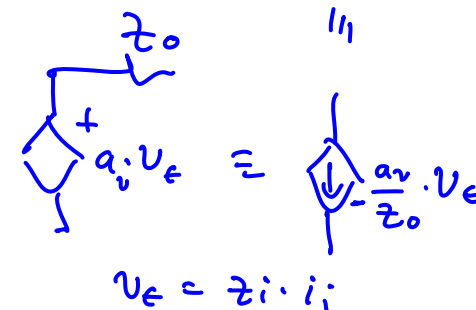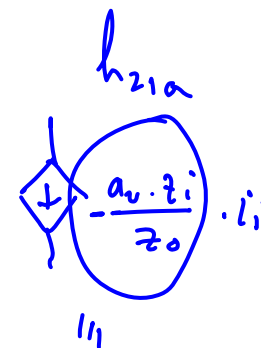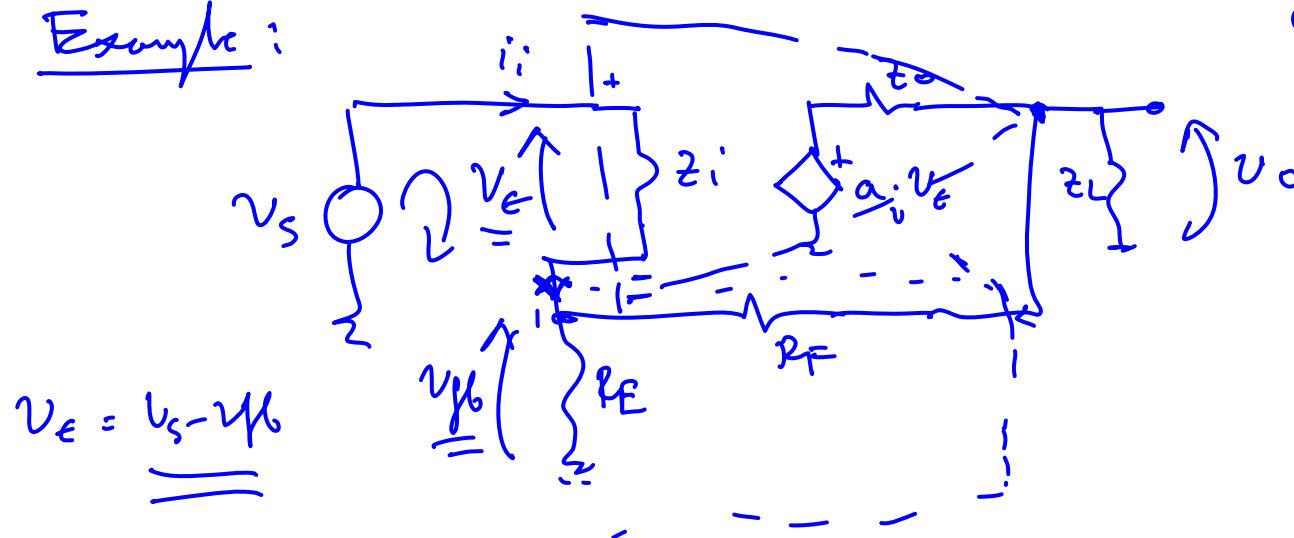


$$h_{22f} = \frac{i_2}{v_2} \Big|_{i_1=0} = \frac{1}{R_E + R_F}$$


$$h_{11f} = \frac{v_1}{i_1} \Big|_{v_2=0} = R_E \parallel R_F$$

$$f = h_{12f} = \frac{v_1}{v_2} \Big|_{i_1=0} = \frac{R_E}{R_E + R_F}$$




$$h_{21f} = \frac{i_2}{i_1} \Big|_{v_2=0} = -\frac{R_E}{R_E + R_F}$$

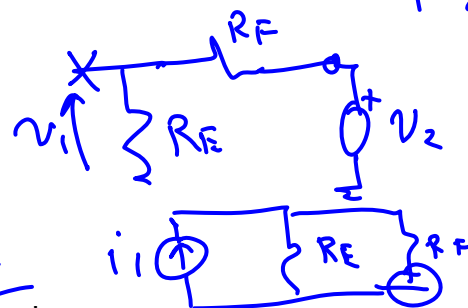

$$|h_{21a}| > |h_{21f}|$$

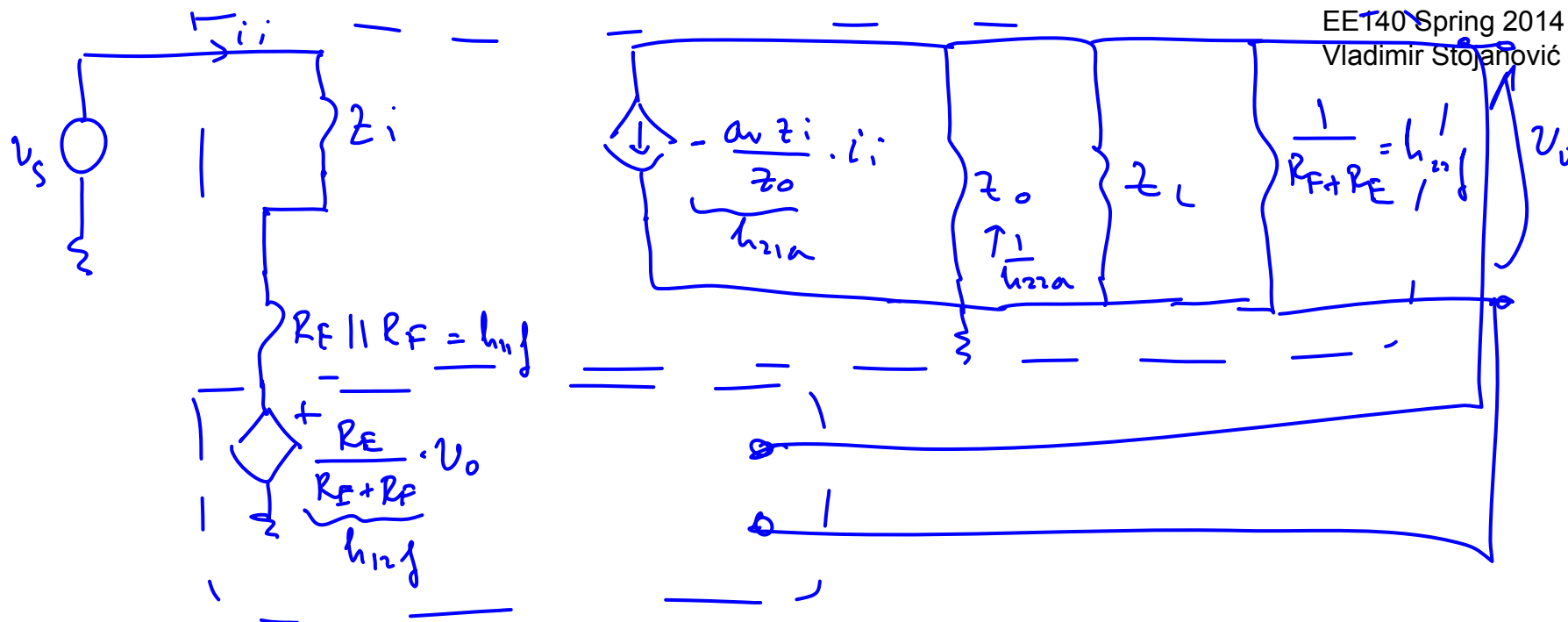
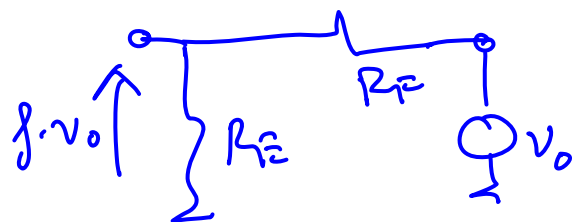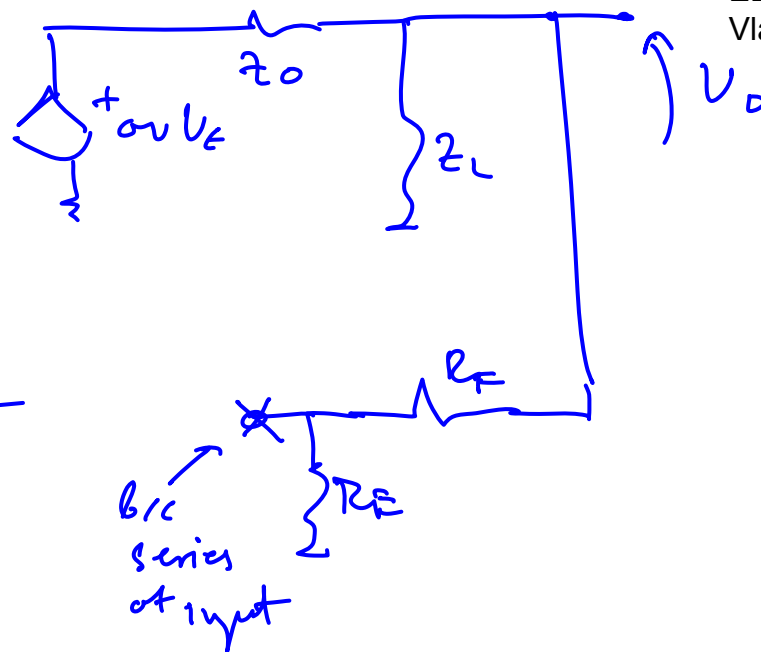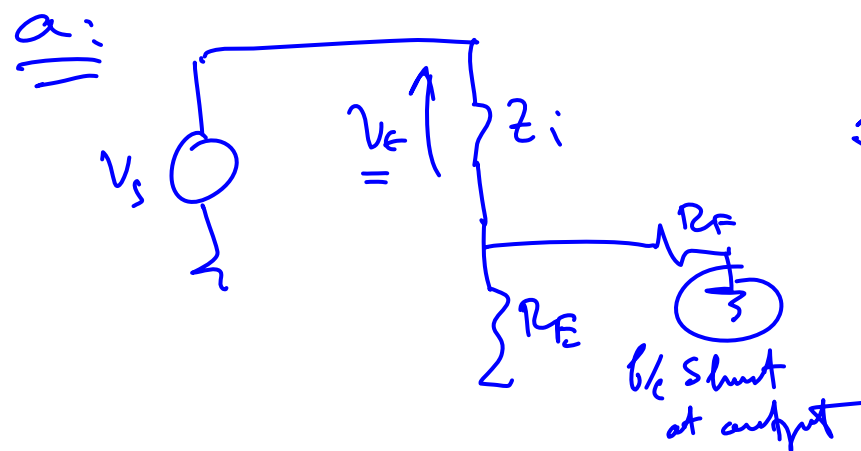
$$\begin{aligned}
 A &= - \frac{h_{21a}}{y_{oi} z_{in}} = - \frac{- \frac{a_v z_i}{z_o}}{\left( \frac{1}{z_o} + \frac{1}{z_L} + \frac{1}{R_F + R_E} \right) (z_i + R_F \parallel R_F)} = \\
 &= \frac{z_i}{z_i + R_F \parallel R_F} \cdot a_v \cdot \frac{z_L \parallel (R_E + R_F)}{z_o + z_L \parallel (R_E + R_F)} \quad \text{in practice.}
 \end{aligned}$$






$$\underline{a} = \underline{h_{12}} = \frac{R_E}{R_E + R_F}$$

$$\underline{a} = \frac{Z_i}{Z_i + R_E \parallel R_F} \cdot a_v \cdot \frac{Z_L \parallel (R_E + R_F)}{Z_o + Z_L \parallel (R_E + R_F)}$$



$$Z_{in} = Z_i + R_E \parallel R_F, \quad Z_{out} = Z_o \parallel Z_L \parallel (R_E + R_F)$$

$$Z_i = Z_{in} (1 + \beta), \quad Z_o = \frac{Z_{out}}{1 + \beta}$$


Example 2.

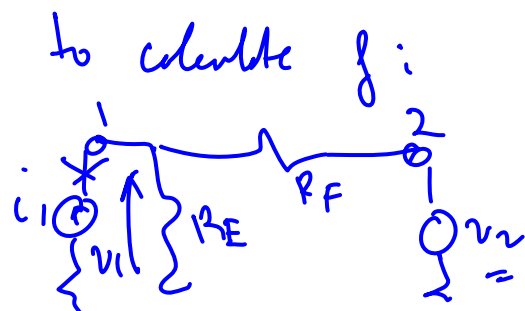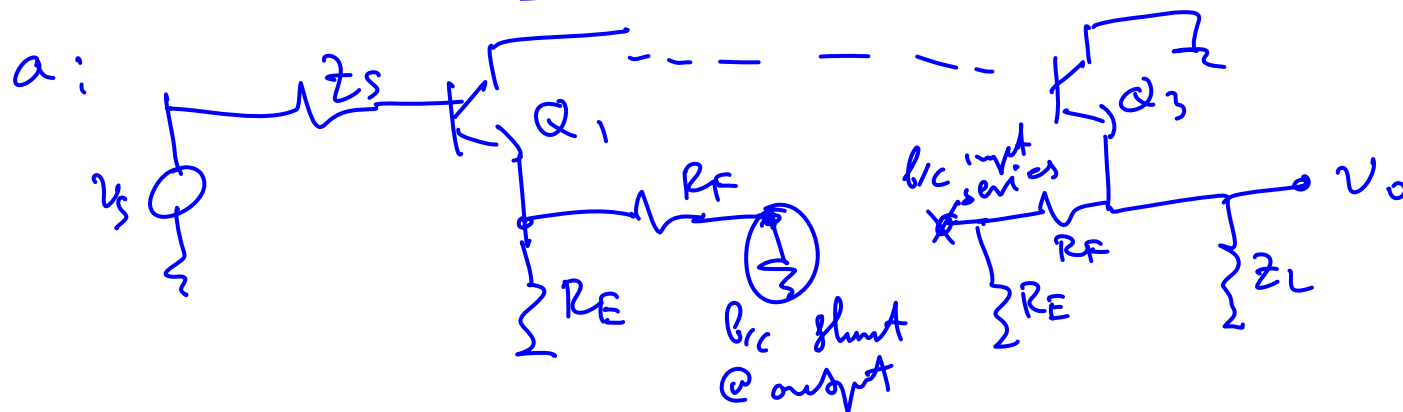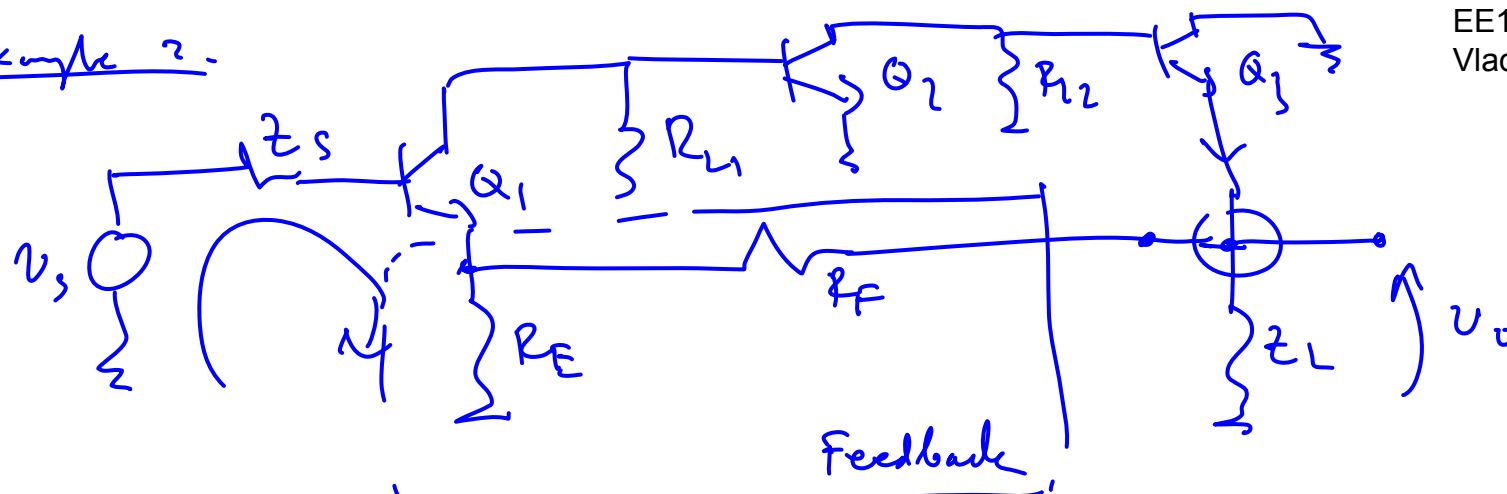


$$g = \frac{R_E}{R_E + R_F}$$

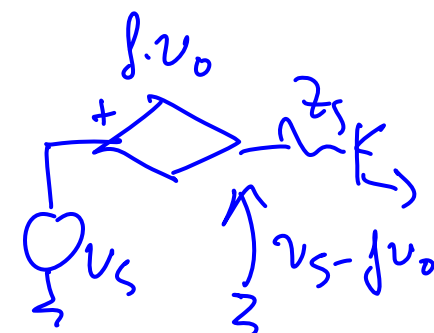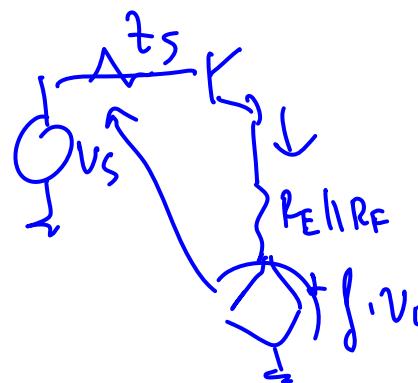


Shunt - Series feedback:

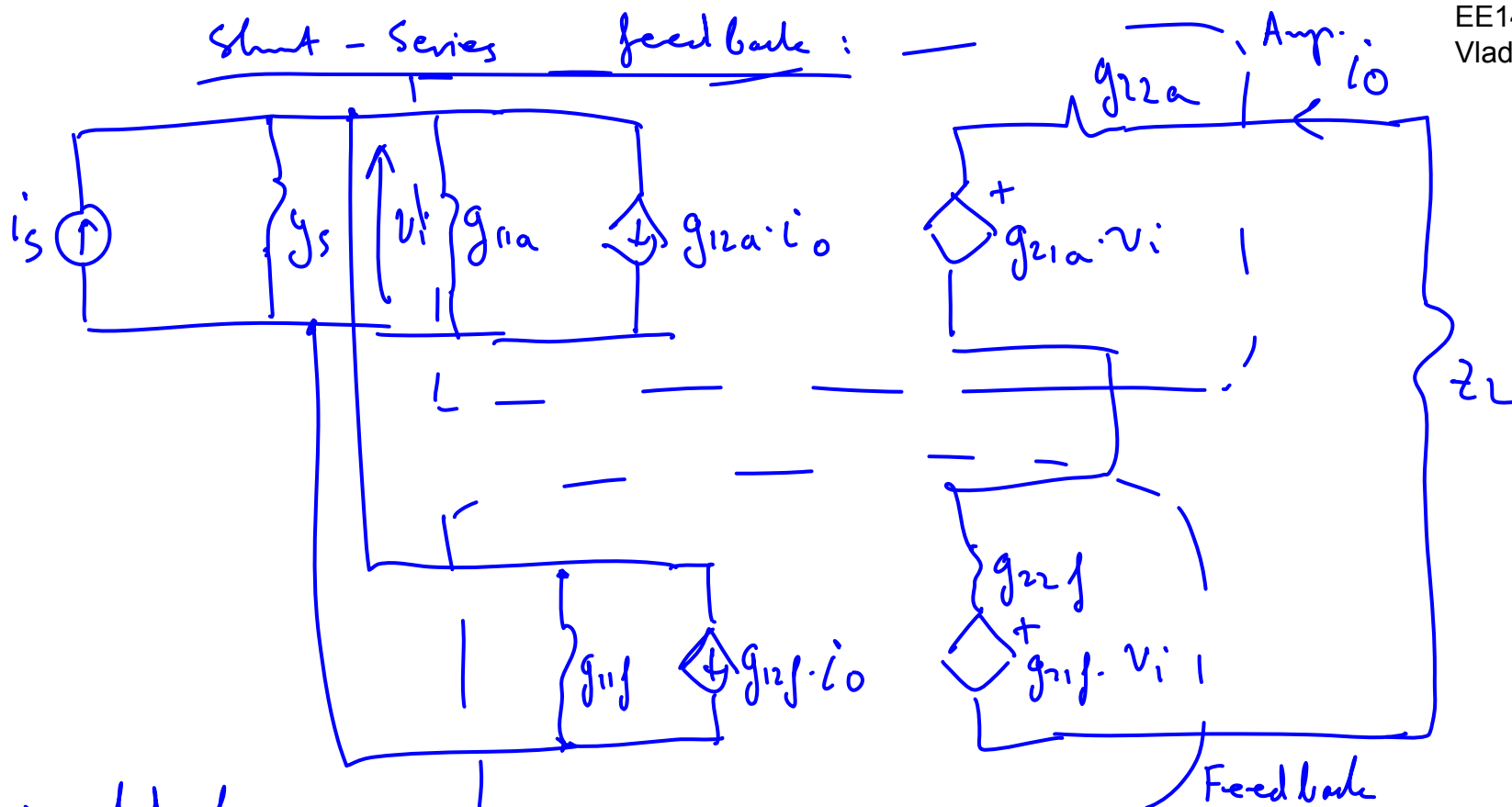


unilateral:

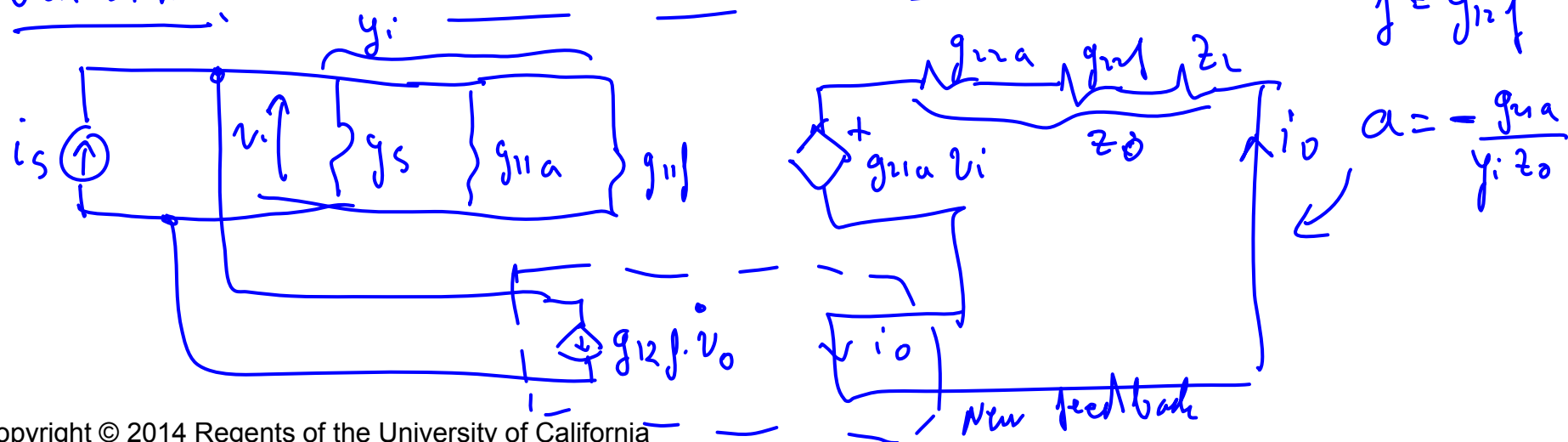

Example:

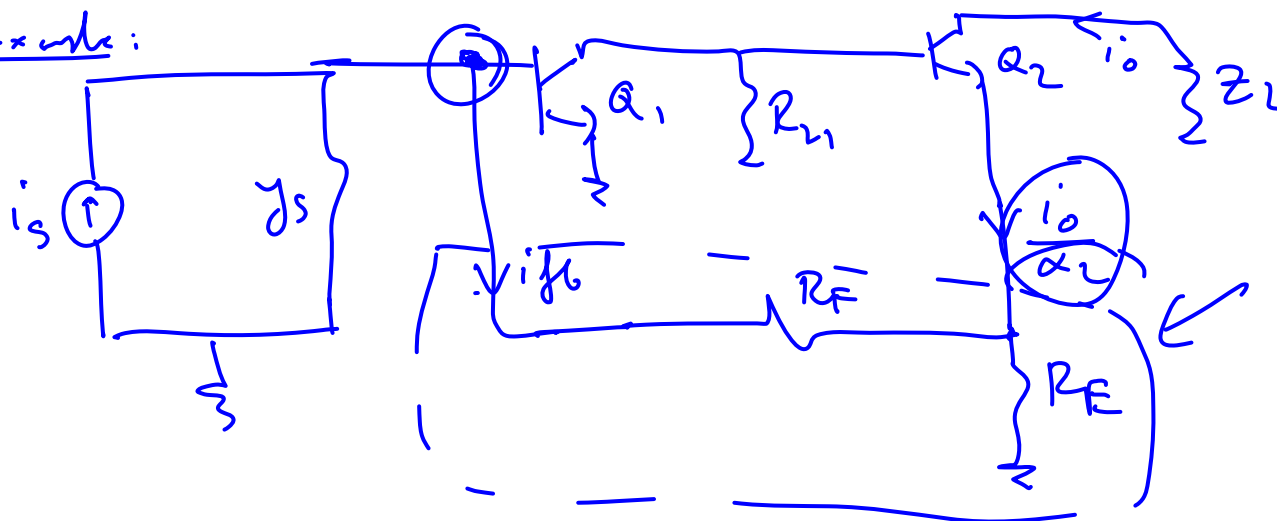


For a:

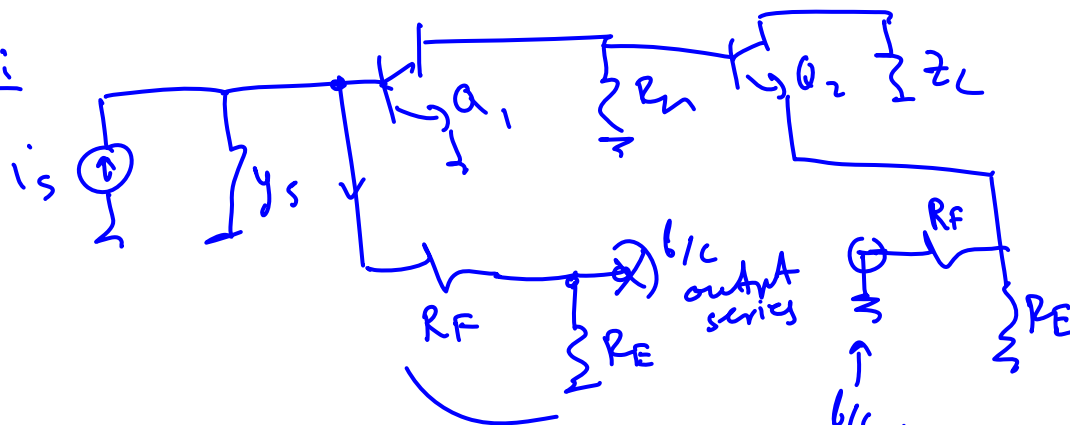

$\Rightarrow a$

$g_{11f}, g_{22f}$

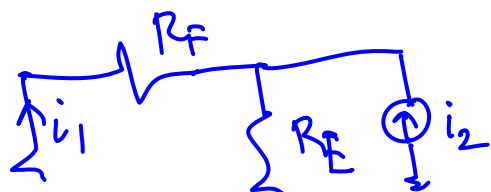

$$g_{12f} = \frac{i_1}{i_2} \Big|_{v_1=0} = -\frac{R_E}{R_E + R_F}$$

$$f = -\frac{R_E}{(R_F + R_E)\alpha_2}$$