






Summary Feedback type	2-port parameters	Output value	Input value	T.F.	Z_i	Z_o	To calc. loading		
							At input	At output	
shunt-shunt	y	v_o	i_s	$\frac{v_o}{i_s}$ trans- resist.	Low	Low	s.c. output feedback node	s.c. input feedback node	Apply voltage at output, and s.c. input f.b. ports & measure current \leftarrow $f = \frac{i_{in}}{v_o}$ 
<u>shunt-series</u>	g	i_o	i_s	$\frac{i_o}{i_s}$ current gain	Low	High	o.c. output feedback node	s.c. input feedback node	Apply current at output and s.c. input f.b. port & measure current $f = \frac{i_{in}}{i_o}$ 
<u>series-shunt</u>	h	v_o	v_s	$\frac{v_o}{v_s}$ voltage gain	High	Low	s.c. output feedback node	o.c. input feedback node	$f = \frac{v_{in}}{v_o}$ 
series-series	z	i_o	v_s	$\frac{i_o}{v_s}$ trans cond.	High	High	o.c. output feedback node	o.c. input feedback node	Apply voltage at output and o.c. input f.b. port & measure voltage. $f = \frac{v_{in}}{i_o}$ 


$$g_m \approx 38.4 \text{ mS}$$

$$r_{\pi} = 5.7 \text{ k}\Omega$$

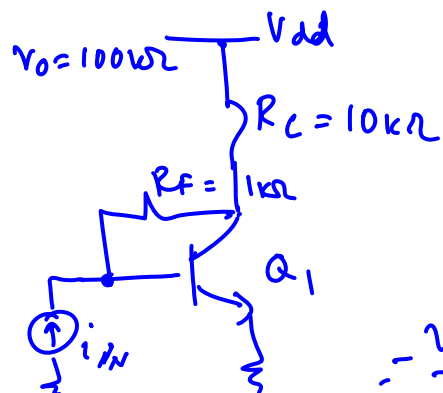Comparing $\underline{\underline{RR}}$ with a.f.
return ratio loop gain (T)





$\underline{\underline{RR}}$:

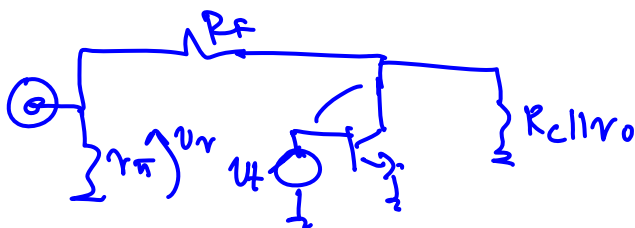


$$-\frac{v_r}{v_t} = RR = g_m \cdot r_{\pi} \frac{R_C || r_o}{r_{\pi} + R_F + R_C || r_o} = \frac{g_m}{R_F} (r_{\pi} || R_F) (r_o || R_C || (r_{\pi} + R_F))$$

$$RR \approx \underline{\underline{119}}$$

2-port:

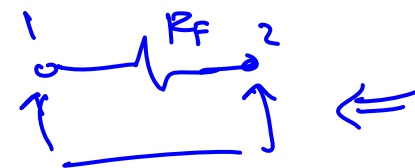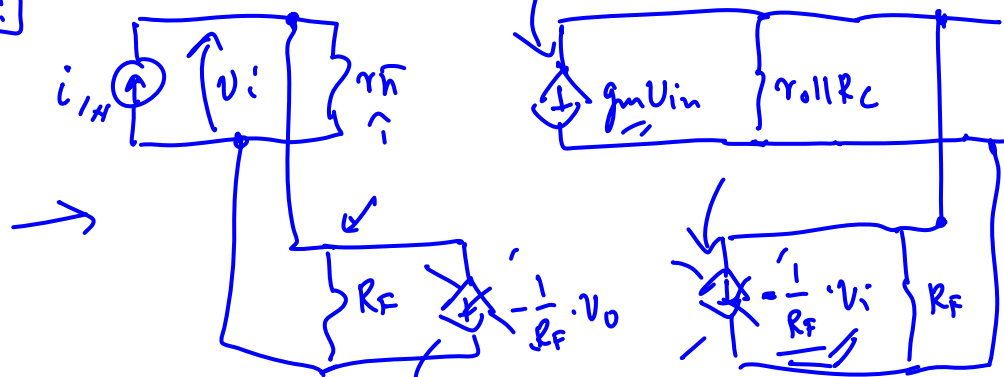

$$a.f. = -(g_m - \frac{1}{R_F}) (r_{\pi} || R_F) (R_F || r_o || R_C)$$

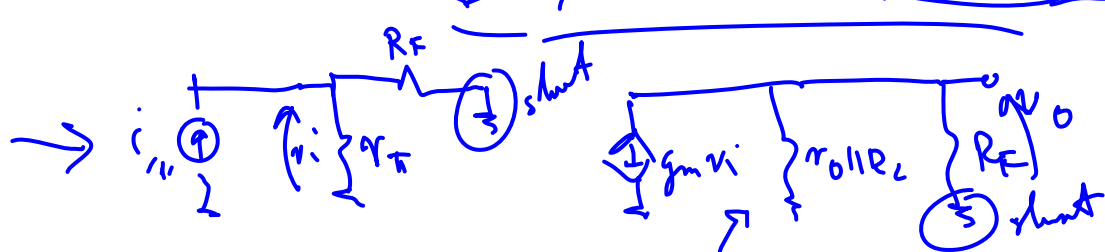

unilateral approx: $(-\frac{1}{R_F})$


$$|y_{21}| = \frac{1}{R_F} = 1 \text{ mS} \ll |y_{21c}| = g_m \approx 38.4 \text{ mS}$$

$$a \cdot f = \underline{28} \quad \approx 29 \quad \text{with milot omission (i.e. neglect } (-\frac{1}{R_F}) = g_{m1f} \text{)}$$

$$A_{c,2} = \frac{1}{f} \cdot \frac{af}{1+af} = -966 \Omega \quad \approx -967 \Omega$$



$$A_{eq} = -g_m \cdot (r_o || R_C || (r_{\pi} + R_F)) \cdot (r_{\pi} || R_F) = (-R_F) \cdot R_R$$

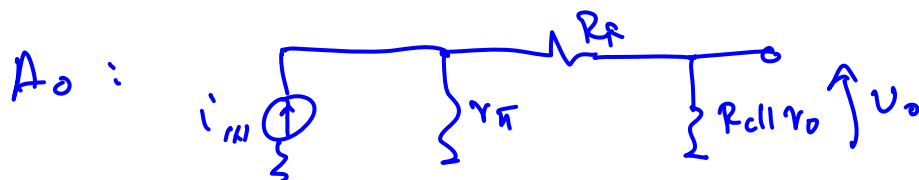

$$A_o = \frac{r_{\pi}}{R_F + r_{\pi} + R_C || r_o} \cdot R_C || r_o$$

$$A_{c,2} = \frac{A_{eq} + A_o}{1 + R_R} = \left(-R_F + \frac{1}{g_m} \right) \frac{R_R}{1 + R_R} = \frac{1}{R_F} \cdot (r_{\pi} || R_F) (R_C || r_o || (r_{\pi} + R_F))$$

$$\approx \frac{R_R}{g_m}$$

$$= (-974 \Omega) \cdot \frac{119}{120} \approx \boxed{-966 \Omega}$$

When is $RR = a.f$?

$$RR \approx a.f$$

when:

$$① \quad |y_{21a}| \gg |y_{21f}|$$

$$② \quad |(y_{11a} + y_{11f})(y_{22a} + y_{22f})| \gg |(y_{12a} + y_{12f}) \cdot y_{21f}|$$

$$\underline{RR(y_{11a})} = a.f$$

replace y with g, h, z

y_s, y_z lumped into y_{11a}, y_{22a}

