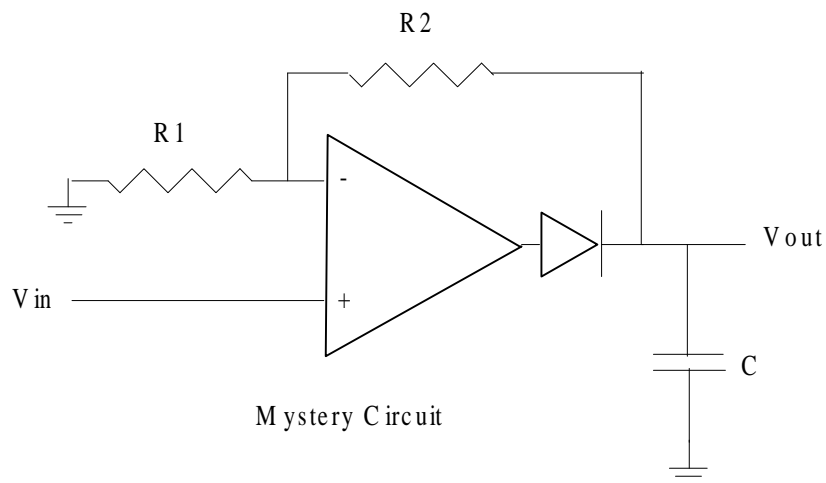


# Some Notes on Operational Amplifier Based Circuits

by  
Shane Cantrell




## Ideal Operational Amplifiers

Ideal operational amplifiers have infinite gain. If the voltage at the + terminal is larger than the voltage at the - terminal then the output voltage will increase until it reaches the positive power supply. Likewise, if the voltage at the + terminal is smaller than the voltage at the - terminal then the output voltage will decrease until it reaches the negative power supply. Of course, if both terminals are equal, the output will no longer be driven by the op amp. These characteristics allow feedback to be used in order to drive the output of the op amp to a useful value, and, for that reason, all of the circuits that I will be discussing use feedback.
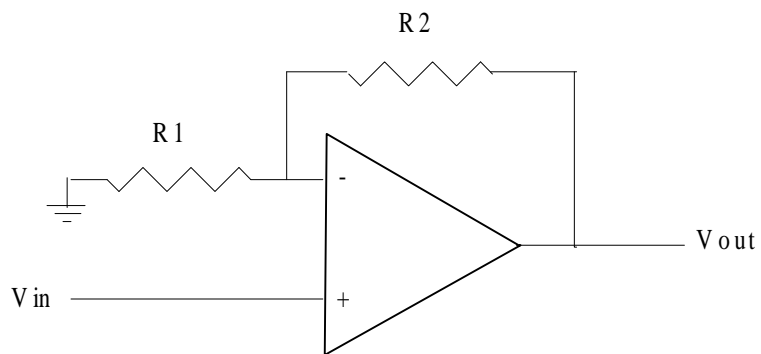
## Non Inverting Amplifier

Non inverting amplifiers are very powerful because you can amplify a signal without having a negative rail (depending on the op amp's specifications). When a voltage is applied to  $V_{in}$ ,  $V_{out}$  begins to rise because of the infinite amplification. This rising voltage is consequently applied across the voltage divider of  $R_1$  and  $R_2$  in such a way that the voltage at the negative terminal of the op amp begins to rise as well. Once the voltage at the negative terminal has reached the same value as the positive terminal, the amplification stops and  $V_{out}$  remains constant. If for some reason the output voltage is pushed further up, the voltage at  $R_1$  will go up causing the op amp to have a negative voltage across it and pull  $V_{out}$  back down again. The formula expressing the ideal  $V_{out}$  is


$$V_{in} \left( \frac{R_1 + R_2}{R_1} \right)$$



Non Inverting Amplifier
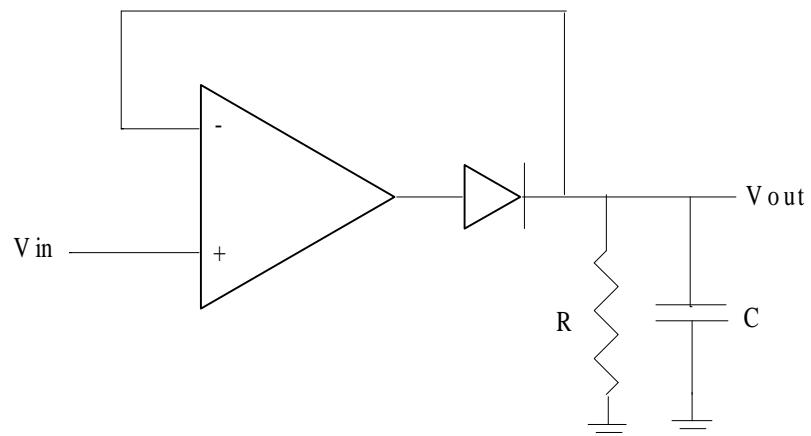
## Non Inverting Peak Detector

Peak detectors allow you to determine the highest voltage value that a signal produces over a period of time. The one shown here does not do precisely this, but for many slowly varying signals it is good enough. The diode located at the output of the op amp allows the op amp to add charge to the capacitor  $C$  while not allowing it to discharge the capacitor. Because of this,  $V_{out}$  will rise until both the -




Simple Peak Detector

and + terminals of the op amp are equal. Then, if  $V_{in}$  drops, the op amp will no longer be pumping charge into the capacitor, and the resistor  $R$  will allow charge to slowly escape and the voltage at  $V_{out}$  to drop.  $R$  and  $C$  must be picked based on how fast you want  $V_{out}$  to drop after detecting a peak.
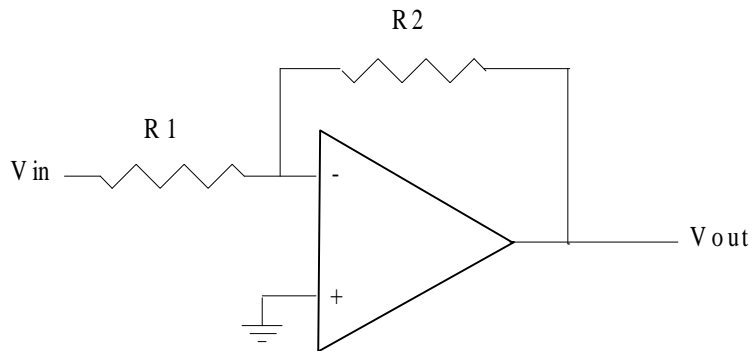
### Inverting Amplifier

Inverting amplifiers invert your signal and, as a result, require a negative power supply (assuming  $V_{in}$  is positive). In this circuit, the current flowing from  $V_{in}$  goes through both  $R_1$  and  $R_2$ . As you can see from the location of the + and - terminals, the op amp will pull down  $V_{out}$  until the voltage at the - terminal is equal to ground. Once this happens  $V_{out}$  can be found by the following equation:

$$V_{out} = -V_{in} \left( \frac{R_2}{R_1} \right)$$




Inverting Amplifier

### Inverting Voltage Adder

The inverting voltage adder is based on the exact same principle as the inverting amplifier. The op amp pulls  $V_{out}$  down such that the - terminal is the same as ground and the currents produced by  $V_1$  and  $V_2$  both add at the negative terminal and produce a summed voltage drop across the third resistor on the way to  $V_{out}$ . Thus  $V_{out}$  can be calculated by the following equation:

$$V_{out} = -(V_1 + V_2)$$

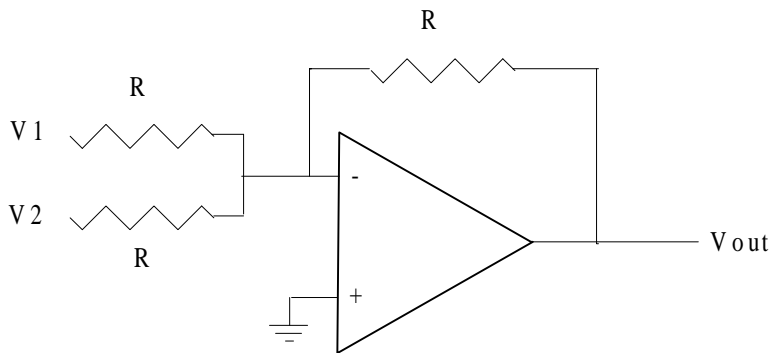Additional voltage inputs can also be tied to the - terminal if necessary.



Inverting Voltage Adder