

# EE247


## Lecture 17

### ADC Converters



- Sampling
  - Sampling switch induced distortion
    - Sampling switch conductance dependence on input voltage
  - Sampling switch charge injection
    - Complementary switch
    - Use of dummy device
    - Bottom-plate switching
  - Track & hold circuit
  - S/H circuit incorporating gain
- ESD protection impact on converter performance
 
### Practical Sampling

- kT/C noise
$$C \geq 12k_B T \left( \frac{2^B - 1}{V_{FS}} \right)^2$$
- Finite  $R_{sw}$  → limited bandwidth
$$R \ll -\frac{1}{2f_s C} \frac{1}{\ln(2^B - 1)}$$
- $g_{sw} = f(V_{in})$  → distortion
$$g_{ON} = g_o \left( 1 - \frac{V_{in}}{V_{DD} - V_{th}} \right) \quad \text{for} \quad g_o = mC_{ox} \frac{W}{L} (V_{DD} - V_{th})$$
- Switch charge injection
- Clock jitter




## Sampling Distortion

  

- Effect of lower supply voltage on sampling distortion  
 $\rightarrow$  HD3 increases by  $(V_{DD1}/V_{DD2})^2$   
 $\rightarrow$  HD2 increases by  $(V_{DD1}/V_{DD2})$


 
## Sampling Distortion

- SFDR is sensitive to sampling distortion to improve distortion
  - Larger VDD
  - Higher sampling bandwidth
- Solutions:
  - Overdesign  $\rightarrow$  Larger switches  
 $\rightarrow$  Increased switch charge injection  
 $\rightarrow$  Increased nonlinear S & D junction C
  - Maximize VDD/VFS  
 $\rightarrow$  Decreased dynamic range if VDD const.
  - Complementary switch
  - Constant & max.  $V_{GS}$  ?  
 $f(V_{in})$




10bit ADC    $T/\tau = 20$   
 $V_{DD} - V_{th} = 2V$     $V_{FS} = 1V$

# Complementary Switch

  


- Complementary n & p switch advantages:
  - Increases the overall conductance
  - Linearize the switch conductance for the range  $V_{tp} < V_I < V_{dd} - V_{tn}$
 
## Complementary Switch Issues Supply Voltage Evolution




- Supply voltage scales down with technology scaling
- Threshold voltages do not scale accordingly
 
## Complementary Switch Effect of Supply Voltage Scaling




- As supply voltage scales down input voltage range for constant  $g_o$  shrinks  
→ Complementary switch not effective when  $V_{DD}$  becomes comparable to  $V_{th}$

## Boosted & Constant $V_{GS}$ Sampling

 

- Increase gate overdrive voltage as much as possible + keep  $V_{GS}$  constant
  - Switch overdrive voltage is independent of signal level
  - Error from finite  $R_{on}$  is linear (to first order)
  - Lower  $R_{on}$  achieved → lower time constant


## Constant $V_{GS}$ Sampling

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 9


## Constant $V_{GS}$ Sampling Circuit

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 10


# Clock Voltage Doubler

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 11

## Constant $V_{GS}$ Sampler: $\Phi$ LOW

 


EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 12


## Constant $V_{GS}$ Sampler: $\Phi$ HIGH

Constant  $V_{GS}$  Switch: P is HIGH

 


- $C3$  previously charged to  $VDD$
- $M8$  &  $M9$  are on:  $C3$  across G-S of  $M11$
- $M11$  on with constant  $V_{GS} = VDD$

## Constant $V_{GS}$ Sampling

 


## Complete Circuit

 


Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.

## Advanced Clock Boosting

 

[H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6μm CMOS with over 80-dB SFDR," IEEE J. Solid-State Circuits, pp. 1769-1780, Dec. 2000]


## Advanced Clock Boosting

 


[M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Techn. Papers, pp. 314.]

- Gate tracks average of input and output, reduces effect of I-R drop at high frequencies
- Bulk also tracks signal  $\Rightarrow$  reduced body effect (technology used allows connecting bulk to S)
- SFDR = 76.5dB at  $f_{in}=200\text{MHz}$  (measured)
 
## Switch Off-Mode Feedthrough Cancellation



 
High-pass feedthrough paths past an open switch



Feedthrough cancellation with a dummy switch


Ref: [M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Techn. Papers, pp. 314.]

# Practical Sampling

 

- $R_{sw} = f(V_{in}) \rightarrow$  distortion
- Switch charge injection


## Sampling Switch Charge Injection

 


- First assume  $V_{IN}$  is a DC voltage
- When switch turns off  $\rightarrow$  offset voltage induced on  $C_s$
- Why?
 
## Sampling Switch Charge Injection

MOS xtor operating in triode region  
Cross section view





 Distributed channel resistance &  
gate & junction capacitances




- Channel → distributed RC network
- Channel to substrate junction capacitance → distributed & variable
- Over-lap capacitance  $C_{ov} = L_D \cdot W \cdot C_{ox}$  associated with GS & GD overlap

## Switch Charge Injection Slow Clock

  

- Since clock fall time  $\gg$  device speed  
→ During the period ( $t$ - to  $t_{off}$ ) current in channel discharges channel charge into source
- Only source of error → Charge transfer from  $C_{ov}$  into  $C_s$

## Switch Charge Injection Slow Clock

 


$$\Delta V = -\frac{C_{ov}}{C_{ov} + C_s} (V_i + V_{th} - V_L)$$


$$\approx -\frac{C_{ov}}{C_s} (V_i + V_{th} - V_L)$$

$$V_o = V_i (I + \epsilon) + V_{os}$$
 
$$\text{where } \epsilon = -\frac{C_{ov}}{C_s}; V_{os} = -\frac{C_{ov}}{C_s} (V_{th} - V_L)$$



 
## Switch Charge Injection Slow Clock- Example





$$C_{ov} = 0.3fF/\text{m} \quad C_{os} = 5fF/\text{m}^2 \quad V_{th} = 0.5V$$

$$\epsilon = -\frac{C_{ov}}{C_s} = -\frac{12\text{m} \times 0.3fF/\text{m}}{1pF} = -.36\% \rightarrow 7-bit$$
 
$$V_{os} = -\frac{C_{ov}}{C_s} (V_{th} - V_L) = -1.8mV$$



## Switch Charge Injection Fast Clock

  

- Sudden gate voltage drop  $\rightarrow$  no gate voltage to establish current in channel  $\rightarrow$  channel charge has no choice but to escape out towards S & D

## Switch Charge Injection Fast Clock


$$\Delta V_o = -\frac{C_{ov}}{C_{ov} + C_s} (V_H - V_L) - \frac{I}{2} \times \frac{Q_{ch}}{C_s}$$

$$\approx -\frac{C_{ov}}{C_{ov} + C_s} (V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}(L-2L_D)((V_H - V_i - V_{th}))}{C_s}$$

$$V_o = V_i(1+\epsilon) + V_{os}$$



$$\text{where } \epsilon = -\frac{1}{2} \times \frac{WC_{ox}L}{C_s}$$
 
$$V_{os} = -\frac{C_{ov}}{C_s} (V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L(V_H - V_{th})}{C_s}$$



- Assumption  $\rightarrow$  channel charge divided between S & D 50% & 50%
- Source of error  $\rightarrow$  channel charge transfer + charge transfer from  $C_{ov}$  into  $C_s$
  
## Switch Charge Injection Fast Clock- Example




$$C_{ov} = 0.3fF/m \quad C_{ox} = 5fF/m^2 \quad V_{th} = 0.5V \quad V_{DD} = 3V$$

$$e = -I/2 \frac{WLC_{ox}}{C_s} = \frac{12m \times 0.35 \times 5fF/m}{1pF} = -2.1\% \rightarrow 4.5-bit$$

$$V_{os} = -\frac{C_{ov}}{C_s}(V_H - V_L) - \frac{I}{2} \times \frac{WC_{ox}L(V_H - V_{th})}{C_s} = -9mV - 26.3mV = -45.3mV$$

## Switch Charge Injection

 

→ Both errors are a function of clock fall time, input voltage level, source impedance & sampling capacitance

## Switch Charge Injection Error Reduction

- How do we reduce the error?  
→ Reduce size switch?




$$t = R_{ON} C_s = \frac{C_s}{m C_{ox} \frac{W}{L} (V_{GS} - V_{th})}$$
$$\Delta V_o = -\frac{I Q_{ch}}{2 C_s}$$
$$FOM = t \times \Delta V_o \approx \frac{C_s}{m C_{ox} \frac{W}{L} (V_{GS} - V_{th})} \times \frac{I}{2} \times \frac{W C_{ox} L ((V_H - V_i) - V_{th})}{C_s}$$
$$FOM \approx \frac{L^2}{m}$$

→ Reducing switch size increases  $\tau$  → increased distortion → not a viable solution  
→ Small  $\tau$  and  $\Delta V$  → use minimum channel length  
→ For a given technology  $\tau \propto \Delta V = \text{conts.}$

## Sampling Switch Charge Injection Summary

- Extra charge injected onto sampling capacitor @ switch device turn-off
  - Charge sharing with  $C_{ov}$
  - Channel charge transfer
- Issues:
  - DC offset
  - Input dependant error voltage → distortion
- Solutions:
  - Complementary switch?
  - Addition of dummy switches?
  - Bottom-plate sampling?
   
## Switch Charge Injection Complementary Switch



- In slow clock case if area of devices are equal  $\rightarrow$  effect of overlap capacitor for n & p devices cancel to first order (matching n & p area)

## Switch Charge Injection Complementary Switch


$$Q_{ch-n} = W_n C_{ox} L_n (V_H - V_i - |V_{th-n}|)$$

$$Q_{ch-p} = W_p C_{ox} L_p (V_i - V_L - |V_{th-p}|)$$


$$\Delta V_o = \frac{I}{2} \left( \frac{Q_{ch-p}}{C_s} - \frac{Q_{ch-n}}{C_s} \right)$$

$$V_o = V_i (1 + e) + V_{os}$$

 
$$e = -\frac{I}{2} \times \frac{W_n C_{ox} L_n + W_p C_{ox} L_p}{C_s}$$



 - In fast clock case
  - Offset cancelled for equal device area
  - Input voltage dependant error worse!




## Switch Charge Injection Dummy Switch

 


- Dummy switch same L and main switch but half W
- Main device clock goes low, dummy device goes high → dummy switch acquires same amount of channel charge main switch needs to lose
- Effective only if exactly half of the charge transferred to M2 and good matching between clock fall/rise

## Switch Charge Injection Dummy Switch

 

- To guarantee half of charge goes to each side → create the same environment on both sides
  - Add C equal to sampling capacitor to the other side of the switch + add fixed resistor
- Degrades sampling bandwidth
 
## Dummy Switch Dummy Switch Effectiveness Test




- Dummy switch  
 $\rightarrow W = 1/2 W_{\text{main}}$
- Note large  $L_s$   
 $\rightarrow$  good device area matching

$V_{in}$	UNCOMPENSATED SWITCH	COMPENSATED WITH DUMMY	BALANCED SWITCH
0v	-160mV	-45mV	6mV
5v	-105mV	-30mV	1mV
10v	-40mV	-11mV	0 ± 5mV


Ref: L. A. BIENSTMAN et al, "An Eight-Channel 8 13bit Microprocessor Compatible NMOS D/A Converter with Programmable Scaling", IEEE JSSC, VOL. SC-15, NO. 6, DECEMBER 1980
 
## Switch Charge Injection Bottom Plate Sampling



- Switches M2A@ B are opened slightly earlier compared to M1A&B  
 $\rightarrow$  Injected charge by the opening or M2AB is constant & eliminated when used differentially
- Since bottom plate of  $C_s$  is open when M1A&B are opened  $\rightarrow$  no charge injected on  $C_s$


## Flip-Around T/H

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 37


## Flip-Around T/H

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 38


## Flip-Around T/H

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 39

## Flip-Around T/H - Timing

 


EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 40


## Charge Injection

- At the instant of sampling, some of the charge stored in sampling switch S1 is dumped onto C
- With "Bottom Plate Sampling", charge injection comes only from S1 and is to first-order independent of  $v_{IN}$ 
  - Only a dc offset is added to the input signal
  - This dc offset can be removed with a differential architecture

## Flip-Around T/H

 

## Flip-Around T/H

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 43


## Flip-Around T/H

- S1 is an n-channel MOSFET
- Since it always switches the same voltage, its on-resistance,  $R_{S1}$ , is signal-independent (to first order)
- Choosing  $R_{S1} \gg R_{S1A}$  minimizes the non-linear component of  $R = R_{S1A} + R_{S1}$ 
  - S1A is a wide (much lower resistance than S1) constant  $V_{GS}$  switch
  - In practice size of S1A is limited by the (nonlinear) S/D capacitance that also adds distortion
  - If S1A's resistance is negligible, aperture delay depends only on S1 resistance
  - S1 resistance is independent of  $v_{IN}$ ; hence, aperture delay is independent of  $v_{IN}$

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 44


## S/H Combined with Gain Stage

 

- Gain=4Cl/Ci=4


Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

## S/H Combined with Gain Stage

 

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

## S/H Combined with Gain Stage

 

- Gain=4C/C=4

Ref: S. H. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" IEEE JSSC, VOL. SC-22, NO. 6, DECEMBER 1987

## ESD Protection ADC Architectures

# What is ESD?


- Electrostatic discharge
  - Example: Charge built up on human body while walking on carpet...
  - Charged objects near or touching IC pins can discharge through on-chip devices
  - Without dedicated protection circuitry, ESD events are destructive



EECS 247 Lecture 17: Data Converters


© 2004 H.K. Page 49

## Model and Protection Circuit

 

**Figure 1.** Human Body Model for ESD testing.

[http://www.idt.com/docs/AN\_123.pdf]

 

[<http://www.ce-mag.com/archive/03/ARG/dunnahoo.html>]

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 50

## Equivalent Circuit


 


Fig. 1. Equivalent input circuit.

[I. E. Opris, "Bootstrapped pad protection structure," IEEE J.Solid-State Circuits, pp. 300, Feb. 1998.]

- Nonlinear capacitance causes distortion
- Distortion increases with frequency
  - Today's converters: High frequency, low distortion!

## ESD Circuit Distortion

 


[I. E. Opris, "Bootstrapped pad protection structure," IEEE J.Solid-State Circuits, pp. 300, Feb. 1998.]

$$C(V_{in}) = 2..4\text{pF} \text{ for } V_{in}=2..0\text{V}$$
 
# ESD Circuit Distortion


- Analysis: Volterra Series (see handout on the web)
- Example:



EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 53

# ESD Circuit Distortion

 

EECS 247 Lecture 17: Data Converters

© 2004 H.K. Page 54

## ESD Circuit Distortion

- Distortion from ESD circuits approaches state of-the-art ADC performance!
- If you are working on a new, record breaking ADC, better think about ESD now...
- Ref.: A. Wang, "Recent developments in ESD protection for RF IC," *Proc. DAC Conference*, Jan. 2003
- Solutions still pre-mature
- Lots of company IP