

EE247

Lecture 19


ADC Converters

- ADC architectures
- Comparator architectures
 - High gain amplifier with differential analog input & single-ended large swing output
 - Latched comparators; in response to a strobe, input stage disabled & digital output stored in a latch till next strobe
 - Sample-data comparators
 - Offset cancellation

ADC Architectures


- Slope Converters
- Successive approximation
- Flash
- Folding
- Time-interleaved / parallel converter
- Residue type ADCs
 - Two-step
 - Pipeline
 - Algorithmic
 - ...
- Oversampled ADCs

Residue Type ADC

 


- Quantization error output (“residuum”) enables cascading for higher resolution
- Great flexibility for stages: flash, oversampling ADC, ...
- Optional S/H enables parallelism (pipelining)
- Fast: one clock per conversion (with S/H), latency

Pipelined ADC

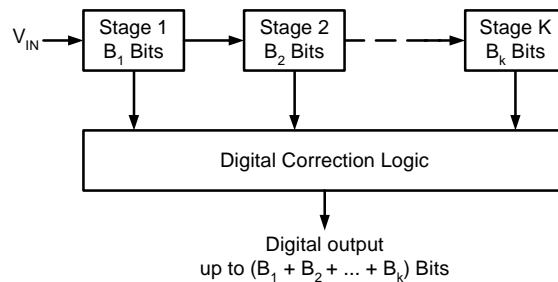


- Approaches speed of flash, but much lower complexity
- One clock per conversion, but K clocks latency
- Efficient digital calibration possible
- Versatile: from 16Bits / 1MS/s to 14Bits / 100MS/s

Algorithmic ADC

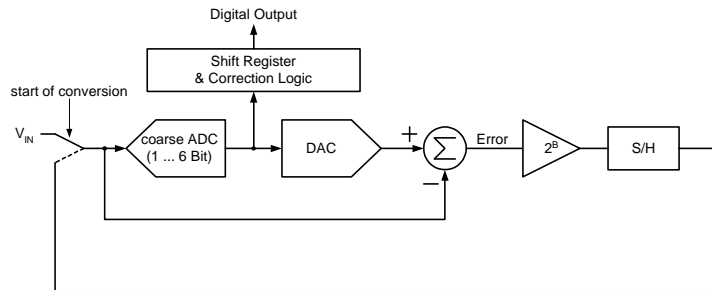


- Essentially same as pipeline, but a single stage is used for all partial conversions
- K clocks per conversion

Oversampled ADC

 


- Hard to comprehend ... “easy” to build
- Input is oversampled (M times faster than output rate)
- Reduces Anti-Aliasing filter requirements and capacitor size
- Accuracy independent of component matching
- Very high resolution achievable (> 20 Bits)

Throughput Rate Comparison

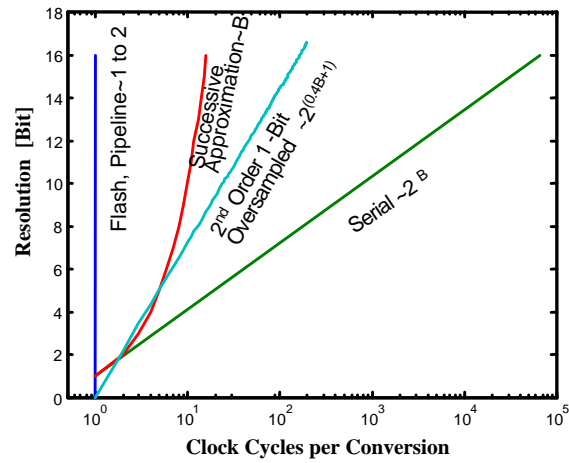

Speed-Resolution Map

 


High-Speed A/D Converters


- Flash Converter
 - Comparator design considerations
 - Binary Encoder
- Interpolation
- Folding
- Pipelined ADCs

Flash Converter

 - Very fast: only 1 clock cycle per conversion
- High complexity: 2^B-1 comparators
- High input capacitance



Voltage Comparators

 

Function: compare the instantaneous value of two analog signals

Important features:

- Maximum clock rate $f_s \rightarrow$ settling time, slew rate, small signal bandwidth
- Resolution \rightarrow gain, offset
- Overdrive recovery
- Input capacitance (and linearity!)
- Power dissipation
- Common-mode rejection
- Kickback noise
- ...

Ref: Prof. B. Wooley, Course notes EE315 Stanford University

Voltage Comparator Architectures

Comparator architectures

- High gain amplifier with differential analog input & single-ended large swing output
 - Output swing compatible with driving digital logic circuits
 - Open-loop amplification \rightarrow no frequency compensation required
 - Precise gain not required
- Latched comparators; in response to a strobe, input stage disabled & digital output stored in a latch till next strobe
 - Two options for implementation :
 - High-gain amplifier + simple digital latch
 - Low-gain amplifier + a high-sensitivity latch
- Sample-data comparators
 - S/H input
 - Offset cancellation
 - Pipelined stages


Comparators w/ High-Gain Amplification

Amplify $V_{in}(\text{min})$ to V_{DD}
 $V_{in}(\text{min})$ determined by ADC resolution
 Example: 12-bit res. & full-scale input 2V \rightarrow 1LSB=0.5mV


\rightarrow For 2.5V output:

$$A_v = \frac{2.5V}{0.25mV} = 10,000$$

$$V_{os} < 1 \text{ LSB}$$

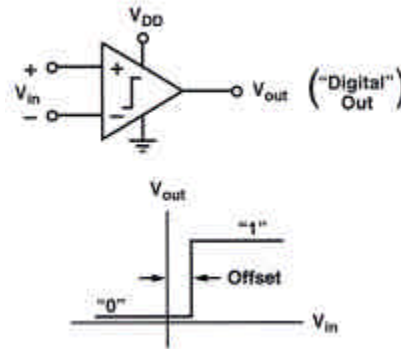

Comparators w/ High-Gain Amplification

 

f_u = unity gain frequency, f_0 = -3dB frequency


$$f_0 = \frac{f_u}{A_v} = \frac{1\text{GHz}}{10,000} = 100\text{kHz}$$

$$t_0 = \frac{1}{2\pi f_0} = 1.6\text{msec}$$


Too slow!

\rightarrow Cascade of lower gain stages to broadband response

Open Loop Cascade of Amplifiers

 

The stages identical \rightarrow small-signal model for the cascades:

 

For 1-stage only:

$$|A_V(0)| = g_m R_L$$

$$\omega_{3dB} = -3\text{dB frequency} = \frac{1}{R_L C_T}$$

$$\omega_u = -\text{unity gain frequency} = G \times BW = \frac{g_m}{C_T}$$

$$\therefore \omega_{3dB} = \frac{\omega_u}{|A_V(0)|}$$

Open Loop Cascade of Amplifiers

For Cascade of N-stages:

$$A_T(j\omega) = [A_V(j\omega)]^N = \frac{[A_V(0)]^N}{(1 - j\frac{\omega}{\omega_u})^N}$$

Define

ω_{3dB} = -3dB frequency of the N-stage cascade.

Then

$$|A_T(j\omega_{3dB})| = \frac{|A_V(0)|^N}{\sqrt{2}}$$

and

$$\omega_{3dB} = \omega_u / \sqrt{2^{1/N} - 1} = \frac{\omega_u}{|A_V(0)|} \sqrt{2^{1/N} - 1}$$

For a specified $|A_T(0)|$

$$|A_V(0)| = |A_T(0)|^{1/N}$$

$$\Rightarrow \omega_{3dB} = \frac{\omega_u}{|A_T(0)|^{1/N}} \sqrt{2^{1/N} - 1}$$

Thus,

$$\frac{\omega_{3dB}}{\omega_{3dB}} = \frac{\omega_u}{|A_T(0)|^{1/N}} \sqrt{2^{1/N} - 1} \left/ \left(\frac{\omega_u}{|A_T(0)|} \right) \right.$$

$$= |A_T(0)|^{\frac{N-1}{N}} \sqrt{2^{1/N} - 1}$$

Open Loop Cascade of Amplifiers

For $|A_T(\text{DC})|=10,000$

N	ω_{0N}/ω_{01}	$ A_V(0) $
1	1	10,000
2	64	100
3	236	21.5
4	435	10
5	611	6.3
10	1067	2.5
20	1185	1.6

Example :

$$N = 3, f_u = 1\text{GHz}, A_T(0) = 10000$$

$$f_{0N} = \frac{1\text{GHz}}{(10,000)^{1/3}} \sqrt{2^{1/3} - 1} = 24\text{MHz}$$


$$t_{0N} = \frac{1}{2\pi f_{0N}} = 7\text{nsec} \quad (1.6\text{ms for 1-stage})$$

$$5t_{0N} = 35\text{nsec}$$

Cascade of 3-stage

→ speed 236 higher compared to 1-stage (constant overall gain & f_u)

 Open Loop Cascade of Amplifiers Offset Voltage



• Cascade of amplifiers

→ Input-referred offset increases


• Choice of # of stages important

→ Speed vs offset tradeoff

Example:

For 3-stage case with gain/stage ~22

→ Increase in offset ~ 4.5%

 


$$A_T = A_1 \cdot A_2 \cdot A_3$$

$$V_{oi} = V_{oi1} + \frac{V_{oi2}}{A_1} + \frac{V_{oi3}}{A_1 \cdot A_2}$$

Open Loop Cascade of Amplifiers Step Response

•Assuming linear behavior

 

$$v_{o1} = \frac{1}{C} \int_0^t g_m v_{in} dt = \frac{g_m}{C} v_{in} t$$


$$v_{o2} = \frac{1}{C} \int_0^t g_m v_{o1} dt = \frac{g_m}{C} \int_0^t \frac{g_m}{C} v_{in} dt = \frac{1}{2} \left(\frac{g_m}{C} \right)^2 v_{in} t^2$$

$$v_{o3} = \frac{1}{C} \int_0^t g_m v_{o2} dt = \frac{g_m}{C} \int_0^t \left[\frac{1}{2} \left(\frac{g_m}{C} \right)^2 v_{in} t^2 \right] dt$$

$$= \frac{1}{3} \left(\frac{g_m}{C} \right)^3 v_{in} t^3$$

Open Loop Cascade of Amplifiers Step Response

•Assuming linear behavior

 

N Stages

$$v_{oN} = \left(\frac{g_m}{C} \right)^N \left(\frac{t^N}{N!} \right) v_{in}$$

For the output to reach a specified v_{out} (i.e., $v_{oN} = v_{out}$) the delay is

$$\tau_D = \left(\frac{C}{g_m} \right) \left[(N!) \left(\frac{v_{out}}{v_{in}} \right) \right]^{1/N}$$

Open Loop Cascade of Amplifiers Delay/(C/g_m)

- Minimum total delay broad function of N
- Relationship between # of stages that minimize delay (N_{op}) and gain (V_{out}/V_{in}) approximately:

$$N_{op} = 1.1 \times \ln(V_{out}/V_{in}) + 0.79$$

for gain < 1000

- Or gain of 10dB (sqrt(10)) per stage results in near optimum delay

Delay/(C/g_m)

V_{out}/V_{in} N	10	100	1000	10K
1	10	100	1000	10K
2	4.5	14.1	44.7	141
3	3.9	9.4	18.2	39.1
4	3.9	7.0	12.4	22.1
5	4.1	6.5	10.4	16.4
6	4.4	6.4	9.5	13.9
7	4.7	6.5	9.1	12.6
8	5.0	6.7	8.9	11.9
9	5.4	6.9	8.8	11.5
10	5.7	7.2	8.8	11.4
11	6.1	7.5	8.8	11.3
12	6.4	7.8	8.8	11.4
20	9.3	10.5	11.7	13.2


Ref: J.T. Wu, et al., "A 100-MHz pipelined CMOS comparator" *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 1379 - 1385, December 1988.

Offset Cancellation

- Disadvantage of using cascade of amplifiers:
 - Increased overall input-referred offset
- Sampled-data cascade of amplifiers V_{os} can be cancelled
 - Store on ac-coupling capacitors in series with amplifier stages
- Offset associated with a specific amplifier can be cancelled by storing it in series with either the input or the output of that stage


Offset Cancellation Output Series Cancellation

 - Amp modeled as ideal + V_{os} (input referred)



- Store offset:

 
- S1, S4 → open
- S2, S3 → closed
- $V_C = A \times V_{os}$



Offset Cancellation Output Series Cancellation

- Amplify:

 - S1, S4 → closed
- S2, S3 → open
- $V_C = A \times V_{os}$




- Circuit requirements:


- Amp not saturate during offset storage
- High-impedance (C) load → C_c not discharged
- $C_c \gg C_L$ to avoid attenuation
- $C_c \gg C_{switch}$ offset due to charge injection

$$\begin{aligned} V_{out} &= A(V_{in} + V_{os}) - V_C \\ &= A(V_{in} + V_{os}) - A \cdot V_{os} \\ &= A V_{in} \end{aligned}$$

 
Offset Cancellation Cascaded Output Series Cancellation



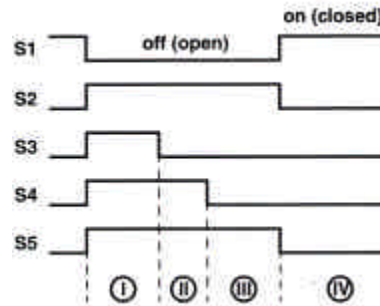Note: Extra offset cancellation phase required
→ Overall speed compromised



 Offset Cancellation Cascaded Output Series Cancellation




1- S1 → open, S2,3,4,5 closed


$$V_{C1} = A_1 \times V_{os1}$$

$$V_{C2} = A_2 \times V_{os2}$$

$$V_{C3} = A_3 \times V_{os3}$$

 

 Offset Cancellation Cascaded Output Series Cancellation



2- S3 → open


- Feedthrough from S3 → offset on X
- Switch offset, ϵ_2 stored on C1
- Since S4 remains closed, offset associated with ϵ_2 → stored on C2

$$V_X = \epsilon_2$$

$$V_{C1} = A_1 \times V_{os1} - \epsilon_2$$

$$V_{C2} = A_2 \times (V_{os2} + \epsilon_2)$$

 Offset Cancellation Cascaded Output Series Cancellation



3- S4 → open


- Feedthrough from S4 → offset on Y
- Switch offset, ϵ_3 stored on C2
- Since S5 remains closed, offset associated with ϵ_3 → stored on C3

$$V_Y = \epsilon_3$$

$$V_{C2} = A_2 \times (V_{os2} + \epsilon_2) - \epsilon_3$$

$$V_{C3} = A_3 \times (V_{os3} + \epsilon_3)$$

 Offset Cancellation Cascaded Output Series Cancellation



4- S2 → open, S1 → closed, S5 → open

- S1 closed & S2 open → since input connected to low impedance source charge injection not of major concern
- Switch offset, ϵ_4 introduced due to S5 opening
- ϵ_4 not cancelled
- As shown in the following analysis, ϵ_4 referred to the input will be attenuated by the overall gain

Offset Cancellation Cascaded Output Series Cancellation

$$V_X = A_1 (V_{in} + V_{os1}) - V_{C1}$$

$$= A_1 (V_{in} + V_{os1}) - (A_1 V_{os1} - \epsilon_2)$$

$$= A_1 V_{in} + \epsilon_2$$

$$V_Y = A_2 (V_X + V_{os2}) - V_{C2}$$

$$= A_2 (A_1 V_{in} + \epsilon_2 + V_{os2}) - [A_2 (V_{os2} + \epsilon_2) - \epsilon_3]$$

$$= A_1 A_2 V_{in} + \epsilon_3$$

$$V_{out} = A_3 (V_Y + V_{os3}) - V_{C3}$$

$$= A_3 (A_1 A_2 V_{in} + \epsilon_3 + V_{os3}) - [A_3 (V_{os3} + \epsilon_3) - \epsilon_4]$$

$$= A_1 A_2 A_3 V_{in} + \epsilon_4$$

Offset Cancellation Cascaded Output Series Cancellation

$$V_{out} = A_1 \cdot A_2 \cdot A_3 \left(V_{in} + \frac{E_4}{A_1 \cdot A_2 \cdot A_3} \right)$$


$$\text{Input-Referred Offset} = \left(\frac{E_4}{A_1 \cdot A_2 \cdot A_3} \right)$$

Example:
3-stage open-loop differential amplifier with offset cancellation + output amplifier
(see ref.)

$A_{Total}(DC) = 2 \times 10^6 = 120\text{dB}$
Input-referred offset $< 5\mu\text{V}$
Input-referred offset drift $< 0.05\mu\text{V}$

Ref: R. Poujois and J. Borel, "A low drift fully integrated MOSFET operational amplifier," *IEEE Journal of Solid-State Circuits*, vol. 13, pp. 499 - 503, August 1978.

 
Offset Cancellation Input Series Cancellation



Offset Cancellation Input Series Cancellation

Store offset

S1 = 0 (off)
S2, S3 = 1 (conducting)

 

$$V_C = -A(V_C - V_{os})$$


$$= \left(\frac{A}{A+1}\right)V_{os} - V_{os}$$

Note: Amplifier has to be compensated for unity gain stability

Offset Cancellation Input Series Cancellation

Amplify

S2, S3 → open
S1 → closed

 

$$V_{out} = -A(V_{in} + V_C - V_{os}) = -A\left[V_{in} + V_{os}\left(\frac{A}{A+1} - 1\right)\right]$$

$$\therefore V_{out} = -A\left(V_{in} - \frac{V_{os}}{A+1}\right)$$


and

$$\text{Input-Referred Offset} = \frac{V_{os}}{A+1}$$

Offset Cancellation Cascaded Input Series Cancellation

$$V_{out} = A_1 A_2 \left[V_{in} + \frac{V_{os2}}{A_1(A_2 + 1)} - \frac{\epsilon_2}{A_1} \right]$$
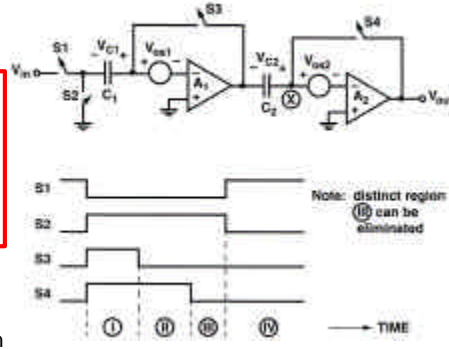
$$\text{Input-Referred Offset} = \frac{V_{os2}}{A_1(A_2 + 1)} - \frac{\epsilon_2}{A_1}$$




ϵ_2 → opening of S4 charge injection

- Amplifier A1 offset → fully cancelled
- Amplifier A2 offset → attenuated by $1/A_1.A_2$
- Error associated with opening of S4 charge injection attenuated by $1/A_1$


CMOS Comparators Cascade of Gain Stages

Fully differential gain stages → 1st order cancellation of switch feedthrough & charge injection offsets

1-Output series offset cancellation

 


2- Input series offset cancellation

 

CMOS Comparators Cascade of Gain Stages

 
3-Combined input & output series offset cancellation



V_{os1} & V_{os2} are both stored on a single pair of coupling capacitors.

CMOS Latched Comparators

 
Comparator amplification need not be linear
→ can use a latch → regeneration



→ Amplification + positive feedback

CMOS Latched Comparators

 Latch can be modeled as a single-pole amp + positive feedback



CMOS Latched Comparators Delay

$$g_m v = \frac{v}{R_L} + C \frac{dv}{dt}$$

$$\frac{g_m}{C} \left(1 - \frac{1}{g_m R_L} \right) v = C \frac{dv}{dt}$$

$$\frac{g_m}{C} \left(1 - \frac{1}{g_m R_L} \right) \int_{v_1}^{v_2} dt = \int_{v_1}^{v_2} \frac{1}{v} dv$$

Latch Delay

$$\tau_D = t_2 - t_1 = \frac{C}{g_m} \left(\frac{1}{1 - \frac{1}{g_m R_L}} \right) \ln \left(\frac{v_2}{v_1} \right)$$

where $\frac{v_2}{v_1} = A_L = \text{"LATCH GAIN"}$

For $g_m R_L \gg 1$

$$\tau_D \approx \left(\frac{C}{g_m} \right) \ln(A_L)$$

Normalized Latch Delay

A_L	$\frac{\tau_D}{(C/g_m)}$
10	2.3
100	4.6
1000	6.9
10K	9.2

$\tau_D(\text{3-state amp}) = 18.2(C/g_m)$

Compared to a 3-stage open-loop cascade of amps for equal gain of 1000

→ Latch faster by about x3


Only drawback → high latch offset (typically 10- 100mV)

→ Use preamp w/gain = 10-100 to reduce

input-referred latch offset

→ Or use offset cancellation


Latched Comparator

 

- Clock rate f_s
- Resolution
- Overload recovery
- Input capacitance (and linearity!)
- Power dissipation
- Common-mode rejection
- Kickback noise
- ...

Comparators Overdrive Recovery

 
Linear model for a single-pole amplifier:



$U \rightarrow$ amplification after time t_a

During reset amplifier settles exponentially to its zero input condition with $\tau_0 = RC$

 Assume $V_m \rightarrow$ maximum input normalized to $1/2lsb (=1)$




Example: Worst case input/output waveforms


\rightarrow Limit output voltage swing by

 1. Passive clamp
2. Active restore
3. Low gain/stage

Comparators Overdrive Recovery Limiting Output




Clamp
Adds parasitic capacitance

 

Active Restore
After outputs are latched \rightarrow Activate ϕ_R & equalize output nodes


CMOS Comparator Example

 

- Flash ADC: 8bits, $\pm 1/2$ LSB INL @ $f_s=15$ MHz ($V_{ref}=3.8$ V)
- No offset cancellation


A. Yukawa, "A CMOS 8-Bit High-Speed A/D Converter IC," JSSC June 1985, pp. 775-9.

Comparator with Auto-Zero

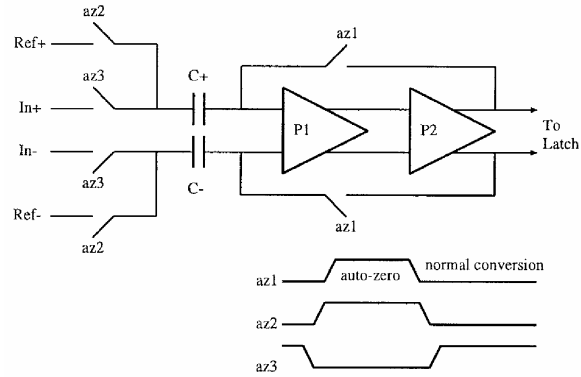

I. Mehr and L. Singer, "A 500-Msample/s, 6-Bit Nyquist-Rate ADC for Disk-Drive Read-Channel Applications," JSSC July 1999, pp. 912-20.

Auto-Zero Implementation

 

Ref: I. Mehr and L. Singer, "A 55-mW, 10-bit, 40-Msample/s Nyquist-Rate CMOS ADC," JSSC March 2000, pp. 318-25.

Comparator Example

- Variation on Yukawa latch used w/o preamp

- No dc power when ϕ high


- Good for low resolution ADCs

- M11 & M12 added to vary comparator threshold

- To 1st order, for $W1=W2$ & $W11=W12$

$$V_{th}^{latch} = W11/W1 \times V_R$$

where $V_R = V_{R+} - V_{R-}$.

 

Ref: T. B. Cho and P. R. Gray, "A 10 b, 20 Msample/s, 35 mW pipeline A/D converter," *IEEE Journal of Solid-State Circuits*, vol. 30, pp. 166 - 172, March 1995.

Comparator Example



- Used in a pipelined ADC with digital correction
→ no offset cancellation

- Note differential reference

- M7, M8 operate in triode region


- Preamp gain ~10

- Input buffers suppress kick-back

 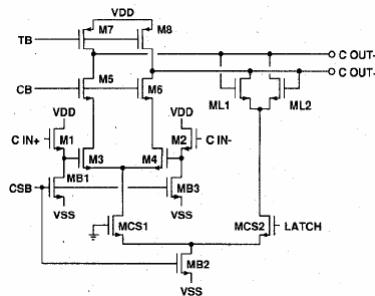


Ref: S. Lewis, et al., "A Pipelined 5-Msample/s 9-bit Analog-to-Digital Converter" *IEEE JSSC*, NO. 6, Dec. 1987

Flash Converter Errors

 


- Comparator input:
 - Offset
 - Nonlinear input capacitance
 - Kickback noise (disturbs reference)
 - Signal dependent sampling time
- Comparator output:
 - Sparkle codes (... 111101000 ...)
 - Metastability

Typical Flash Output Decoder

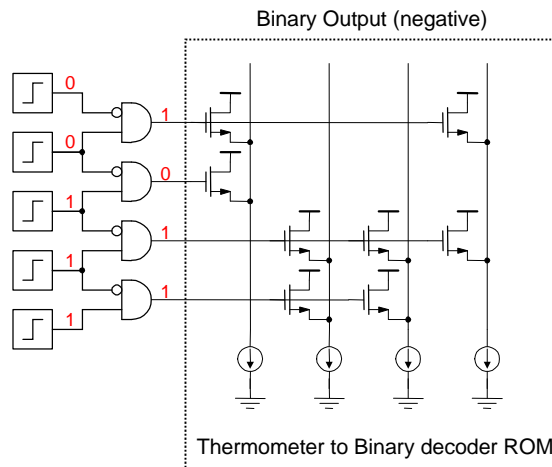

Sparkle Codes

Binary Output (negative)

 


Erronous 0
(comparator
offset?)

Correct Output:
0110 ... 1000

Actual Output:
1110

Sparkle Tolerant Encoder


Binary Output (negative)

 

Protects against a *single* sparkle.

Ref: C. Mangelsdorf et al, "A 400-MHz Flash Converter with Error Correction," JSSC February 1990, pp. 997-1002.

Meta Stability

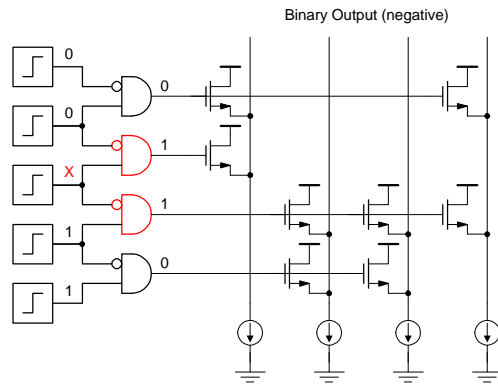

Different gates interpret metastable output X differently

Correct Output: 0111 or 1000

Actual Output: 1111

Solutions:

- Latches (high power)
- Gray encoding

Ref: C. Portmann and T. Meng, "Power-Efficient Metastability Error Reduction in CMOS Flash A/D Converters," JSSC August 1996, pp. 1132-40.

Gray Encoding

Thermometer Code							Gray			Binary		
T ₁	T ₂	T ₃	T ₄	T ₅	T ₆	T ₇	G ₃	G ₂	G ₁	B ₃	B ₂	B ₁
0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	1	0	0	1
1	1	0	0	0	0	0	0	1	1	0	1	0
1	1	1	0	0	0	0	0	1	0	0	1	1
1	1	1	1	0	0	0	1	1	0	1	0	0
1	1	1	1	1	0	0	1	1	1	1	0	1
1	1	1	1	1	1	0	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0	0	1	1	1

$$G_1 = T_1 \overline{T_3} + T_5 \overline{T_7}$$

$$G_2 = T_2 \overline{T_6}$$

$$G_3 = T_4$$

- Each T_i affects only one G_i
→ Avoids disagreement of interpretation by multiple gates
- Protects also against sparkles
- Follow Gray encoder by (latch and) binary encoder