 


EE247

Lecture 25

- Higher order $\Sigma\Delta$ modulators
 - Last lecture \rightarrow Cascaded $\Sigma\Delta$ modulators (MASH)
 - This lecture \rightarrow Forward path multi-order filter
 - Example: 5th order $\Sigma\Delta$
 - Modeling
 - Noise shaping
 - Effect of various nonidealities on the $\Sigma\Delta$ performance

Higher Order $\Sigma\Delta$ Modulators Forward Path Multi-Order Filter



$$Y(z) = \frac{H(z)}{1+H(z)}X(z) + \frac{1}{1+H(z)}E(z)$$

$$NTF = \frac{Y(z)}{E(z)} = \frac{1}{1+H(z)}$$

- Zeros of NTF (poles of $H(z)$) can be positioned to flatten baseband noise spectrum
- Main issue \rightarrow Ensuring stability for 3rd and higher orders

Overview

- Building behavioral models in stages
- A 5th-order, 1-Bit $\Sigma\Delta$ modulator
 - Noise shaping
 - Complex loop filters
 - Stability
 - Voltage scaling
 - Effect of component nonidealities

Building Models in Stages

- When modeling a complex system like a 5th-order $\Sigma\Delta$ modulator, model development proceeds in stages
 - Each stage builds on its predecessor
- Design goal → detect and eliminate problems at the highest possible level of abstraction
 - Each successive stage consumes progressively more engineering time
- Our $\Sigma\Delta$ model development proceeds in stages:
 - Stage 0 gets to the starting line: Collect references, talk to veterans
 - Stage 1 develops a practical system built with ideal subcircuits
 - Stage 2 models key subcircuit nonidealities and translates the results into real-world subcircuit performance specifications
 - Real-world model development includes a critical stage 3: Adding elements to earlier stages to model significant surprises found in silicon

Stage 1

- In stage 1, we'll study a model for a practical $\Sigma\Delta$ modulator topology built with ideal blocks
- Stage 1 model focus
 - Signal amplitudes
 - Stability
 - Worst-case inputs
 - Unstable systems can't graduate to stage 2
 - Quantization noise shaping
- Verify performance and functionality for all regions of operation, find and test worst-case inputs
- Determine appropriate performance metrics and build up (software) infrastructure

$\Sigma\Delta$ Modulator Filter Design


- Procedure
 - Establish requirements
 - Design noise-transfer function, NTF
 - Determine loop-filter, H
 - Synthesize filter
 - Evaluate performance, stability

Ref: R. W. Adams and R. Schreier, "Stability Theory for $\Delta\Sigma$ Modulators," in Delta-Sigma Data Converters, S. Norsworthy et al. (eds), IEEE Press, 1997, pp. 141-164.

Example: Modulator Specification

- Example: Audio ADC
 - Dynamic range DR 16 Bits
 - Signal bandwidth B 20 kHz
 - Nyquist frequency f_N 44.1 kHz
 - Modulator order L 5
 - Oversampling ratio $M = f_s/f_N$ 64
 - Sampling frequency f_s 2.822 MHz
- The order L and oversampling ratio M are chosen based on
 - SQNR > 120dB (20dB below thermal noise)

Modulator Block Diagram

 


$$\text{STF} = \frac{Y(z)}{X(z)} = \frac{H(z)}{1+H(z)}$$

$$\text{NTF} = \frac{Y(z)}{E(z)} = \frac{1}{1+H(z)}$$

Approach:
Design NTF and solve for H(z)


Noise Transfer Function, NTF(z)
 
```
% stop-band attenuation Rstop ...  
  
Rstop = 80;  
[b,a] = cheby2(L, Rstop, 1/M, 'high');  
  
% normalize  
b = b/b(1);  
NTF = filt(b, a, 1/fs);
```




Loop-Filter, H(z)
 
$$\text{NTF} = \frac{Y(z)}{E(z)} = \frac{1}{1+H(z)}$$
$$\rightarrow H(z) = \frac{1}{\text{NTF}} - 1$$



Modulator Topology Simulation Model

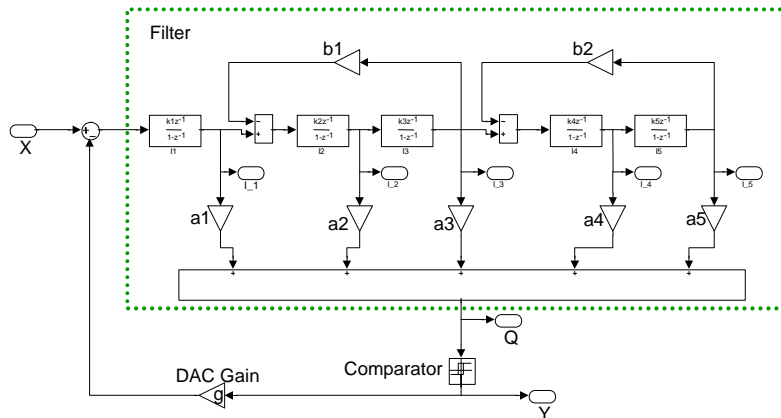


Rounded Filter Coefficients

$a1=1;$	$k1=1;$	$b1=1/1024;$
$a2=1/2;$	$k2=1;$	$b2=1/16-1/64;$
$a3=1/4;$	$k3=1/2;$	
$a4=1/8;$	$k4=1/4;$	
$a5=1/8;$	$k5=1/8;$	$g = 1;$


Ref: Nav Sooch, Don Kerth, Eric Swanson, and Tetsuro Sugimoto, "Phase Equalization System for a Digital-to-Analog Converter Using Separate Digital and Analog Sections", U.S. Patent 5061925, 1990, figure 3 and table 1.

5th Order Noise Shaping

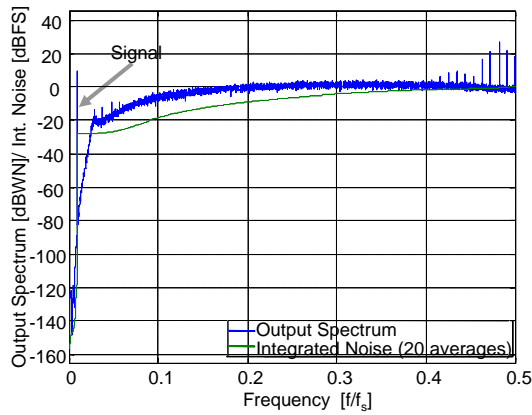


- Mostly quantization noise, except at low frequencies
- Let's zoom into the baseband portion...

5th Order Noise Shaping

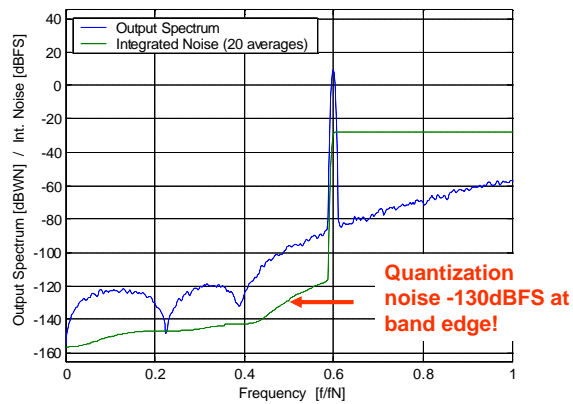


5th Order Noise Shaping

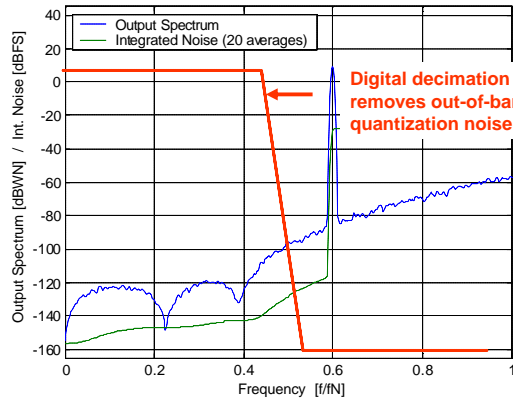

sigma_delta_L5.m


- SQNR > 120dB
- Sigma-delta modulators are usually designed for negligible quantization noise
- Other error sources dominate, e.g. thermal noise

In-Band Noise Shaping

 

- Lot's of gain in the pass-band
- Remember that
 - NTF $\sim 1/H$
 - STF = $H/(1+H)$

Stability Analysis

 


- Approach: linearize quantizer and use linear system theory!
- Effective quantizer gain

$$G_{eff}^2 = \frac{\overline{y^2}}{q^2}$$


- Obtain G_{eff} from simulation

Modulator Root-Locus

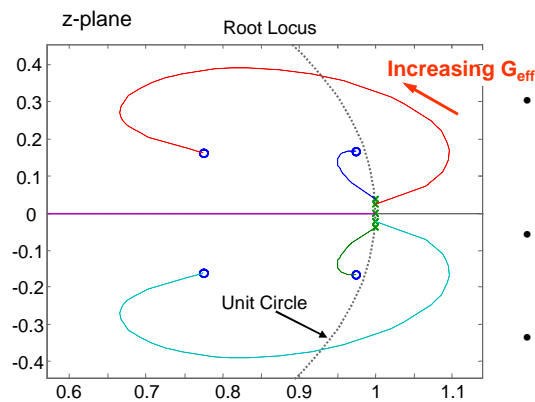


- As G_{eff} increases, poles of STF move from
 - poles of $H(z)$ ($G_{eff} = 0$) to
 - zeros of $H(z)$ ($G_{eff} = 8$)
- Pole-locations inside unit-circle correspond to stable STF and NTF
- $G_{eff} > 0.45$ for stability

Effective Quantizer Gain, G_{eff}

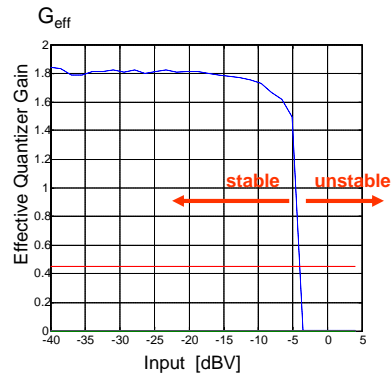

- Large inputs \rightarrow comparator input grows
- Output is fixed (± 1)
 - $\rightarrow G_{\text{eff}}$ drops
 - \rightarrow modulator unstable for large inputs
- Solution:
 - Limit input amplitude
 - Detect instability (long sequence of +1 or -1) and reset integrators
 - Beware of "worst-case inputs" (e.g. square waves near high-Q poles – attenuate with anti-aliasing filter)
 - Note that signals grow slowly for nearly stable systems \rightarrow use long simulations

Loop Voltages

 


- Internal signal amplitudes are weak function of input level (except near overload)
- Exceed supply voltage
- Solutions:
 - Reduce V_{ref} ??
 - Scaling

Loop Voltage Scaling

- If we scale k_1 by 0.1,
 - All state variables and Q scale by 0.1
 - But since the comparator output is fixed and input is decreased by 10, G increases 10X
- The change in k_1 doesn't change the shape of the root locus, either
 - The effective gain for each root position is increased 10X
 - $G > 4$ is now required for stability

5th Order Modulator – Scaling

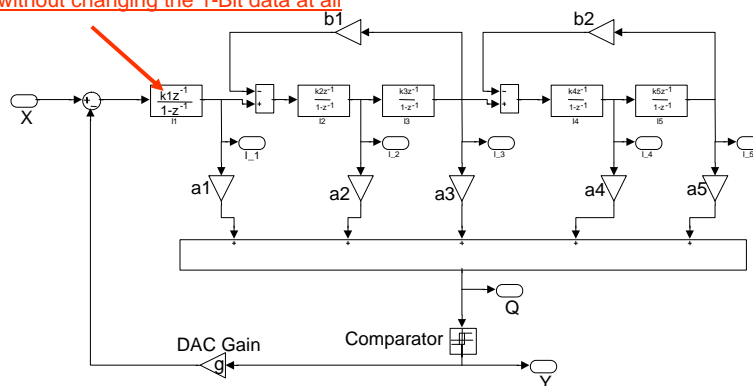
Only the sign of Q matters,
so we can make k_1 whatever we want
without changing the 1-Bit data at all




Loop Voltage Scaling (cont.)

- Note that $\int 3$, $\int 4$, and $\int 5$ have substantially larger swings than $\int 1$ and $\int 2$
- Just about any filter topology allows node scaling which change internal state variable amplitudes without changing the filter output
 - The next slide shows an example

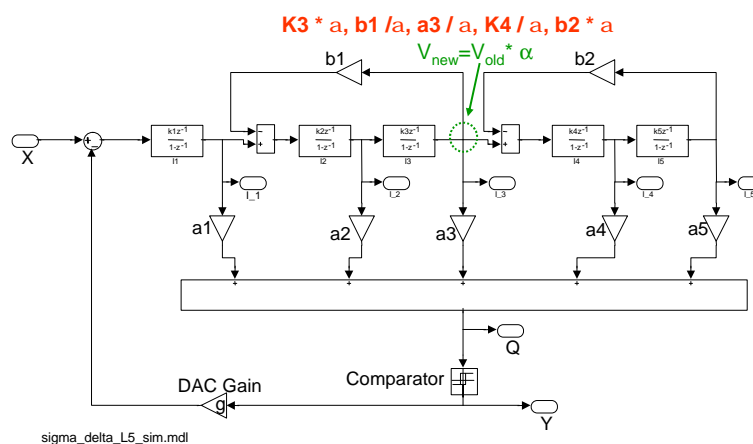Node Scaling Example: 3rd Integrator Output Voltage Scaled by α



Voltage Scaling

 


$k_1=1/10;$
 $k_2=1;$
 $k_3=1/4;$
 $k_4=1/4;$
 $k_5=1/8;$
 $a_1= 1;$
 $a_2=1/2;$
 $a_3=1/2;$
 $a_4=1/4;$
 $a_5=1/4;$
 $b_1=1/512;$
 $b_2=1/16-1/64;$
 $g =1;$

- Integrator output range is fine now
- But: maximum input signal limited to -5dB (-7dB with safety) – fix?

Input Range Scaling

Increasing the DAC levels by g reduces the analog to digital conversion gain:
 
$$\frac{D_{OUT}(z)}{V_{IN}(z)} = \frac{H(z)}{1 + gH(z)} \cong \frac{1}{g}$$




Increasing v_{IN} & g by the same factor leaves 1-Bit data unchanged


Input Range Scaling

- Scaling the DAC output levels adjusts the modulator input range
 - If V_{IN} and the DAC outputs are scaled up by the same factor g , the 1-Bit data is completely unchanged
 - Of course, increasing the range also increases the quantization noise ... the dynamic range and peak SQNR stay the same!
 - If the DAC output levels are increased and the analog full scale is held constant, the stability margin improves ... at the expense of reduced SQNR

Scaled Stage 1 Model

 


Scaled Stage 1 Model

 


Summary

- Stage 1 model verified – stable and meets SQNR specification
- Stage 2 issues in 5th order $\Sigma\Delta$ modulator
 - DC inputs
 - Tones
 - Dither
 - kT/C noise

5th Order Modulator

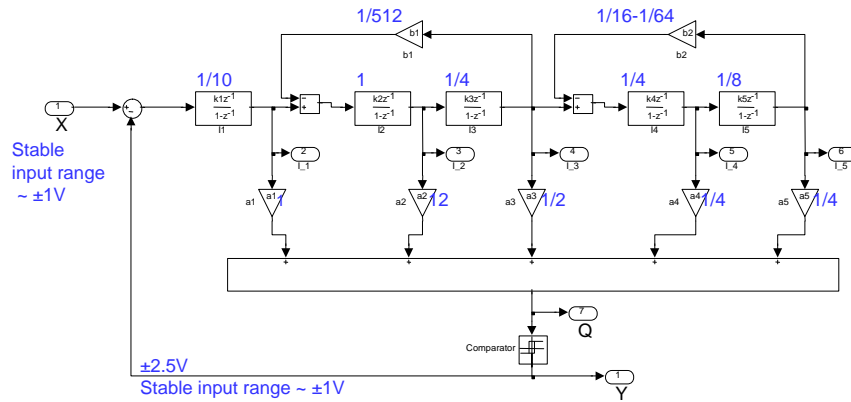


5th Order Noise Shaping

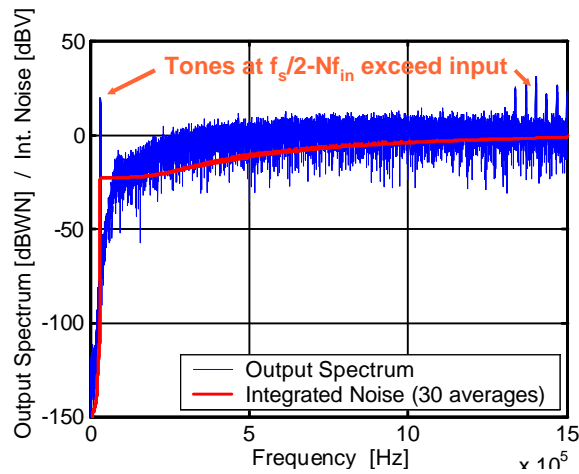


Input: 0.1V, sinusoid
2¹⁵ point DFT
30 averages

In-Band Noise

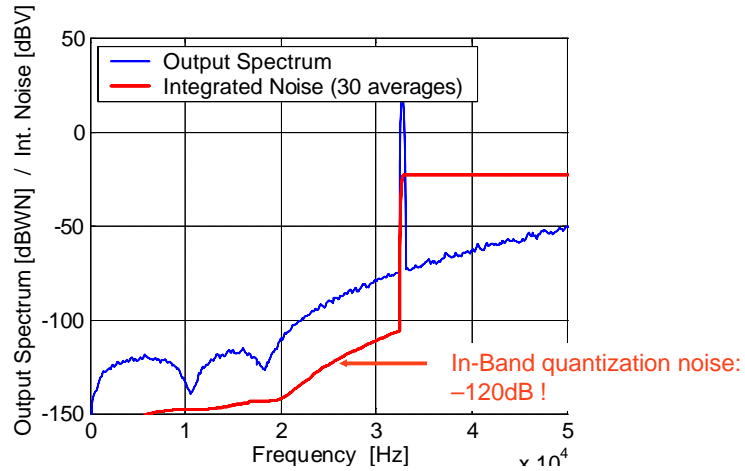


5th Order Noise Shaping

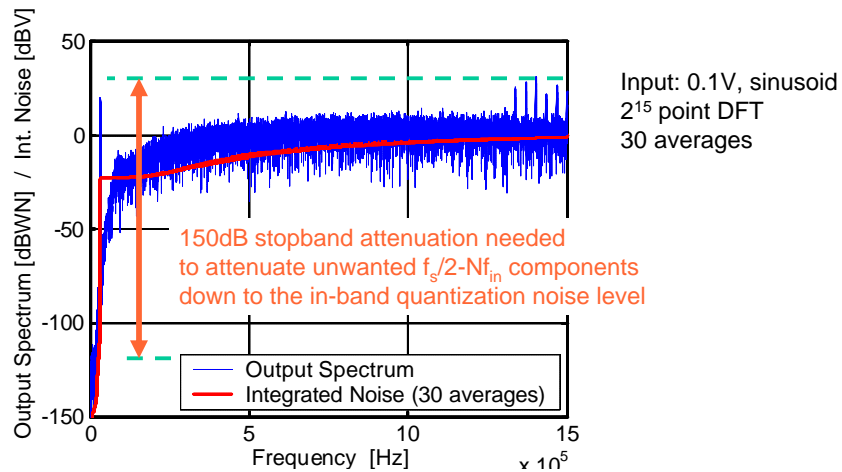

Out-of-Band vs In-Band Signals

- A digital (low-pass) filter with suitable coefficient precision can eliminate out-of-band quantization noise
- No filter can attenuate unwanted in-band components without attenuating the signal
- We'll spend some time making sure the components at $f_s/2 - Nf_{in}$ will not "mix" down to the signal band
- But first, let's look at the modulator response to small DC inputs (or offset) ...

$\Sigma\Delta$ Tones

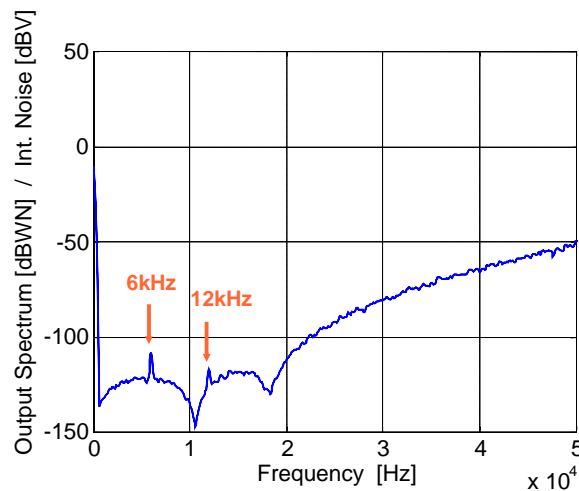

5mV DC input
($V_{DAC} \rightarrow 2.5V$)

Simulation technique:
A random 1st sample randomizes the noise from DC input and enables averaging. Otherwise the small tones are not visible.

Limit Cycles

- Representing a DC term with a -1/+1 pattern ... e.g.

$$\frac{1}{11} \rightarrow \left\{ \underbrace{-1 +1}_1 \quad \underbrace{-1 +1}_2 \quad \underbrace{-1 +1}_3 \quad \underbrace{-1 +1}_4 \quad \underbrace{-1 +1}_5 \quad +1 \right\}$$

$\underbrace{\hspace{15em}}_{\langle 0 \rangle}$
 $\underbrace{\hspace{15em}}_{\langle 1/11 \rangle}$

- Spectrum

$$\frac{f_s}{11} \quad 2\frac{f_s}{11} \quad 3\frac{f_s}{11} \quad \dots$$

Limit Cycles

- Fundamental


$$\begin{aligned} f_d &= f_s \frac{V_{DC}}{V_{DAC}} \\ &= 3\text{MHz} \frac{5\text{mV}}{2.5\text{V}} \\ &= \underline{6\text{kHz}} \end{aligned}$$

- Tone velocity (useful for debugging)

$$\frac{df_d}{dV_{DC}} = \frac{f_s}{V_{DAC}}$$

$$\frac{df_d}{dV_{DC}} = \underline{1.2\text{kHz/mV}}$$

$\Sigma\Delta$ Tones

 

$\Sigma\Delta$ Tones

- In-band tones look like signals
- Can be a big problem in some applications
 - E.g. audio \rightarrow even tones with power below the quantization noise floor can be audible
- Tones near $f_s/2$ can be aliased down into the signal band
 - Since they are often strong, even a small alias can be a big problem
 - We will look at mechanisms that alias tones later
- First let's look at dither as a means to reduce or eliminate in-band tones

Dither


- DC inputs can of course be represented by many possible bit patterns
- Including some that are random but still average to the DC input
- The spectrum of such a sequence has no tones
- How can we get a $\Sigma\Delta$ modulator to produce such “randomized” sequences?

Dither

- The target DR for our audio $\Sigma\Delta$ is 16 Bits, or 98dB
- Let's choose the sampling capacitor such that it limits the dynamic range:

$$DR = \frac{\frac{1}{2}(V_{FS})^2}{\sqrt{v_n^2}} \quad V_{FS} = 1Vp$$
$$\rightarrow \sqrt{v_n^2} = \sqrt{\frac{1}{2DR}}(V_{FS}) = \underline{9\mu V}$$


Dither

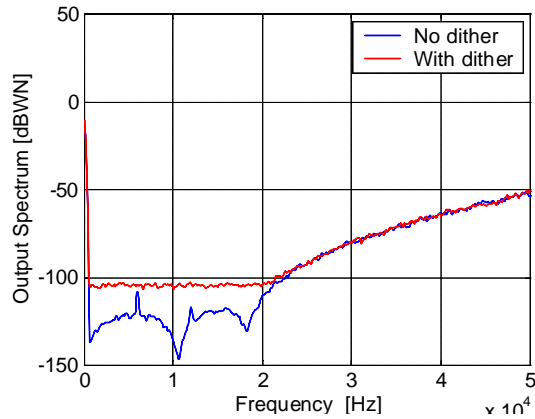

2mV DC input

- Tones disappear
- Note: they are not just buried
- How can we tell?

Dither

 


Dither at an amplitude which buries the in-band tones has virtually no effect on tones near $f_s/2$

kT/C Noise


- So far we've looked at noise added to the input of the $\Sigma\Delta$ modulator, which is also the input of the first integrator
- Now let's add noise also to the input of the second integrator
- Let's assume a 1/12 sampling capacitor for the 2nd integrator wrt the 1st integrator
 - This gives 32 μ V rms noise

kT/C Noise

 


- 5mV DC input
- Noise from 2nd integrator
 - smaller than 1st integrator noise
 - shaped
- Why?

kT/C Noise

 

- Noise from 1st integrator is added directly to the input
 - Noise from 2nd integrator is first-order noise shaped
 - Noise from subsequent integrators is attenuated even further
- Especially for high oversampling ratios, only the first 1 or 2 integrators add significant thermal noise. This is true also for other imperfections.

Dither

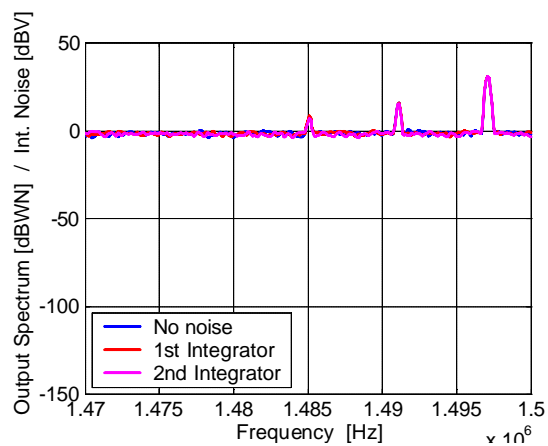


No practical amount of dither eliminates the tones near $f_s/2$

Full-Scale Inputs

- With practical levels of thermal noise added, let's try a 5kHz sinusoidal input near full-scale
- No distortion is visible in the spectrum
 - 1-Bit modulators are intrinsically linear
 - But tones exist at high frequencies
 - to the oversampled modulator, a sinusoidal input looks like two “slowly” alternating DCs ... hence giving rise to limit cycles


Full-Scale Inputs

 

V_{ref} Interference

- Dither successfully removes in-band tones that would corrupt the signal
- The high-frequency tones in the quantization noise spectrum will be removed by the digital filter following the modulator
- What if some of these strong tones are demodulated to the base-band before digital filtering?
- Why would this happen?

AM Modulation

 


$$x_1(t) = X_1 \cos(\omega_1 t)$$

$$x_2(t) = X_2 \cos(\omega_2 t)$$

$$x_1(t) \times x_2(t) = \frac{X_1 X_2}{2} [\cos(\omega_1 t + \omega_2 t) + \cos(\omega_1 t - \omega_2 t)]$$

AM Modulation in DAC

 


$$y(t) = D_{out} = \pm 1$$


$$V_{ref} = 2.5V + 1mV \cdot f_s/2 \text{ square wave}$$

$$v(t) = y(t) \times V_{ref}$$


AM Modulation in DAC

 

V_{ref} Interference

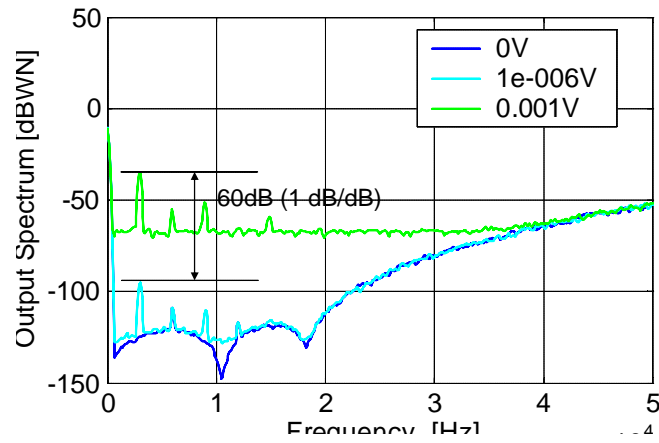


V_{ref} Interference

 

Symmetry of the spectra at $f_s/2$ and DC confirm that this is AM modulation


V_{ref} Tone Velocity

 

V_{ref} Interference

- Simulations are for specified amounts of $f_s/2$ interference in the DAC reference
- Interference demodulates the high-frequency tones
- Since the high frequency tones are strong, a small amount ($1\mu\text{V}$) of interference suffices to create huge base-band tones
- Stronger interference (1mV) raises the noise floor also
- Amplitude of demodulated tones is proportional to interference
- The velocity of AM demodulated tones is half that of the native tone
- Such differences help debugging of real silicon
- How clean does the reference have to be?

V_{ref} Interference

 

Summary

- Our stage 2 model can drive almost all capacitor sizing decisions
 - Gain scaling
 - kT/C noise
 - Dither
 - Dither removes effectively in-band tones
 - Actual tonality determined by demodulation of limit cycles near $f_s/2$
 - Extremely high clock-to- V_{ref} isolation is required for digital audio applications
 - Next we will add relevant component imperfections, e.g.
 - Real capacitors aren't perfect
 - Real opamps aren't ideal
- Effect of component nonlinearities on $\Sigma\Delta$ performance