

EE247

Lecture 26

- Administrative

- Final exam:

- Date: Wed. Dec. 15th
 - Time: 12:30pm-3:30pm
 - Location: 289 Cory

 - Closed book/course notes
 - No calculators/cell phones/PDAs/Computers
 - You can bring **two** 8x11 paper with your own notes
 - Final exam covers the entire course material

Oversampled Converters Cont'd

- Higher order $\Sigma\Delta$ modulators
 - Single-loop single-quantizer modulators with multi-order filtering in the forward path
 - Example: 5th order $\Sigma\Delta$
 - Modeling
 - Noise shaping
 - Complex loop filters
 - Stability
 - Voltage scaling, input range scaling
 - Tones, Dither, kT/C noise
 - Interference via V_{ref}
 - Effect of component nonlinearities on $\Sigma\Delta$ performance


Modeling $\Sigma\Delta$ Nonlinearities

- Many component nonlinearities contribute errors
 - Important to identify the ones which incur significant errors and analyze those only
 - Unnecessarily complex models reduce the chance to find relevant problems, and, perhaps, solutions
 - As with all nonidealities, model one at a time
- Expect errors from the 2nd integrator to be reduced by the gain of the 1st integrator
 - Errors further downstream are even less significant

Capacitor Voltage Coefficient


- Ideal capacitor
$$Q = CV$$
- Practical capacitor (1st order model)
$$Q = C(V)V \quad \text{with}$$
$$Q(V) = C_o(1 + \mathbf{a}V + \dots)V$$
- Typical voltage coefficients
 - Poly-poly capacitors 10 ppm/V
 - Metal-metal capacitors 1 ... 10 ppm/V

Integrator 1

 


C_{IN} 's voltage coefficient causes initial charge to vary nonlinearly with v_{IN} \Rightarrow harmonic distortion

Integrator 1

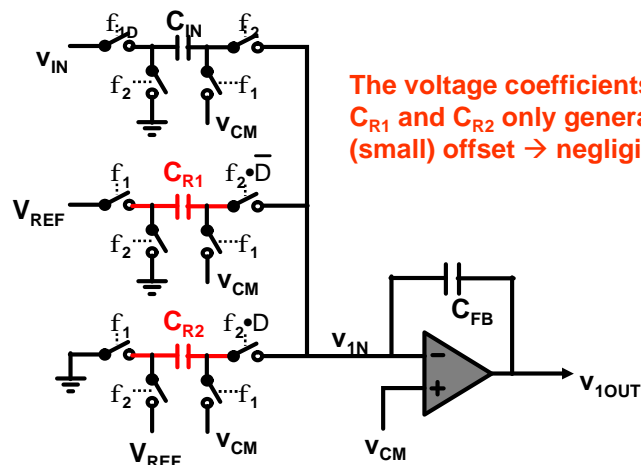

The voltage coefficients of C_{R1} and C_{R2} only generates a (small) offset \rightarrow negligible

Integrator 1

 


The effect of C_{FB} 's voltco is non-obvious, so we'll have to analyze it

C_{IN} Voltage Coefficient

- From charge conservation ($V_{CM}=0$, $C_{R1}=C_{R2}=C_R$):


$$\begin{aligned}
 V_{1OUT}(k) = & \underbrace{V_{1OUT}(k-1)}_{\text{integration}} \\
 & + \underbrace{\frac{C_{IN}}{C_{FB}} V_{IN}(k-1) + a \frac{C_{IN}}{C_{FB}} V_{IN}^2(k-1)}_{\text{converter input}} \\
 & - \underbrace{D \frac{C_R}{C_{FB}} V_{REF}}_{\text{1-bit feedback}}
 \end{aligned}$$

C_{IN} Voltage Coefficient

 


- $V_{in} = V_{FS} = 1V$
- Spectrum scaled for $V_{FS} \rightarrow 0dB$
(window lowers peak)
- Noise integral excludes DC, fundamental
- $\alpha = 10 \text{ ppm/V}$
- **2nd harmonic at -103dB dominates noise!**
- Let's characterize it ...

C_{IN} Voltage Coefficient

 

2nd harmonic increases 1dB per 1dB increase of α

C_{IN} Voltage Coefficient

 

2nd harmonic increases 2dB per 1dB increase of the input signal amplitude

C_{FB} Voltage Coefficient

- Let's look next at the voltage coefficient of the feedback capacitor in the 1st integrator
- We "turn off" all other nonidealities – C_{IN} voltage coefficients, noise, etc.
 - Makes it easier to find the effect of C_{FB} on the modulator
 - Downside: we miss potential interactions between nonidealities
 - Often they are negligible: nonidealities (like voltage coefficients) produce small errors ... linear superposition applies
 - Of course it's a good idea to run a complete verification at the end
 - And we'll get to diagnose the "real thing" soon enough ... without the insight gained from such idealized simulations it's next to impossible to diagnose a complex chip
- Evaluating the effect of the C_{FB} voltage coefficient requires solving a quadratic equation, as shown in the next slide ...

C_{FB} Voltage Coefficient


$$V_{OUT1} = \frac{Q_{FB}}{C_{FB1}(V_{OUT1})}$$

$$= \frac{-1 + \sqrt{1 + \frac{4\alpha Q_{FB}}{C_{FB1}}}}{2\alpha}$$


$$Q_{FB}(k) = Q_{FB}(k-1) + C_{IN}V_{IN} + DC_R V_{REF}$$

(same as output from linear integrator)

C_{FB} Voltage Coefficient

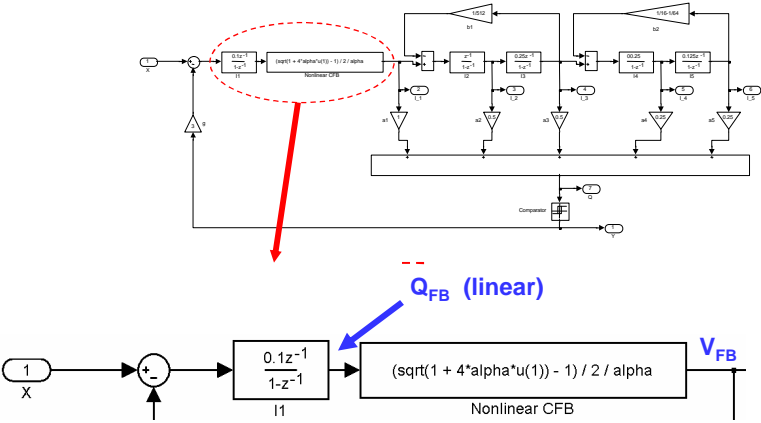


C_{FB} Voltage Coefficient

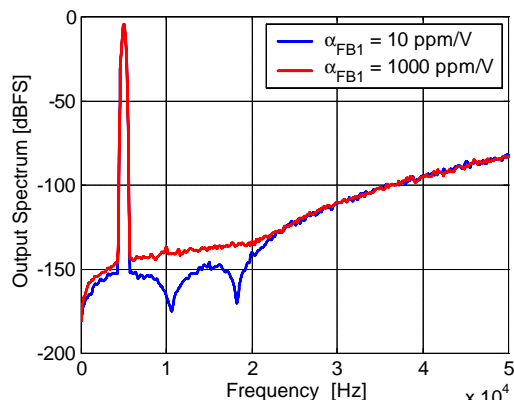


- Effect less pronounced than for C_{IN}
- Noise remains zero at DC
- First order noise for large α
- Nonlinearities operating on shaped noise change the shape of the noise ...
 - No linear model can predict this
- No harmonics ... why?

1st Integrator Output

 

- The input signal appears much attenuated at the output of the 1st Integrator
- This signal appears across C_{FB} ... and since it contains no strong tones it produces no harmonics

DC Input

 

- For $\alpha = 1000$ ppm/V, tones produced by C_{FB} are **much larger than native tones**, but move with the same velocity as native tones (1.2kHz/mV)
- Where are these tones coming from?

Quantization Noise Nonlinearity

- Native tones at a frequency f_D close to $f_s/2$ have much higher power than in-band tones

$$f_D = \frac{f_s}{2} - \frac{f_d}{2}$$

- When this tone passes a nonlinearity in the modulator loop filter, it produces distortion

$$\sin^2(2pf_D t) = \frac{1}{2} - \frac{1}{2} \cos[2p(2f_D)t]$$

Quantization Noise Nonlinearity

$$\sin^2(2\mathbf{p}f_D t) = \frac{1}{2} - \frac{1}{2} \cos[2\mathbf{p}(2f_D)t]$$


- In the sampled data system,

$$2f_D = f_s - f_d$$

maps to f_d

- Small nonlinearities applied to aggressively shaped quantization noise can produce big tone problems ...

C_{FB} Voltage Coefficient

 

$\alpha = 10$ ppm/V used in simulation

- Tones appear near $f_s/2$, as expected
- Apparently these are "folded" to the base-band
- As long as the tones are below -100dB \rightarrow acceptable

Effect of Circuit Non-Idealities

- In principle, the digital filter removes out-of-band tones
 - Except their distortion components falling in the baseband, caused by nonlinearities in the modulator loop filter
 - Except components that are mixed down to baseband due to noise in the DAC reference
- The C_{FB1} voltage coefficient adds only a small nonlinearity to the quantization noise path
 - Fortunately this nonlinearity is applied to the integral of the quantization noise and sees only a small signal component
- Nonlinearities in the amplifier are much more Other source of nonlinearity → switch induced distortion
 - Including those in the model is left as an exercise ...including effect of 3rd order nonlinearities
- **Maintaining extremely high levels of linearity in $H(z)$ is the most significant transistor-level design challenge of high resolution $\Sigma\Delta$ modulators**


Summary Oversampled ADCs

- Speed is traded for resolution
- Noise shaping utilized to reduce baseband quantization noise power
- Reduced precision requirement for analog building blocks compared to Nyquist rate converters
- Relaxed transition band requirements for analog anti-aliasing filters
- Utilizes low cost, low power digital filtering

Material Covered in EE247

- Filters
 - Continuous-time filters
 - Biquads & ladder type filters
 - Opamp-RC, Opamp-MOSFET-C, gm-C filters
 - Automatic frequency tuning
 - Switched capacitor (SC) filters
- Data Converters
 - D/A converter architectures
 - A/D converter
 - Nyquist rate ADC- Flash, Interpolating & Folding, Pipeline ADCs,....
 - Self-calibration techniques
 - Oversampled converters

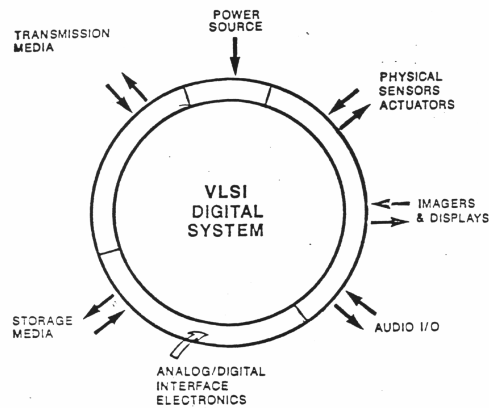
Role of Analog Interfaces in VLSI Systems



Systems Including Analog-Digital Interface Circuitry


- Wireline communications
 - Telephone related (DSL, ISDN, CODEC)
 - Television circuitry (Cable modems, TV tuners...)
 - Ethernet (Gigabit, 10/100BaseT...)
- Wireless
 - Cellular telephone (CDMA, Analog, GSM....)
 - Wireless LAN (Blue tooth, 802.11a/b/g.....)
 - Radio (analog & digital), Television
- Disk drives
- Fiber-optics systems

Frequency Range

 


Wireline Communications Telephone Based

 Data Transmission Over Existing Twisted-Pair Phone Lines




- Data transmitted over existing phone lines covering distances close to 3.5 miles
 - ISDN
 - HDSL, SDSL,.....
 - ADSL

 Data Transmission Over Twisted-Pair Phone Lines ISDN (U-Interface) Transceiver




- Full duplex transmission (RX & TX signals sent simultaneous)
- 160kbit/sec baseband data (80kHz signal bandwidth)
- Standardized line code 2B1Q (4 level code 3:1:-1:-3)
- Max. desired loop coverage 18kft (~36dB signal attenuation)
- BER (bit-error-rate) 10^{-7} → (min. SNDR=27dB)

Analog Front-End Transmit Pulse Shape

 


Standard mandates a pulse mask → Ensure min. high-frequency content on the line to avoid spurious coupling into other lines

 
ISDN (U-Interface) Transceiver Echo Problem



 - Transformer coupling to line
 - For a perfectly matched system, no leakage of TX signal into RX path.
 - Unfortunately, system has poor matching + complicating factor of bridged-taps




 ISDN (U-Interface) Transceiver Echo Problem




- System full duplex transmission → RX & TX signals sent simultaneous (& at the same frequency band)
 - Leakage of TX signal to RX path (echo)
 - In the worst case the echo could be **30dB** higher compared to the received signal!!!

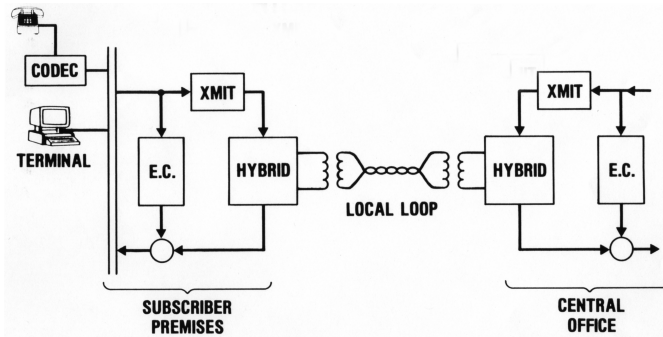ISDN (U-Interface) Transceiver Echo Cancellation



- Echo cancellation performed in the digital domain
 - Transversal adaptive digital filter → echo cancellation
- Any non-linearity incurred by the analog circuitry makes echo canceller much more complex
 - Desirable to have high linearity analog circuitry (75dB range)


Simplified Transceiver Block Diagram

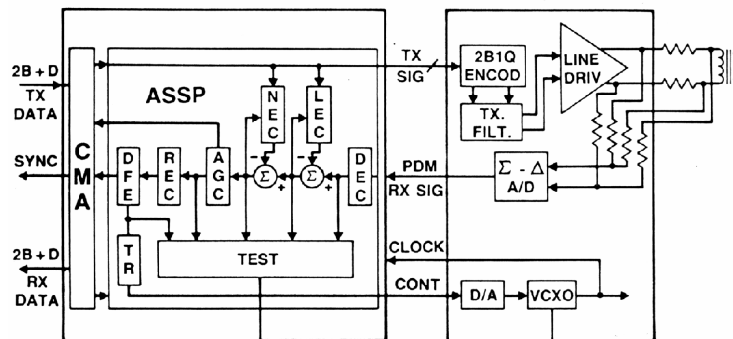

- CMA → Control, maintenance & access unit
- DFE → Decision feedback equalizer
- DEC → Decimation filter
- REC → Reconstruction filter
- LEC & NEC → Linear/non-linear echo-canceller

Ref: H. Khorrabadi, O. E. Agazzi, et. al "An ANSI standard ISDN transceiver chip set," *IEEE International Solid-State Circuits Conference*, vol. XXXII, pp. 256 - 257, February 1989.


Analog Front-End

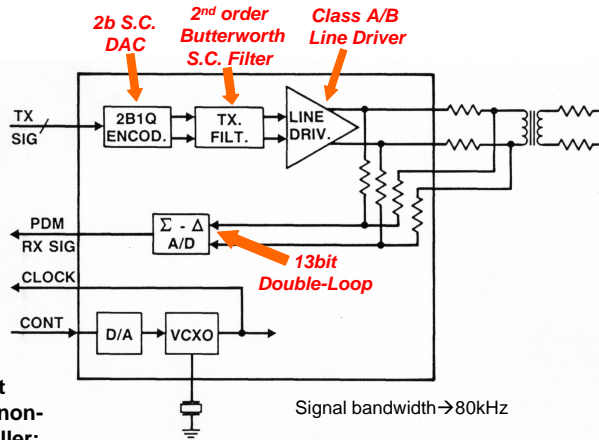

To avoid stringent requirements for non-linear echo canceller:
-> high linearity analog circuitry needed (~ 75dB)


Chip Photo

 Data Transmission Over Twisted-Pair Phone Lines DSL (Digital Subscriber Loop)



- HDSL & SDSL more like ISDN @ higher frequencies
 - Full duplex transmission with RX & TX signals on the same frequency band

 
Data Transmission Over Twisted-Pair Phone Lines ADSL (Digital Subscriber Loop)




- In USA mostly ADSL → FDM (frequency division multiplex)
 - Signal from CO to customer on a different band compared to customer to CO
 - Echo cancellation can be performed by simple filtering
 - Data rates up to 8Mbps (much higher compared to ISDN)

ADSL Signal Characteristics

 - Main difference compared to ISDN: TX & RX signals on different frequency bands
 - Downstream (*fast*, from CO to customer) 138kHz to 1.1MHz
 - Upstream (*slow*, from customer to CO) 30kHz to 138kHz
 - Echo cancellation much easier
- More severe signal attenuation at high frequencies (1MHz DSL v.s. 80kHz ISDN)




Typical ADSL Analog Front-End

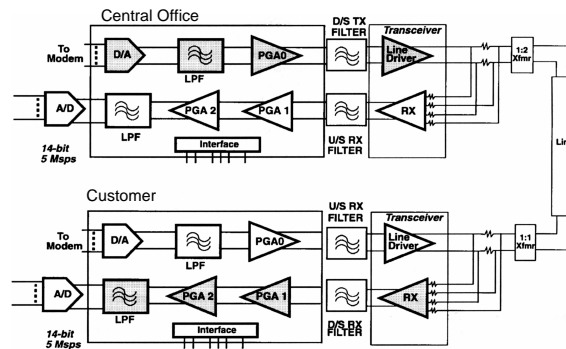

- ADC 16/14b with 14bit linearity, pipeline with auto. calibration @ 4.4Ms/s
- DAC 16/14b with 14bit linearity, S.C. with auto. calibration
- On-chip filters 3rd to 4th order LPF with f_c 1.1MHz for downstream and 138kHz upstream (typically continuous-time type filters with on-chip frequency tuning)

Ref: D.S. Langford, et al, "A BiCMOS Analog Front-End Circuit for an FDM-Based ADSL System," *IEEE Journal of Solid State Circuits*, Vol. 33, No. 9, pp. 1383-1393, Dec. 1998.

Typical ADSL Analog Front-End

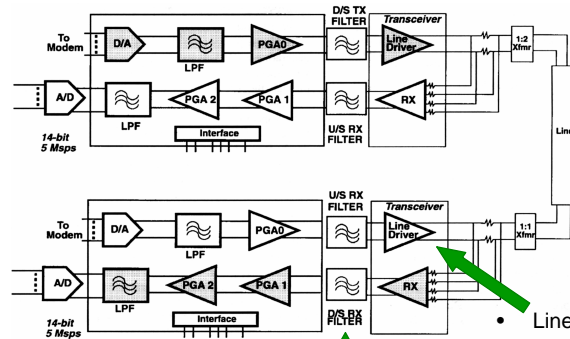

- Notice band selection filters are off-chip due to stringent noise requirements ($3\text{nV}/\text{rtHz}$)
 - Discrete LC type


• Line driver on a separate bipolar chip to achieve the required high output signal levels with high power efficiency

Wireless Communication Circuits


Wireless Circuits

- Differ from wired comm. circuits
 - Includes RF circuitry+IF circuitry+baseband circuits (three different frequency ranges)
 - Signal scenarios in wireless receivers more challenging
 - Requirement for received signal BER in the order of 10^{-3} →(min. SNR~9dB)

Typical Cellular Phone Block Diagram

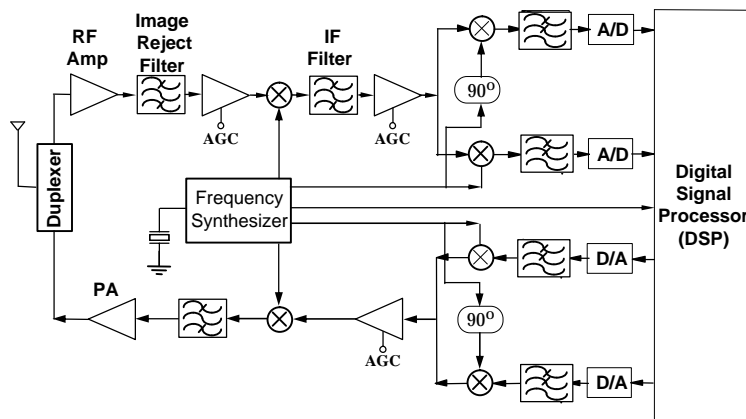


Superheterodyne Receiver

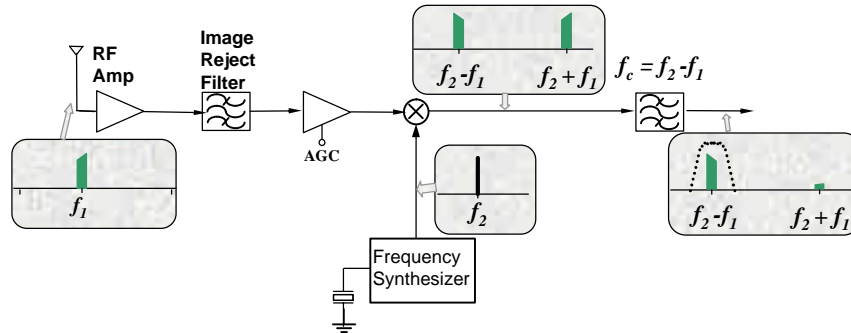


- One or more intermediate frequency (IF)
- Periodic signal at a frequency equal to the desired RX signal + or - IF frequency is provided by a Local Oscillator
- RX signal is frequency shifted to a fixed frequency (IF filter center frequency)

 RF Superheterodyne Receiver Example: CDMA Receiver




- Received frequency is mixed down to a fixed IF frequency and then filtered with a bandpass filter

Why Image Reject Filter?

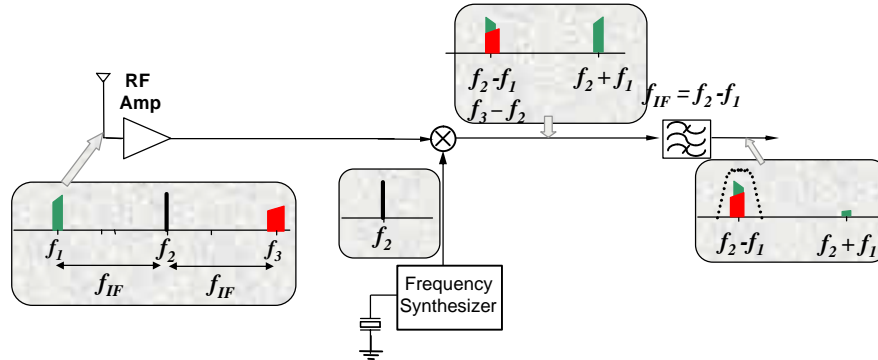


- Any signal @ the image frequency of the RX signal with respect to Osc. frequency will fall on the desired RX signal and cause impairment

Why Image Reject Filter?

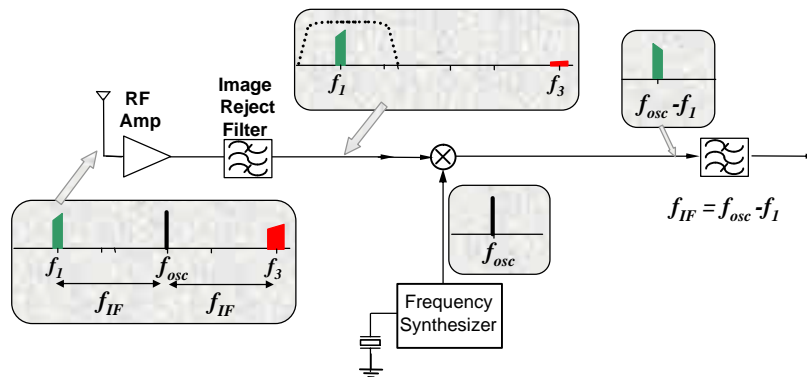


- Image reject filter attenuate signals out of the RX band
- Typically, image reject filters are ceramic or LC type filters

Quadrature Downconversion

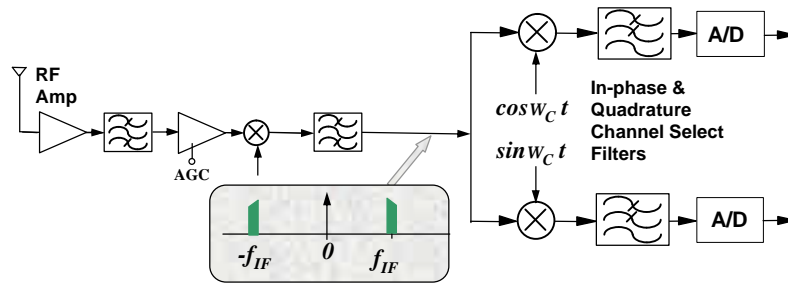

- In systems with phase or freq. modulation, since signal is not symmetric around f_{IF} , directly converting down to baseband corrupts the sidebands
 → Quadrature downconversion overcomes the problem

Effect of Adjacent Channels

 

- Adjacent channels can be as much as 60dB higher compared to the desired RX signal!
- Linearity of stages prior and including channel selection filters extremely important

Effect of Adjacent Channels


- Due to existence of large unwanted signals & limited dynamic range for the front-end circuitry:
 - Can not amplify the signal up front due to linearity issues
 - Need to allocate amplification/filtering numbers to RX blocks carefully
 - Can only amplify when unwanted signals are filtered adequately
 - System design critical with respect to tradeoffs affecting:
 - Gain
 - Linearity
 - Power dissipation
 - Chip area

Wireless Communications Linearity

- Most critical contributor to non-linearity in wireless communications circuits 3rd order intermod.:
- Two forms of linearity measurements:
 - 1dB compression point → Useful for the cases where the desired received channel is strong
 - 3rd order intercept point → Good measure for when interferers much larger compared to the desired channel

Wireless Communications Measure of Linearity


1dB Compression Point

 

$$V_{out} = a_1 V_{in} + a_2 V_{in}^2 + a_3 V_{in}^3 + \dots$$

Wireless Communications Measure of Linearity Third

Order Intercept Point

 

$$V_{out} = a_1 V_{in} + a_2 V_{in}^2 + a_3 V_{in}^3 + \dots$$


$$\begin{aligned} IM_3 &= \frac{3rd}{1st} \\ &= \frac{3 a_3 V_{in}^2}{4 a_1} + \frac{25 a_5 V_{in}^4}{8 a_1} + \dots \\ &= 1 @ IP3 \end{aligned}$$

Typically:


$$IIP_3 - P_{1dB} = 9.6dB$$

Most common measure of linearity for wireless circuits:

 → OIP3 & IIP3, Third order output/input intercept point




Homodyne Receiver

 


- No intermediate frequency, signal mixed down to baseband
- Almost all of the filtering performed at baseband
 - Higher levels of integration possible
 - Issue to be aware of:
 - Requirements for the baseband filters very stringent
 - Since the local oscillator frequency is exactly at the same freq. as the RX signal freq. → can cause major DC offsets can drive the receiver front-end into non-linear region

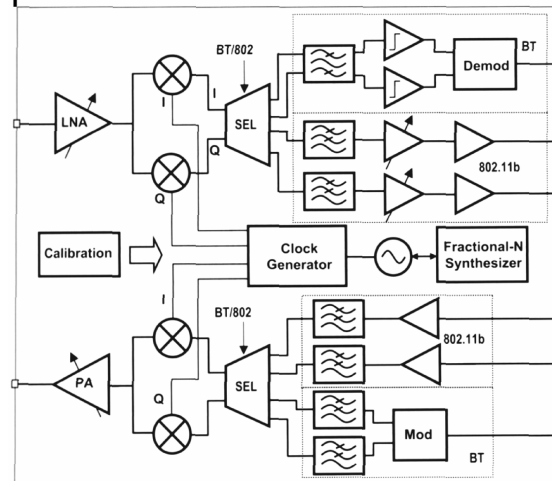Example: Wireless LAN 802.11b & Bluetooth




Ref: H. Darabi, et al, "A Dual Mode 802.11b/Bluetooth Radio in 0.35um CMOS," *International Solid State Circuits Conference*, 2003 pp. 86-87.

Digital IF Receiver (IF sampling)

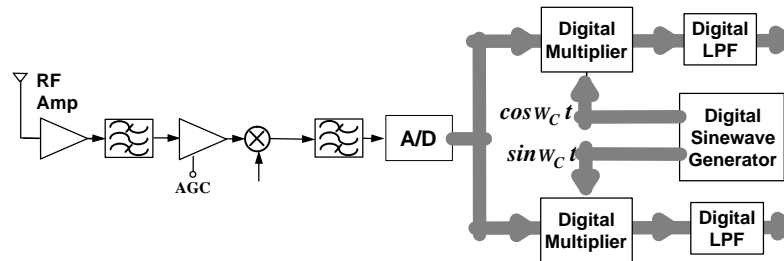


- IF signal is converted to digital → most of signal processing performed in the digital domain
- Performance requirement for ADC extremely demanding in terms of noise, linearity, and dynamic range!
- With advancement of ADCs may be the architecture of choice in the future

Typical Wireless Transmitter

 

- Transmit signal shipped from DSP to the analog front-end in the form of I & Q signals
- Signal converted to analog form by D/A
- Lowpass filter provides pulse shaping
- In-phase & Quad. Components combined and then mixed up to RF
- Power amplifier amplifies and provides the low-impedance output

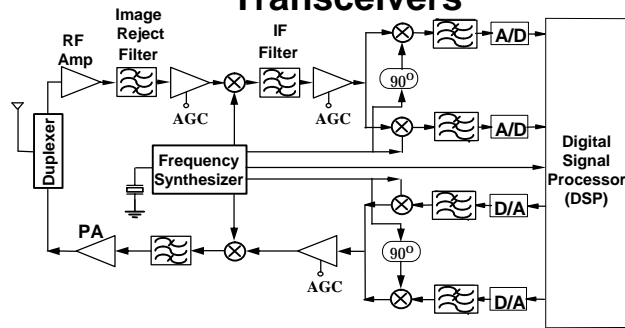Analog Filters in Typical Wireless Transceivers



Filters

RF Filter
 IF Filter
 Base-band Filters


Function

Image Rejection
 Channel selection
 Channel Selection
 & Anti-aliasing for ADC

Type

Ceramic or LC
 SAW
 Integrated Cont.-Time
 or S.C.

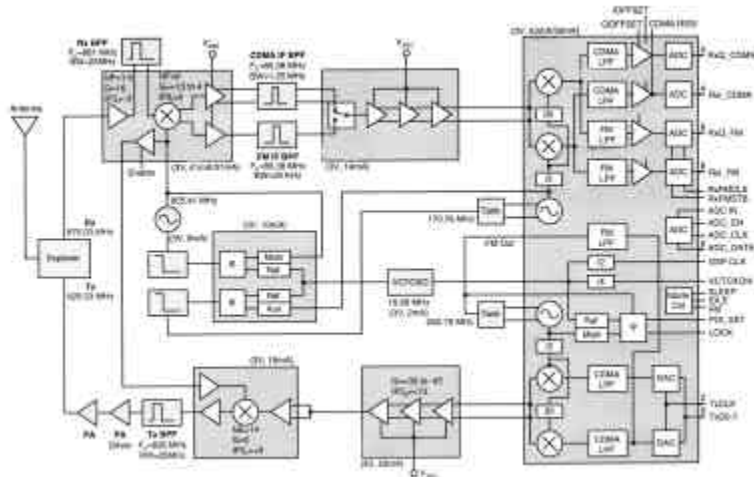Example: Dual Mode CDMA (IS95)& Analog Cellular Phone



Example: Dual Mode CDMA (IS95)& Analog Cellular Phone

- Baseband analog circuitry includes:
 - CDMA
 - 4bit flash type ADC clock rate 10MHz
 - 8bit segmented TX DAC clock rate 10MHz (shared with FM)
 - 7th order elliptic RX lowpass filter corner freq. 650kHz
 - 3rd order chebyshev TX lowpass filter corner freq. 650kHz
 - FM (analog)
 - 8bit successive approximation ADCs clock rate 360kHz
 - 5th order chebyshev RX lowpass filter corner frequency 14kHz
 - 3rd order butterworth TX lowpass filter corner frequency 27kHz

Summary

- Examples from wireline & wireless systems utilizing analog & RF circuitry discussed
- Analog circuits still remain the interface → connecting the digital world to the real world!