


# EE247

## Lecture 10

### Supplemental Material for S.C. Filters
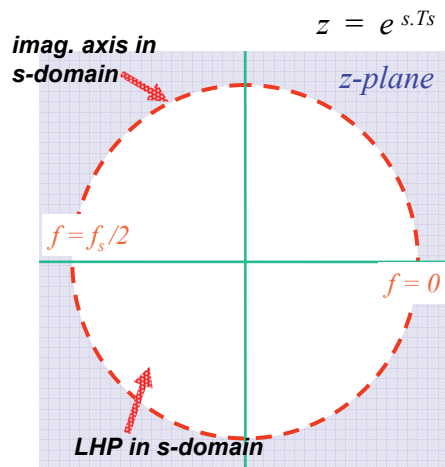
## z-Domain Frequency Response

- The  $j\omega$  axis maps onto the unit-circle
- LHP singularities in s-plane map into inside of unit-circle in z-domain
- RHP singularities in s-plane map into outside of unit-circle in z-domain
- Particular values:
  - $f = 0 \rightarrow z = 1$
  - $f = f_s/2 \rightarrow z = -1$




## z-Domain Frequency Response

- The frequency response is obtained by evaluating  $H(z)$  on the unit circle at:

$$z = e^{j\omega T} = \cos(\omega T_s) + j \sin(\omega T_s)$$

- Once  $z = -1$  ( $f_s/2$ ) is reached, the frequency response repeats, as expected

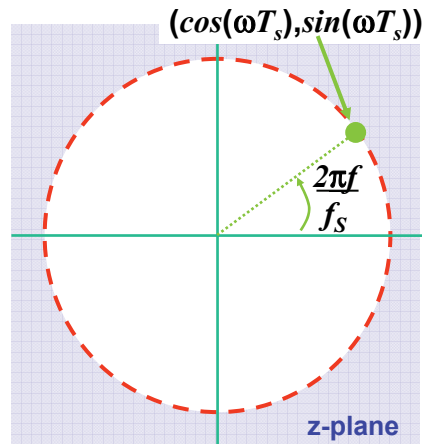- The angle to the pole is equal to  $360^\circ$  (or  $2\pi$  radians) times the ratio of the pole frequency to the sampling frequency




## DDI Integrator Pole-Zero Map in z-Plane

$z - 1 = 0 \rightarrow z = 1$   
on unit circle


Pole from  $f \rightarrow 0$   
in s-plane mapped to  $z = +1$

As frequency increases  $z$   
domain point moves on unit  
circle (CCW)  $f = f_s/2$

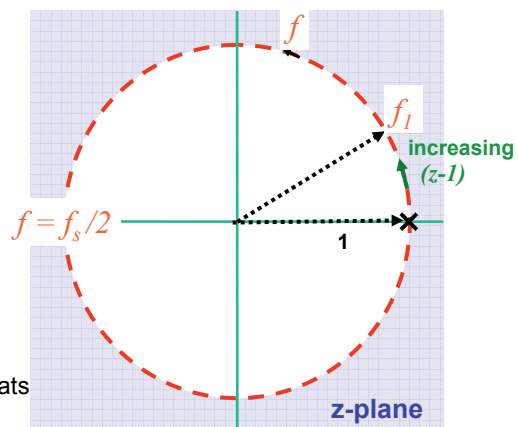
Once frequency gets to:  
 $z = -1$  ( $f = f_s/2$ )  
 $\rightarrow$  frequency response repeats


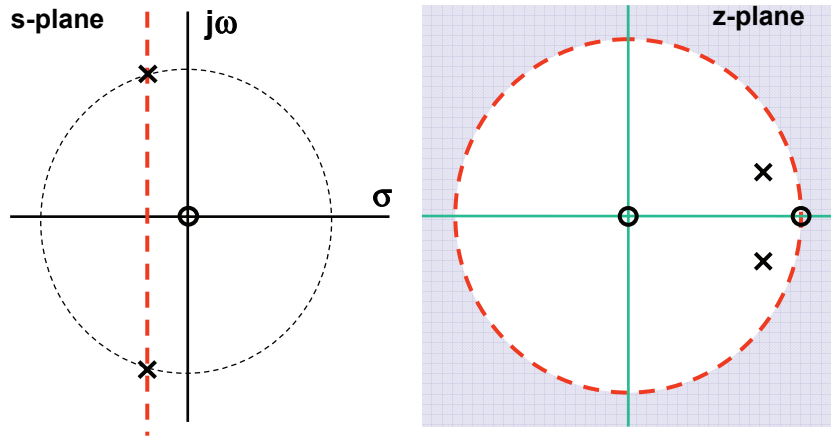
# Example: 2<sup>nd</sup> Order LDI Bandpass Filter s-Plane versus z-Plane



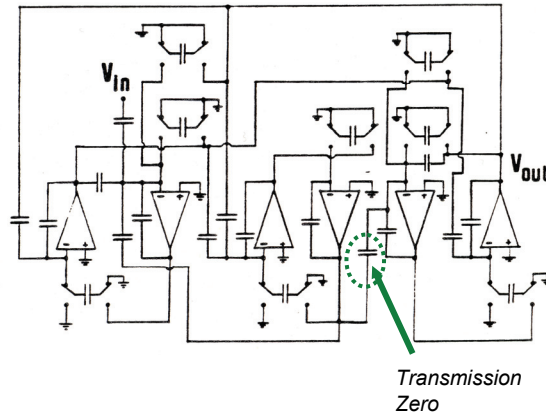
## Sixth-Order Elliptic LDI Bandpass Filter




Ref: Tat C. Choi, "High-Frequency CMOS Switched-Capacitor Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, May 1983 (ERL Memorandum No. UCB/ERL M83/31).

## Use of T-Network

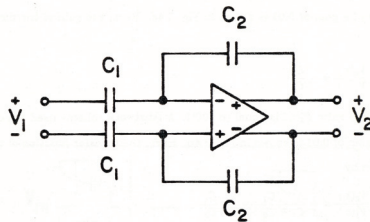

$$C_2:C_1 = 100:1$$

$$\frac{V_2}{V_1} = -\frac{C_1}{C_2}$$

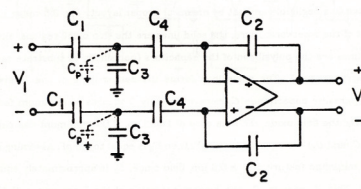


$$C_4:C_3:C_2:C_1 = 1:8:10:1$$

$$\frac{V_2}{V_1} = -\frac{C_1}{C_2} \times \frac{C_4}{C_1 + C_3 + C_4}$$

**High Q filter → large cap. ratio for Q & transmission zero implementation  
To reduce large ratios required → T-networks utilized**

Ref: Tat C. Choi, "High-Frequency CMOS Switched-Capacitor Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, May 1983 (ERL Memorandum No. UCB/ERL M83/31).

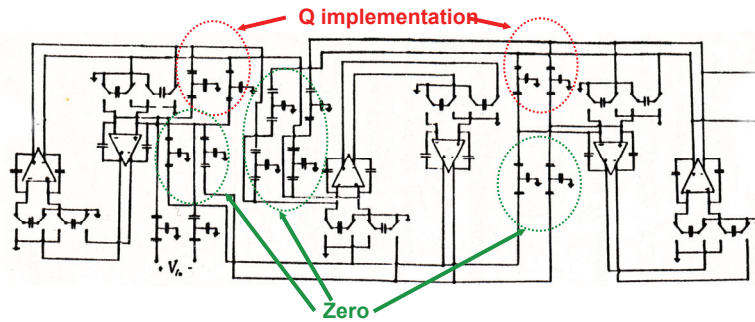
## Sixth Order Elliptic Bandpass Filter Utilizing T-Network



- T-networks utilized for:
  - Q implementation
  - Transmission zero implementation

Ref: Tat C. Choi, "High-Frequency CMOS Switched-Capacitor Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, May 1983 (ERL Memorandum No. UCB/ERL M83/31).

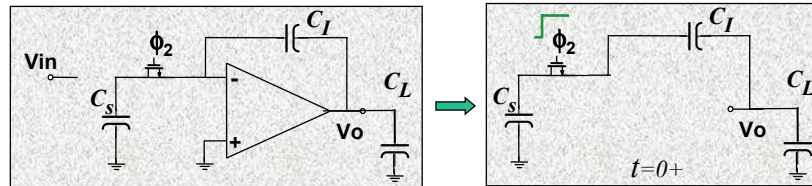
## More Realistic Switched-Capacitor Circuit Slew Scenario



At the instant  $C_s$  connects to input of opamp ( $t=0+$ )

- Opamp not yet active at  $t=0+$  due to finite opamp bandwidth → delay
- Feedforward path from input to output generates a voltage spike at the output with polarity opposite to final  $V_o$  step- spike magnitude function of  $C_p$ ,  $C_L$ ,  $C_s$
- Spike increases slewing period
- Eventually, opamp becomes active - starts slewing followed by subsequent settling
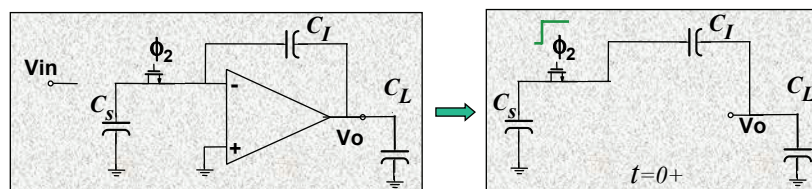
## Switched-Capacitor Circuit Opamp not Active @ $t=0+$



Charge sharing :  $C_s V_{Cs}^{t0-} = V_{Cs}^{t0+} (C_s + C_{eq})$  where  $C_{eq} = \frac{C_I C_L}{C_I + C_L}$


$$\Delta V_{out}^{t0+} = V_{Cs}^{t0+} \frac{C_I}{C_I + C_L} = V_{Cs}^{t0-} \frac{C_s}{C_s + C_{eq}} \times \frac{C_I}{C_I + C_L}$$

Assuming  $C_L \ll C_s \ll C_I \rightarrow C_{eq} \approx C_L \rightarrow C_s V_{Cs}^{t0-} \approx V_{Cs}^{t0+} (C_s + C_L) \rightarrow V_{Cs}^{t0-} \approx V_{Cs}^{t0+}$

$$\rightarrow \Delta V_{out}^{t0+} \approx V_{Cs}^{t0-} \frac{C_s}{C_s + C_L} \times \frac{C_I}{C_I + C_L} \approx V_{Cs}^{t0-}$$

Note that  $\Delta V_{out}^{final} \approx -\frac{C_s}{C_I} V_{Cs}^{t0+} \approx -\frac{C_s}{C_I} V_{Cs}^{t0-}$
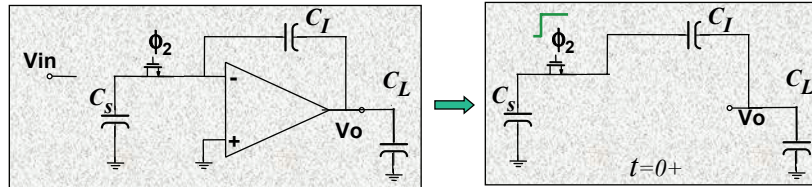
## More Realistic Switched-Capacitor Circuit Slew Scenario




Notice that if  $C_L$  is large  $\rightarrow$  some of the charge stored on  $C_s$  is lost prior to opamp becoming effective  $\rightarrow$  operation loses accuracy

$$\text{Charge sharing: } C_s V_{C_s}^{t=0-} = V_{C_s}^{t=0+} (C_s + C_{eq}) \quad \text{where } C_{eq} = \frac{C_f C_L}{C_f + C_L}$$

$$V_{C_s}^{t=0+} = V_{C_s}^{t=0-} \frac{C_s}{C_s + C_{eq}} = V_{C_s}^{t=0-} \frac{C_s}{C_s + \frac{C_f C_L}{C_f + C_L}}$$

$\rightarrow$  Partly responsible for S.C. filters only good for low-frequency applications

## More Realistic S.C. Slew Scenario

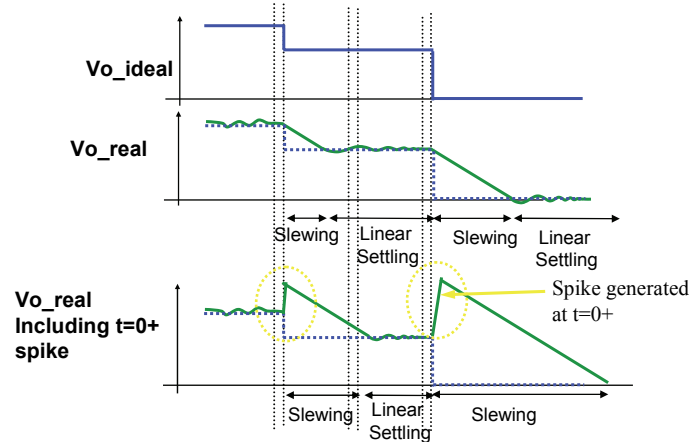


Ref: R. Castello, "Low Voltage, Low Power Switched-Capacitor Signal Processing Techniques," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, Aug. '84 (ERL Memorandum No. UCB/ERL M84/67).

## Extending the Maximum Achievable Critical Frequency of Switched-Capacitor Filters

Consider a switched-capacitor resonator:

Regular sampling:  
Each opamp is busy settling only during one of the two clock phases

→ Idle during the other clock phase

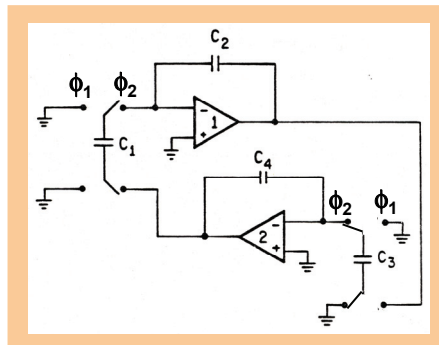


Note: During  $\phi_1$  both opamps are idle



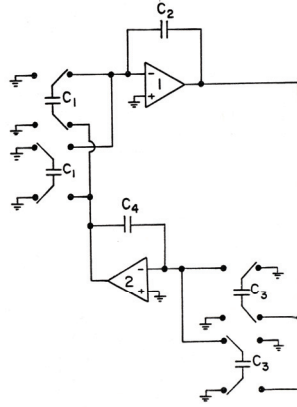
## Switched-Capacitor Resonator Using Double-Sampling

Double-sampling:

- 2<sup>nd</sup> set of switches & sampling caps added to all integrators
- While one set of switches/caps sampling the other set transfers charge into the intg. cap
- Opamps busy during both clock phases
- **Effective sampling freq. twice the clock freq. while opamp bandwidth requirement remains the same**



## Double-Sampling Issues

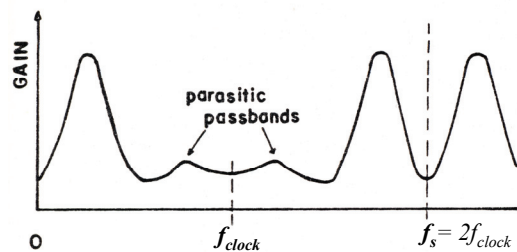


Issues to be aware of:

- Jitter in the clock
  - Unequal clock phases
  - Mismatch in sampling caps.
- parasitic passbands


Ref: Tat C. Choi, "High-Frequency CMOS Switched-Capacitor Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, May 1983 (ERL Memorandum No. UCB/ERL M83/31).
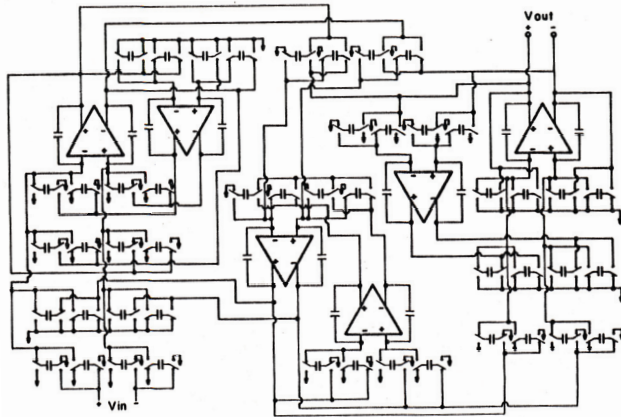
## Double-Sampled Fully Differential S.C. 6<sup>th</sup> Order All-Pole Bandpass Filter




Ref: Tat C. Choi, "High-Frequency CMOS Switched-Capacitor Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, May 1983 (ERL Memorandum No. UCB/ERL M83/31).

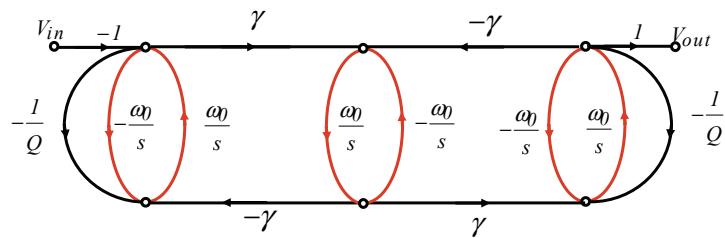
## Sixth Order Bandpass Filter Signal Flowgraph


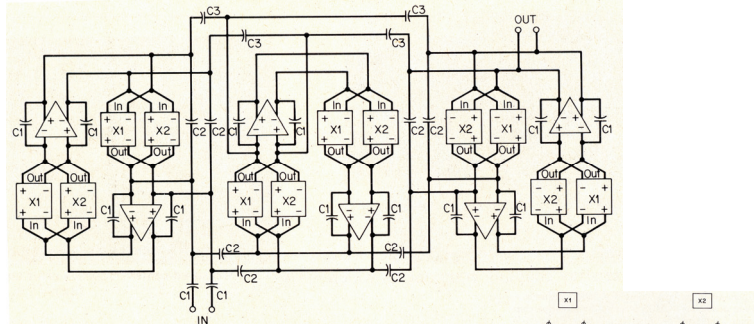
### Double-Sampled Fully Differential 6<sup>th</sup> Order S.C. All-Pole Bandpass Filter



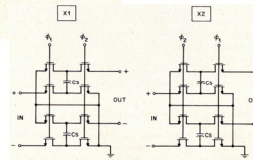- Cont. time termination (Q) implementation
- Folded-Cascode opamp with  $f_u = 100\text{MHz}$  used
- Center freq.  $3.1\text{MHz}$  (Measured error  $> 1\%$ ), filter  $Q=55$
- Clock freq.  $12.83\text{MHz}$   $\rightarrow$  effective oversampling ratio  $8.27$
- Measured dynamic range  $46\text{dB}$  ( $IM3=1\%$ )



Ref: B.S. Song, P.R. Gray "Switched-Capacitor High-Q Bandpass Filters for IF Applications,"  
*IEEE Journal of Solid State Circuits*, Vol. 21, No. 6, pp. 924-933, Dec. 1986.