

# EE247 Lecture 17


## • Nyquist rate ADC converters

### – Sampling

#### • Sampling switch considerations

- Thermal noise due to switch resistance (last lecture)
- Clock jitter related non-idealities
- Sampling switch bandwidth limitations
- Switch induced distortion
  - Sampling switch conductance dependence on input voltage
  - Clock voltage boosters
- Sampling switch charge injection & clock feedthrough

## Practical Sampling Issues

 


- Switch induced noise due to M1 finite channel resistance
- Clock jitter
- Finite  $R_{sw}$   $\rightarrow$  limited bandwidth  $\rightarrow$  finite acquisition time
- $R_{sw} = f(V_{in}) \rightarrow$  distortion
- Switch charge injection & clock feedthrough

# Clock Jitter

- The error voltage is

$$e = x'(t_0)(t_J - t_0)$$

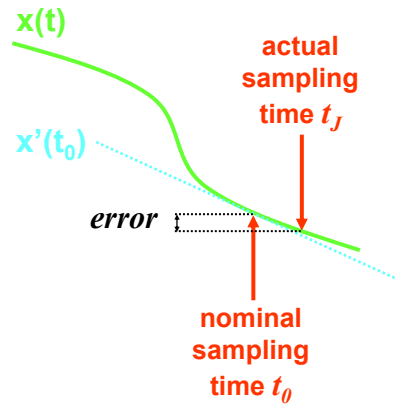

## Effect of Clock Jitter on Sampling of a Sinusoidal Signal

Sinusoidal input

Amplitude:  $A$   
 Frequency:  $f_x$   
 Jitter:  $dt$

$$x(t) = A \sin(2\pi f_x t)$$

$$x'(t) = 2\pi f_x A \cos(2\pi f_x t)$$

$$|x'(t)|_{max} \leq 2\pi f_x A$$

Requirement:

$$|e(t)| \leq |x'(t)|_{max} dt$$

$$|e(t)| \leq 2\pi f_x A dt$$

Worst case

$$A = A_{FS}/2 \quad f_x = f_s/2$$

$$|e(t)| \ll \frac{\Delta}{2} \equiv \frac{A_{FS}}{2^{B+1}}$$

$$dt \ll \frac{1}{2^B \pi f_s}$$

# of Bits	$f_s$	$dt \ll$
12	1 MHz	78 ps
16	20 MHz	0.24 ps
10	1000 MHz	0.3 ps

## Law of Jitter

- The worst case looks pretty stringent ...  
what about the “average”?
- Let’s calculate the mean squared jitter error (variance)
- If we’re sampling a sinusoidal signal  
 $x(t) = A\sin(2\pi f_x t)$ ,  
then
  - $x'(t) = 2\pi f_x A\cos(2\pi f_x t)$
  - $E\{[x'(t)]^2\} = 2\pi^2 f_x^2 A^2$
- Assume the jitter has variance  $E\{(t_J - t_0)^2\} = \tau^2$


## Law of Jitter

- If  $x'(t)$  and the jitter are independent  
–  $E\{[x'(t)(t_J - t_0)]^2\} = E\{[x'(t)]^2\} E\{(t_J - t_0)^2\}$
- Hence, the jitter error power is  
$$E\{e^2\} = 2\pi^2 f_x^2 A^2 \tau^2$$
- If the jitter is uncorrelated from sample  
to sample, this “jitter noise” is white

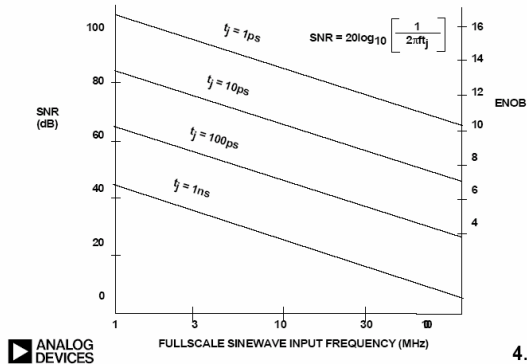
# Law of Jitter

$$\begin{aligned}
 DR_{\text{jitter}} &= \frac{A^2/2}{2\pi^2 f_x^2 A^2 \tau^2} \\
 &= \frac{1}{2\pi^2 f_x^2 \tau^2} \\
 &= -20 \log_{10}(2\pi f_x \tau)
 \end{aligned}$$

SNR DUE TO APERTURE AND SAMPLING CLOCK JITTER



## Example: ADC Spectral Tests

 

Ref: W. Yang et al., "A 3-V 340-mW 14-b 75-Msample/s CMOS ADC with 85-dB SFDR at Nyquist input," *IEEE J. of Solid-State Circuits*, Dec. 2001

## More on Jitter


- In cases where clock signal is provided from off-chip → have to choose a source with low enough jitter
  - On-chip precautions to keep the clock jitter less than single-digit pico-second :
    - Separate supplies as much as possible
    - Separate analog and digital clocks
    - Short inverter chains between clock source and destination
  - Few, if any, other analog-to-digital conversion non-idealities have the same symptoms as sampling jitter:
    - RMS noise proportional to input signal frequency
    - RMS noise proportional to input signal amplitude
- In cases where clock jitter limits the dynamic range, it's easy to tell, but may be difficult to fix...

## Sampling Acquisition Bandwidth

- The resistance  $R$  of switch  $S1$  turns the sampling network into a lowpass filter with finite time constant:


$$\tau = RC$$

 - Assuming  $V_{in}$  is constant during the sampling period and  $C$  is initially discharged



$$v_{out}(t) = v_{in}(1 - e^{-t/\tau})$$

 - Need to allow enough time for the output to settle to less than 1 ADC LSB → determines minimum duration for  $\phi_1$  or maximum clock frequency



## Sampling: Effect of Switch On-Resistance

$$V_{in}^{tx} - V_{out}^{tx} \ll \Delta \quad \text{since } V_{out} = V_{in}(1 - e^{-t/\tau})$$

$$\rightarrow V_{in} e^{-T_s/2\tau} \ll \Delta \quad \text{or } \tau \ll \frac{T_s}{2} \frac{1}{\ln(V_{in}/\Delta)}$$

Worst Case:  $V_{in} = V_{FS}$


$$\tau \ll \frac{T_s}{2} \frac{1}{\ln(2^B - 1)} \approx \frac{0.72 \times T_s}{B}$$

$$R \ll \frac{1}{2f_s C \ln(2^B - 1)} \approx \frac{0.72}{B f_s C}$$

 Example:

$$B = 14, \quad C = 13\text{pF}, \quad f_s = 100\text{MHz}$$

$$T_s/\tau \gg 19.4, \quad \text{or } 10\tau \ll T_s/2 \rightarrow R \ll 40 \Omega$$



## Switch On-Resistance


Switch  $\rightarrow$  MOS operating in triode mode:

$$I_{D(\text{triode})} = \mu C_{ox} \frac{W}{L} \left( V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS}, \quad \frac{1}{R_{ON}} \equiv \left. \frac{dI_{D(\text{triode})}}{dV_{DS}} \right|_{V_{DS} \rightarrow 0}$$

$$R_{ON} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{DD} - V_{th} - V_{in})}$$

Let us call  $R @ V_{in}=0$   $R_o$  then  $R_o = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{DD} - V_{th})}$
 
$$R_{ON} = \frac{R_o}{1 - \frac{V_{in}}{V_{DD} - V_{th}}}$$



# Sampling Distortion

Simulated 10-Bit ADC &

$$T_s/2 = 5\tau$$

$$V_{DD} - V_{th} = 2V$$


$$V_{FS} = 1V$$

Sampling switch modeled:

$$v_{out} = v_{in} \left( 1 - e^{-\frac{T}{2\tau} \left( 1 - \frac{V_{in}}{V_{DD} - V_{th}} \right)} \right)$$

→ Results in
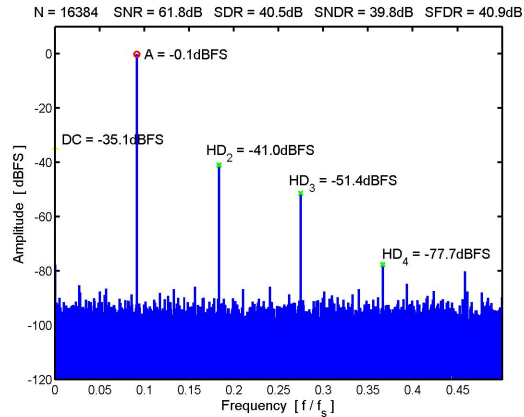
$$HD_2 = -41\text{dBFS} \text{ \& } HD_3 = -51.4\text{dBFS}$$



# Sampling Distortion

Doubling sampling time (or 1/2 time constant)


Results in:

HD2 improved from -41dBFS to -70dBFS ~30dB

HD3 improved from -51.4dBFS to -76.3dBFS ~25dB

Allowing enough time for the sampling network settling →

 
Reduces distortion due to switch R non-linear behavior to a tolerable level




$$10\text{bit ADC } T_s/2 = 10\tau$$

$$V_{DD} - V_{th} = 2V \quad V_{FS} = 1V$$
 
## Sampling Distortion Effect of Supply Voltage



 10bit ADC &  $T_s/2 = 5\tau$   
 $V_{DD} - V_{th} = 2V$   $V_{FS} = 1V$




10bit ADC &  $T_s/2 = 5\tau$   
 $V_{DD} - V_{th} = 4V$   $V_{FS} = 1V$

- Effect of higher supply voltage on sampling distortion
  - HD3 decrease by  $(V_{DD1}/V_{DD2})^2$
  - HD2 decrease by  $(V_{DD1}/V_{DD2})$
 
## Sampling Distortion

- SFDR → sensitive to sampling distortion - improve linearity by:
  - Larger  $V_{DD}/V_{FS}$ ?
    - Decreased dynamic range if  $V_{DD}$  const.
  - Larger switches?
    - Issue:
      - Increased switch charge injection
      - Increased nonlinear  $S$  &  $D$  junction cap.
  - Complementary switch
  - Constant & max.
    - $V_{GS} \neq f(V_{in})$



10bit ADC  $T_s/\tau = 20$   
 $V_{DD} - V_{th} = 2V$   $V_{FS} = 1V$



## Practical Sampling Summary So Far!

- $kT/C$  noise


$$C \geq 12k_B T \frac{2^{2B}}{V_{FS}^2}$$

- Finite  $R_{sw}$   $\rightarrow$  limited bandwidth



$$R \ll \frac{0.72}{B f_s C}$$

- $g_{sw} = f(V_{in}) \rightarrow$  distortion
 
$$g_{ON} = g_o \left( 1 - \frac{V_{in}}{V_{DD} - V_{th}} \right) \quad \text{for} \quad g_o = \mu C_{ox} \frac{W}{L} (V_{DD} - V_{th})$$



  
## Sampling: Use of Complementary Switches



- Complementary n & p switch advantages:

- ✓ Increase in the overall conductance
- ✓ Linearize the switch conductance for the range  $|V_{th}^p| < V_{in} < V_{dd} - |V_{th}^n|$

 
## Complementary Switch Issues Supply Voltage Evolution



- Supply voltage has scaled down with technology scaling
- Threshold voltages do not scale accordingly


Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.
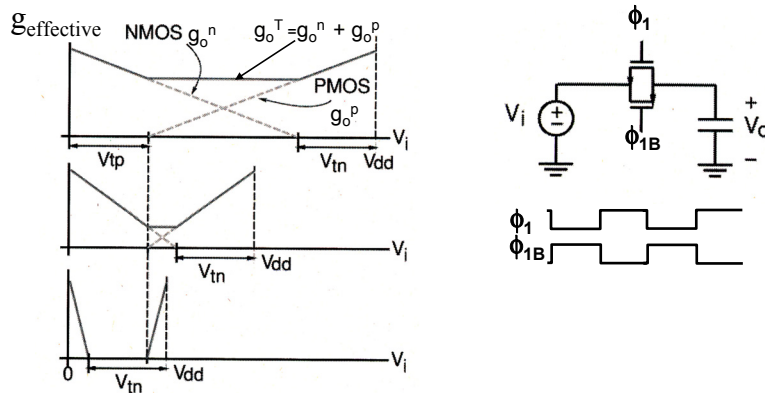
## Complementary Switch Effect of Supply Voltage Scaling



- As supply voltage scales down input voltage range for constant  $g_o$  shrinks  
 → Complementary switch not effective when  $V_{DD}$  becomes comparable to  $2xV_{th}$


## Boosted & Constant $V_{GS}$ Sampling

 


- Gate voltage  $V_{GS} = \text{low}$ 
  - Device off
  - Beware of signal feedthrough due to parasitic capacitors

- Increase gate overdrive voltage as much as possible + keep  $V_{GS}$  constant
  - Switch overdrive voltage independent of signal level
  - Error due to finite  $R_{ON}$  linear (to 1st order)
  - Lower  $R_{on} \rightarrow$  lower time constant

## Constant $V_{GS}$ Sampling

 

## Constant $V_{GS}$ Sampling Circuit

 

This Example: All device sizes:  $W/L=10\mu/0.35\mu$


All capacitor size: 1pF (except for Chold)

Note: Each critical switch requires a separate clock booster


Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.

Sampling switch & C

## Clock Voltage Doubler

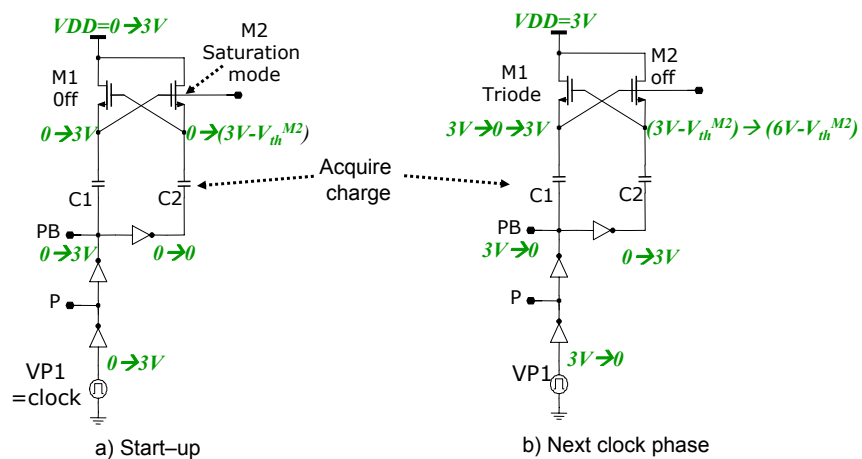


# Clock Voltage Doubler

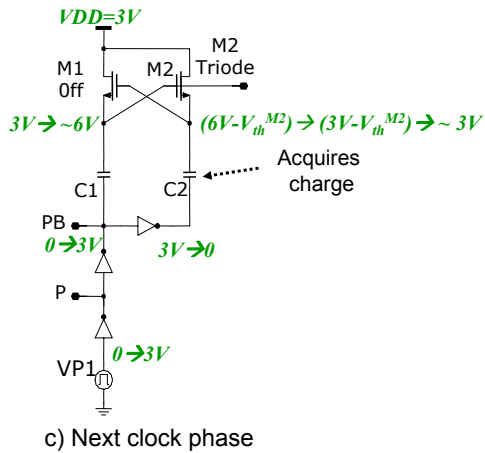


- Both C1 & C2 → charged to VDD after one clock cycle
- Note that bottom plate of C1 & C2 is either 0 or VDD while top plates are at VDD or 2VDD

# Clock Voltage Doubler

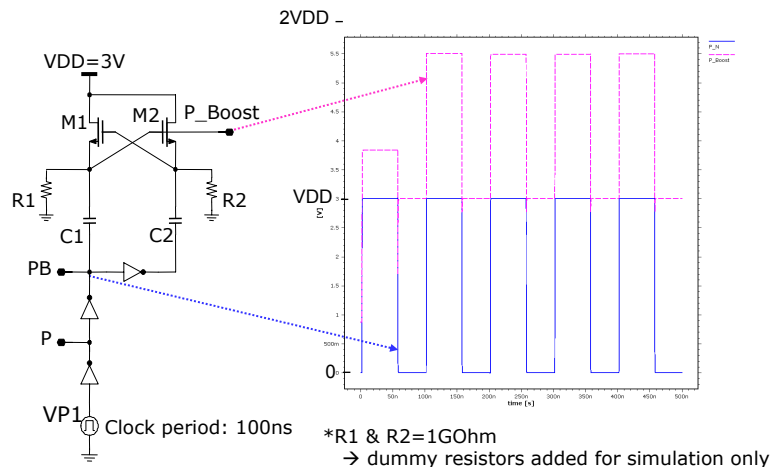


## Constant $V_{GS}$ Sampler: $\Phi$ Low

 

- Sampling switch M11 is OFF

- C3 charged to  $\sim VDD$
 
## Constant $V_{GS}$ Sampler: $\Phi$ High




- C3 previously charged to VDD


- M8 & M9 are on:  
C3 across G-S of M11

- M11 on with constant  $V_{GS} = VDD$

# Constant $V_{GS}$ Sampling

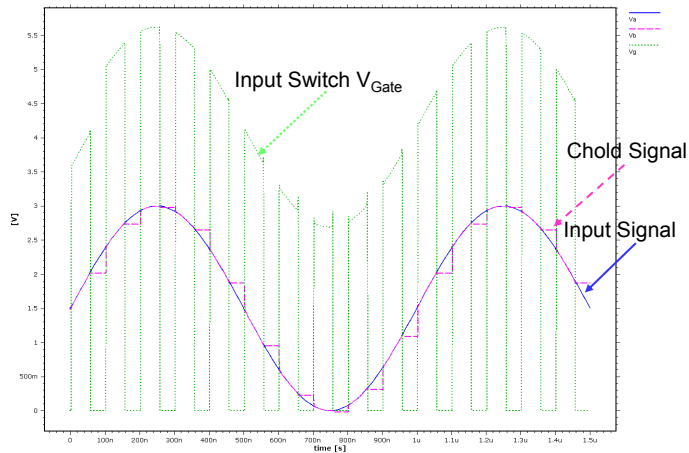

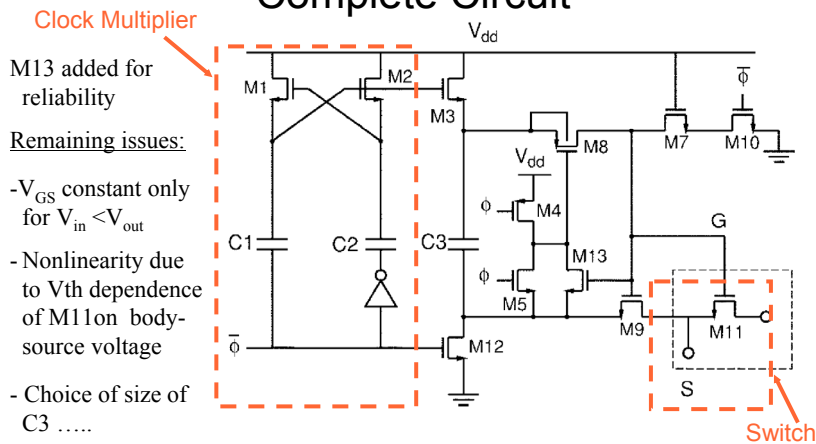
# Boosted Clock Sampling Complete Circuit




Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.

# Advanced Clock Boosting Technique

 

Ref: M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Tech. Papers, pp. 314


# Advanced Clock Boosting Technique

 

- clk → low
  - Capacitors C1a & C1b → charged to VDD
  - MS → off
  - Hold mode




## Advanced Clock Boosting Technique

 

- clk → high
  - Top plate of C1a & C1b connected to gate of sampling switch
  - Bottom plate of C1a connected to  $V_{IN}$
  - Bottom plate of C1b connected to  $V_{OUT}$
  - VGS & VGD of MS both @  $V_{DD}$  & ac signal on G of MS → average of  $V_{IN}$  &  $V_{OUT}$


## Advanced Clock Boosting Technique

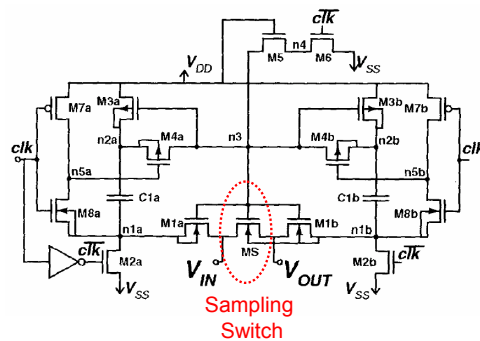

Ref: M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," ISSCC 2002, Dig. Tech. Papers, pp. 314


- Gate tracks average of input and output, reduces effect of I-R drop at high frequencies
- Bulk also tracks signal ⇒ reduced body effect (technology used allows connecting bulk to S)
- Reported measured SFDR = 76.5dB at  $f_{in}=200\text{MHz}$

# Constant Conductance Switch

 


Ref: H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6 $\mu$ m CMOS with over 80-dB SFDR," *IEEE J. Solid-State Circuits*, pp. 1769-1780, Dec. 2000

# Constant Conductance Switch

 

Ref: H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6 $\mu$ m CMOS with over 80-dB SFDR," *IEEE J. Solid-State Circuits*, pp. 1769-1780, Dec. 2000

## Constant Conductance Switch

 

M2 → Constant current  
→ constant  $g_{ds}$


M1 → replica of M2  
& same  $V_{GS}$   
as M2  
→ M1 also  
constant  $g_{ds}$

- Note: Authors report requirement of 280MHz GBW for the opamp for 12bit 50Ms/s ADC


- Also, opamp common-mode compliance for full input range required

Ref: H. Pan et al., "A 3.3-V 12-b 50-MS/s A/D converter in 0.6 $\mu$ m CMOS with over 80-dB SFDR," *IEEE J. Solid-State Circuits*, pp. 1769-1780, Dec. 2000
 
## Switch Off-Mode Feedthrough Cancellation



 
High-pass feedthrough paths past an open switch



Feedthrough cancellation with a dummy switch



Ref: M. Waltari et al., "A self-calibrated pipeline ADC with 200MHz IF-sampling frontend," *ISSCC 2002, Dig. Techn. Papers*, pp. 314

# Practical Sampling

 

- $R_{sw} = f(V_i) \rightarrow$  distortion
- ➔ • Switch charge injection & clock feedthrough

  
## Sampling Switch Charge Injection & Clock Feedthrough Switching from Track to Hold




- First assume  $V_i$  is a DC voltage
- When switch turns off  $\rightarrow$  offset voltage induced on  $C_s$
- Why?
 
## Sampling Switch Charge Injection

MOS xtor operating in triode region  
Cross section view





 Distributed channel resistance & gate & junction capacitances




- Channel  $\rightarrow$  distributed RC network formed between G,S, and D
- Channel to substrate junction capacitance  $\rightarrow$  distributed & voltage dependant
- Drain/Source junction capacitors to substrate  $\rightarrow$  voltage dependant
- Over-lap capacitance  $C_{ov} = L_D \times W \times C_{ox}$  associated with G-S & G-D overlap

## Switch Charge Injection Slow Clock

  

- Slow clock  $\rightarrow$  clock fall time  $\gg$  device speed  
 $\rightarrow$  During the period  $(t- \text{ to } t_{off})$  current in channel discharges channel charge into low impedance signal source
- Only source of error  $\rightarrow$  Clock feedthrough from  $C_{ov}$  to  $C_s$

## Switch Clock Feedthrough Slow Clock

 

$$\Delta V = -\frac{C_{ov}}{C_{ov} + C_s}(V_i + V_{th} - V_L)$$


$$\approx -\frac{C_{ov}}{C_s}(V_i + V_{th} - V_L)$$

$$V_o = V_i + \Delta V$$



$$V_o = V_i - \frac{C_{ov}}{C_s}(V_i + V_{th} - V_L) = V_i \left(1 - \frac{C_{ov}}{C_s}\right) - \frac{C_{ov}}{C_s}(V_{th} - V_L)$$

$$V_o = V_i(1 + \varepsilon) + V_{os}$$
 
$$\text{where } \varepsilon = -\frac{C_{ov}}{C_s}; V_{os} = -\frac{C_{ov}}{C_s}(V_{th} - V_L)$$


  
## Switch Charge Injection & Clock Feedthrough Slow Clock- Example





$$C'_{ov} = 0.1fF/\mu \quad C_{ox} = 9fF/\mu^2 \quad V_{th} = 0.4V \quad V_L = 0$$

$$\varepsilon = -\frac{C_{ov}}{C_s} = -\frac{10\mu \times 0.1fF/\mu}{1pF} = -0.1\%$$

Allowing  $\varepsilon = 1/2LSB \rightarrow ADC \text{ resolution} < \sim 9bit$

$$V_{os} = -\frac{C_{ov}}{C_s}(V_{th} - V_L) = -0.4mV$$
  
## Switch Charge Injection & Clock Feedthrough Fast Clock



- Sudden gate voltage drop → no gate voltage to establish current in channel  
→ channel charge has no choice but to escape out towards S & D

## Switch Charge Injection & Clock Feedthrough Fast Clock

Clock Fall-Time  $\ll$  Device Speed:


$$\Delta V_o = -\frac{C_{ov}}{C_{ov} + C_s}(V_H - V_L) - \left(\frac{1}{2}\right) \times \frac{Q_{ch}}{C_s}$$

$$\approx -\frac{C_{ov}}{C_{ov} + C_s}(V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L((V_H - V_i - V_{th}))}{C_s}$$

$$V_o = V_i(1 + \epsilon) + V_{os}$$



where  $\epsilon = -\frac{1}{2} \times \frac{WC_{ox}L}{C_s}$
 
$$V_{os} = -\frac{C_{ov}}{C_s}(V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L(V_H - V_{th})}{C_s}$$



- For simplicity it is assumed channel charge divided equally between S & D
- Source of error → channel charge transfer + clock feedthrough via  $C_{ov}$  to  $C_s$
  
## Switch Charge Injection & Clock Feedthrough Fast Clock- Example




$$C_{ov} = 0.1 \frac{fF}{\mu}, \quad C_{ox} = 9 \frac{fF}{\mu^2}, \quad V_{th} = 0.4V, \quad V_{DD} = 1.8V, \quad V_L = 0$$


$$\epsilon = 1/2 \frac{WLC_{ox}}{C_s} = \frac{10\mu \times 0.18\mu \times 9fF / \mu^2}{1pF} = 1.6\% \rightarrow \sim 5\text{-bit}$$

$$V_{os} = -\frac{C_{ov}}{C_s}(V_H - V_L) - \frac{1}{2} \times \frac{WC_{ox}L(V_H - V_{th})}{C_s} = -1.8mV - 14.6mV = -16.4mV$$
 
## Switch Charge Injection & Clock Feedthrough Slow Clock versus Fast Clock




Slow Clock

 

Fast Clock


 
## Switch Charge Injection & Clock Feedthrough Example-Summary



Error function of:

- Clock fall time
- Input voltage level
- Source impedance
- Sampling capacitance size
- Switch size

⚡ → Clock fall/rise should be controlled not to be faster (sharper) than necessary

## Switch Charge Injection Error Reduction

- How do we reduce the error?
  - Reduce switch size to reduce channel charge?

$$\Delta V_o = -\frac{1}{2} \frac{Q_{ch}}{C_s} \downarrow$$

$$\tau = R_{ON} C_s = \frac{C_s}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})} \uparrow \quad (\text{note: } \frac{T_s}{2} = k\tau)$$

Consider the figure of merit (FOM):

$$FOM = \frac{I}{\tau \times \Delta V_o} \approx \frac{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})}{C_s} \times 2 \times \frac{C_s}{W C_{ox} L ((V_H - V_i - V_{th}))}$$

$$\rightarrow FOM \propto \mu / L^2$$

- ❖ Reducing switch size increases  $\tau$  → increased distortion → not a viable solution
- ❖ Small  $\tau$  and small  $\Delta V$  → use minimum channel length (mandated by technology)
- ❖ For a given technology  $\tau \times \Delta V \sim \text{constant}$

## Sampling Switch Charge Injection & Clock Feedthrough Summary

- Extra charge injected onto sampling capacitor @ switch device turn-off
  - Channel charge injection
  - Clock feedthrough to  $C_s$  via  $C_{ov}$
- Issues due to charge injection & clock feedthrough:
  - DC offset induced on hold C
  - Input dependant error voltage → distortion
- Solutions:
  - Complementary switch?
  - Addition of dummy switches?
  - Bottom-plate sampling?