

EE247

Lecture 19


ADC Converters

- Track & hold (continued)
 - T/H aperture uncertainty
- ADC architectures and design
 - Serial- slope type
 - Successive approximation
 - Flash ADC and its sources of error: comparator offset, sparkle code & meta-stability
- Comparator design
 - Single-stage open-loop amplifier
 - Cascade of open-loop amplifiers
 - Problem associated with DC offset
 - Cascaded output series cancellation
 - Input series cancellation
 - Offset cancellation through additional input pair plus offset storage capacitors



EE247

Midterm Exam Results

 Average \rightarrow 85.5/100
Standard Deviation \rightarrow 6.5
Maximum=97/100
Minimum=71/100



Track & Hold Aperture Time Error

  


Transition from track to hold:
Occurs when device turns fully off

$$\rightarrow V_{CLK} = V_{in} + V_{TH}$$

Sharp fall-time wrt signal change
 \rightarrow no aperture error

Track & Hold Aperture Time Error

 

Slow falling clock \rightarrow aperture error

$$V_{in} = A \sin(2\pi f_{in} t)$$

$$\epsilon = f_{in} \times A \times t_{fall} / V_{CLK}$$

$SDR = -20 \log \epsilon - 4$ [dB] (empirical see Ref.)

Example:

Nyquist rate 10-bit ADC & $A = V_{CLK}/4$

$$\rightarrow SQNR = 62 \text{ dB}$$

for distortion due to aperture error
< quant noise

$$\rightarrow t_{fall} < 2 \times 10^{-3} / f_{in}$$

$$\rightarrow \text{Worst case: } f_{in} = f_s / 2$$

$$\rightarrow t_{fall} < 4 \times 10^{-3} / f_s$$

$$\rightarrow \text{e.g. } f_s = 100 \text{ MHz, } t_{fall} < 40 \text{ psec}$$

Ref: P. J. Lim and B. A. Wooley, "A high-speed sample-and-hold technique using a Miller hold capacitance," *IEEE Journal of Solid-State Circuits*, vol. 26, pp. 643 - 651, April 1991.

Track & Hold Aperture Time Error

- Aperture error analysis applies to simple sampling network
 - Bottom plate sampling → minimizes aperture error
 - Boosted clock → reduces aperture error
- Clock edge fall/rise trade-off between switch charge injection versus aperture error


Ref: P. J. Lim and B. A. Wooley, "A high-speed sample-and-hold technique using a Miller hold capacitance," *IEEE Journal of Solid-State Circuits*, vol. 26, pp. 643 - 651, April 1991.

ADC Architecture & Design


ADC Architectures

- Slope type converters
- Successive approximation
- Flash
- Time-interleaved / parallel converter
- Folding
- Residue type ADCs
 - Two-step
 - Pipeline
 - ...
- Oversampled ADCs

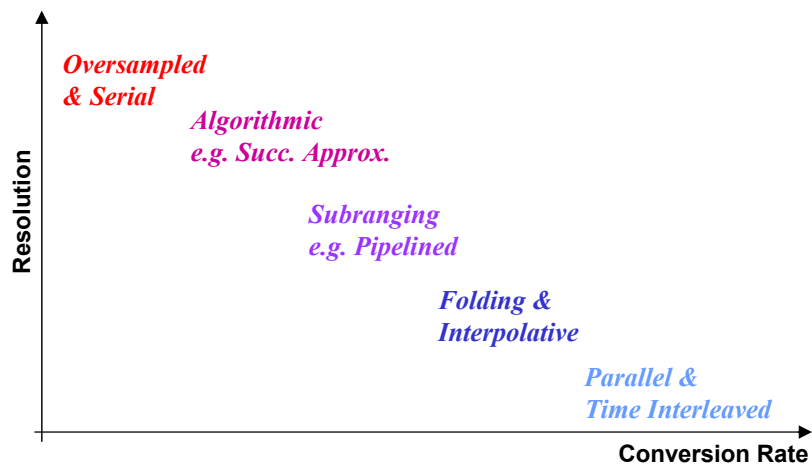Various ADC Architectures Resolution/Conversion Rate



Serial ADC Single Slope

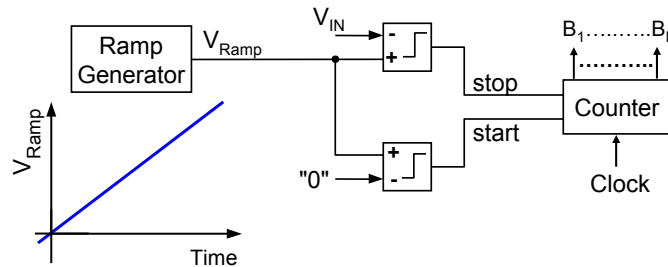


- Counter starts counting @ $V_{\text{Ramp}} = 0$
- Counter stops counting for $V_{\text{IN}} = V_{\text{Ramp}}$
 → Counter output proportional to V_{IN}

Single Slope ADC


- Advantages:
 - Low complexity & simple
 - INL depends on ramp linearity & not component matching
 - Inherently monotonic
- Disadvantages:
 - Slow (2^N clock pulses for N-bit conversion) (e.g. N=16
 $f_{\text{clock}} = 1\text{MHz} \rightarrow \text{needs } 65000 \times 1\mu\text{s} = 65\text{ms/conversion}$)
 - Hard to generate precise ramp required for high resolution ADCs
 - Need to calibrate ramp slope versus V_{IN}
- Better: Dual Slope, Multi-Slope

Serial ADC Dual Slope

 

- First: V_{IN} is integrated for a fixed time ($2^N \times T_{CLK}$)
 $\rightarrow V_o = 2^N \times T_{CLK} \times V_{IN} / \tau_{intg}$
- Next: V_o is de-integrated with V_{REF} until $V_o = 0$
 $\rightarrow \text{Counter output} = 2^N \times V_{IN} / V_{REF}$

Dual Slope ADC

 

http://www.maxim-ic.com/appnotes.cfm/appnote_number/1041



- Integrate V_{in} for fixed time (T_{INT}), de-integrate with V_{REF} applied $\rightarrow T_{De-Int} \sim 2^N \times T_{CLK} \times V_{in} / V_{REF}$
- Most laboratory DVMs use this type of ADC

Dual Slope ADC

- Advantage:
 - Accuracy to 1st order independent of integrator time-constant and clock period
 - Comparator offset referred to input is attenuated by integrator high DC gain
 - Insensitive to most linear error sources
 - DNL is a function of clock jitter
 - Power line (60Hz) xtalk effect on reading can be canceled by: choosing conversion time multiple of 1/60Hz
 - High accuracy achievable (16+bit)
- Disadvantage:
 - Slow (maximum $2 \times 2^N \times T_{clk}$ per conversion)
 - Integrator opamp offset results in ADC offset (can cancel)
 - Finite opamp gain gives rise to INL


Successive Approximation ADC SAR

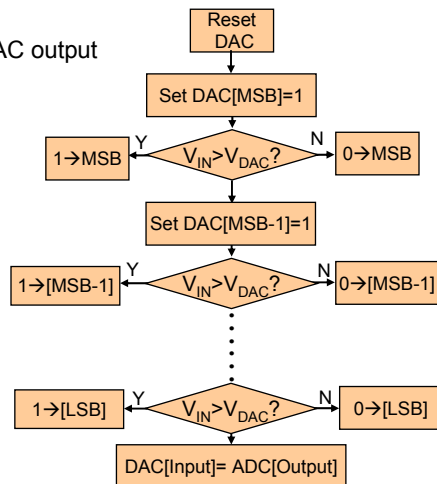 - Algorithmic type ADC
- Based on binary search over DAC output




Successive Approximation ADC

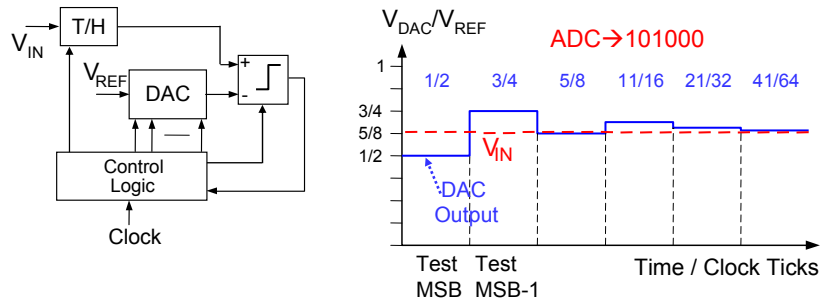Example: 6-bit ADC & $V_{IN} = 5/8 V_{REF}$




- High accuracy achievable (16+ Bits)
- Required N clock cycles for N-bit conversion (much faster than slope type)
- Moderate speed proportional to N (typically MHz range)

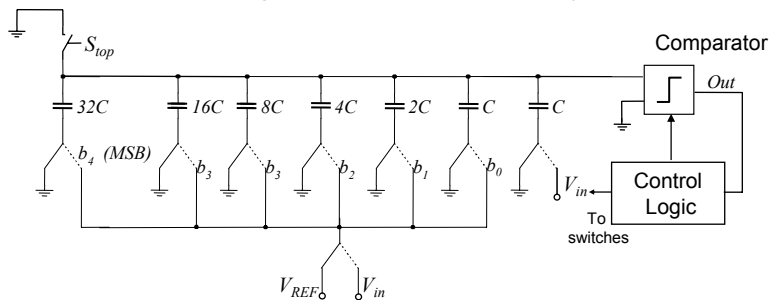Example: SAR ADC Charge Redistribution Type




- Built with binary weighted capacitors, switches, comparator & control logic
- T/H inherent in DAC

 Charge Redistribution Type SAR DAC Operation: MSB



- Operation starts by connecting all top plate to gnd and all bottom plates to V_{in}
- To test the MSB all top plate are opened bottom plate of $32C$ connected to V_{REF} & rest of bottom plates connected to ground \rightarrow input to comparator = $-V_{in} + V_{REF}/2$
- Comparator is strobed to determine the polarity of input signal:
 - If negative MSB=1, else MSB=0
- The process continues until all bits are determined

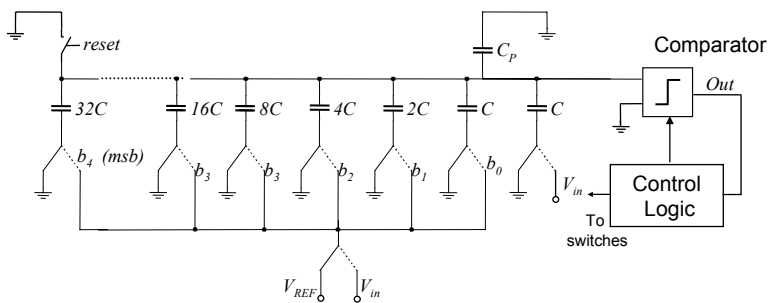Example: SAR ADC Charge Redistribution Type




- To 1st order parasitic (C_p) insensitive since top plate driven from initial 0 to final 0 by the global negative feedback
- Linearity is a function of accuracy of C ratios
- Possible to add a C ratio calibration cycle (see Ref.)

Ref: H. Lee, D. A. Hodges, and P. R. Gray, "A self-calibrating 15 bit CMOS A/D converter," *IEEE Journal of Solid-State Circuits*, vol. 19, pp. 813 - 819, December 1984.


Flash ADC

- B-bit flash ADC:

 - DAC generates all possible $2^B - 1$ levels
- $2^B - 1$ comparators compare V_{IN} to DAC outputs
- Comparator output:
 - If $V_{DAC} < V_{IN} \rightarrow 1$
 - If $V_{DAC} > V_{IN} \rightarrow 0$
- Comparator outputs form thermometer code
- Encoder converts thermometer to binary code




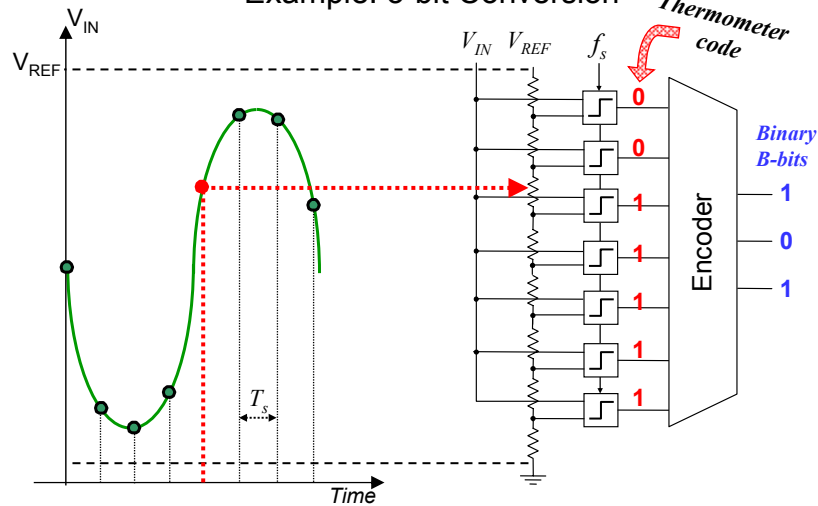Flash ADC Converter Example: 3-bit Conversion




Flash Converter Characteristics

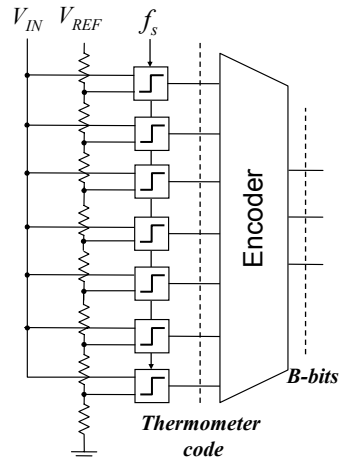- Very fast: only 1 clock cycle per conversion
 - $\frac{1}{2}$ clock cycle $\rightarrow V_{IN}$ & V_{DAC} comparison
 - $\frac{1}{2}$ clock cycle $\rightarrow 2^B - 1$ to B encoding
- High complexity: $2^B - 1$ comparators
- Input capacitance of $2^B - 1$ comparators connected to the input node:
 - \rightarrow High capacitance @ input node



Flash Converter Example: 8-bit ADC Design Considerations

 - 8-bit \rightarrow 255 comparators
- $V_{REF} = 1V \rightarrow 1\text{LSB} = 4\text{mV}$
- $\text{DNL} < 1/2\text{LSB} \rightarrow$ Comparator input referred offset $< 2\text{mV}$
- Assuming close to 100% yield, $2\text{mV} = 6\sigma_{\text{offset}}$
 - $\rightarrow \sigma_{\text{offset}} < 0.33\text{mV}$



Flash ADC Converter Example: 8-bits ADC (continued)

$$\rightarrow 1\sigma_{\text{Offset}} < 0.33\text{mV}$$

- Let us assume in the technology used:

- Voffset-per-unit-sqrt(WxL)=3 mVx μ

$$V_{\text{offset}} = \frac{3\text{mV}}{\sqrt{W \times L}} = 0.33\text{mV} \rightarrow W \times L = 83\mu^2$$

$$\text{Assuming: } C_{\text{ox}} = 9\text{fF}/\mu^2 \rightarrow C_{\text{GS}} = \frac{2}{3}C_{\text{ox}}W \times L = 496\text{fF}$$

$$\rightarrow \text{Total input capacitance: } 255 \times 0.496 = 126.5\text{pF!}$$

- Issues:

- Si area quite large
- Large ADC input capacitance
- Since depending on input voltage different number of comparator input transistors would be on/off- total input capacitance varies as input varies
- Nonlinear input capacitance could give rise to signal distortion

Ref: M. J. M. Pelgrom, A. C. J. Duinmaijer, and A. P. G. Welbers, "Matching properties of MOS transistors," *IEEE Journal of Solid-State Circuits*, vol. 24, pp. 1433 - 1439, October 1989.

Flash ADC Converter Example (continued)


Trade-offs:

- Allowing larger DNL e.g. 1LSB instead of 0.5LSB:
 - Increases the maximum allowable input-referred offset voltage by a factor of 2
 - Decreases the required device WxL by a factor of 4
 - Reduces the input device area by a factor of 4
 - Reduces the input capacitance by a factor of 4!
- Reducing the ADC resolution by 1-bit
 - Increases the maximum allowable input-referred offset voltage by a factor of 2
 - Decreases the required device WxL by a factor of 4
 - Reduces the input device area by a factor of 4
 - Reduce the input capacitance by a factor of 4


Flash Converter Maximum Tolerable Comparator Offset versus ADC Resolution

Assumption:
 $DNL = 0.5LSB$

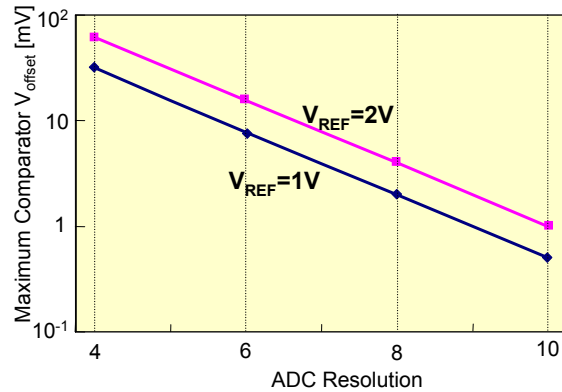Note:
Graph shows max. tolerable offset, note that depending on min acceptable yield, the derived offset numbers are associated with 2σ to 6σ offset voltage




Flash Converter Sources of Error

 


- Comparator input:
 - Offset
 - Nonlinear input capacitance
 - Feedthrough of input signal to reference ladder
 - Kickback noise (disturbs reference)
 - Signal dependent sampling time
- Comparator output:
 - Sparkle codes (... 111101000 ...)
 - Metastability


Typical Flash Output Encoder

 

Sparkle Codes

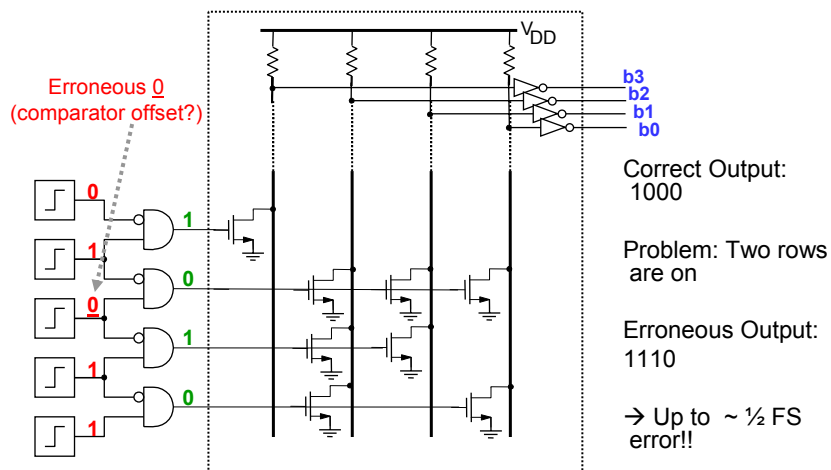


Sparkle Tolerant Encoder

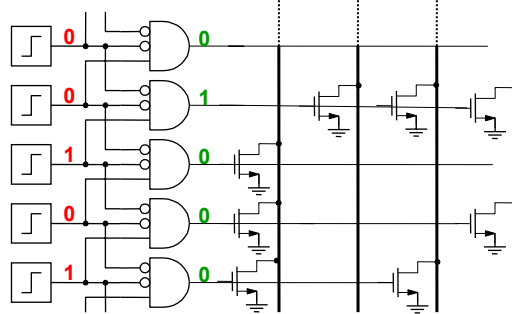

- Protects against a *single* sparkle.
- Possible to improve level of sparkle protection by increasing # of NAND gate inputs

Ref: C. Mangelsdorf et al, "A 400-MHz Flash Converter with Error Correction," JSSC February 1990, pp. 997-1002

Meta-Stability

 

Different gates interpret metastable output X differently

Correct output: 1000

Erroneous output: 0000

Solutions:

- Latches (high power)
- Gray encoding

Ref: C. Portmann and T. Meng, "Power-Efficient Metastability Error Reduction in CMOS Flash A/D Converters," JSSC August 1996, pp. 1132-40

Gray Encoding Example: 3bit ADC

Thermometer Code							Gray			Binary		
T ₇	T ₆	T ₅	T ₄	T ₃	T ₂	T ₁	G ₃	G ₂	G ₁	B ₃	B ₂	B ₁
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	1	0	0	1
0	0	0	0	0	1	1	0	1	1	0	1	0
0	0	0	0	1	1	1	0	1	0	0	1	1
0	0	0	1	1	1	1	1	1	0	1	0	0
0	0	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0	0	1	1	1


$$G_1 = T_1 \overline{T_3} + T_5 \overline{T_7}$$

$$G_2 = T_2 \overline{T_6}$$

$$G_3 = T_4$$

- Each T_i affects only one G_j
→ Avoids disagreement of interpretation by multiple gates
- Protects also against sparkles
- Follow Gray encoder by (latch and) binary encoder

Voltage Comparators

 

Play an important role in majority of ADCs

Function: Compare the instantaneous value of two analog signals & generate a digital output voltage based on the sign of the difference:

$$\text{If } V_{i+} - V_{i-} > 0 \rightarrow V_{out} = "1"$$

$$\text{If } V_{i+} - V_{i-} < 0 \rightarrow V_{out} = "0"$$

Voltage Comparator Architectures

Comparator architectures:

- High gain amplifier with differential analog input & single-ended large swing output
 - Output swing has to be compatible with driving digital logic circuits
 - Open-loop amplification → no frequency compensation required
 - Precise gain not required
- Latched comparators; in response to a strobe (clock edge), input stage disabled & digital output stored in a latch till next strobe
 - Two options for implementation :
 - Latch-only comparator
 - Low-gain preamplifier + high-sensitivity latch
- Sampled-data comparators
 - T/H input
 - Offset cancellation


Comparators Built with High-Gain Amplifier

Amplify $V_{in(min)}$ to V_{DD}
 → $V_{in(min)}$ determined by ADC resolution

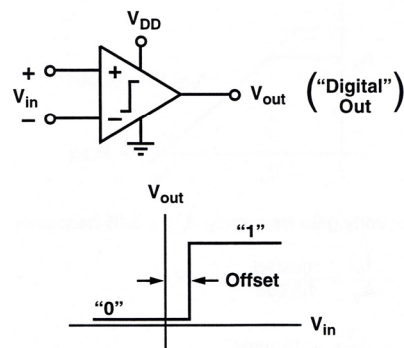Example: 12-bit ADC with:
 - $V_{FS} = 1.5V \rightarrow 1LSB = 0.36mV$
 - $V_{DD} = 1.8V$

→ For 1.8V output & 0.5LSB precision:

$$A_v^{Min} = \frac{1.8V}{0.18mV} \approx 10,000$$



Comparators

1-Single-Stage Amplification

f_u = unity-gain frequency, f_o = -3dB frequency

$$f_o = \frac{f_u}{A_V}$$


Example: $f_u = 10\text{GHz}$ & $A_V = 10,000$

$$f_o = \frac{10\text{GHz}}{10,000} \approx 1\text{MHz}$$

$$\tau_{\text{settling}} = \frac{1}{2\pi f_o} = 0.16\mu\text{sec}$$

Allow a few τ for output to settle
 
$$f_{\text{Clock}}^{\text{Max.}} \rightarrow \frac{1}{5\tau_{\text{settling}}} \approx 1.26\text{MHz}$$




Assumption: Single pole amplifier

Too slow for majority of applications!


→ Try cascade of lower gain stages to broaden frequency of operation

Comparators

2- Cascade of Open Loop Amplifiers

 

 The stages identical → small-signal model for the cascades:



One stage:

$$|A_V(0)| = g_m R_L$$

$$\omega_o = \text{-3dB frequency} = \frac{1}{R_L C_T}$$

$$\omega_u = \text{-unity gain frequency} = G \times BW = \frac{g_m}{C_T}$$

$$\therefore \omega_o = \frac{\omega_u}{|A_V(0)|}$$

Open Loop Cascade of Amplifiers

For an N-stage cascade:

$$A_T(j\omega) = [A_V(j\omega)]^N = \frac{[A_V(0)]^N}{\left(1 + j\frac{\omega}{\omega_0}\right)^N}$$

Define

$\omega_{oN} \equiv$ -3dB frequency of the N-stage cascade

Then

$$|A_T(j\omega_{oN})| = \frac{[A_V(0)]^N}{\sqrt{2}}$$

and

$$\omega_{oN} = \omega_0 \sqrt{2^{1/N} - 1} = \frac{\omega_u}{[A_V(0)]} \sqrt{2^{1/N} - 1}$$

Example: $N=4 \rightarrow \omega_{oN}=0.43\omega_0$

\therefore For a specified $|A_T(0)|$

$$|A_V(0)| = |A_T(0)|^{1/N}$$

$$\Rightarrow \omega_{oN} = \frac{\omega_u}{|A_T(0)|^{1/N}} \sqrt{2^{1/N} - 1}$$

Thus,

$$\begin{aligned} \frac{\omega_{oN}}{\omega_{o1}} &= \left[\frac{\omega_u}{|A_T(0)|^{1/N}} \sqrt{2^{1/N} - 1} \right] \bigg/ \left[\frac{\omega_u}{|A_T(0)|} \right] \\ &= |A_T(0)|^{\left(\frac{N-1}{N}\right)} \sqrt{2^{1/N} - 1} \end{aligned}$$

Example: $N=4, A_T=10000 \rightarrow \omega_{oN}=430\omega_{o1}$

Open Loop Cascade of Amplifiers

For $|A_T(\text{DC})|=10,000$

N	ω_{oN}/ω_{o1}	$ A_V(0) $
1	1	10,000
2	64	100
3	236	21.5
4	435	10
5	611	6.3
10	1067	2.5
20	1185	1.6

Example:

$N=3, f_u=10\text{GHz} \ \& \ |A_T(0)|=10000$

$$f_{oN} = \frac{10\text{GHz}}{(10,000)^{1/3}} \sqrt{2^{1/3} - 1} \approx 237\text{MHz}$$

$$\tau_{\text{settling}} = \frac{1}{2\pi f_o} = 0.7\text{nsec}$$


Allow a few τ for output to settle

$$f_{\text{Clock}}^{\text{Max}} \rightarrow \frac{1}{5\tau_{\text{settling}}} \approx 290\text{MHz}$$


f_{max} improved from 1.26MHz to 290MHz $\rightarrow X236$

Open Loop Cascade of Amplifiers Offset Voltage

 - From offset point of view: high gain/stage is preferred



 - Choice of # of stage
→ bandwidth vs offset tradeoff




$$A_T = A_1 \cdot A_2 \cdot A_3$$

$$\text{Input-referred offset} \rightarrow V_{os} = V_{os1} + \frac{V_{os2}}{A_1} + \frac{V_{os3}}{A_1 \cdot A_2}$$

Open Loop Cascade of Amplifiers Step Response

 - Assuming linear behavior (not slew limited)



$$v_{o1} = \frac{1}{C} \int_0^t g_m v_{in} dt = \frac{g_m}{C} v_{in} t$$


$$v_{o2} = \frac{1}{C} \int_0^t g_m v_{o1} dt = \frac{g_m}{C} \int_0^t \frac{g_m}{C} v_{in} dt = \frac{1}{2} \left(\frac{g_m}{C} \right)^2 v_{in} t^2$$

$$v_{o3} = \frac{1}{C} \int_0^t g_m v_{o2} dt = \frac{g_m}{C} \int_0^t \left[\frac{1}{2} \left(\frac{g_m}{C} \right)^2 v_{in} t^2 \right] dt$$

$$= \frac{1}{3} \left(\frac{g_m}{C} \right)^3 v_{in} t^3$$

Open Loop Cascade of Amplifiers Step Response

• Assuming linear behavior

 

N Stages

$$v_{oN} = \left(\frac{g_m}{C}\right)^N \left(\frac{t^N}{N!}\right) v_{in}$$

For the output to reach a specified v_{out} (i.e., $v_{oN} = v_{out}$) the delay is

$$\tau_D = \left(\frac{C}{g_m}\right) \left[(N!) \left(\frac{v_{out}}{v_{in}}\right) \right]^{1/N}$$

Open Loop Cascade of Amplifiers Delay/(C/g_m)

- Minimum total delay broad function of N
- Relationship between # of stages resulting in minimize delay (N_{opt}) and gain (V_{out}/V_{in}) approximately:

$$N_{opt} \approx 1 + \log_2 A_T \quad \text{for } A < 1000$$

$$N_{opt} \approx 1.2 \ln A_T \quad \text{for } A \geq 1000$$

		Delay/(C/g _m)			
		10	100	1000	10K
N	V _{out} /V _{in}	10	100	1000	10K
	1	10	100	1000	10K
	2	4.5	14.1	44.7	141
	3	3.9	8.4	18.2	39.1
	4	3.9	7.0	12.4	22.1
	5	4.1	6.5	10.4	16.4
	6	4.4	6.4	9.5	13.9
	7	4.7	6.5	9.1	12.6
	8	5.0	6.7	8.9	11.9
	9	5.4	6.9	8.9	11.5
	10	5.7	7.2	9.0	11.4
	11	6.1	7.5	9.2	11.3
	12	6.4	7.8	9.4	11.4
20	9.3	10.5	11.7	13.2	

Ref: J.T. Wu, et al., "A 100-MHz pipelined CMOS comparator" *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 1379 - 1385, December 1988.


Offset Cancellation

- In sampled-data cascade of amplifiers V_{os} can be cancelled
→ Store on ac-coupling caps in series with amp stages
- Offset associated with a specific amp can be cancelled by storing it in series with either the input or the output of that stage
- Offset can be cancelled by adding a pair of auxiliary inputs to the amplifier and storing the offset on capacitors connected to the aux. inputs during offset cancellation phase


Ref: J.T. Wu, et al., "A 100-MHz pipelined CMOS comparator" *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 1379 - 1385, December 1988.

Offset Cancellation Output Series Cancellation

 - Amp modeled as ideal
+ V_{os} (input referred)



 - Store offset:
 - S1, S4 → open
 - S2, S3 → closed
 - $V_C = A \cdot V_{os}$




$$V_C = A \cdot V_{os}$$

Ref: J.T. Wu, et al., "A 100-MHz pipelined CMOS comparator" *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 1379 - 1385, December 1988.

Offset Cancellation Output Series Cancellation

Amplify:

 - S2, S3 → open
 - S1, S4 → closed
- $V_C = A \cdot V_{OS}$




Circuit requirements:


- Amp not saturate during offset storage
- High-impedance (C) load → C_c not discharged
- $C_c \gg C_L$ to avoid attenuation
- $C_c \gg C_{switch}$ avoid excessive offset due to charge injection

$$\begin{aligned} V_{out} &= A \cdot (V_{in} + V_{os}) - V_C \\ &= A \cdot (V_{in} + V_{os}) - A \cdot V_{os} \\ &= A \cdot V_{in} \end{aligned}$$

 
Offset Cancellation Cascaded Output Series Cancellation



 Note: Offset storage capacitors in series with the amplifier outputs



 Offset Cancellation Cascaded Output Series Cancellation




1- S1 → open, S2,3,4,5 closed


$$V_{C1} = A_1 \times V_{os1}$$

$$V_{C2} = A_2 \times V_{os2}$$

$$V_{C3} = A_1 \times V_{os3}$$

 

 Offset Cancellation Cascaded Output Series Cancellation



2- S3 → open first


- Feedthrough from S3 → offset on X
- Switch offset, ϵ_3 induced on node X
- Since S4 remains closed, offset associated with ϵ_3 → stored on C2

$$V_X = \epsilon_3$$

$$V_{C1} = A_1 \times V_{os1} - \epsilon_3$$

$$V_{C2} = A_2 \times (V_{os2} + \epsilon_3)$$

 Offset Cancellation Cascaded Output Series Cancellation



3- S4 → open


- Feedthrough from S4 → offset on Y
- Switch offset, ϵ_4 induces error on node Y
- Since S5 remains closed, offset associated with ϵ_4 → stored on C3

$$V_Y = \epsilon_4$$

$$V_{C2} = A_2 \times (V_{os2} + \epsilon_3) - \epsilon_4$$

$$V_{C3} = A_3 \times (V_{os3} + \epsilon_4)$$

 Offset Cancellation Cascaded Output Series Cancellation



4- S2 → open, S1 → closed, S5 → open

- S1 closed & S2 open → since input connected to low impedance source charge injection not of major concern
- Switch offset, ϵ_5 introduced due to S5 opening

$$V_X = A_1 \times (V_{in} + V_{os1}) - V_{C1}$$

$$= A_1 \times (V_{in} + V_{os1}) - (A_1 \cdot V_{os1} - \epsilon_3)$$

$$= A_1 \cdot V_{in} + \epsilon_3$$

Offset Cancellation Cascaded Output Series Cancellation

$$\begin{aligned}
 V_y &= A_2 x (V_x + V_{os2}) - V_{C2} \\
 &= A_2 x (A_1 V_{in} + \epsilon_3 + V_{os2}) - [A_2 \cdot (V_{os2} + \epsilon_3) - \epsilon_4] \\
 &= A_1 \cdot A_2 \cdot V_{in} + \epsilon_4
 \end{aligned}$$

$$\begin{aligned}
 V_{out} &= A_3 x (V_y + V_{os3}) - V_{C3} \\
 &= A_3 \cdot (A_2 x A_1 V_{in} + \epsilon_4 + V_{os3}) - [A_3 \cdot (V_{os3} + \epsilon_4) - \epsilon_5] \\
 &= A_1 \cdot A_2 \cdot A_3 \cdot V_{in} + \epsilon_5
 \end{aligned}$$

Offset Cancellation Cascaded Output Series Cancellation

$$\begin{aligned}
 V_{out} &= A_1 \cdot A_2 \cdot A_3 \cdot (V_{in} + \epsilon_5 / A_1 \cdot A_2 \cdot A_3) \\
 \text{Input-Referred Offset} &= \epsilon_5 / A_1 \cdot A_2 \cdot A_3
 \end{aligned}$$

Example:

3-stage open-loop differential amplifier with offset cancellation + output amplifier (see Ref.)


$$\begin{aligned}
 A_{\text{Total}}(\text{DC}) &= 2 \times 10^6 = 126\text{dB} \\
 \text{Input-referred offset} &< 5\mu\text{V}
 \end{aligned}$$

Ref: R. Poujois and J. Borel, "A low drift fully integrated MOSFET operational amplifier," *IEEE Journal of Solid-State Circuits*, vol. 13, pp. 499 - 503, August 1978.

Offset Cancellation Output Series Cancellation

- Advantages:
 - Almost complete cancellation
 - Closed-loop stability not required
- Disadvantages:
 - Gain per stage must be small
 - Offset storage C in the signal path- could slow down overall performance

 Offset Cancellation Input Series Cancellation




Ref: R. Poujois and J. Borel, "A low drift fully integrated MOSFET operational amplifier," *IEEE Journal of Solid-State Circuits*, vol. 13, pp. 499 - 503, August 1978.

Offset Cancellation Input Series Cancellation

Store offset

S1 = 0 (off)
S2, S3 = 1 (conducting)

 

Note: Mandates
closed-loop
stability

$$V_C = -A(V_C - V_{os})$$


$$= \left(\frac{A}{A+1}\right)V_{os}$$

Ref: R. Poujois and J. Borel, "A low drift fully integrated MOSFET operational amplifier," *IEEE Journal of Solid-State Circuits*, vol. 13, pp. 499 - 503, August 1978.

Offset Cancellation Input Series Cancellation

Amplify

S2, S3 → open
S1 → closed

 

$$V_{out} = -A(V_{in} + V_C - V_{os}) = -A\left[V_{in} + V_{os}\left(\frac{A}{A+1} - 1\right)\right]$$

$$\therefore V_{out} = -A\left(V_{in} - \frac{V_{os}}{A+1}\right)$$

and


$$\text{Input-Referred Offset} = \frac{V_{os}}{A+1}$$

Example: A=4
→ Input-referred
offset = $V_{os}/5$

Offset Cancellation Cascaded Input Series Cancellation

$$V_{out} = A_1 A_2 \left[V_{in} + \frac{V_{os2}}{A_1(A_2 + 1)} - \frac{\epsilon_2}{A_1} \right]$$
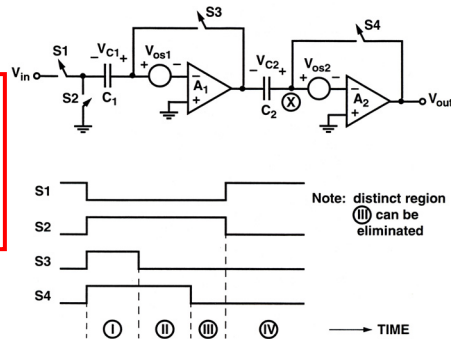
$$\text{Input-Referred Offset} = \frac{V_{os2}}{A_1(A_2 + 1)} - \frac{\epsilon_2}{A_1}$$



ϵ_2 → charge injection associated with opening of S4


Offset Cancellation Input Series Cancellation

- Advantages:
 - In applications such as C-array successive approximation ADCs can use C-array to store offset
- Disadvantages:
 - Cancellation not complete
 - Requires closed loop stability
 - Offset storage C in the signal path- could slow down overall performance


CMOS Comparators Cascade of Gain Stages

Fully differential gain stages \rightarrow 1st order cancellation of switch feedthrough offset

1- Output series offset cancellation

 


2- Input series offset cancellation

 

CMOS Comparators Cascade of Gain Stages

 3-Combined input & output series offset cancellation




V_{os1} & V_{os2} are both stored on a single pair of coupling capacitors

Offset Cancellation

- Cancel offset by additional pair of inputs (Lecture 18 slide 46 -48)


Latched Comparators

 

Compares two input voltages at time t_x & generates a digital output:


$$\text{If } V_{i+} - V_{i-} > 0 \rightarrow V_{out} = \text{"1"}$$
 
$$\text{If } V_{i+} - V_{i-} < 0 \rightarrow V_{out} = \text{"0"}$$




CMOS Latched Comparators

 Comparator amplification need not be linear
→ can use a latch → regeneration




Latch → Amplification + positive feedback

Simplest Form of CMOS Latch

 

CMOS Latched Comparators Small Signal Model

 Latch can be modeled as a:
→ Single-pole amp + positive feedback



CMOS Latched Comparator Latch Delay

$$g_m V = \frac{V}{R_L} + C \frac{dV}{dt}$$

$$\frac{g_m}{C} \left(1 - \frac{1}{g_m R_L} \right) V = \frac{dV}{dt} \quad \frac{g_m}{C} \left(1 - \frac{1}{g_m R_L} \right) dt = \frac{dV}{V}$$


Integrating both sides: $\frac{g_m}{C} \left(1 - \frac{1}{g_m R_L} \right) \int_{t_1}^{t_2} dt = \int_{V_1}^{V_2} \frac{1}{V} dV \quad \left(\int_b^a \frac{1}{x} dx = \ln x \Big|_b^a = \ln a - \ln b = \ln \frac{a}{b} \right)$

Latch Delay:

$$t_D = t_2 - t_1 = \frac{C}{g_m} \left(\frac{1}{1 - \frac{1}{g_m R_L}} \right) \ln \left(\frac{V_2}{V_1} \right)$$

For $g_m R_L \gg 1$
 
$$t_D \approx \frac{C}{g_m} \ln \left(\frac{V_2}{V_1} \right)$$



CMOS Latched Comparators

Normalized Latch Delay

$$t_D \approx \frac{C}{g_m} \ln \left(\frac{V_2}{V_1} \right)$$

$$\frac{V_2}{V_1} \rightarrow \text{Latch Gain} = A_L$$

$$\rightarrow t_D \approx \frac{C}{g_m} \ln A_L$$

$$\tau_D(\text{3-stage amp}) = 18.2(C/g_m)$$

A_L	$\frac{t_D}{C/g_m}$
10	2.3
100	4.6
1000	6.9
10K	9.2


Compared to a 3-stage open-loop cascade of amps for equal overall gain of 1000

→ Latch faster by about x3

Latch-Only Comparator

- Much faster compared to cascade of open-loop amplifiers
- Main problem associated with latch-only comparator topology:
 - High input-referred offset voltage (as high as 100mV!)
 - Solution:
 - Use preamplifier to amplify the signal and reduce overall input-referred offset

 Pre-Amplifier + Latch Overall Input-Referred Offset




Latch offset attenuated by preamp gain when referred to preamp input.
Assuming the two offset sources are uncorrelated:

$$\sigma_{\text{Input-Referred_Offset}} = \sqrt{\sigma_{V_{os_Preamp}}^2 + \frac{1}{A_{Preamp}^2} \sigma_{V_{os_Latch}}^2}$$

Example: $\sigma_{V_{os_Preamp}} = 4mV$ & $\sigma_{V_{os_Latch}} = 50mV$ & $A_{Preamp} = 10$

$$\sigma_{\text{Input-Referred_Offset}} = \sqrt{4^2 + \frac{1}{10^2} 50^2} = 6.4mV$$

Pre-Amplifier Tradeoffs

 

- Example:

- Latch offset 50 to 100mV
- Preamp DC gain 10X
- Preamp input-referred latch offset 5 to 10mV
- Input-referred preamplifier offset 2 to 10mV
- Overall input-referred offset 5.5 to 14mV

→ Addition of preamp reduces the latch input-referred offset reduced by ~7 to 9X → ~allows extra 3-bit resolution!