

EE247 Lecture 26

- Administrative

- Project submission:
 - Project reports due Dec. 5th
 - Please make an appointment with the instructor for a 15minute meeting on Monday Dec. 8th
 - Prepare to give a 3 to 7 minute presentation regarding the project during the class period on Dec. 9th
 - Highlight the important aspects of your approach towards the implementation of the ADC
 - If the project is joint effort, one or both could present

EE247 Lecture 26

- Homework for oversampled data converters
 - Due to the time consuming nature of the project, homework covering oversampled converters will not be given. Please review relevant previous year homeworks & solutions e.g.
 - http://www-inst.eecs.berkeley.edu/~ee247/fa07/files07/homework/HW9_2_07.pdf
 - http://www-inst.eecs.berkeley.edu/~ee247/fa07/files07/homework/HW9_sol_Lynn_Wang.pdf

EE247 Lecture 26


- Final course grading
 - Homeworks (7) 30%
 - Project 20%
 - Midterm exam 20%
 - Final exam 30%

EE247 Lecture 26

Oversampled ADCs (continued)

- 2nd order $\Sigma\Delta$ modulator
 - Implementation example
- Higher order $\Sigma\Delta$ modulators
 - Cascaded modulators (multi-stage)
 - Single-loop single-quantizer modulators with multi-order filtering in the forward path
- Bandpass $\Sigma\Delta$ modulators
- Testing of $\Sigma\Delta$ modulator front-end

 
2nd Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications



→ Measured & simulated spurious tones performance as a function of DC input signal
 → Sampling rate=12.8MHz, M=256

Ref: B. P. Brandt, et. al, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

 2nd Order $\Sigma\Delta$ Implementation Example: Digital Audio Applications



Sampling rate=12.8MHz,
M=256

→ Measured & simulated noise tone performance for near zero DC worst case input → 0.00088Δ

Ref: B. P. Brandt, et. al, "Second-order sigma-delta modulation for digital-audio signal acquisition," IEEE Journal of Solid-State Circuits, vol. 26, pp. 618 - 627, April 1991.

Higher Order $\Sigma\Delta$ Modulator Dynamic Range

$$Y(z) = z^{-1}X(z) + (1 - z^{-1})^L E(z) \quad , \quad L \rightarrow \Sigma\Delta \text{ order}$$

$$\overline{S_X} = \frac{1}{2} \left(\frac{\Delta}{2} \right)^2 \quad \text{sinusoidal input, } STF = 1$$

$$\overline{S_Q} = \frac{\pi^{2L}}{2L+1} \frac{1}{M^{2L+1}} \frac{\Delta^2}{12}$$


$$\frac{\overline{S_X}}{\overline{S_Q}} = \frac{3(2L+1)}{2\pi^{2L}} M^{2L+1}$$

$$DR = 10 \log \left[\frac{3(2L+1)}{2\pi^{2L}} M^{2L+1} \right]$$

$$DR = 10 \log \left[\frac{3(2L+1)}{2\pi^{2L}} \right] + (2L+1) \times 10 \times \log M$$

$2X$ increase in $M \rightarrow (6L+3)$ dB or $(L+0.5)$ -bit increase in DR

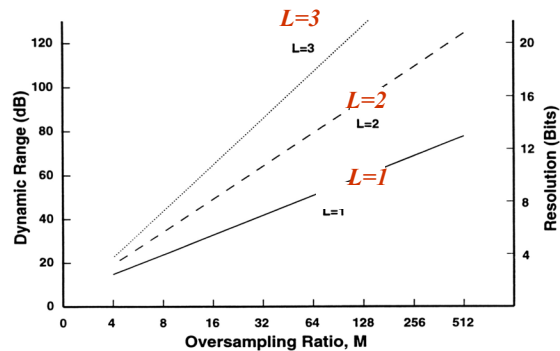$\Sigma\Delta$ Modulator Dynamic Range As a Function of Modulator Order




- Potential stability issues for $L > 2$

Higher Order $\Sigma\Delta$ Modulators


- Extending $\Sigma\Delta$ Modulators to higher orders by adding integrators in the forward path (similar to 2nd order)
 - Issues with stability
- Two different architectural approaches used to implement $\Sigma\Delta$ modulators of order >2
 1. Cascade of lower order modulators (multi-stage)
 2. Single-loop single-quantizer modulators with multi-order filtering in the forward path

 Higher Order $\Sigma\Delta$ Modulators (1) Cascade of 2-Stages $\Sigma\Delta$ Modulator



- Main $\Sigma\Delta$ quantizes the signal
- The 1st stage quantization error is then quantized by the 2nd quantizer
- The quantized error is then subtracted from the results in the digital domain

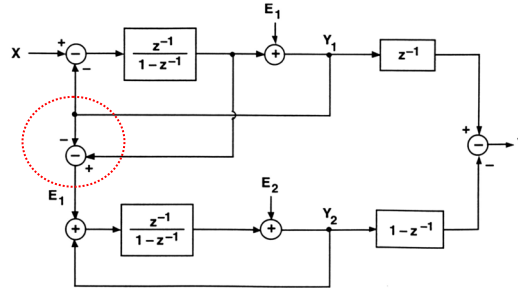2nd Order (1-1) Cascaded $\Sigma\Delta$ Modulators



$$Y_1(z) = z^{-1}X(z) + (1 - z^{-1})E_1(z)$$

$$Y_2(z) = z^{-1}E_1(z) + (1 - z^{-1})E_2(z)$$

$$Y(z) = z^{-1}Y_1(z) - (1 - z^{-1})Y_2(z)$$

$$= z^{-2}X(z) + z^{-1}(1 - z^{-1})E_1(z) - z^{-1}(1 - z^{-1})E_1(z) - (1 - z^{-1})^2E_2(z)$$


$$Y(z) = z^{-2}X(z) - (1 - z^{-1})^2E_2(z)$$

← 2nd order noise shaping

– Cascade of two 1st order $\Sigma\Delta$ s \rightarrow 2nd order $\Sigma\Delta$

3rd Order Cascaded $\Sigma\Delta$ Modulators (a) Cascade of 1-1-1 $\Sigma\Delta$ s

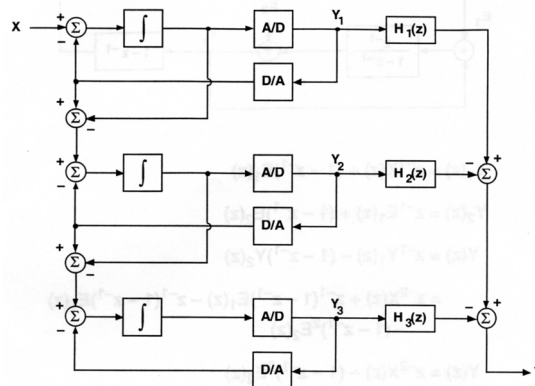- Can implement 3rd order noise shaping with 1-1-1
- This is also called MASH (multi-stage noise shaping)




– Cascade of two 1st order $\Sigma\Delta$ s \rightarrow 3rd order $\Sigma\Delta$

3rd Order Cascaded $\Sigma\Delta$ Modulators (b) Cascade of 2-1 $\Sigma\Delta$ s

Advantages of 2-1 cascade:

 - Low sensitivity to precision matching of analog/digital paths
- Low spurious limit cycle tone levels
- No potential instability



$$Y_1(z) = z^{-2}X(z) + (1 - z^{-1})^2E_1(z)$$

$$Y_2(z) = z^{-1}E_1(z) + (1 - z^{-1})E_2(z)$$


$$Y(z) = z^{-1}Y_1(z) - (1 - z^{-1})^2Y_2(z)$$

$$= z^{-3}X(z) + z^{-1}(1 - z^{-1})^2E_1(z) - z^{-1}(1 - z^{-1})^2E_1(z) - (1 - z^{-1})^3E_2(z)$$


3rd order noise shaping \rightsquigarrow

$$Y(z) = z^{-3}X(z) - (1 - z^{-1})^3E_2(z)$$

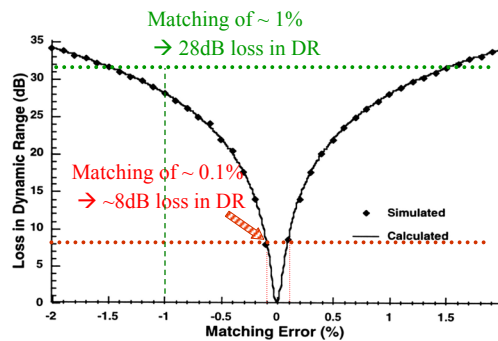Sensitivity of Cascade of (1-1-1) $\Sigma\Delta$ Modulators to Matching of Analog & Digital Paths



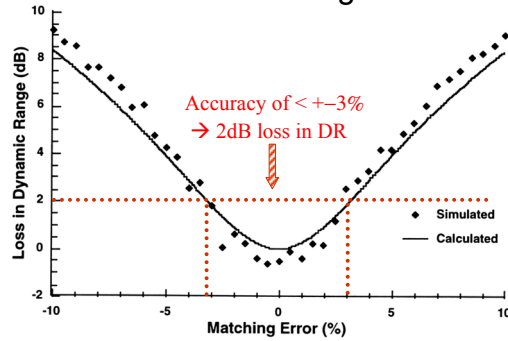
Sensitivity of Cascade of (2-1) $\Sigma\Delta$ Modulators to Matching Error



Main advantage of 2-1 cascade compared to 1-1-1 topology:


- Low sensitivity to matching of analog/digital paths (in excess of one order of magnitude less sensitive compared to (1-1-1)!)

2-1 Cascaded $\Sigma\Delta$ Modulators

 

Ref: L. A. Williams III and B. A. Wooley, "A third-order sigma-delta modulator with extended dynamic range," *IEEE Journal of Solid-State Circuits*, vol. 29, pp. 193 - 202, March 1994.

2-1 Cascaded $\Sigma\Delta$ Modulators

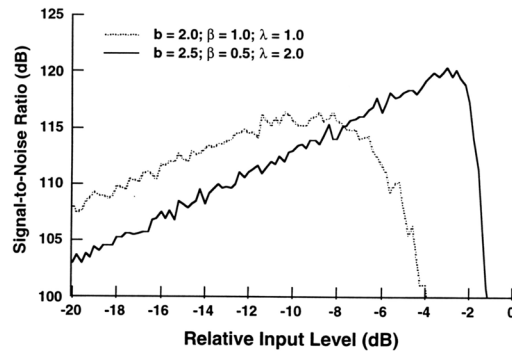


Effect of gain parameters on signal-to-noise ratio

Comparison of 2nd order & Cascaded (2-1) $\Sigma\Delta$ Modulator

Digital Audio Application, $f_N = 50\text{kHz}$ (Does not include Decimator)		
Reference	Brandt, JSSC 4/91	Williams, JSSC 3/94
Architecture	2 nd order	(2+1) Order
Dynamic Range	98dB (16-bits)	104dB (17-bits)
Peak SNDR	94dB	98dB
Oversampling rate	256 (theoretical \rightarrow SNR=109dB)	128 (theoretical \rightarrow SNR=128dB)
Differential input range	4V _{ppd} 5V supply	8V _{ppd} 5V supply
Power Dissipation	13.8mW	47.2mW
Active Area	0.39mm ² (1 μ tech.)	5.2mm ² (1 μ tech.)

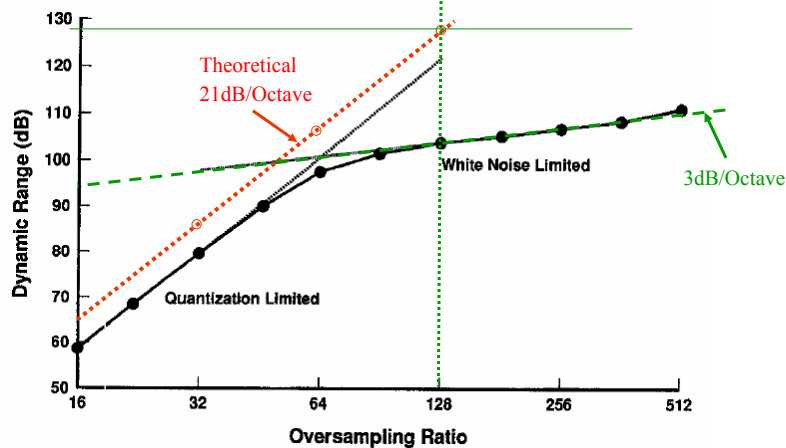2-1 Cascaded $\Sigma\Delta$ Modulators Measured Dynamic Range Versus Oversampling Ratio




Ref: L. A. Williams III and B. A. Wooley, "A third-order sigma-delta modulator with extended dynamic range," *IEEE Journal of Solid-State Circuits*, vol. 29, pp. 193 - 202, March 1994.

Higher Order $\Sigma\Delta$ Modulators (1) Cascaded Modulators Summary

- Cascade two or more stable $\Sigma\Delta$ stages
- Quantization error of each stage is quantized by the succeeding stage and subtracted digitally
- Order of noise shaping equals sum of the orders of the stages
- Quantization noise cancellation depends on the precision of analog/digital signal paths
- Quantization noise further randomized \rightarrow less limit cycle oscillation problems
- Typically, no potential instability

 Higher Order $\Sigma\Delta$ Modulators (2) Multi-Order Filter



$$Y(z) = \frac{H(z)}{1+H(z)}X(z) + \frac{1}{1+H(z)}E(z)$$

$$NTF = \frac{Y(z)}{E(z)} = \frac{1}{1+H(z)}$$

- Zeros of NTF (poles of $H(z)$) can be strategically positioned to suppress in-band noise spectrum
- **Approach:** Design NTF first and solve for $H(z)$

Example: Modulator Specification

- Example: Audio ADC


– Dynamic range	DR	18 Bits
– Signal bandwidth	B	20 kHz
– Nyquist frequency	f_N	44.1 kHz
– Modulator order	L	5
– Oversampling ratio	$M = f_s/f_N$	64
– Sampling frequency	f_s	2.822 MHz
- The order L and oversampling ratio M are chosen based on
 - SQNR > 120dB

Noise Transfer Function, NTF(z)

```
% stop-band attenuation Rstop=80dB, L=5,
bandwidth-20kHz ...
L=5;
Rstop = 80;
B=20000;
[b,a] = cheby2(L, Rstop, B, 'high');
```

```
NTF = firlt(b, a, ...);
```

 
Chebyshev II filter chosen
→ zeros in stop-band




Loop-Filter Characteristics H(z)

$$NTF = \frac{Y(z)}{E(z)} = \frac{1}{1 + H(z)}$$

$$\rightarrow H(z) = \frac{1}{NTF} - 1$$

 

Modulator Topology Simulation Model

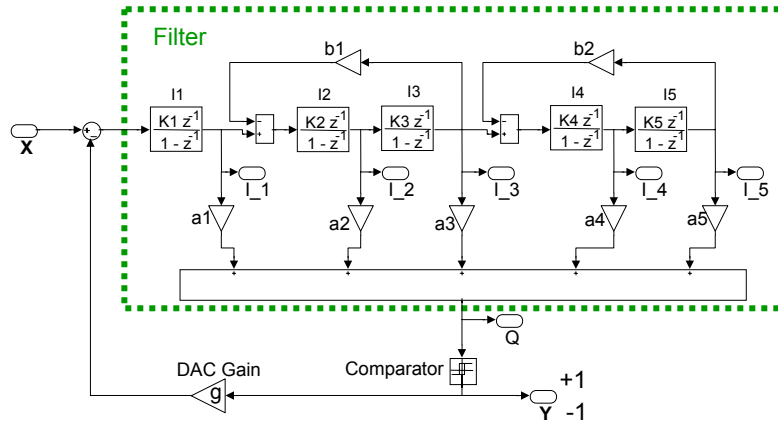


Filter Coefficients

$$\begin{array}{lll}
 a_1=1; & k_1=1; & b_1=1/1024; \\
 a_2=1/2; & k_2=1; & b_2=1/16-1/64; \\
 a_3=1/4; & k_3=1/2; & \\
 a_4=1/8; & k_4=1/4; & \\
 a_5=1/8; & k_5=1/8; & g = 1;
 \end{array}$$


Ref: Nav Souch, Don Kerth, Eric Swanson, and Tetsuro Sugimoto, "Phase Equalization System for a Digital-to-Analog Converter Using Separate Digital and Analog Sections", U.S. Patent 5061925, 1990, figure 3 and table 1

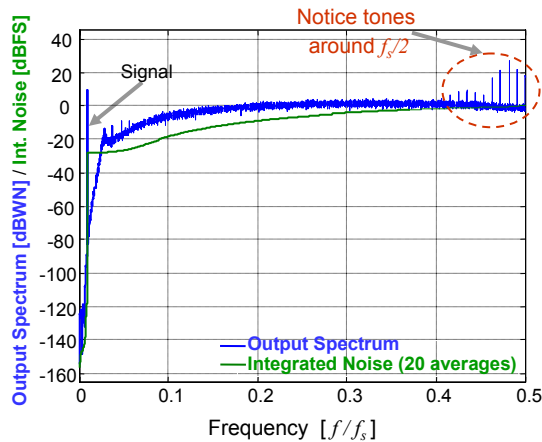5th Order Noise Shaping Simulation Results




- Mostly quantization noise, except at low frequencies
- Let's zoom into the baseband portion...

5th Order Noise Shaping

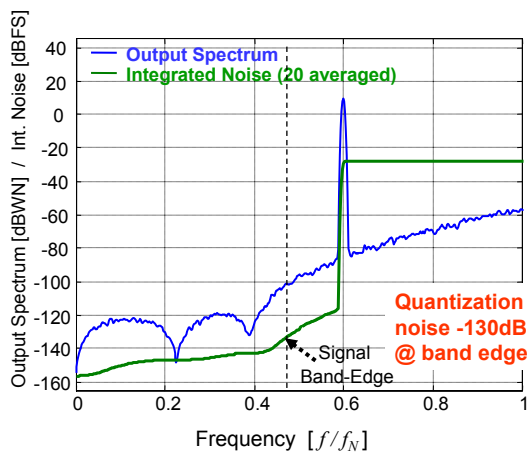


- SQNR > 120dB
- Sigma-delta modulators are usually designed for negligible quantization noise
- Other error sources dominate, e.g. thermal noise are allowed to dominate & thus provide dithering to eliminate limit cycle oscillations

In-Band Noise Shaping

 


- Lot's of gain in the loop filter pass-band
- Forward path filter not necessarily stable!
- Remember that:
 - ✓ NTF $\sim 1/H \rightarrow$ small within passband since H is large
 - ✓ STF $= H/(1+H) \rightarrow \sim 1$ within passband

Internal Node Voltages

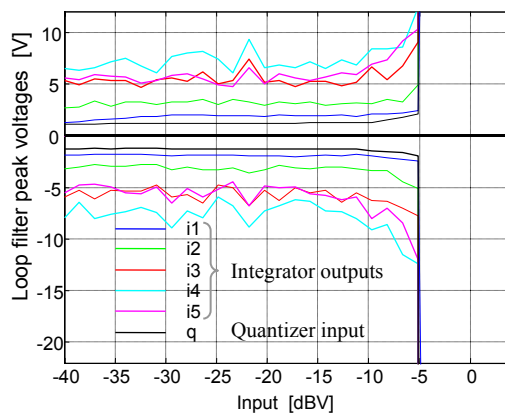


- Internal signal peak amplitudes are weak function of input level (except near overload)
- Maximum peak-to-peak voltage swing approach $\pm 10V!$ Exceed supply voltage!
- Solutions:
 - Reduce V_{ref} ??
 - Node scaling

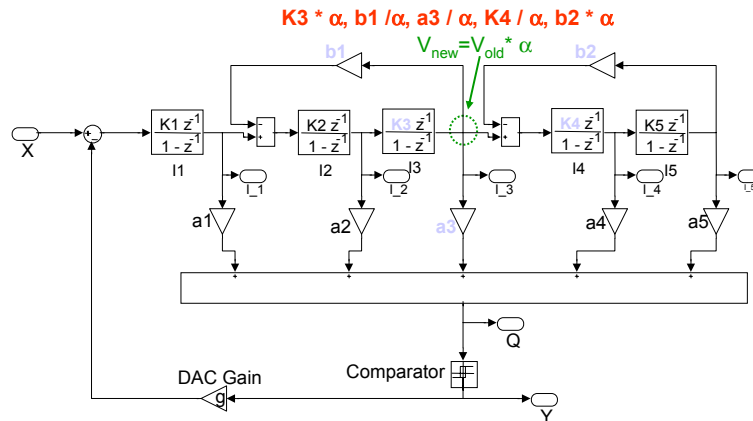Node Scaling Example: 3rd Integrator Output Voltage Scaled by α



Node Voltage Scaling

 


$\alpha = 1/10$
 \rightarrow
 $k1 = 1/10;$
 $k2 = 1;$
 $k3 = 1/4;$
 $k4 = 1/4;$
 $k5 = 1/8;$
 $a1 = 1;$
 $a2 = 1/2;$
 $a3 = 1/2;$
 $a4 = 1/4;$
 $a5 = 1/4;$
 $b1 = 1/512;$
 $b2 = 1/16 - 1/64;$
 $g = 1;$

- Integrator output range reasonable for new parameters
- But: maximum input signal limited to -5dB (-7dB with safety) – fix?

Input Range Scaling


Increasing the DAC levels by using higher value for g reduces the analog to digital conversion gain:
 
$$\frac{D_{OUT}(z)}{V_{IN}(z)} = \frac{H(z)}{1 + gH(z)} \approx \frac{1}{g}$$



Increasing V_{IN} & g by the same factor leaves 1-Bit data unchanged


Scaled Stage 1 Model

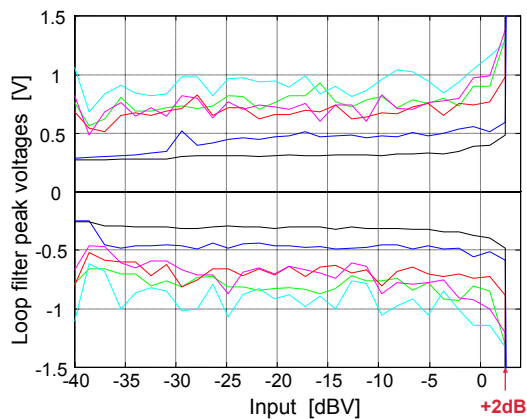

g modified:
From 1 to 2.5;

→ Overload
input level
shifted up by
8dB

Stability Analysis

 



- Approach: linearize quantizer and use linear system theory!
- One way of performing stability analysis → use RLocus in Matlab with $H(z)$ as argument and G_{eff} as variable
- Effective quantizer gain

$$G_{eff}^2 = \frac{y^2}{q^2}$$

- Can obtain G_{eff} from simulation

Ref: R. W. Adams and R. Schreier, "Stability Theory for $\Delta\Sigma$ Modulators," in Delta-Sigma Data Converters- S. Norsworthy et al. (eds), IEEE Press, 1997

Quantizer Gain (G_{eff})

  

Stability Analysis


$$STF = \frac{G \cdot H(z)}{1 + G \cdot H(z)}$$

$$H(z) = \frac{N(z)}{D(z)}$$

$$\rightarrow STF = \frac{G \cdot N(z)}{D(z) + G \cdot N(z)}$$

- Zeros of STF same as zeros of H(z)
- Poles of STF vary with G
- For G=0 (no feedback) poles of the STF same as poles of H(z)
- For G=large, poles of STF move towards zeros of H(z)
- Draw root-locus: for G values for which poles move to LHP (s-plane) or inside unit circle (z-plane) → system is stable


Modulator z-Plane Root-Locus

 

- As G_{eff} increases, poles of STF move from
 - poles of H(z) ($G_{\text{eff}} = 0$) to
 - zeros of H(z) ($G_{\text{eff}} = \infty$)
- Pole-locations inside unit-circle correspond to stable STF and NTF
- Need $G_{\text{eff}} > 0.45$ for stability


– Note: Final exam does NOT include Root Locus

Effective Quantizer Gain, G_{eff}

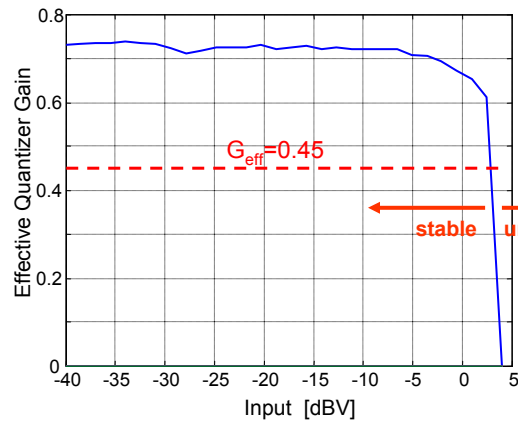

- Large inputs \rightarrow comparator input grows
- Output is fixed (± 1)
 - $\rightarrow G_{eff}$ drops
 - \rightarrow modulator unstable for large inputs
- Solution:
 - Limit input amplitude
 - Detect instability (long sequence of +1 or -1) and reset integrators
- Be ware that signals grow slowly for nearly stable systems \rightarrow use long simulations

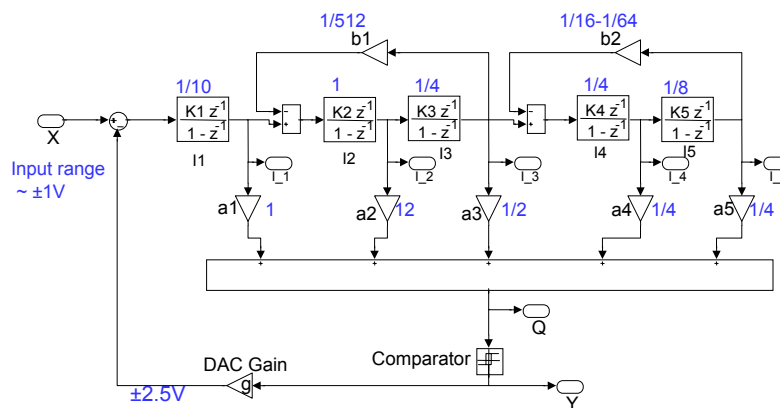5th Order Modulator Final Parameter Values




Stable input range with margin $\sim \pm 1V$

Summary

- Oversampled ADCs to 1st order, decouple SQNR from circuit complexity and accuracy
- If a 1-Bit DAC is used, the converter is to 1st order, inherently linear—independent of component matching
- Typically, used for high resolution & low frequency applications – e.g. digital audio
- 2nd order $\Sigma\Delta$ used extensively due to lower levels of limit cycle related spurious tones compared to 1st order
- $\Sigma\Delta$ modulators of order greater than 2:
 - Cascaded (multi-stage) modulators
 - Single-loop, single-quantizer modulators with multi-order filtering in the forward path

Bandpass $\Delta\Sigma$ Modulator

 

- Replace the integrator in 1st order lowpass $\Sigma\Delta$ with a resonator
→ 2nd order bandpass $\Sigma\Delta$


Bandpass $\Delta\Sigma$ Modulator Example: 6th Order

Measured output
for a bandpass $\Sigma\Delta$
(prior to digital
filtering)

Key Point:

NTF \rightarrow notch
type
shape

STF \rightarrow bandpass
shape

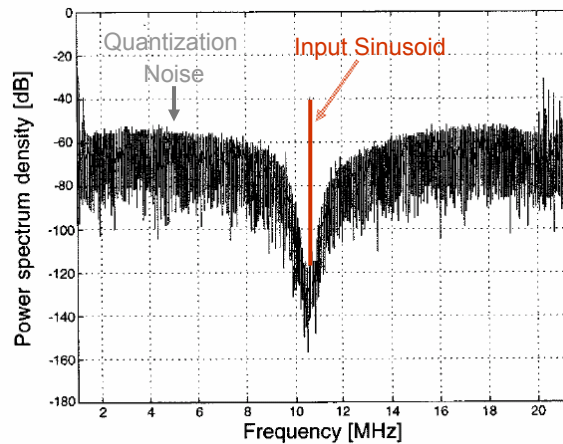


Ref:

Paolo Cusinato, et. al, "A 3.3-V CMOS 10.7-MHz Sixth-Order Bandpass Modulator with 74-dB Dynamic Range", IEEE JSSCC, VOL. 36, NO. 4, APRIL 2001

Bandpass $\Sigma\Delta$ Characteristics


- Oversampling ratio defined as $f_s/2B$ where B = signal bandwidth
- Typically, sampling frequency is chosen to be $f_s = 4xf_{center}$ where $f_{center} \rightarrow$ bandpass filter center frequency
- STF has a bandpass shape while NTF has a notch shape
- To achieve same resolution as lowpass, need twice as many integrators

 Bandpass $\Sigma\Delta$ Modulator Dynamic Range As a Function of Modulator Order (K)




- Bandpass $\Sigma\Delta$ resolution for order K is the same as lowpass $\Sigma\Delta$ resolution with order $L = K/2$

 Example: Sixth-Order Bandpass $\Sigma\Delta$ Modulator



Simulated noise transfer function

 

Simulated signal transfer function

Ref:

Paolo Cusinato, et. al, "A 3.3-V CMOS 10.7-MHz Sixth-Order Bandpass Modulator with 74-dB Dynamic Range", IEEE JSSCC, VOL. 36, NO. 4, APRIL 2001

Example: Sixth-Order Bandpass $\Sigma\Delta$ Modulator

Features & Measured Performance


Analog input full-scale	4.4V (differential)
Sampling frequency (F_s)	42.8MHz $\leftarrow f_s = 4 \times f_{center}$
Center frequency (f_0)	10.7MHz
Signal bandwidth	200kHz $\leftarrow B$
OSR	107 $\leftarrow OSR = f_s / 2B$
Dynamic range	74dB (200kHz band) 88dB (9kHz band)
Peak SNDR	61dB
IMD (@-15dB)	71dBc
Active die area	1mm ²
Power supply	3.3V
Power consumption	76mW (adaptive biasing) 126mW (standard biasing)
Technology	0.35 μ m CMOS

Ref:

Paolo Cusinato, et. al, "A 3.3-V CMOS 10.7-MHz Sixth-Order Bandpass Modulator with 74-dB Dynamic Range", IEEE JSSCC, VOL. 36, NO. 4, APRIL 2001

Modulator Front-End Testing

- Should make provisions for testing the modulator (AFE) separate from the decimator (digital back-end)
- Data acquisition board used to collect 1-bit digital output at f_s rate
- Analyze data in a PC environment or dedicated test equipment in manufacturing environments can be used
- Need to run DFT on the collected data and also make provisions to perform the function of digital decimation filter in software
- Typically, at this stage, parts of the design phase behavioral modeling effort can be utilized
- Good testing strategy vital for debugging/improving challenging designs

 

Summary Oversampled ADCs

- Noise shaping utilized to reduce baseband quantization noise power
- Reduced precision requirement for analog building blocks compared to Nyquist rate converters
- Relaxed transition band requirements for analog anti-aliasing filters due to oversampling
- Takes advantage of low cost, low power digital filtering
- Speed is traded for resolution
- Typically used for lower frequency applications compared to Nyquist rate ADCs